 


AHDL (Chapters 6 & 7)



Using TTL Library Functions with HDL



- MSI chips such as adders and ALU ICs are the building blocks of digital systems.
- How to use these components in HDL? → macrofunction
- A macrofunction is a self-contained description of a logic circuit with all its inputs, outputs and operational characteristics defined.
- Good documentation on the macrofunction is critical.



Function Prototype

- Example: 74382 (p. 343) 4-bit ALU with 8 different operations.


```
FUNCTION 74382(s[2..0], a[3..0], b[3..0], cin) )  
RETURNS (ovr, cn4, f[3..0])
```



AHDL Macrofunctions

- Comments/documentation first
- Then Function prototype
- Then constant and global definitions
- INCLUDE derivative is allowed.
- Includes files with extension: .inc

Graphic Description of an 8-bit ALU

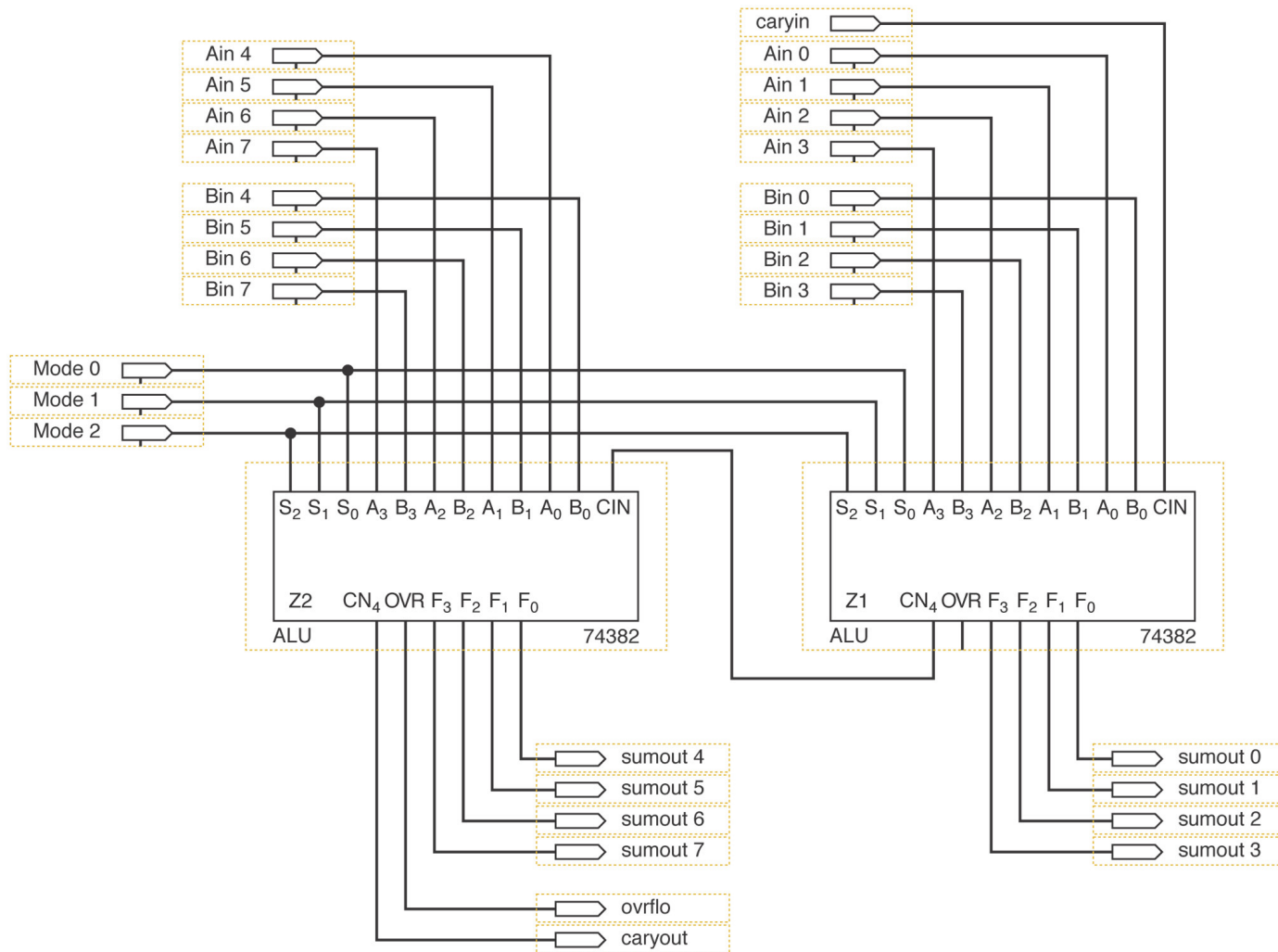

AHDL definition of an 8-bit ALU



```
1  %      8-bit ALU cascaded 74382 ALU in AHDL
2      Digital Systems 9th ed
3      MAY 22, 2002      %
4  FUNCTION 74382 (s[2..0], a[3..0], b[3..0], cin)
5  RETURNS (ovr, cn4, f[3..0]);
6
7  SUBDESIGN fig6_21
8  (
9      caryin      :INPUT;
10     mode[2..0]   :INPUT;      -- add/subtract controls
11     bin[7..0]    :INPUT;
12     ain[7..0]    :INPUT;
13     sumout[7..0] :OUTPUT;
14     caryout      :OUTPUT;
15     ovrflo       :OUTPUT;
16 )
17 VARIABLE
18     z1      :74382;
19     z2      :74382;
20 BEGIN
21     z1.s[] = mode[];      -- both ALUs in same mode
22     z1.a[] = ain[3..0];   -- low nibble A
23     z1.b[] = bin[3..0];   -- low nibble B
24     z1.cin = caryin;
25     z2.s[] = mode[];      -- both ALUs in same mode
26     z2.a[] = ain[7..4];   -- high nibble A
27     z2.b[] = bin[7..4];   -- high nibble B
28     z2.cin = z1.cn4;      -- low Cout to high Cin
29
30     caryout = z2.cn4;      -- 9th bit out
31     sumout[3..0] = z1.f[]; -- low nibble result
32     sumout[7..4] = z2.f[]; -- high nibble result
33     ovrflo = z2.ovr;
34 END;
```

Logic Operation on Bit Arrays



```
SUBDESIGN bitwise_and
( d[3..0], g[3..0]    : INPUT;
  xx[3..0]           : OUTPUT;)
BEGIN
  xx[] = d[] & g[];
END; -- Note: x is a reserved identifier in
      AHDL, use xx
```

HDL Adders





AUGEND	A ₃	A ₂	A ₁	A ₀	A
ADDEND	B ₃	B ₂	B ₁	B ₀	B
CARRYin	C ₃	C ₂	C ₁	C ₀	Cin
SUM	S ₃	S ₂	S ₁	S ₀	S

Generate sum
 $S = A \oplus [B \oplus Cin]$

AUGEND	A ₃	A ₂	A ₁	A ₀	A
ADDEND	B ₃	B ₂	B ₁	B ₀	B
CARRYin	C ₃	C ₂	C ₁	C ₀	Cin
CARRYout	C ₄	C ₃	C ₂	C ₁	Cout

 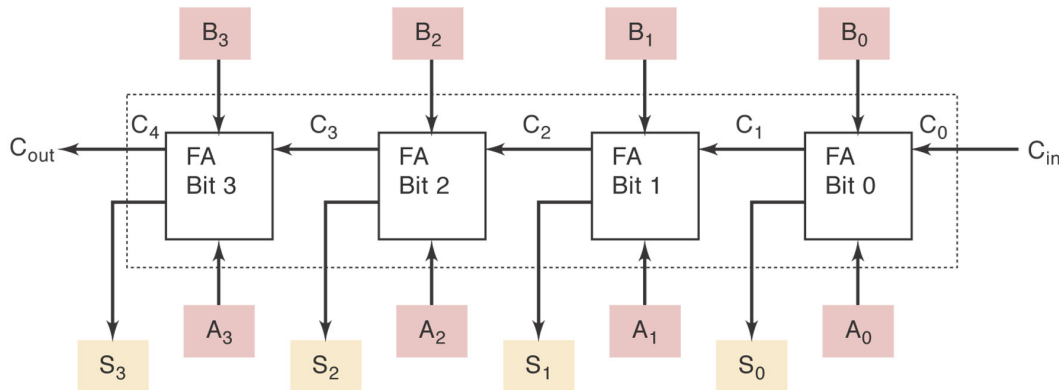Generate carry bits
 $Cout = A \cdot B + A \cdot Cin + B \cdot Cin$



Block Symbol

AHDL 4-bit Adder



```
SUBDESIGN fig6_25
(
    cin          :INPUT;      -- carry in
    a[3..0]       :INPUT;      -- augend
    b[3..0]       :INPUT;      -- addend
    s[3..0]       :OUTPUT;     -- sum
    cout         :OUTPUT;     -- carry OUT
)
VARIABLE
    c[4..0]       :NODE;      -- carry array is 5 bits long!

BEGIN
    c[0] = cin;
    s[] = a[] $ b[] $ c[3..0]; -- generate sum
    c[4..1] = (a[] & b[]) # (a[] & c[3..0]) # (b[] & c[3..0]);
    cout = c[4];              -- carry out
END;
```

N-bit Adder/Subtractor



```
1  CONSTANT number_of_bits = 8;           -- set total number of bits
2  CONSTANT n = number_of_bits - 1;       -- n is highest bit index
3
4  SUBDESIGN fig6_27
5  (
6      add          :INPUT;               -- add control
7      sub          :INPUT;               -- subtract control and LSB Carry in
8      a[n..0]      :INPUT;               -- Augend bits
9      bin[n..0]    :INPUT;               -- Addend bits
10     s[n..0]       :OUTPUT;              -- Sum bits
11     caryout       :OUTPUT;              -- MSB carry OUT
12 )
13 VARIABLE
14     c[n+1..0]     :NODE;                -- intermediate carry vector
15     b[n..0]       :NODE;                -- intermediate operand vector
16 BEGIN
17     b[] = bin[] & add # NOT bin[] & sub;
18     c[0] = sub;                               --Read the carry in to group variable
19     s[] = a[] $ b[] $ c[n..0];               --Generate the sums
20     c[n+1..1] = (a[] & b[]) # (a[] & c[n..0]) # (b[] & c[n..0]);
21     caryout = c[n+1];                       -- output the carry of the MSB.
22 END;
```

Library of Parameterized Modules



- Megafunctions: include a library of parameterized modules (LPMs)
- Offers a generic solution for the various types of logic circuits that are useful in digital systems.
- *Parameterized* means that when you instantiate a function from the library, you are specify some parameters that define certain attributes for the circuit.
- Example: LPM_ADD_SUB megafunction has a parameter LPM_WIDTH.

AHDL LPM Adder/Subtractor



```
1  INCLUDE "LPM_ADD_SUB.INC";
2
3  SUBDESIGN fig6_31
4  (
5      a[7..0], b[7..0], caryin, functn    :INPUT;
6      s[7..0], caryout, ovr               :OUTPUT;
7  )
8  VARIABLE
9      eightbit    :LPM_ADD_SUB WITH (LPM_WIDTH = 8);
10
11  BEGIN
12      eightbit.dataa[] = a[];
13      eightbit.datab[] = b[];
14      eightbit.cin     = caryin;
15      eightbit.add_sub = functn;
16      s[] = eightbit.result[];
17      caryout = eightbit.cout;
18      ovr = eightbit.overflow;
19  END;
```



Basic Counters in HDL

- Counters are constructed with FFs.
- In Chapter 5, we describe the FFs using AHDL.
- Becomes too tedious if we have to use multiple FFs.
- Describe circuits with a higher-level of abstraction.
- Will consider synchronous counters only.

Synchronous Counter Design with D FF



- Easier than using J-K FFs.
- The NEXT state of the D FF is the same as its PRESENT D input values.
- Example: Table 7-7

State Transition Description Methods



- List the PRESENT state/NEXT state table.

AHDL MOD-5 Counter



```
1  SUBDESIGN fig7_40
2  (
3      clock      :INPUT;
4      q[2..0]    :OUTPUT;
5  )
6  VARIABLE
7      count[2..0] :DFF;      --create a 3-bit register
8  BEGIN
9      count[].clk = clock;    --connect all clocks in parallel
10
11      CASE count[] IS
12  --          Present          Next
13  -----
14          WHEN 0    =>    count[].d = 1;
15          WHEN 1    =>    count[].d = 2;
16          WHEN 2    =>    count[].d = 3;
17          WHEN 3    =>    count[].d = 4;
18          WHEN 4    =>    count[].d = 0;
19          WHEN OTHERS =>    count[].d = 0;
20      END CASE;
21      q[] = count[];          -- assign register to output pins
22  END;
```


Another Version of MOD-5 Counter



```
1  SUBDESIGN fig7_41
2  (
3      clock      :INPUT;
4      q[2..0]    :OUTPUT;
5  )
6  VARIABLE
7      q[2..0]    :DFF;  -- create a 3-bit register
8  BEGIN
9      q[].clk = clock;  -- connect all clocks in parallel
10     TABLE
11         q[].q =>    q[].d;
12         0      =>    1;
13         1      =>    2;
14         2      =>    3;
15         3      =>    4;
16         4      =>    0;
17         5      =>    0;
18         6      =>    0;
19         7      =>    0;
20     END TABLE;
21 END;
```



Behavioral Description

- The behavioral level of abstraction is a way to describe circuit by describing its behavior in terms very similar to the way you might describe its operation in English.
- Deals more with the cause-and-effect relationship than with the path of data flow or wiring details.

Behavioral Description of a Counter



```
1  SUBDESIGN fig7_44
2  (
3      clock      :INPUT;
4      q[2..0]    :OUTPUT; -- declare 3-bit array of output bits
5  )
6  VARIABLE
7      count[2..0] :DFF; -- declare a register of D flip flops.
8
9  BEGIN
10     count[].clk = clock; -- connect all clocks to synchronous source
11     IF count[].q < 4 THEN -- note; count[] is the same as count[].q
12         count[].d = count[].q + 1; -- increment current value by one
13     ELSE count[].d = 0;          -- recycle to zero: force unused states to 0
14     END IF;
15     q[] = count[];              -- transfer register contents to outputs
16 END;
```

AHDL Full-Featured Counter



```
1 SUBDESIGN fig7_46
2 (
3     clock, clear, load, cntenabl, down, din[3..0]      :INPUT;
4     q[3..0], term_ct :OUTPUT;  -- declare 4-bit array of output bits
5 )
6 VARIABLE
7     count[3..0]      :DFF;          -- declare a register of D flip flops
8
9 BEGIN
10     count[].clk = clock;            -- connect all clocks to synch source
11     count[].clrn= !clear;          -- connect for asynch active HIGH clear
12     IF load THEN count[].d = din[]; -- synchronous load
13         ELSIF !cntenabl THEN count[].d = count[].q; -- hold count
14         ELSIF !down THEN count[].d = count[].q + 1; -- increment
15         ELSIF count[].d = count[].q - 1;          -- decrement
16     END IF;
17     IF ((count[] == 0) & down # (count[] == 15) & !down)& cntenabl
18     THEN      term_ct = VCC;        -- synchronous cascade output signal
19     ELSE term_ct = GND;
20     END IF;
21     q[] = count[];                  -- transfer register contents to outputs
22 END;
```

LPM Counters



```
1  INCLUDE "lpm_counter.inc";
2
3  SUBDESIGN fig7_48
4  (
5      clk, load, enable, clear, updn      :INPUT;
6      d[6..0]                             :INPUT;
7      q[6..0], tc                         :OUTPUT;
8  )
9  VARIABLE
10     counter          :LPM_COUNTER WITH
11                       (LPM_WIDTH=7, LPM_MODULUS="100");
12  BEGIN
13     counter.clock = clk;
14     counter.cnt_en = enable;
15     counter.sload = load;
16     counter.aclr = !clear;
17     counter.updown = updn;
18     counter.data[] = d[];
19     q[] = counter.q[];
20     tc = counter.cout & enable;
21  END;
```

State Machines




```
1  SUBDESIGN fig7_50
2  (  clock, start, full, timesup, dry      :INPUT;
3     water_valve, ag_mode, sp_mode       :OUTPUT;
4  )
5  VARIABLE
6  cycle:  MACHINE
7          WITH STATES (idle, fill, agitate, spin);
8  BEGIN
9  cycle.clk = clock;
10
11  CASE cycle IS
12  WHEN idle =>IF start THEN cycle = fill;
13              ELSE      cycle = idle;
14              END IF;
15  WHEN fill =>IF full THEN cycle = agitate;
16              ELSE      cycle = fill;
17              END IF;
18  WHEN agitate=> IF timesup THEN cycle = spin;
19              ELSE      cycle = agitate;
20              END IF;
21  WHEN spin => IF dry THEN cycle = idle;
22              ELSE      cycle = spin;
23              END IF;
24  WHEN OTHERS => cycle = idle;
25  END CASE;
26
27  TABLE
28  cycle      => water_valve,      ag_mode, sp_mode;
29  idle       => gnd,              gnd,    gnd;
30  fill       => vcc,              gnd,    gnd;
31  agitate    => gnd,              vcc,    gnd;
32  spin       => gnd,              gnd,    vcc;
33  END TABLE;
34  END;
```


AHDL Registers



```
1  INCLUDE "lpm_shiftreg.inc";
2
3  SUBDESIGN fig7_66
4  (
5      clock          :INPUT;
6      din[3..0]      :INPUT;
7      ld/sh          :INPUT;
8      ser_out         :OUTPUT;
9  )
10 VARIABLE
11     shiftreg :LPM_SHIFTREG WITH
12             (LPM_WIDTH = 4);
13 BEGIN
14     shiftreg.clock      = clock;
15     shiftreg.data[]     = din[];
16     shiftreg.load       = ld/sh;
17     shiftreg.shiftin    = GND;
18     ser_out             = shiftreg.shiftout;
19 END;
```


Data Transfers on Shift Registers

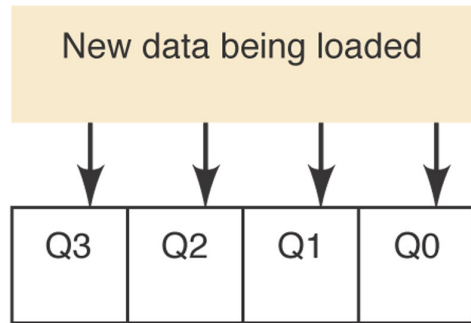


(a) Parallel load

PRESENT

NEXT

 


(b) Shift right

 

(c) Shift left

PRESENT

NEXT

 

(d) Hold data

AHDL Bidirectional Shift Register



```
1  SUBDESIGN fig7_69
2  (
3      clock      :INPUT;
4      din[3..0]  :INPUT;  -- parallel data in
5      ser_in     :INPUT;  -- serial data in from Left or Right
6      model[1..0]:INPUT;  -- MODE Select: 0=hold, 1=right, 2=left, 3=load
7      q[3..0]    :OUTPUT;
8  )
9  VARIABLE
10     ff[3..0] :DFF;      -- define register set
11 BEGIN
12     ff[].clk = clock;    -- synchronous clock
13     CASE mode[] IS
14         WHEN 0 => ff[].d    = ff[].q;          -- hold shift
15         WHEN 1 => ff[2..0].d = ff[3..1].q;      -- shift right
16                 ff[3].d    = ser_in;          -- new data from left
17         WHEN 2 => ff[3..1].d = ff[2..0].q;      -- shift left
18                 ff[0].d    = ser_in;          -- new data bit from right
19         WHEN 3 => ff[].d    = din[];           -- parallel load
20     END CASE;
21     q[] = ff[];          -- update outputs
22 END;
```



AHDL 4-Bit Ring Counter



```
1  SUBDESIGN fig7_71
2  (
3      clk          :INPUT;
4      q[3..0]      :OUTPUT;
5  )
6  VARIABLE
7      ff[3..0]     :DFF;
8      ser_in       :NODE;
9  BEGIN
10     ff[].clk = clk;
11     IF ff[3..1] == B"000" THEN ser_in = VCC;  -- self start
12     ELSE ser_in = GND;
13     END IF;
14     ff[3..0].d = (ser_in, ff[3..1].q);        -- shift right
15     q[] = ff[];
16 END;
```

AHDL Nonretriggerable One-Shot




```
1  SUBDESIGN fig7_73
2  (
3      clock, trigger, reset    : INPUT;
4      delay[3..0]              : INPUT;
5      q                        : OUTPUT;
6  )
7  VARIABLE
8      count[3..0]              : DFF;
9  BEGIN
10     count[].clk = clock;
11     count[].clrn = reset;
12     IF trigger & count[].q == b"0000" THEN
13         count[].d = delay[];
14     ELSIF count[].q == B"0000" THEN count[].d = B"0000";
15     ELSE count[].d = count[].q - 1;
16     END IF;
17     q = count[].q != B"0000"; -- make output pulse
18 END;
```

Simulation

  

Detecting Edges

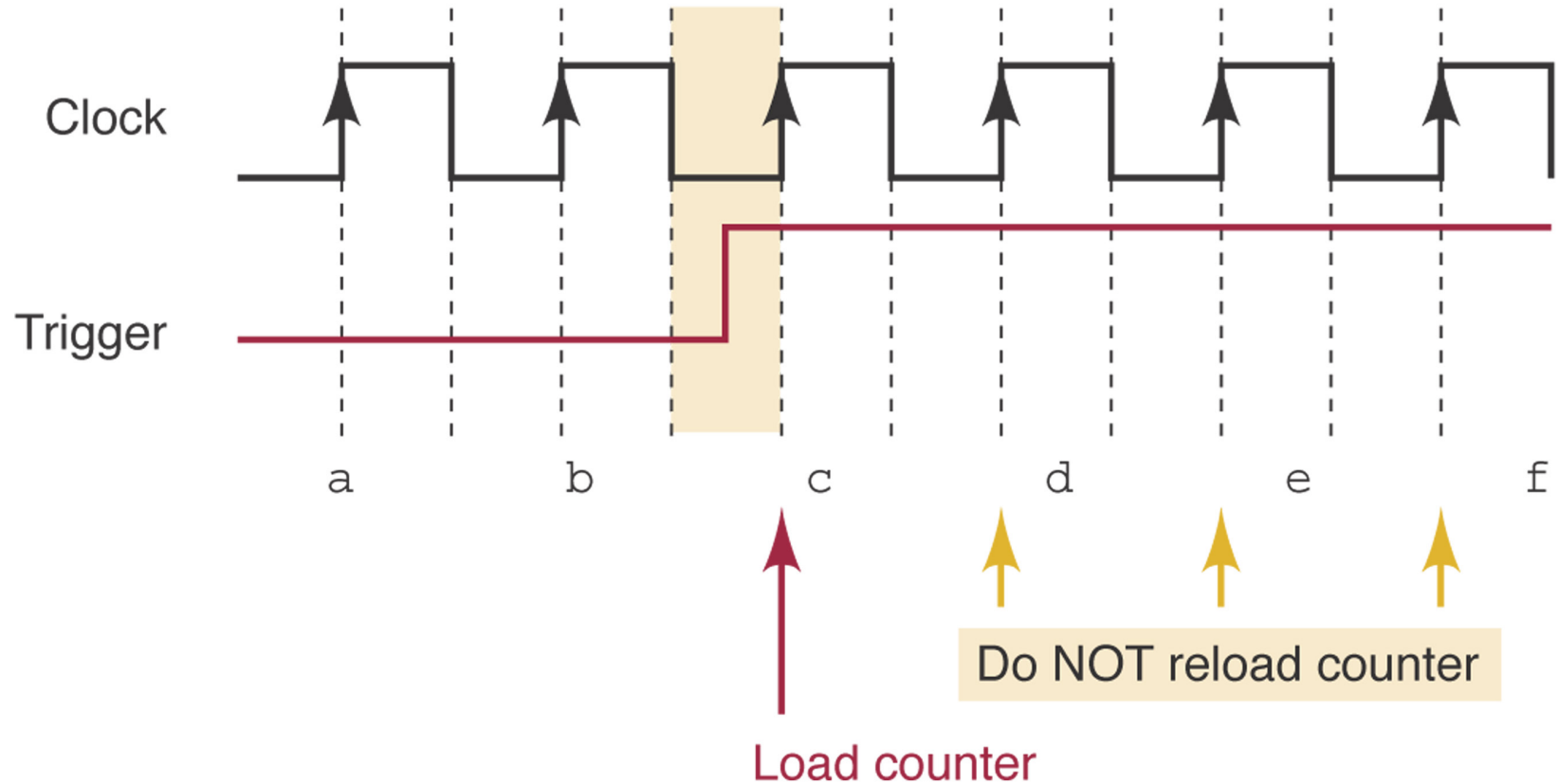

AHDL Retriggerable, Edge-Triggered One-Shot



```
1  SUBDESIGN fig7_77
2  (
3      clock, trigger, reset  : INPUT;
4      delay[3..0]           : INPUT;
5      q                     : OUTPUT;
6  )
7  VARIABLE
8      count[3..0]           : DFF;
9      trig_was              : DFF;
10 BEGIN
11     count[].clk = clock;
12     count[].clrn = reset;
13     trig_was.clk = clock;
14     trig_was.d = trigger;
15
16     IF trigger & !trig_was.q THEN
17         count[].d = delay[];
18     ELSIF count[].q == B"0000" THEN count[].d = B"0000";
19     ELSE count[].d = count[].q - 1;
20     END IF;
21     q = count[].q != B"0000";
22 END;
```