


△ Sinusoids, phasor, complex exponential, impedance

⑥ Complex number and Euler's equation

$$S = a + bj \quad j = \sqrt{-1}$$

$$= r \cdot \cos \theta + r \cdot \sin \theta \cdot j$$
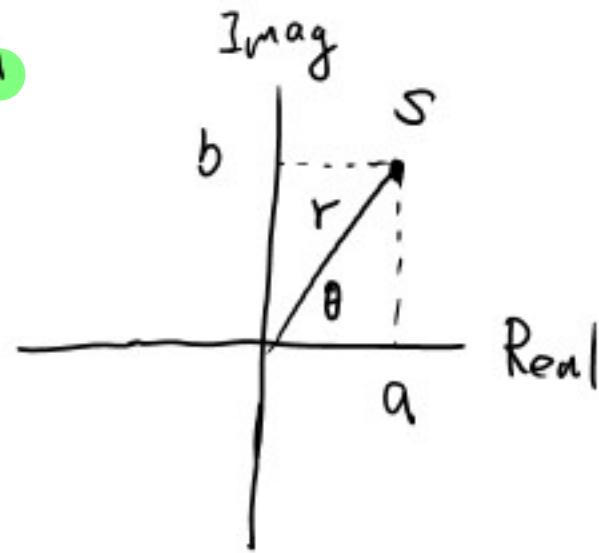
$$r = \sqrt{a^2 + b^2} \quad \theta = \tan^{-1} \frac{b}{a}$$



Euler's equation:  $e^{j\theta} = \cos \theta + j \sin \theta$  complex exponential

$$S = r \cdot e^{j\theta}$$

$$a = \operatorname{Re}\{S\}$$

$$b = \operatorname{Im}\{S\}$$

$e = 2.71828 \dots$  mathematic constant Euler's number.

base of natural logarithm 自然對數的底數

exponential function 指數函數的底數.

$$\frac{10}{a+bj} = 2.36 \cdot e^{j(45^\circ)}$$

sol ①,  $\frac{10 e^{j0^\circ}}{r \cdot e^{j\theta}} = 2.36 e^{j(45^\circ)}$

$$\frac{10}{r} = 2.36 \Rightarrow r = 4.25$$

$$e^{j(0^\circ - \theta)} = e^{j(45^\circ)} \Rightarrow \theta = -45^\circ$$

$$a = r \cdot \cos \theta = 4.25 \cos(-45^\circ) = 3, \quad b = r \cdot \sin \theta = -3$$

sol ②,  $\frac{10}{(a+bj)} \cdot \frac{(a-bj)}{(a-bj)} = \frac{10(a-bj)}{a^2+b^2} = \frac{10}{\sqrt{a^2+b^2}} \left[ \frac{a}{\sqrt{a^2+b^2}} + \frac{-b}{\sqrt{a^2+b^2}} j \right] = 2.36 \cdot e^{j(45^\circ)}$


$$(bj)(bj) = b^2 \cdot j^2 = -b^2$$

$$\frac{10}{\sqrt{a^2+b^2}} = 2.36$$

$$\frac{-b}{a} = \tan(45^\circ) = 1 \Rightarrow a = -b \quad a=3, \quad b=-3$$

⑥ AC signal model = Sinusoids
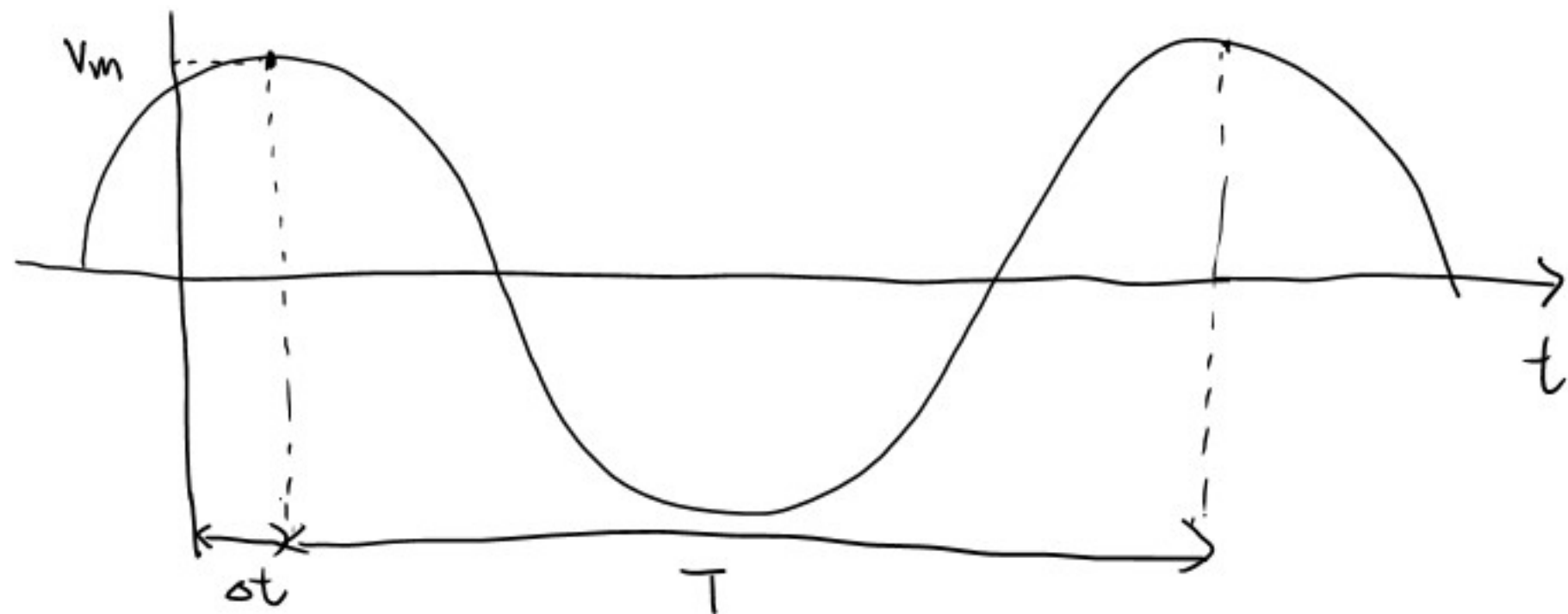
$$V_s(t) = \underline{V_m} \cos(\underline{\omega t} + \underline{\phi})$$



$V_m$  = amplitude (V, A)

$\omega$  = angular frequency ( $\frac{\text{rad}}{\text{s}}$ )

$$\omega = 2\pi \cdot f = \frac{2\pi}{T}$$

$\phi$  = phase (rad)  $\phi = \omega \cdot \Delta t = \frac{2\pi}{T} \cdot \Delta t$

- its natural, most oscillations comes in the form of sinusoids  
For example. mechanical vibrations, propagation of EM waves

- In electric system, power and communications all come in sinusoids.


- In signal processing theory, all AC signals can be expressed as linear combinations of series fundamental Sinusoids

note.  $V_m(t) = \text{Re}\{V_m \cdot e^{j(\omega t + \phi)}\} = \text{Re}\{\underline{V_m} \cdot e^{j\omega t} \cdot \underline{e^{j\phi}}\}$
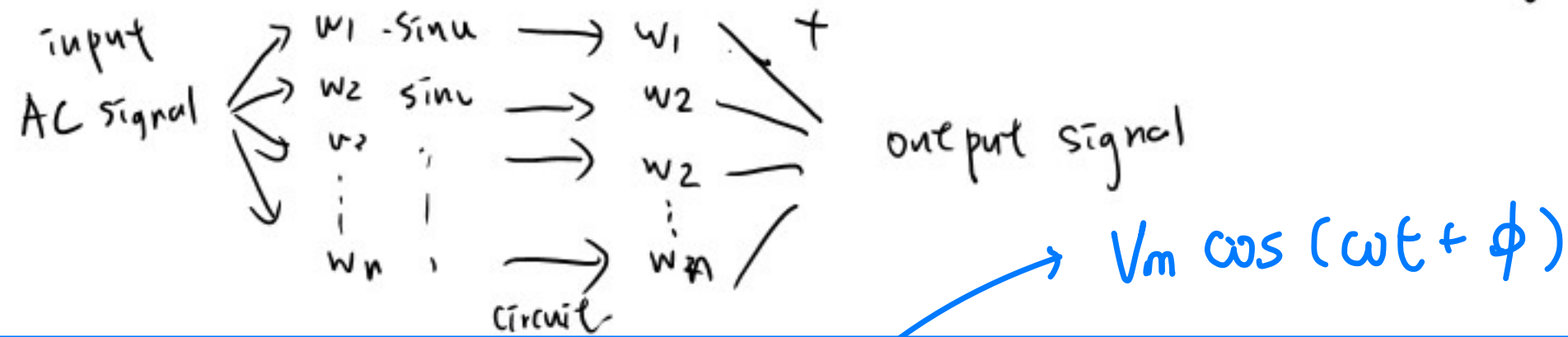
## ⑤ Sinusoids in phasor and complex exponential

- When all independent sources are sinusoids with the same frequency.

phasor and complex exponential can be used to seek for steady state response of the linear circuit



$$V_s(t) = \text{Re} \left\{ V_m \cdot e^{j\omega t} \cdot e^{j\phi} \right\} \quad \dots \rightarrow \text{time domain}$$
$$V_s = V_m \angle \phi = V_m \cdot e^{j\phi} \quad \dots \rightarrow \text{frequency domain}$$

- analyze the response of the circuit by frequency.
- simplify the calculation, avoid differential equations
- easier to conceptualize circuit design.

①  $t \rightarrow f$


- $i(t) = 4 \cos(\omega t - 80^\circ) \rightarrow I = 4 \angle (-80^\circ) = 4 e^{j(-80^\circ)}$

②  $f \rightarrow t$

- $V = 10 \angle (-140^\circ) \rightarrow v(t) = 10 \cos(\omega t - 140^\circ)$

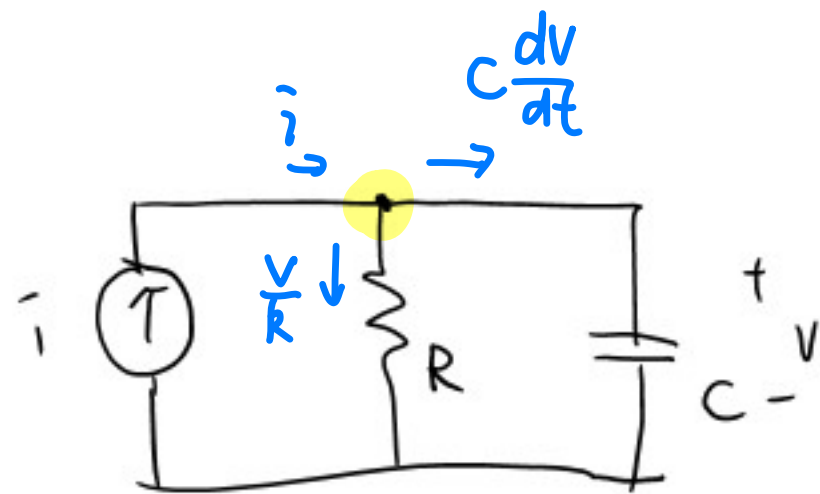- $V = 80 + 75j = \sqrt{80^2 + 75^2} \angle \left( \tan^{-1} \frac{75}{80} \right) = 109.7 \angle (43.2^\circ) = 109.7 e^{j(43.2^\circ)}$   
 $\rightarrow v(t) = 109.7 \cos(\omega t + 43.2^\circ)$






$$R = 1\Omega, \quad C = 10 \text{ mF}, \quad \omega = 100 \text{ rad/s}$$

$$i(t) = 10 \cos(\omega t) = \text{Re} \{ 10 \cdot e^{j\omega t} \}$$
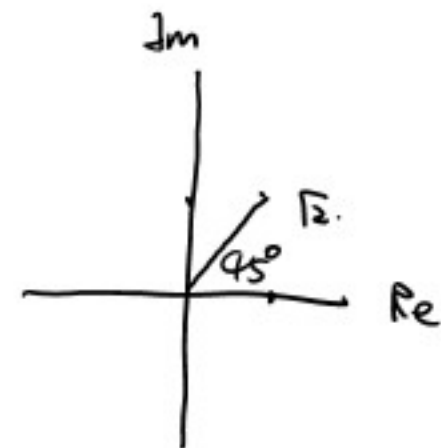
$$V(t) = A \cos(\omega t + \phi) = A \text{Re} \{ e^{j\omega t} \cdot e^{j\phi} \}$$



< Sol 1 > time domain

$$i = \frac{V}{R} + C \frac{dv}{dt} \quad (\text{KCL})$$

$$10 e^{j\omega t} = \frac{A}{R} e^{j\omega t} e^{j\phi} + C \frac{d(A e^{j\omega t} e^{j\phi})}{dt} \rightarrow 10 \underline{[e^{j\omega t}]} = \frac{A}{R} e^{j\phi} \underline{[e^{j\omega t}]} + C \cdot A e^{j\phi} (j\omega) \underline{[e^{j\omega t}]}$$

$$10 = \frac{A}{R} e^{j\phi} + C \cdot A e^{j\phi} (j\omega) \rightarrow 10 \cdot e^{j0} = A \left( \frac{1}{R} + \underline{C \cdot j \cdot \omega} \right) e^{j\phi} = A(1 + j) e^{j\phi} = A(\sqrt{2} e^{45^\circ j}) e^{j\phi}$$

$$= \sqrt{2} A e^{j(\phi + 45^\circ)} \quad 10 = \sqrt{2} A \rightarrow A = \frac{10}{\sqrt{2}} \quad \phi = -45^\circ$$

$$\underline{\underline{V(t) = \frac{10}{\sqrt{2}} \cos(100t - 45^\circ)}}$$

#

<sol 2> frequency domain

$$i = V \left( \frac{1}{R} + j \frac{1}{\omega C} \right)$$

$\omega C \rightarrow$  capacitive reactance  $X_C$

$$\Rightarrow i = V \left( \frac{1}{R} + j \omega C \right)$$

$\rightarrow$  admittance of the capacitor

$$\Rightarrow V = \frac{i}{\frac{1}{R} + j \omega C} \quad \left( \begin{array}{l} i = 10 \angle 0^\circ \\ V = A \angle \phi \end{array} \right)$$

$$= \frac{10 \angle 0^\circ}{\frac{1}{1} + j (100) (10^{-2})}$$

$$= \frac{10 \angle 0^\circ}{1 + j} = \frac{10 \angle 0^\circ}{1 + j} = \frac{10 \angle 0^\circ}{\sqrt{2} \angle 45^\circ} = \frac{10}{\sqrt{2}} \angle -45^\circ$$

$$\left( = \frac{10}{\sqrt{2}} \cos(100t - 45^\circ) \right)^\#$$


⑤ circuit element. in frequency domain ↗ max. voltage

Impedance.  $Z$  (in  $\Omega$ )  $Z = \frac{V}{I} = \frac{V_m \angle \phi}{I_m \angle \theta} = \frac{V_m e^{j\phi}}{I_m e^{j\theta}} = \frac{V_m}{I_m} e^{j(\phi-\theta)}$

$Z$  is a complex number, act as Resistor

Resistor  $v(t) = i(t) \cdot R \rightarrow Z_R = R \angle 0^\circ$

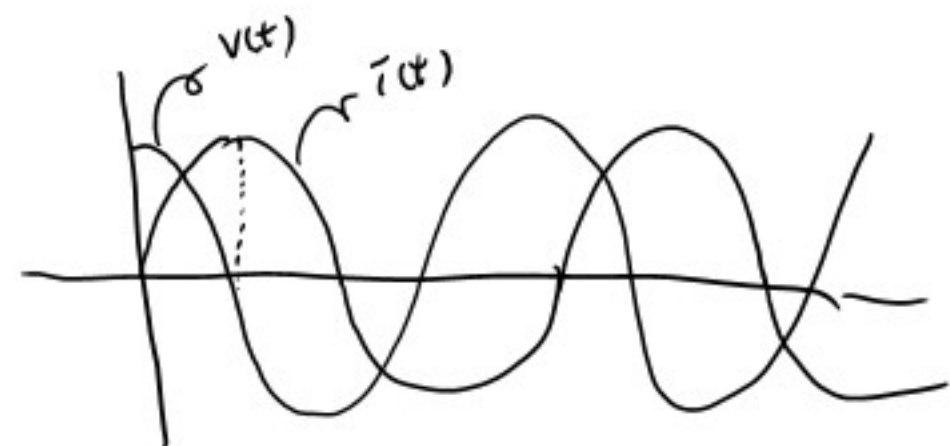capacitor  $i(t) = C \frac{dv(t)}{dt} \rightarrow V_c = V_m e^{j(\omega t + \phi)} \quad I_c = C \cdot V_m (j\omega) e^{j(\omega t + \phi)}$



$$Z_c = \frac{V_c}{I_c} = \frac{V_m e^{j(\omega t + \phi)}}{C \cdot V_m (j\omega) e^{j(\omega t + \phi)}} = \frac{1}{j\omega C} = \frac{1}{\omega C} (-j) = \frac{1}{\omega C} \angle (-90^\circ) = \frac{1}{\omega C} e^{j(-90^\circ)}$$

$f \uparrow \quad \frac{1}{\omega C} \downarrow \quad Z_c \downarrow \quad (low) \quad , \quad f \downarrow \quad \frac{1}{\omega C} \uparrow \quad Z_c \uparrow \quad (high)$





current source.

$$\bar{i}(t) = I_m \cos(\omega t + \theta)$$

$$I = I_m \cdot e^{j\theta}$$

voltage source

$$V(t) = V_m \cos(\omega t + \theta)$$

$$V = V_m e^{j\theta}$$

Resistor

$$V(t) = R \bar{i}(t)$$


$$V(\omega) = [R e^{j0^\circ}] I(\omega)$$

Capacitor

$$i(t) = C \cdot \frac{dv(t)}{dt}$$

$$V(\omega) = \frac{1}{j\omega C} \cdot I(\omega) = \left[ \frac{1}{\omega C} e^{j(-90^\circ)} \right] \cdot I(\omega)$$
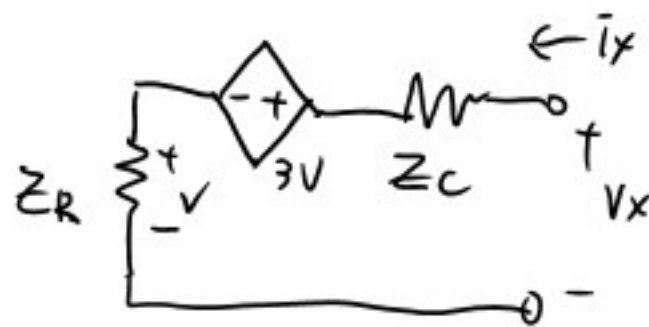
$$V_T = V_{oc} = 10 \cdot I + 3(10I) = 40I = 80 \cdot e^{j(0^\circ)}$$



$$V_x = (Z_R + Z_C) \bar{i}_x + 3(Z_R \bar{i}_x)$$



$$Z_T = \frac{V_x}{\bar{i}_x} = 4Z_R + Z_C$$

$$= 40(e^{j0^\circ}) + 10 \cdot e^{j(-90^\circ)} j$$

$$= 40 - 10j$$


$$= 41.23 e^{j(-14^\circ)}$$

dependent voltage source

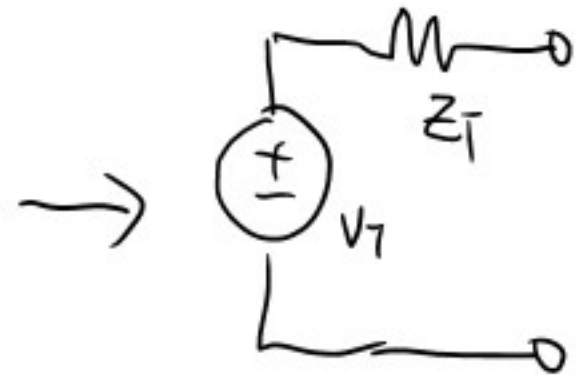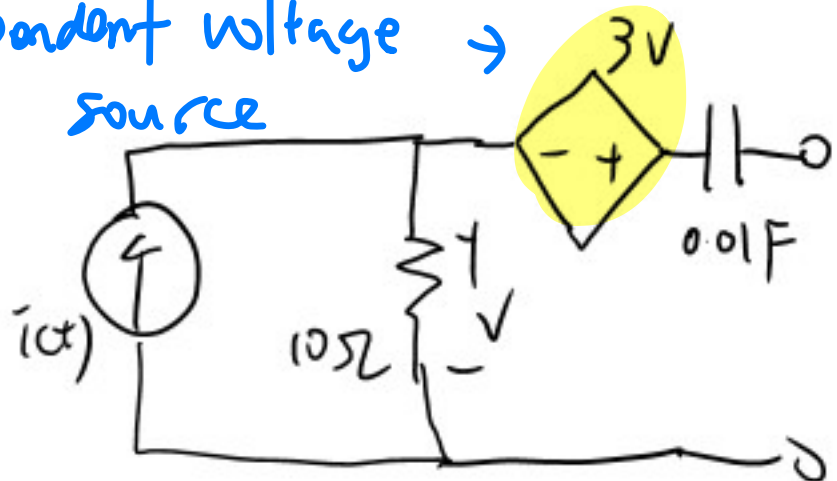

$$\bar{i}(t) = 2 \cos(10t) \rightarrow \bar{I} = 2 e^{j0^\circ}, \omega = 10$$
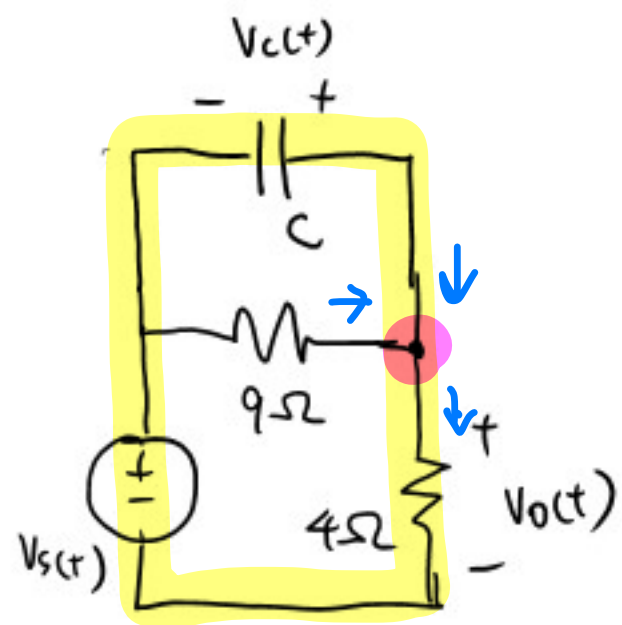
$$Z_C = \frac{1}{j(10)(0.01)} = -10j = 10 e^{j(-90^\circ)}$$



$$\omega = 2 \text{ rad/s} \quad Z_C = \frac{1}{j\omega C} = \frac{1}{2Cj}, \quad V_S = 8.93 e^{j(54^\circ)} = 5.25 + j7.22$$

$$V_o = 3.83 e^{j83^\circ} = 0.47 + j3.8j$$

sol ①

$$V_o = V_C + V_S \rightarrow V_C = (0.47 + j3.8j) - (5.25 + j7.22j) = -4.78 - j3.42j = 5.88 e^{j(216^\circ)}$$

(KVL)

$$\frac{V_o}{4} + \frac{V_C}{9} + \frac{V_C}{Z_C} = 0 \rightarrow \frac{-1}{Z_C} = \frac{9V_o + 4V_C}{36V_C} = \frac{9(0.47 + j3.8j) + 4(-4.78 - j3.42j)}{36(5.88 e^{j(216^\circ)})} = \frac{-14.89 + j20.52j}{36(5.88 e^{j(216^\circ)})}$$

(KCL)

$$V_S(t) = 8.93 \cos(2t + 54^\circ)$$

$$V_o(t) = 3.83 \cos(2t + 83^\circ)$$

$$\frac{-1}{Z_C} = -2Cj = 2C e^{j(-90^\circ)} = \frac{25.35 e^{j126^\circ}}{36 \cdot 5.88 \cdot e^{j216^\circ}} = 0.12 e^{j(-90^\circ)} \rightarrow 2C = 0.12 \rightarrow C = 0.06 \text{ F}$$

$$C = ?$$

sol ②

$$V_o = V_S \cdot \frac{4}{Z_C \parallel 9 + 4} \rightarrow \frac{V_o}{V_S} = \frac{4}{\frac{1}{2Cj + 1/9} + 4} = \frac{4(18Cj + 1)}{9 + 4(18Cj + 1)} = \frac{4 + j72Cj}{13 + j72Cj}$$

in parallel

$$\frac{3.83}{8.93} = \frac{\sqrt{4^2 + 72^2 C^2}}{\sqrt{13^2 + 72^2 C^2}} \rightarrow 0.184 = \frac{16 + (72C)^2}{169 + (72C)^2} \rightarrow (72C)^2 (0.816) = 15.1 \rightarrow C = \frac{9}{72} = 0.06 \text{ F}$$