

PEARSON



Chapter 7 – Counters and Registers

ELEVENTH EDITION

Digital Systems

Principles and Applications

Ronald J. Tocci

Monroe Community College

Neal S. Widmer

Purdue University

Gregory L. Moss

Purdue University


PEARSON

Chapter 7 Objectives

- *Selected areas covered in this chapter:*
 - Operation & characteristics of synchronous and asynchronous counters.
 - Analyzing and evaluating various types of counters.
 - Schemes used to decode different types of counters.
 - Counter circuits using different levels of abstraction in HDL.
 - Operation of various types of IC registers.
 - Shift registers and shift register counters using HDL.
 - Troubleshooting techniques used for combinational logic systems to troubleshoot sequential logic systems.

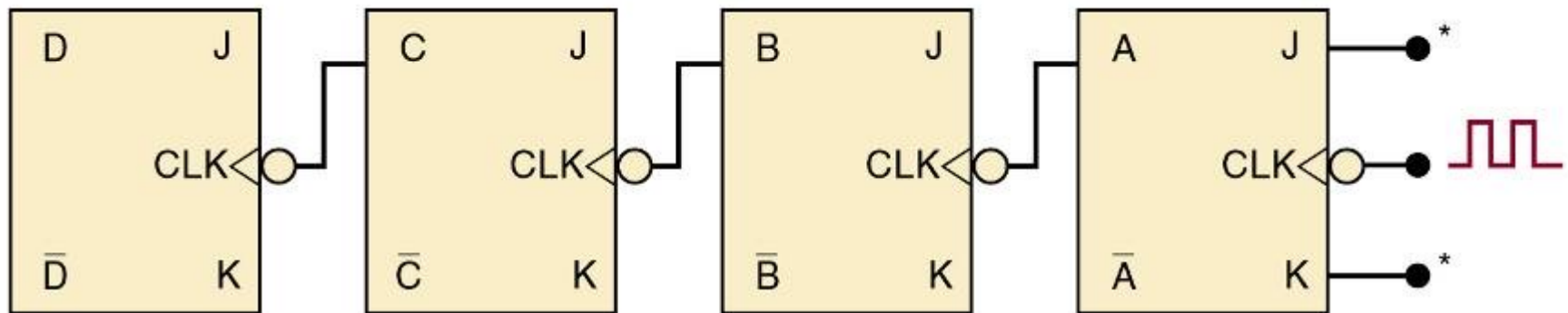7-1 Asynchronous (Ripple) Counters


- Review of four bit counter operation:
 - Clock is applied only *CLK* input to FF *A*.
 - *J* & *K* are HIGH in all FFs.
 - Output of FF *A* is *CLK* of FF *B*, etc.
 - FF outputs *D*, *C*, *B*, and *A*, are a 4-bit binary number with *D* as the MSB.



*All *J* and *K* inputs
assumed to be 1.

 7-1 Asynchronous (Ripple) Counters


- Review of four bit counter operation:
 - After the NGT of the 15th clock pulse, the counter FFs are *recycled* back to 0000.



An asynchronous counter—state is *not* changed in exact synchronism with the clock.

 7-1 Asynchronous (Ripple) Counters – MOD Number


- MOD number is equal to the number of states the counter goes through before recycling.



Adding FFs will increase the MOD number.

 7-1 Asynchronous (Ripple) Counters – MOD Number

- Frequency division – each FF will have an output frequency of 1/2 the input.



Output frequency of the last counter FF will be clock frequency divided by MOD of the counter.

7-1 Asynchronous (Ripple) Counters – Signal Flow

- Schematics are normally drawn from left to right.
 - Counters will be drawn from right to left so that the MSB and LSB appear in the appropriate positions.

7-2 Propagation Delay in Ripple Counters


- Ripple counters are simple—requiring the fewest components to produce a given operation.
 - Cumulative propagation delay can cause problems at high frequencies.
- If the period between input pulses is made longer than the total propagation delay of the counter, problems can be avoided
 - For proper operation: $T_{\text{clock}} \geq N \times t_{\text{pd}}$
 - Maximum frequency: $F_{\text{max}} = 1/N \times t_{\text{pd}}$

7-2 Propagation Delay in Ripple Counters

- Asynchronous counters are not useful at very high frequencies—especially for counters with large numbers of bits.
 - Erroneous count patterns can generate **glitches**
 - Signals produced by systems using asynchronous counters.

 7-3 Synchronous (Parallel) Counters


- In **synchronous** or **parallel counters**, all FFs are triggered simultaneously (in parallel) by the clock.



Synchronous counters can operate at much higher frequencies than asynchronous counters.

 7-3 Synchronous (Parallel) Counters

- Each FF has J & K inputs which are HIGH only when outputs of all lower-order FFs are HIGH.



The total propagation delay will be the *same* for *any* number of FFs.


7-3 Synchronous (Parallel) Counters

For this circuit to count properly, on a given NGT of the clock, only those FF that are supposed to toggle on that NGT should have $J = K = 1$ when NGT occurs.

| Count | D | C | B | A |
|-------|---|------|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 2 | 0 | 0 | 1 | 0 |
| 3 | 0 | 0 | 1 | 1 |
| 4 | 0 | 1 | 0 | 0 |
| 5 | 0 | 1 | 0 | 1 |
| 6 | 0 | 1 | 1 | 0 |
| 7 | 0 | 1 | 1 | 1 |
| 8 | 1 | 0 | 0 | 0 |
| 9 | 1 | 0 | 0 | 1 |
| 10 | 1 | 0 | 1 | 0 |
| 11 | 1 | 0 | 1 | 1 |
| 12 | 1 | 1 | 0 | 0 |
| 13 | 1 | 1 | 0 | 1 |
| 14 | 1 | 1 | 1 | 0 |
| 15 | 1 | 1 | 1 | 1 |
| 0 | 0 | 0 | 0 | 0 |
| . | . | . | . | . |
| . | . | . | . | . |
| . | . | etc. | . | . |

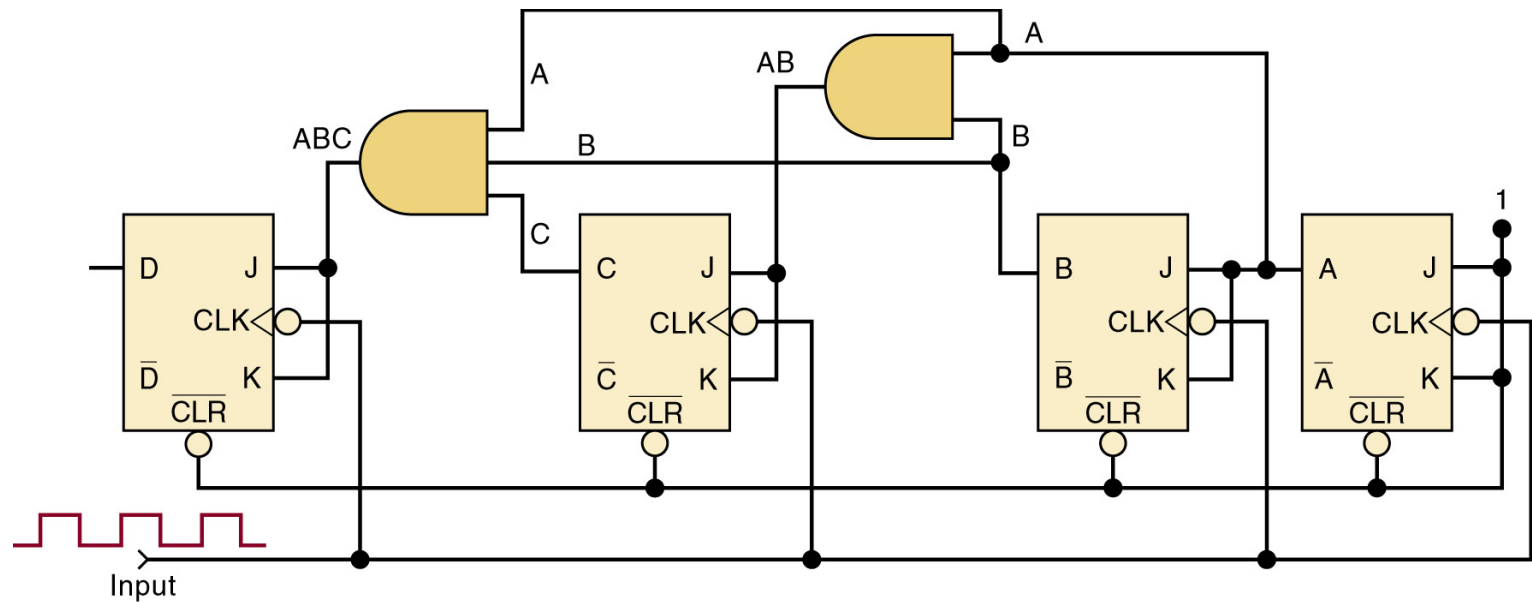
7-4 Counters with MOD Number $\leq 2^N$

- The basic synchronous counter shown is limited to MOD numbers that are equal to 2^N .
 - Where N is the number of FFs.



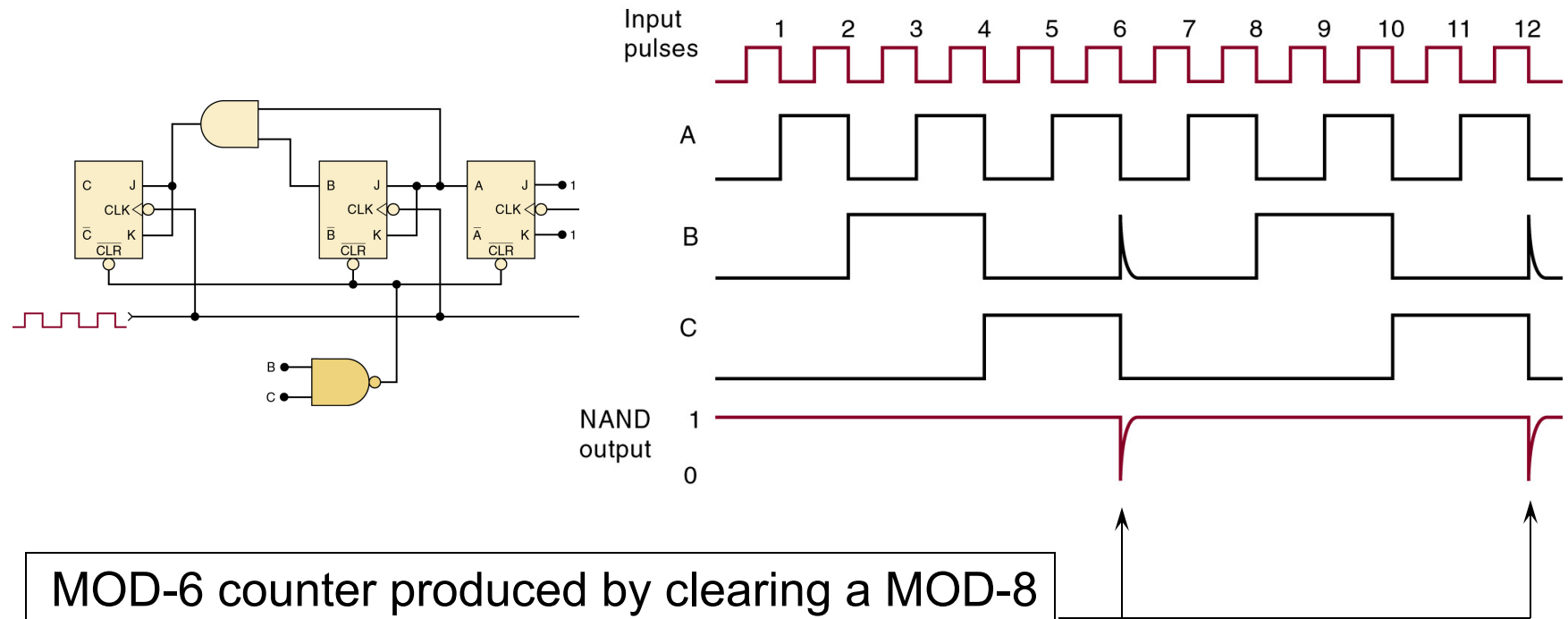7-4 Counters with MOD Number $< 2^N$

- The basic counter can be modified to produce MOD numbers *less than* 2^N .
 - By allowing the counter to *skip states* that are normally part of the counting sequence.




MOD-6 counter produced by clearing a MOD-8 counter when a count of six (110) occurs.

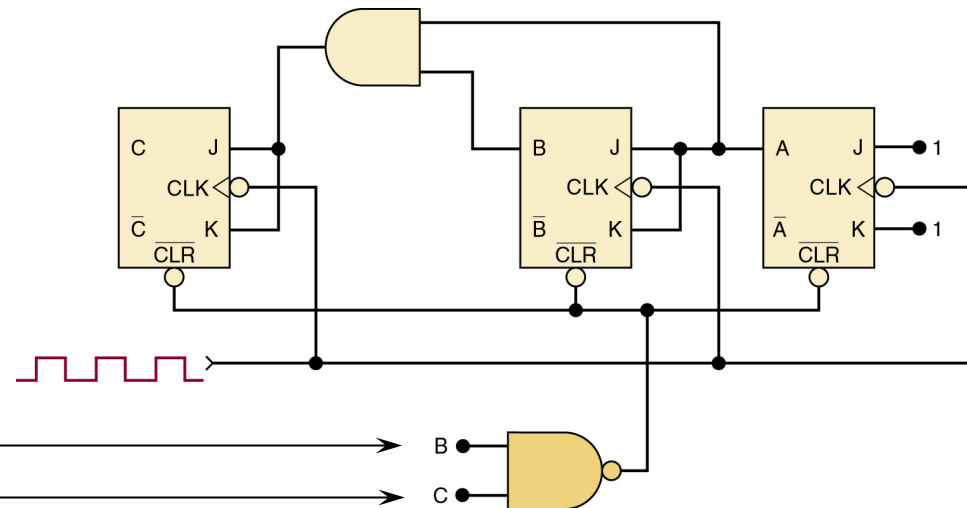7-4 Counters with MOD Number $\leq 2^N$


- Changing the MOD number.
 - Find the smallest MOD required so that 2^N is less than or equal to the requirement.
 - Connect a **NAND** gate to the asynchronous CLEAR inputs of all FFs.

Determine which FFs are **HIGH** at the desired count and connect the outputs of these FFs to the **NAND** gate inputs.



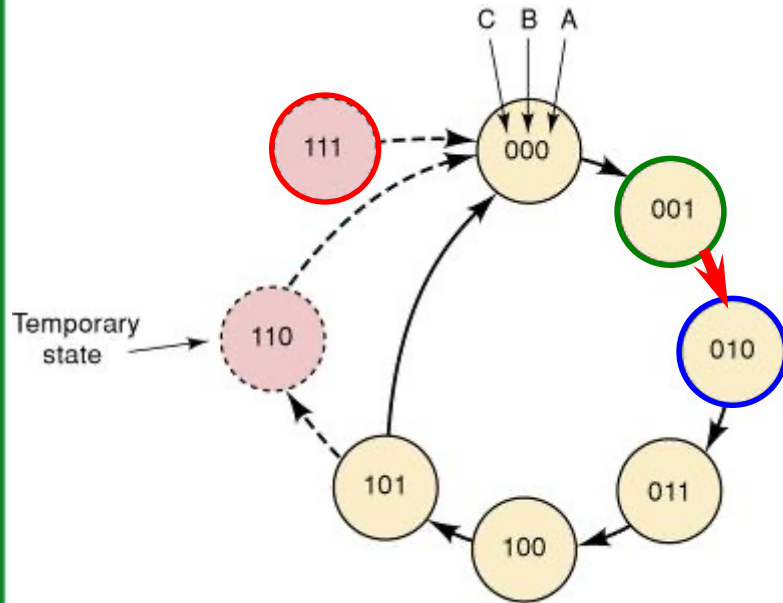7-4 Counters with MOD Number $< 2^N$

State transition diagram for the MOD-6 counter




Each circle represents one of the possible counter states.


Arrows indicate how one state changes to another—in response to an input clock pulse.

There is no arrow to the 111 state as the counter can *never advance* to that state.

 The 111 state *can* occur on power-up when the FFs come up in random states.




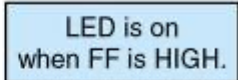**The MOD-6 counter
lights the LED on
HIGH output.**



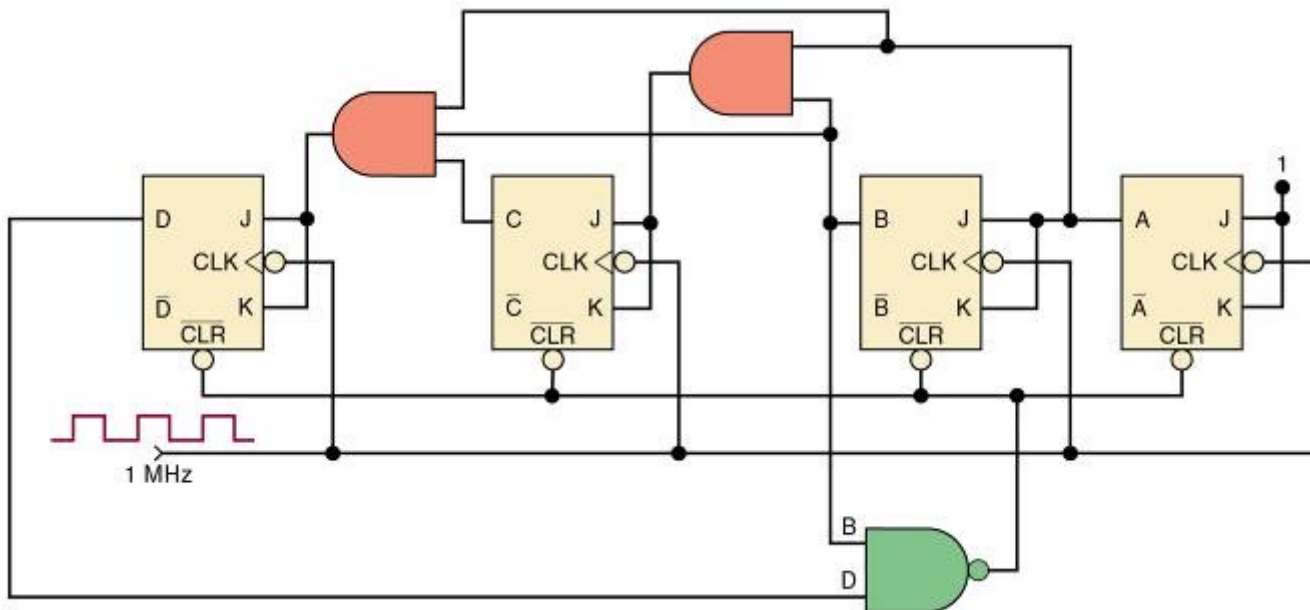7-4 Counters with MOD Number $< 2^N$


- Decade counters are widely used for counting events, and displaying results in decimal form.
 - A decade counter is any counter with 10 distinct states, regardless of the sequence.
 - A BCD counter is a decade counter that counts from binary 0000 to 1001.



**Any MOD-10
counter is a
decade
counter.**

7-4 Counters with MOD Number $< 2^N$


Mod-60 Counter

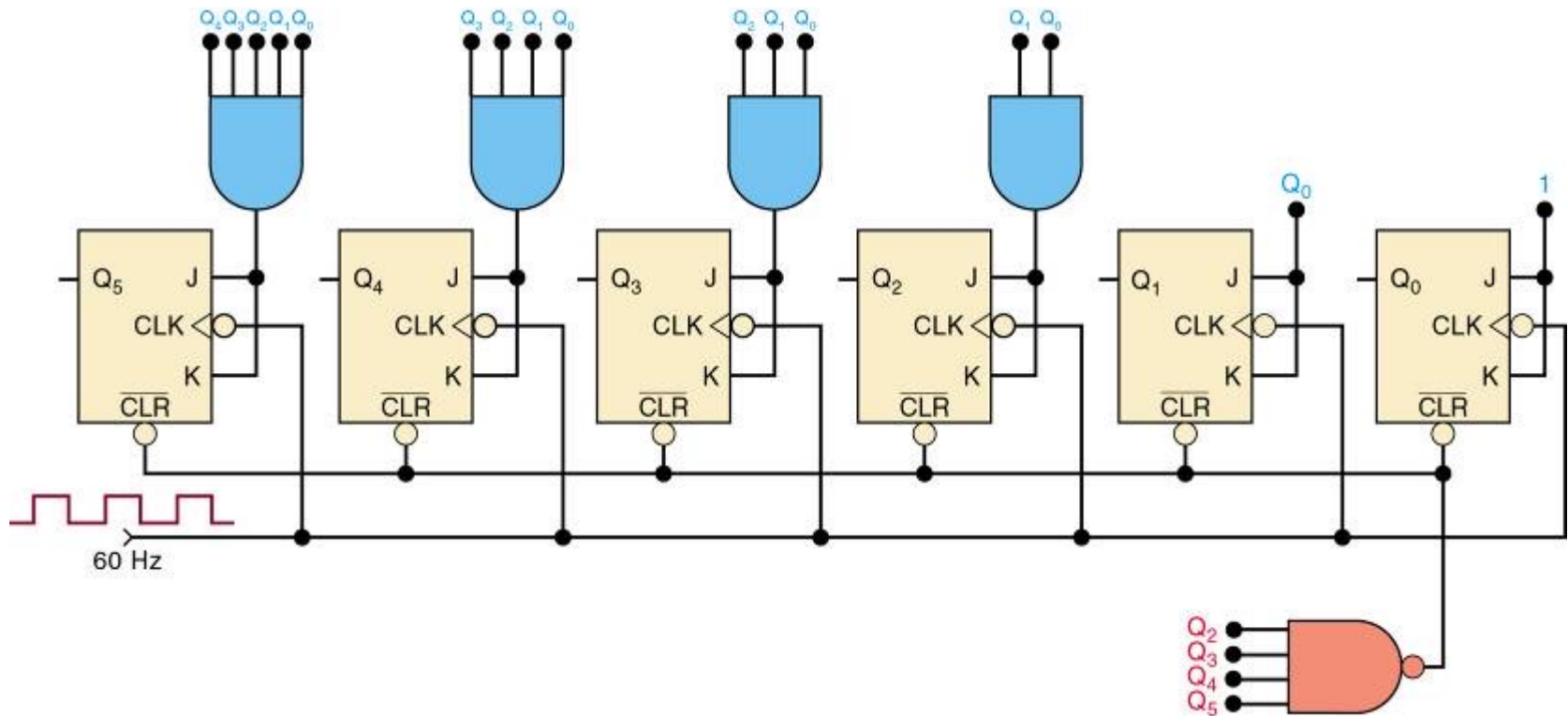

 7-5 Synchronous Down and Up/Down Counters


- A synchronous **down counter** is constructed in a similar manner to an up counter.
 - It uses the inverted FF outputs to control the higher-order J, K inputs.

**Synchronous, MOD-16,
down counter and
output waveforms.**



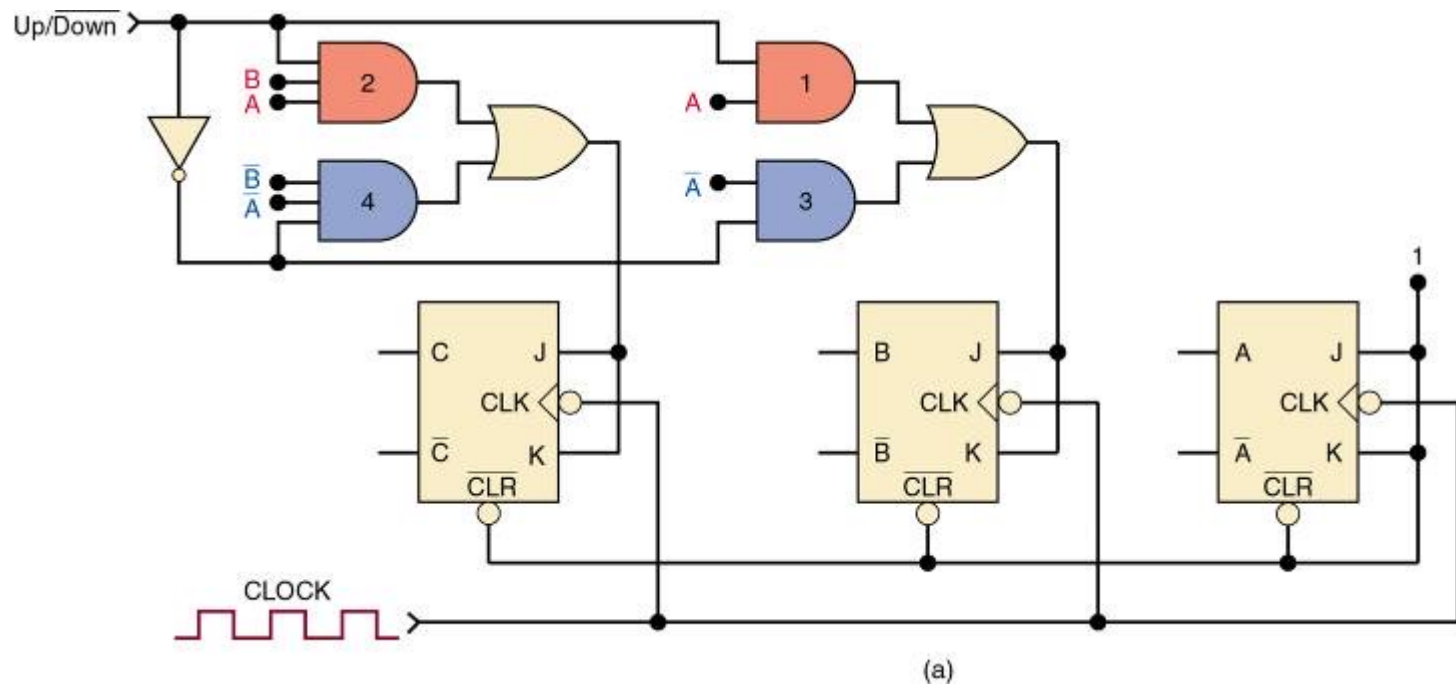
7-5 Synchronous Down and Up/Down Counters

- In a parallel **up/down counter**, the control input controls the values fed to the J and K inputs of the successive FFs.
 - The *normal* FF outputs or the *inverted* FF outputs.



 7-5 Synchronous Down and Up/Down Counters


- For the first five clock pulses, $\text{Up}/\overline{\text{Down}} = 1$.
 - The counter counts up.
- For the last five pulses, $\text{Up}/\overline{\text{Down}} = 0$.
 - The counter counts down.



 
7-5 Synchronous Down and Up/Down Counters

- Note that there are two arrows leaving each state's bubble—a **conditional transition**.


The next state for this counter is dependent upon the logic level applied to the control input.



 - ## Synchronous counter with asynchronous parallel load.



7-7 IC Asynchronous Counters

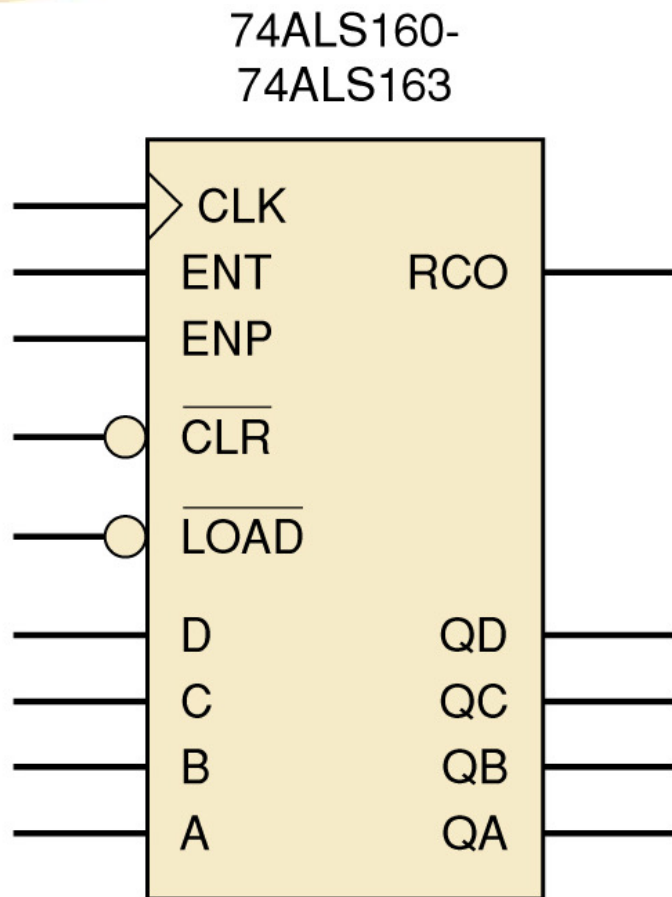

Counter contains four FFs.


FFs are triggered by a PGT at the *CLK* input.

Active-low asynchronous CLEAR input.

Can be preset to any value by applying an active-low LOAD input to the *A*, *B*, *C*, and *D* inputs .

| Part Number | Modulus |
|-------------|---------|
| 74ALS160 | 10 |
| 74ALS161 | 16 |
| 74ALS162 | 10 |
| 74ALS163 | 16 |

7-7 IC Asynchronous Counters

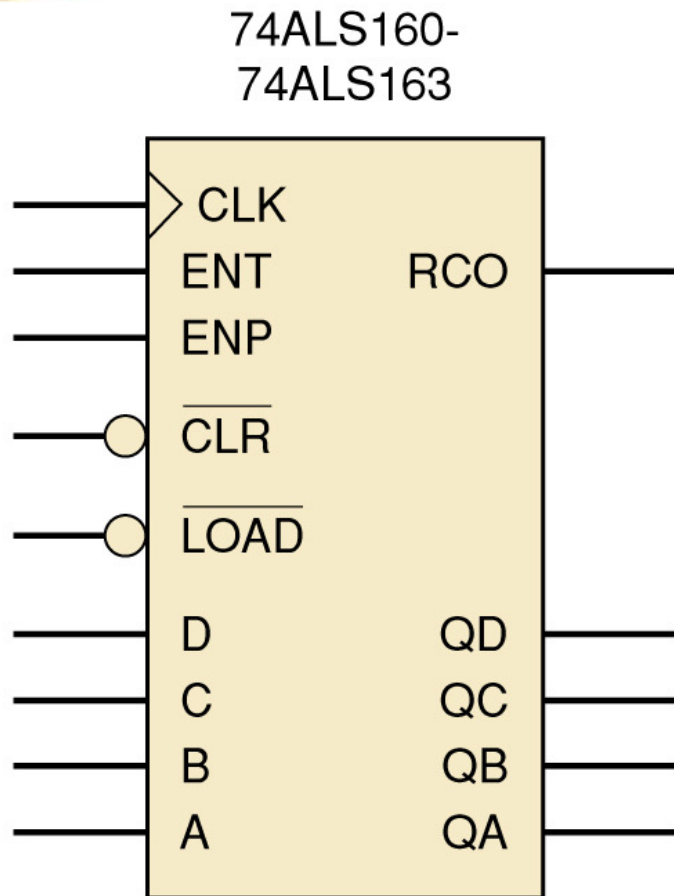

This series of IC counter chips has one more output pin—*RCO*—an active-HIGH output is to detect (*decode*) the last or terminal state of the counter.


Very useful in connecting two or more counter chips in a multistage arrangement to create larger counters.

TTL 74ALS160 – 74ALS163 Function Table

| $\overline{\text{CLR}}$ | $\overline{\text{LOAD}}$ | ENP | ENT | CLK | Function | Part Numbers |
|-------------------------|--------------------------|-----|-----|------------|---------------|---------------------|
| L | X | X | X | X | Asynch. Clear | 74ALS160 & 74ALS161 |
| L | X | X | X | \uparrow | Synchr. Clear | 74ALS162 & 74ALS163 |
| H | L | X | X | \uparrow | Synchr. Load | All |
| H | H | H | H | \uparrow | Count up | All |
| H | H | L | X | X | No change | All |
| H | H | X | L | X | No change | All |

 7-7 IC Asynchronous Counters

**74ALS190 and 74ALS191 series ICs
are recycling, four-bit counters.**




| Part Number | Modulus |
|-------------|---------|
| 74ALS190 | 10 |
| 74ALS191 | 16 |

74ALS190-74ALS191 Function Table

| LOAD | CTEN | D/U | CLK | Function |
|------|------|-----|-----|--------------|
| L | X | X | X | Asynch. Load |
| H | L | L | ↑ | Count up |
| H | L | H | ↑ | Count down |
| H | H | X | X | No change |

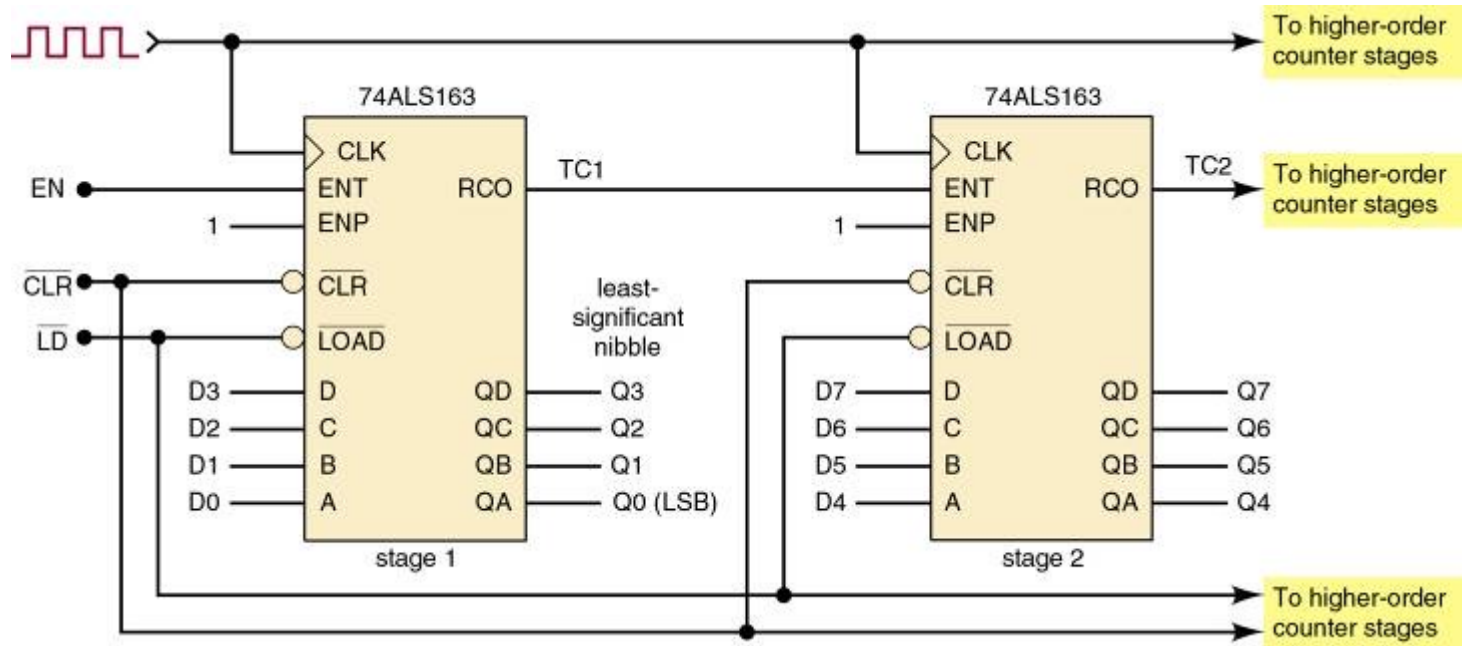7-7 IC Asynchronous Counters


- Many standard IC counters have been designed to make it easy to connect multiple chips to create circuits with a higher counting range.
 - A **multistage** or **cascading** arrangement.



74ALS163s in a two-stage arrangement to extend the maximum counting range.

 7-8 Decoding a Counter


- Digital counters are often used in applications where the count represented by FF states must somehow be determined or displayed.
 - One of the simplest means for displaying contents of a counter is connecting the FF output to an LED.



**Active-HIGH
decoder output.**


The LED method becomes inconvenient as the size (number of bits) of the counter increases. It is much harder to decode the display mentally.

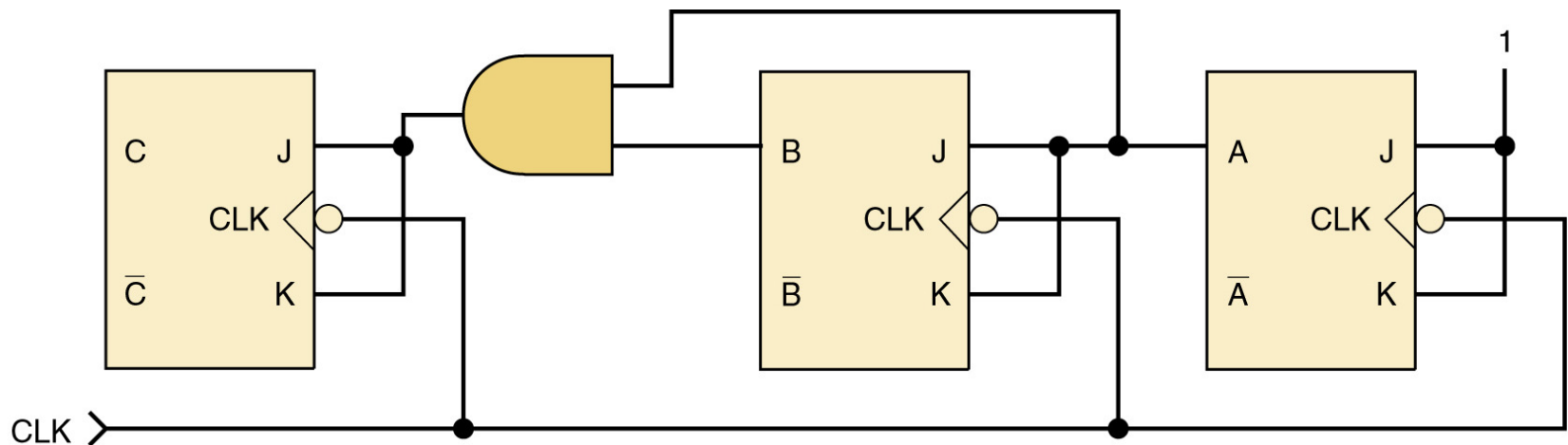- The active-HIGH decoder shown can be used to light an LED representing each decimal number 0 to 7.



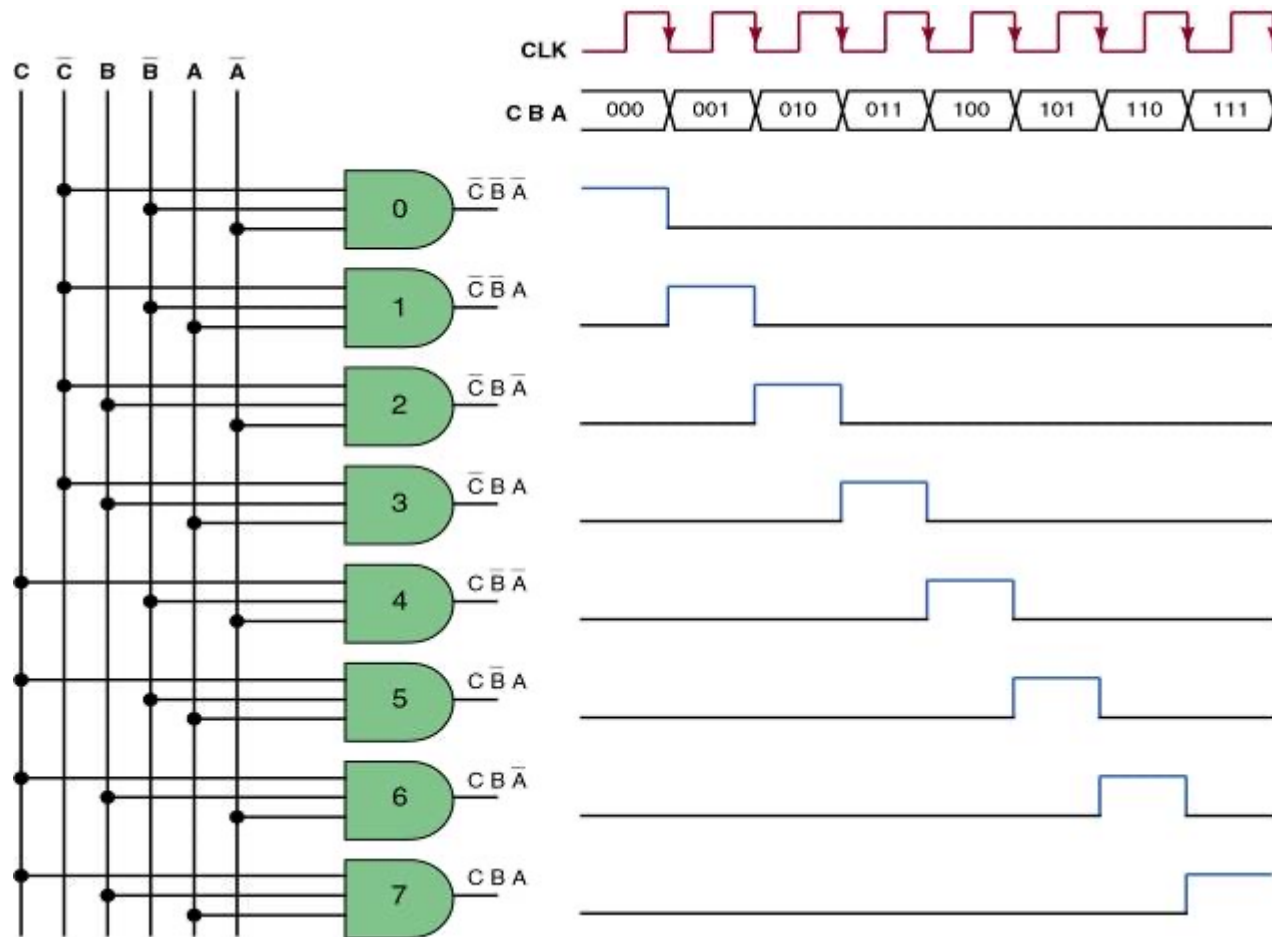7-8 Decoding a Counter

- Decoding** is the conversion of a binary output to a decimal value—a form immediately recognized.




MOD-8
Active-HIGH
decoder output.

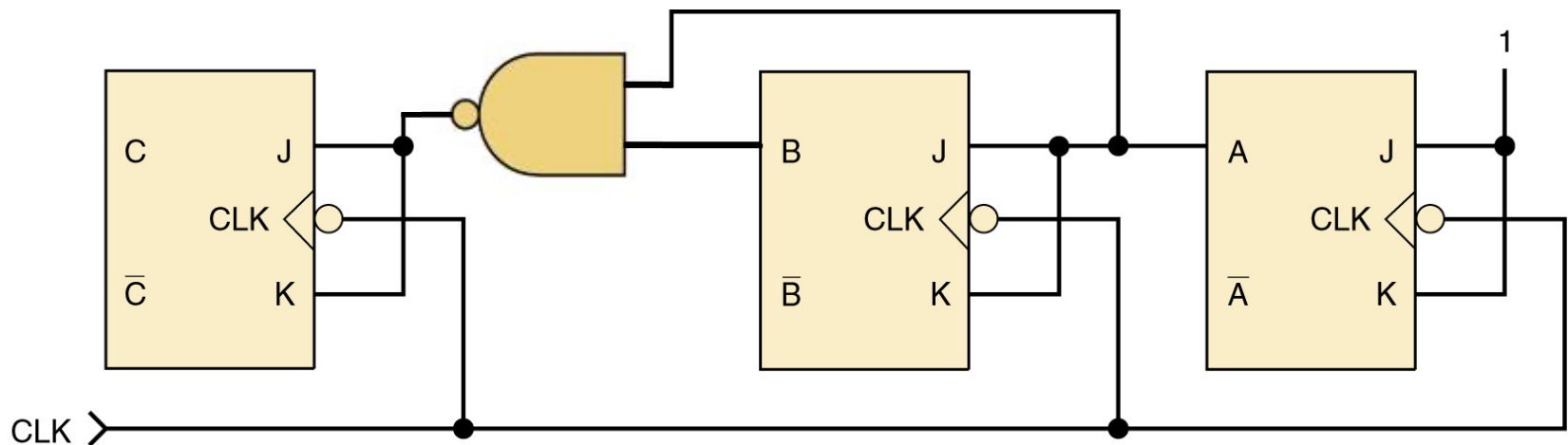7-8 Decoding a Counter

The active-HIGH decoder shown can be changed to an active-LOW type.


Active-LOW decoding is obtained by replacing the **AND** gates with **NAND** gates.




The decoder outputs now produce a normally HIGH signal, which goes LOW only when the number being decoded occurs.

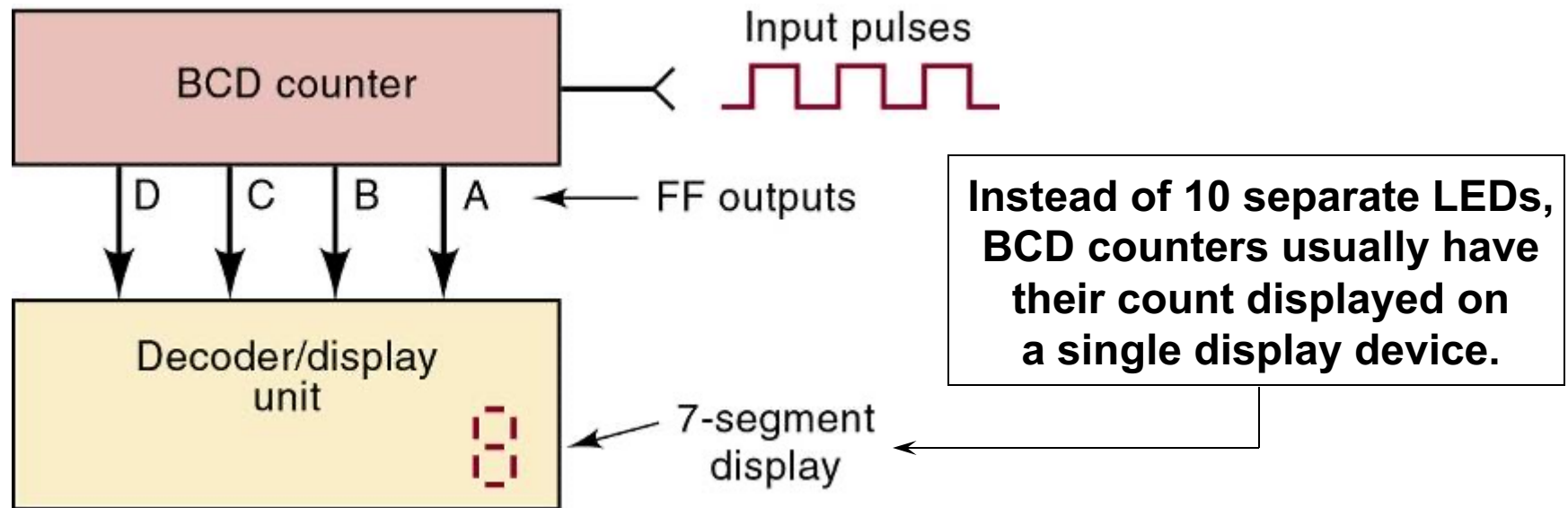7-8 Decoding a Counter

- A BCD counter has 10 states, decoded to provide 10 outputs corresponding to decimal digits 0 – 9.
 - Represented by the states of the counter FFs.
 - The 10 outputs can control 10 individual indicator LEDs for a visual display.




Synchronous up counter.

 

Control input expressions.

$$\begin{aligned} J_C &= A \cdot B \\ K_C &= C \\ J_B &= K_B = \overline{A} \\ J_A &= K_A = \overline{C} \end{aligned}$$

 - Synchronous counters can be custom-designed to generate any desired count sequence.



Synchronous up-counter.

$$\begin{aligned} J_C &= A \cdot B \\ K_C &= C \\ J_B &= K_B = \overline{A} \\ J_A &= K_A = \overline{C} \end{aligned}$$

Control input expressions.



7-9 Analyzing Synchronous Counters

- Analyze counter designs of this type by predicting FF control inputs for each state of the counter.
 - A **PRESENT state/NEXT state table** is very useful for this purpose.

| PRESENT State | | | Control Inputs | | | | | | NEXT State | | |
|---------------|---|---|----------------|----------------|----------------|----------------|----------------|----------------|------------|---|---|
| C | B | A | J _C | K _C | J _B | K _B | J _A | K _A | C | B | A |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 1 |

  7-9 Analyzing Synchronous Counters

Synchronous up counter state transition diagram and waveform.




Highlighted information indicates this counter design is self-correcting.

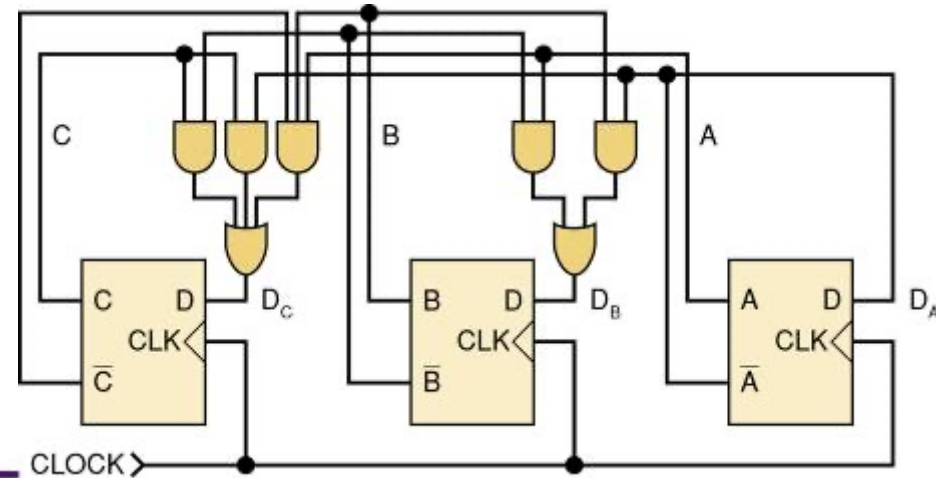7-9 Analyzing Synchronous Counters

Synchronous counter built using D-type FFs.

Control circuitry will typically be more complex than an equivalent JK-type counter,



| PRESENT State | | | Control Inputs | | | NEXT State | | |
|---------------|---|---|----------------|----------------|----------------|------------|---|---|
| C | B | A | D _C | D _B | D _A | C | B | A |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |


The number of synchronous inputs to control is reduced by half

7-10 Synchronous Counter Design

- Common design method using J-K flip-flops in a synchronous counter configuration.
 - Determine the desired number of bits (FFs) and the desired counting sequence.
 - Draw the state transition diagram showing *all* possible states—including those not part of the desired counting sequence.
 - Use the state transition diagram to set up a table that lists *all* PRESENT states and their NEXT states.
 - Add a column for each *J* and *K* input & indicate levels required to produce transition to the NEXT state.
 - Design the logic circuits to generate levels required at each input, and implement the final expressions.

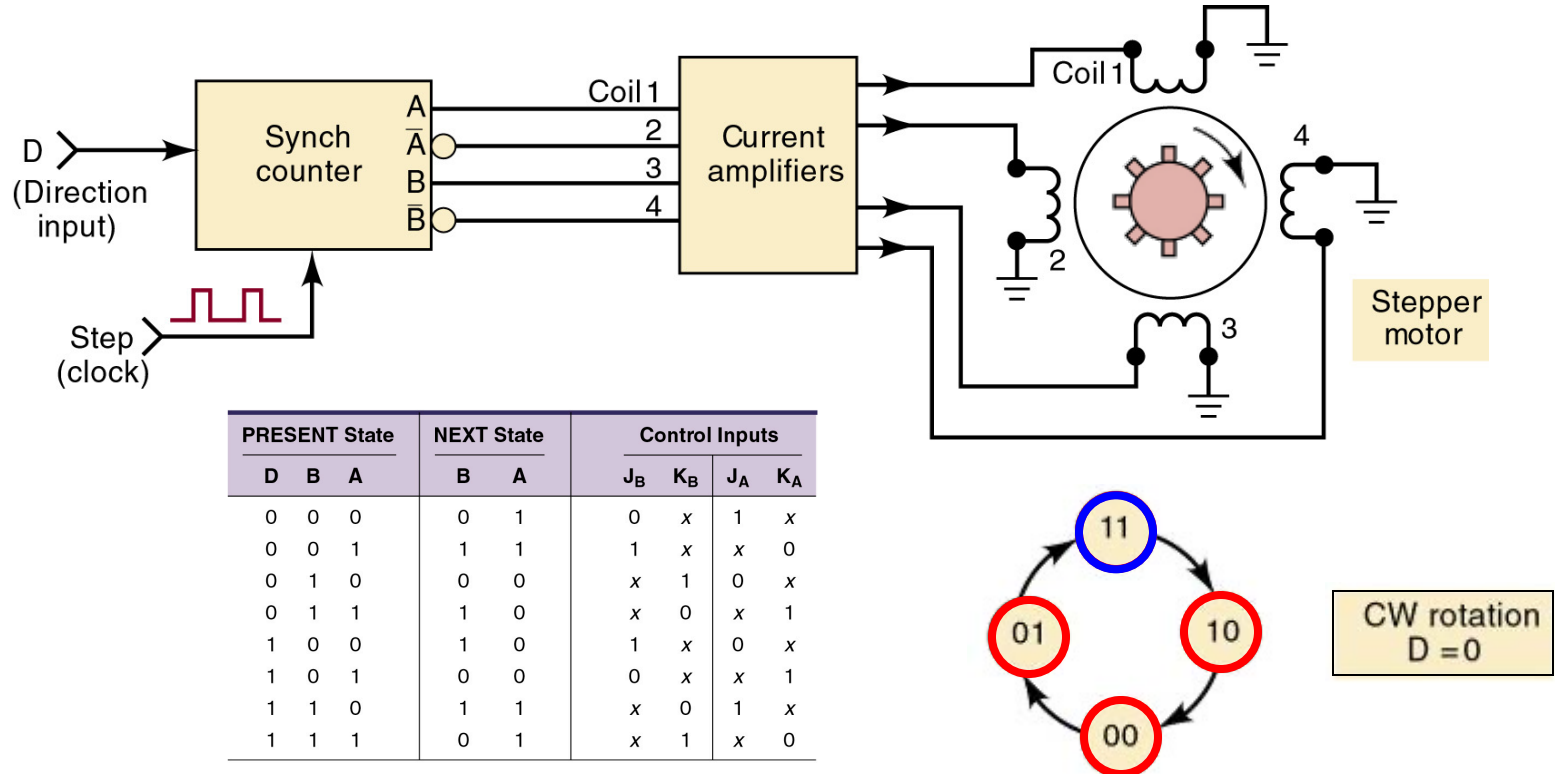
7-10 Synchronous Counter Design

- A stepper motor rotates in steps, not continuous motion—typically 15 degrees per step.
 - A practical application of synchronous counter design.
 - Reversible, depending on output level.



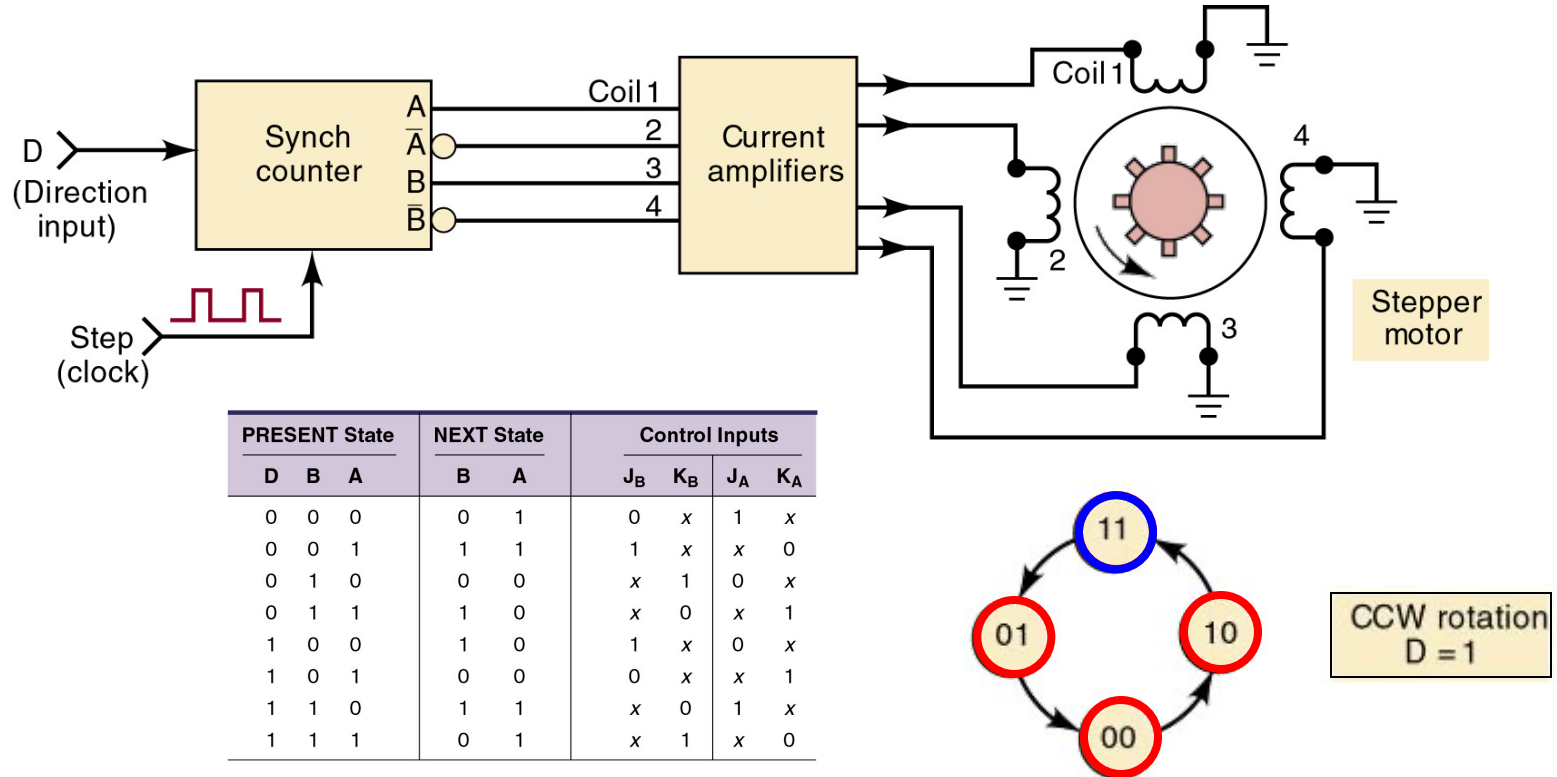
7-10 Synchronous Counter Design

- A stepper motor rotates in steps, not continuous motion—typically 15 degrees per step.
 - A practical application of synchronous counter design.
 - Reversible, depending on output level.



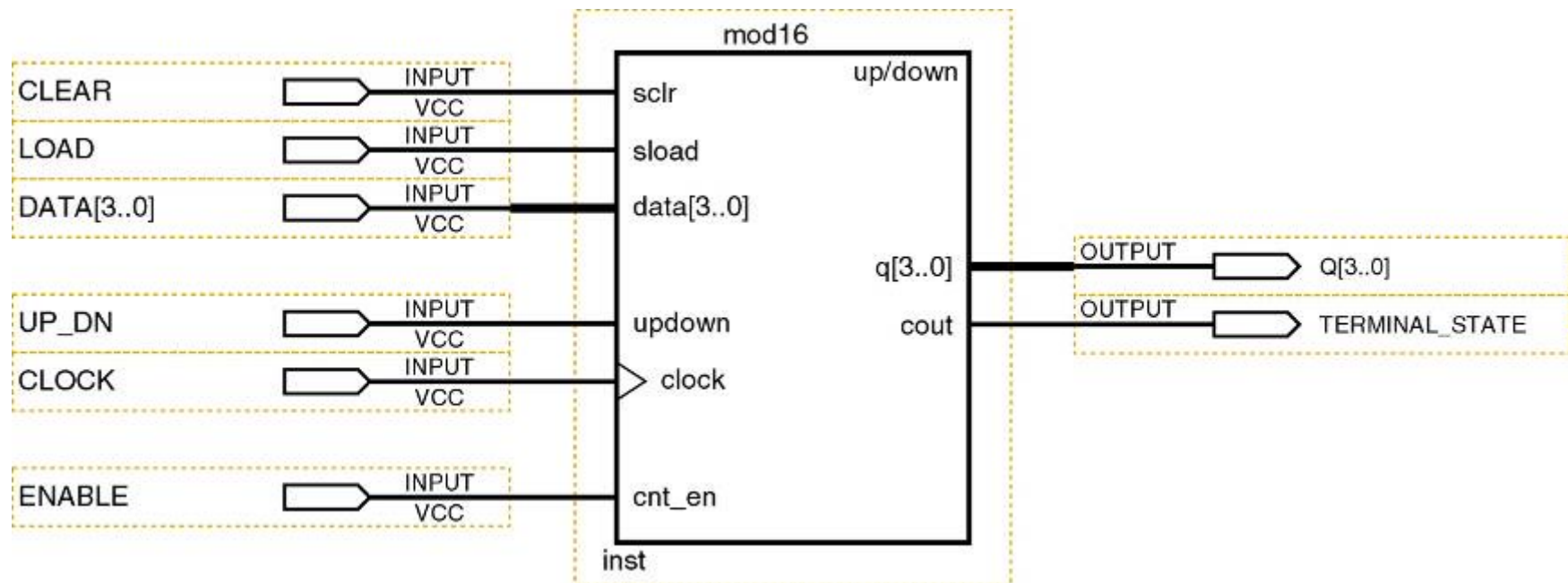7-11 Altera Library Functions for Counters


- The Quartus Block Editor can program a PLD with any counter using flip-flops and gates.
 - These macro-functions are in the *maxplus2* library.




A full-featured MOD-16 up/down counter.

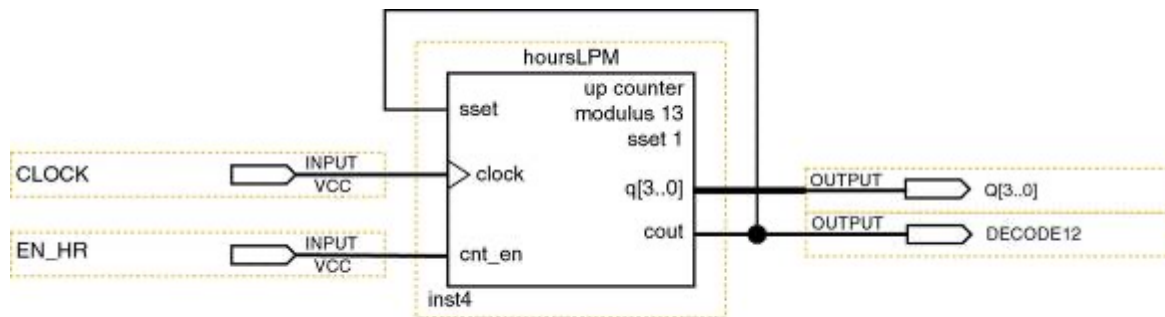7-11 Altera Library Functions for Counters

Digital clock hours counter—block diagram, MegaWizard settings & simulation results.



| | | |
|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| How wide should the 'q' output bus be? <input type="text" value="4"/> bits | Which type of counter do you want? <input type="radio"/> Plain binary <input checked="" type="radio"/> Modulus, with a count modulus of <input type="text" value="13"/> | Do you want any optional inputs? <div>Synchronous inputs <input type="checkbox"/> Clear <input type="checkbox"/> Load <input checked="" type="checkbox"/> Set <div><input type="radio"/> Set to all 1's <input checked="" type="radio"/> Set to <input type="text" value="1"/></div></div> <div>Asynchronous inputs <input type="checkbox"/> Clear <input type="checkbox"/> Load <input type="checkbox"/> Set <div><input checked="" type="radio"/> Set to all 1's <input type="radio"/> Set to 0</div></div> |
| What should the counter direction be? <input checked="" type="radio"/> Up only <input type="radio"/> Down only <input type="radio"/> Create an 'updown' input port to allow me to do both [1 counts up; 0 counts down] | Do you want any optional additional ports? <div><input type="checkbox"/> Clock Enable <input checked="" type="checkbox"/> Count Enable</div> <div><input type="checkbox"/> Carry-in <input checked="" type="checkbox"/> Carry-out</div> | |

 


7-12 HDL Counters

- Methods to describe counter circuits using HDL primarily use synchronous techniques.
 - All flip-flops update simultaneously in response to the same clock event.
 - All bits in a count sequence go from their PRESENT state to their prescribed NEXT state simultaneously,
- State Transition Description Methods
 - The PRESENTstate/NEXT state table is the equivalent of the truth table.

 7-12 HDL Counters

- State descriptions in AHDL
 - The first important step is to declare the counter output pins properly— as a bit array.



7-12 HDL Counters

- State descriptions in AHDL

```
1  SUBDESIGN fig7_43
2  (
3      clock      :INPUT;
4      q[2..0]    :OUTPUT;  -- declare 3-bit array of output bits
5  )
6  VARIABLE
7      count[2..0] :DFF; -- declare a register of D flip flops.
8
9  BEGIN
10     count[].clk = clock; -- connect all clocks to synchronous source
11     IF count[].q < 4 THEN -- note; count[] is the same as count[].q
12         count[].d = count[].q + 1; -- increment current value by one
13     ELSE count[].d = 0;           -- recycle to zero: force unused states to 0
14     END IF;
15     q[] = count[].q;             -- transfer register contents to outputs
16 END;
```

The current state of the counter is evaluated (*count[].q*) on line 11, and if it is less than the highest desired count value, it uses the description *count[].d count.q + 1* (line 12).

7-12 HDL Counters

- State descriptions in AHDL

```
1  SUBDESIGN fig7_43
2  (
3      clock      :INPUT;
4      q[2..0]    :OUTPUT;  -- declare 3-bit array of output bits
5  )
6  VARIABLE
7      count[2..0] :DFF; -- declare a register of D flip flops.
8
9  BEGIN
10     count[].clk = clock; -- connect all clocks to synchronous source
11     IF count[].q < 4 THEN -- note; count[] is the same as count[].q
12         count[].d = count[].q + 1; -- increment current value by one
13     ELSE count[].d = 0;           -- recycle to zero: force unused states to 0
14     END IF;
15     q[] = count[].q;             -- transfer register contents to outputs
16 END;
```




When the counter has reached the highest desired state (or higher), the *IF* statement test will be false, resulting in a NEXT-state input value of zero, which recycles the counter.

7-13 Wiring HDL Modules Together

- Designing large digital systems is much easier if the system is subdivided into smaller, manageable modules that are interconnected.
 - The essence of the concept of **hierarchical design**.
- Consider a recycling, MOD-100 BCD counter with a synchronous clear.
 - Creating a MOD-10 BCD counter module, cascading synchronously two of these in a higher-level design file is the easiest way to do this.

  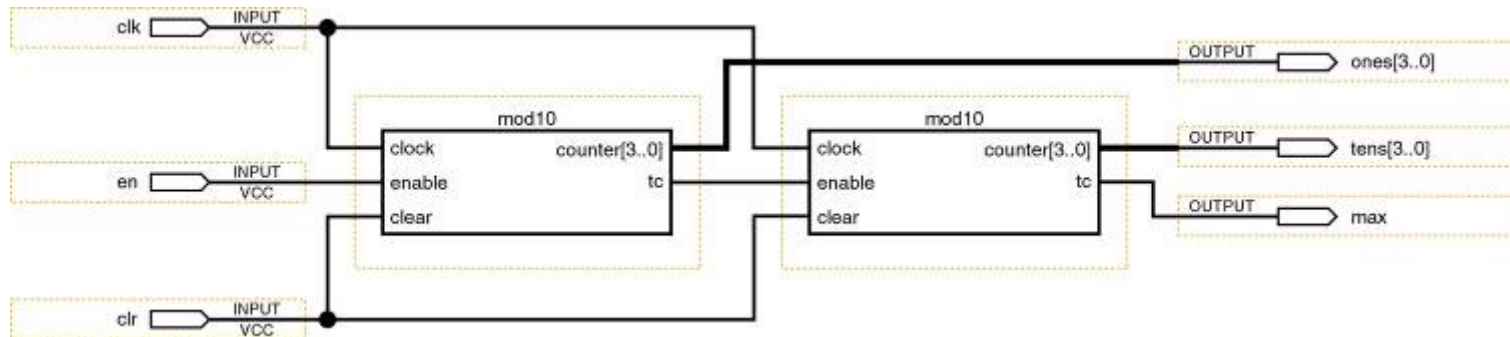7-13 Wiring HDL Modules Together

Block diagram design and simulation results for MOD-100 BCD counter design.



7-13 Wiring HDL Modules Together

- Decoding the AHDL MOD-5 counter


```
1  SUBDESIGN fig7_40
2  (
3      clock      :INPUT;
4      q[2..0]    :OUTPUT;
5  )
6  VARIABLE
7      count[2..0] :DFF;      --create a 3-bit register
8  BEGIN
9      count[].clk = clock;    --connect all clocks in parallel
10
11      CASE count[] IS
12  --          Present      Next
13  -----
14          WHEN 0    =>    count[].d = 1;
15          WHEN 1    =>    count[].d = 2;
16          WHEN 2    =>    count[].d = 3;
17          WHEN 3    =>    count[].d = 4;
18          WHEN 4    =>    count[].d = 0;
19          WHEN OTHERS =>    count[].d = 0;
20      END CASE;
21      q[] = count[];          -- assign register to output pins
22  END;
```


7-14 State Machines

- The term **state machine** refers to a circuit that sequences through a set of predetermined states.
 - Controlled by a clock and other input signals.
- The term *counter* is used for sequential circuits that have a regular numeric count sequence.
 - The things that are counted are actually clock pulses.
 - But the pulses may represent many kinds of events.
- The general distinction between the two terms:
 - A *counter* is commonly used to *count* events,
 - A *state machine* is commonly used to *control* events.

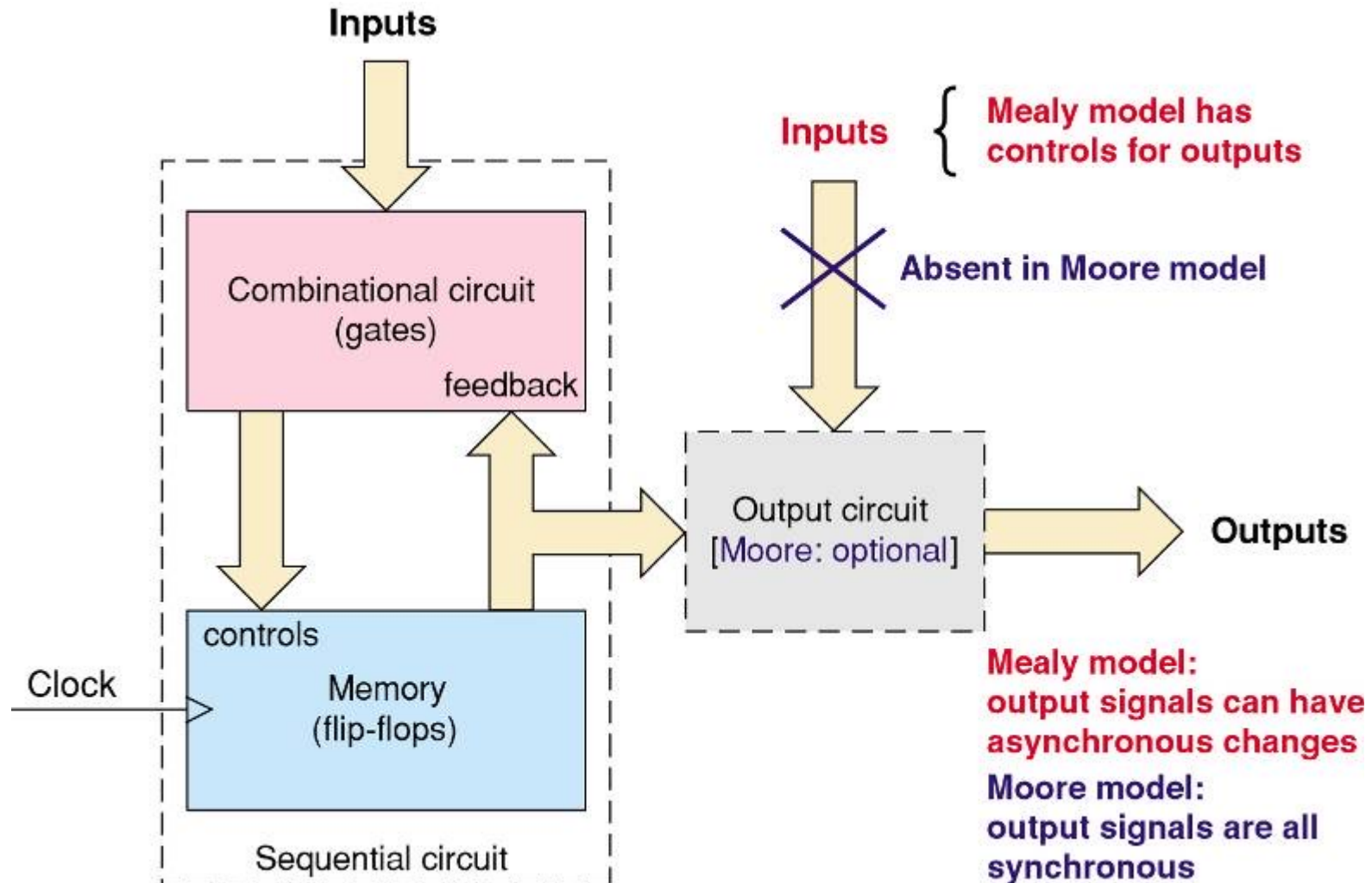
7-14 State Machines

Block diagram for counters and state machines.



7-14 State Machines

Traffic light controller state machine.

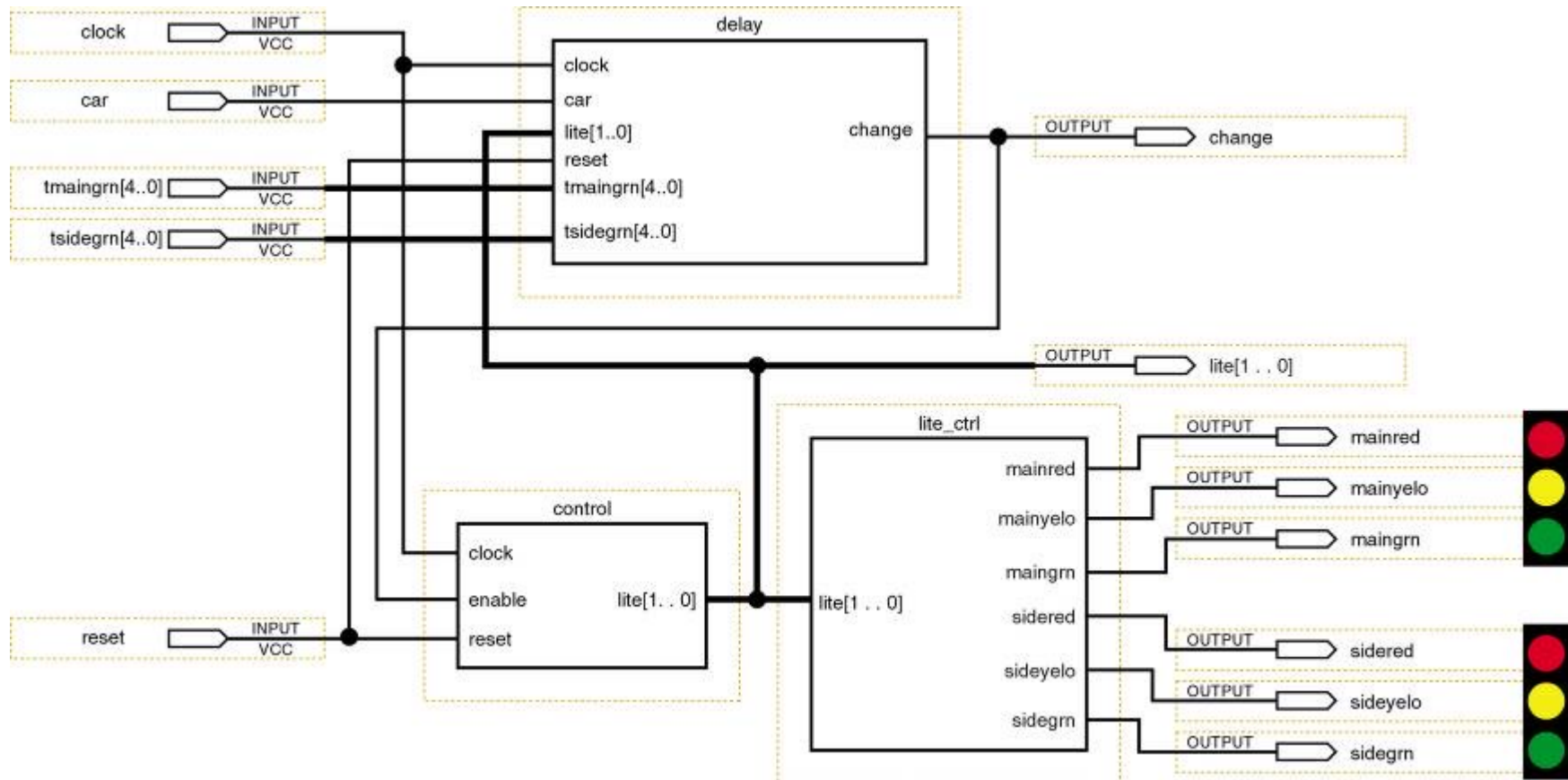


7-15 Register Data Transfer

- The various types of registers can be classified according to...
 - The manner in which data can be entered into the register for storage.
 - The manner in which data are outputted from the register.
- Serial data flow through a register is generally called *shifting*—either to the left or to the right.
 - Serial output data fed back to the input of the same register is called a *data rotate*.
- Parallel inputting of data is often described as a *register load*.


74ALS174/74HC174

Parallel in/parallel out (PIPO)

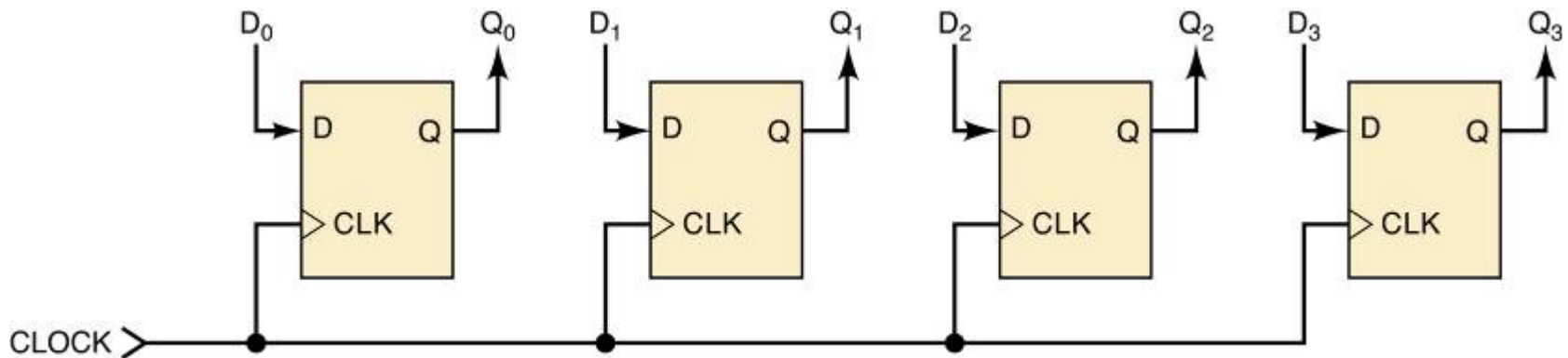


A group of flip-flops that can store multiple bits simultaneously and in which all bits of the stored binary value are directly available.

74ALS174/74HC174

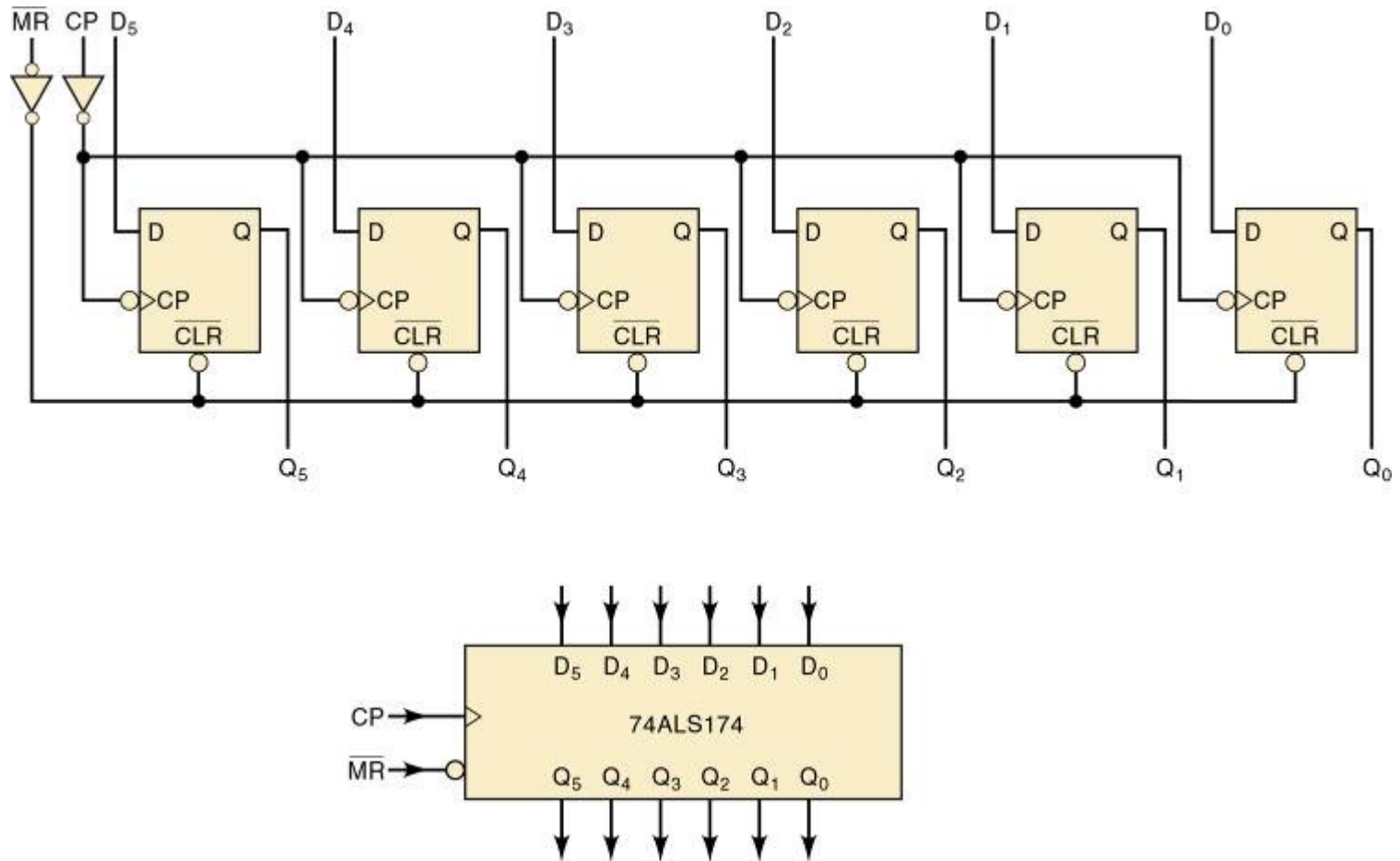


 74ALS166/74HC166 Serial in/serial out (SISO)




Data loaded one bit at a time moves one bit at a time, with each clock pulse through the flip-flops toward the other end of the register, and exit one bit at a time in the same order as originally loaded.

74ALS166/74HC166

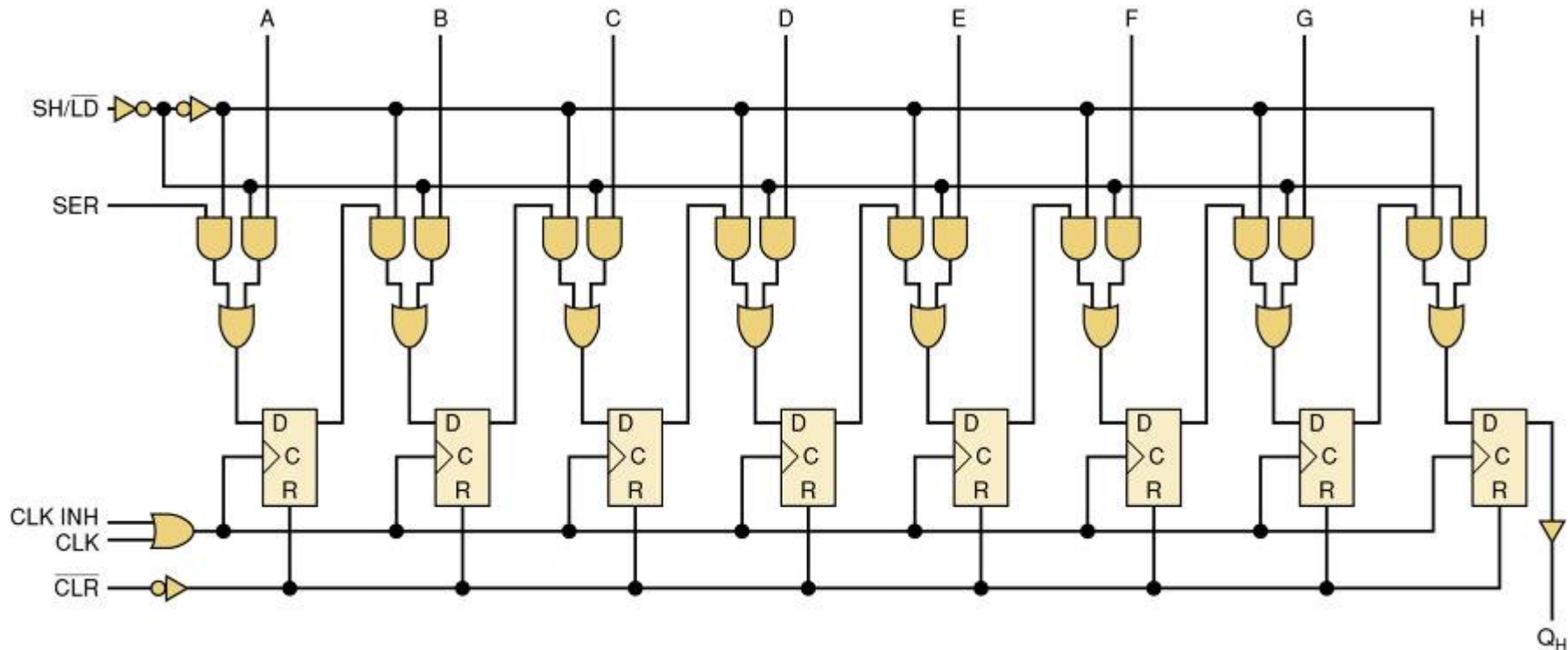

Circuit Diagram

74ALS166/74HC166

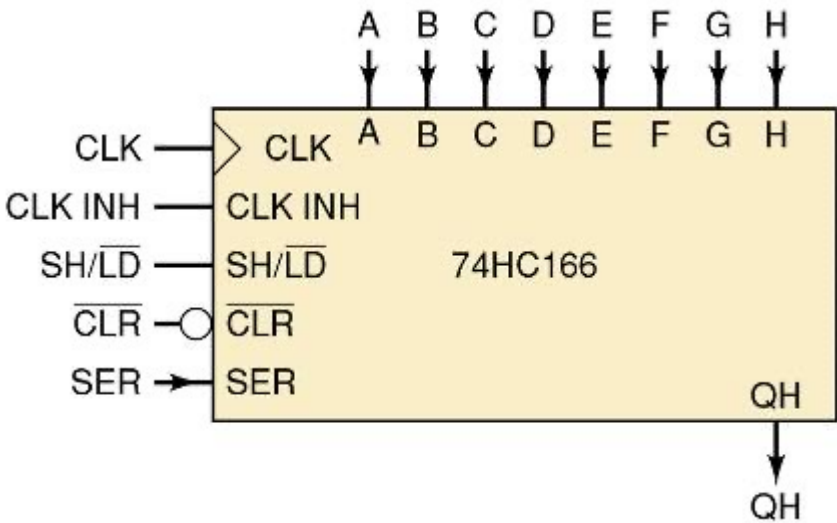


Logic
Symbol

Function
Table

| INPUTS | | | | | | OUTPUTS | | |
|--------|-------|---------|-----|-----|-----------------------|----------|-----|-----|
| | | | | | | INTERNAL | | QH |
| CLR | SH/LD | CLK INH | CLK | SER | PARALLEL A . . . H | QA | QB | |
| L | X | X | X | X | X | L | L | L |
| H | X | L | L | X | X | QA0 | QB0 | QH0 |
| H | L | L | ↑ | X | a . . . h | a | b | h |
| H | H | L | ↑ | H | X | H | QAn | QGn |
| H | H | L | ↑ | L | X | L | QAn | QGn |
| H | X | H | ↑ | X | X | QA0 | QB0 | QH0 |

74ALS165/74HC165


8-bit parallel in/serial out (PISO)

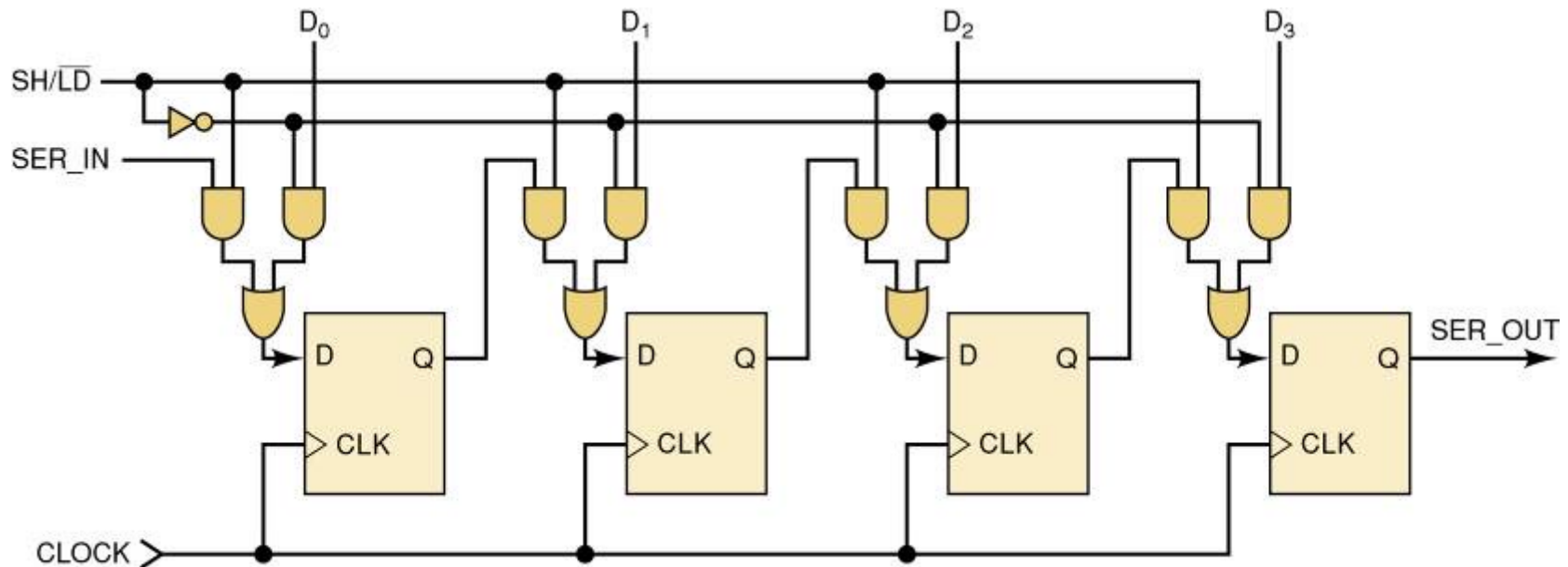

Serial shifting is always synchronous, as the clock is required to ensure the input data moves only one bit at a time with each appropriate clocking edge.

74ALS165/74HC165

8-bit parallel in/serial out (PISO)

 


Function Table

| Inputs | | | Operation |
|--------|----|--------|---------------|
| SH/LD | CP | CP INH | |
| L | X | X | Parallel load |
| H | H | X | No change |
| H | X | H | No change |
| H | ⌄ | L | Shifting |
| H | L | ⌄ | Shifting |


H = high level
 L = low level
 X = immaterial
 ⌄ = PGT

74ALS164/74HC164

8-bit serial in/parallel out (SIPO)

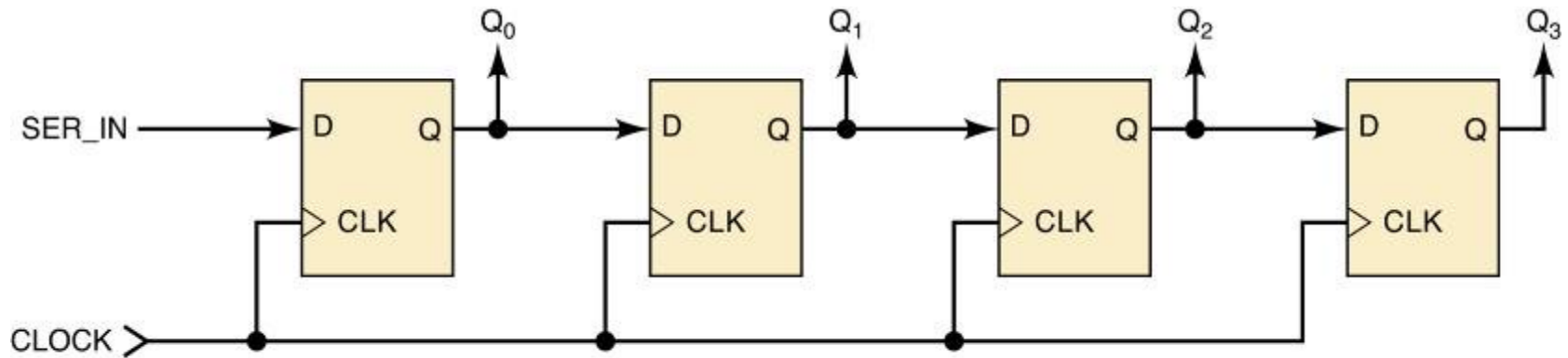


8-bit
shift register
74ALS164

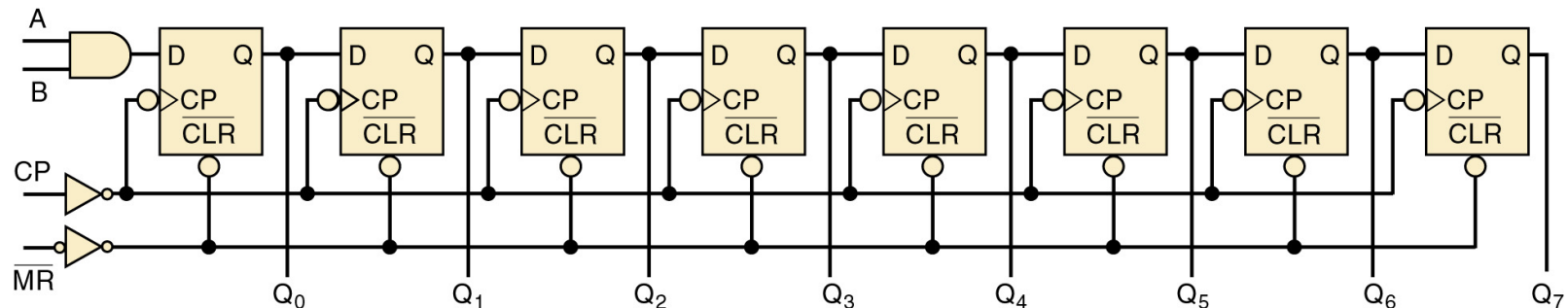

74ALS164/74HC164

8-bit serial in/parallel out (SIPO)


 


7-17 Shift Register Counters


- Shift-register counters use *feedback*—the output of the last FF in the register is connected back to the first FF in some way.

 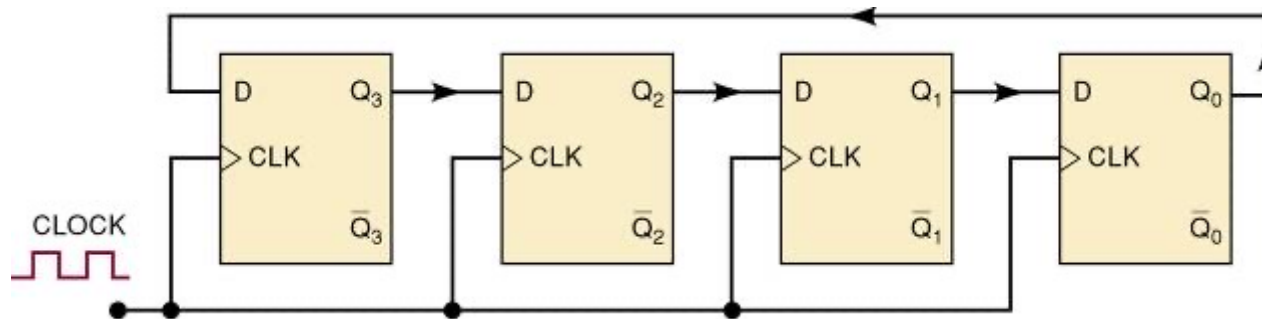7-17 Shift Register Counters

- A **ring counter** is a **circulating shift register** connected so the last FF shifts its value to the first.




| Q ₃ | Q ₂ | Q ₁ | Q ₀ | CLOCK pulse |
|----------------|----------------|----------------|----------------|-------------|
| 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 2 |
| 0 | 0 | 0 | 1 | 3 |
| 1 | 0 | 0 | 0 | 4 |
| 0 | 1 | 0 | 0 | 5 |
| 0 | 0 | 1 | 0 | 6 |
| 0 | 0 | 0 | 1 | 7 |
| . | . | . | . | . |
| . | . | . | . | . |

 

 7-17 Shift Register Counters

- To operate properly, a ring counter must start off with only one FF in the 1 state and all the others in the 0 state.
 - As power-up starting states will be unpredictable, the counter is preset *before* clock pulses are applied.


Circuit for ensuring the ring counter starts in the 1000 state on power-up.



7-17 Shift Register Counters






- In the **Johnson** or **twisted-ring counter** *inverted* output of the last FF is connected to the input of the first FF.

| Q ₂ | Q ₁ | Q ₀ | CLOCK pulse |
|----------------|----------------|----------------|-------------|
| 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 2 |
| 1 | 1 | 1 | 3 |
| 0 | 1 | 1 | 4 |
| 0 | 0 | 1 | 5 |
| 0 | 0 | 0 | 6 |
| 1 | 0 | 0 | 7 |
| 1 | 1 | 0 | 8 |
| . | . | . | . |
| . | . | . | . |
| . | . | . | . |

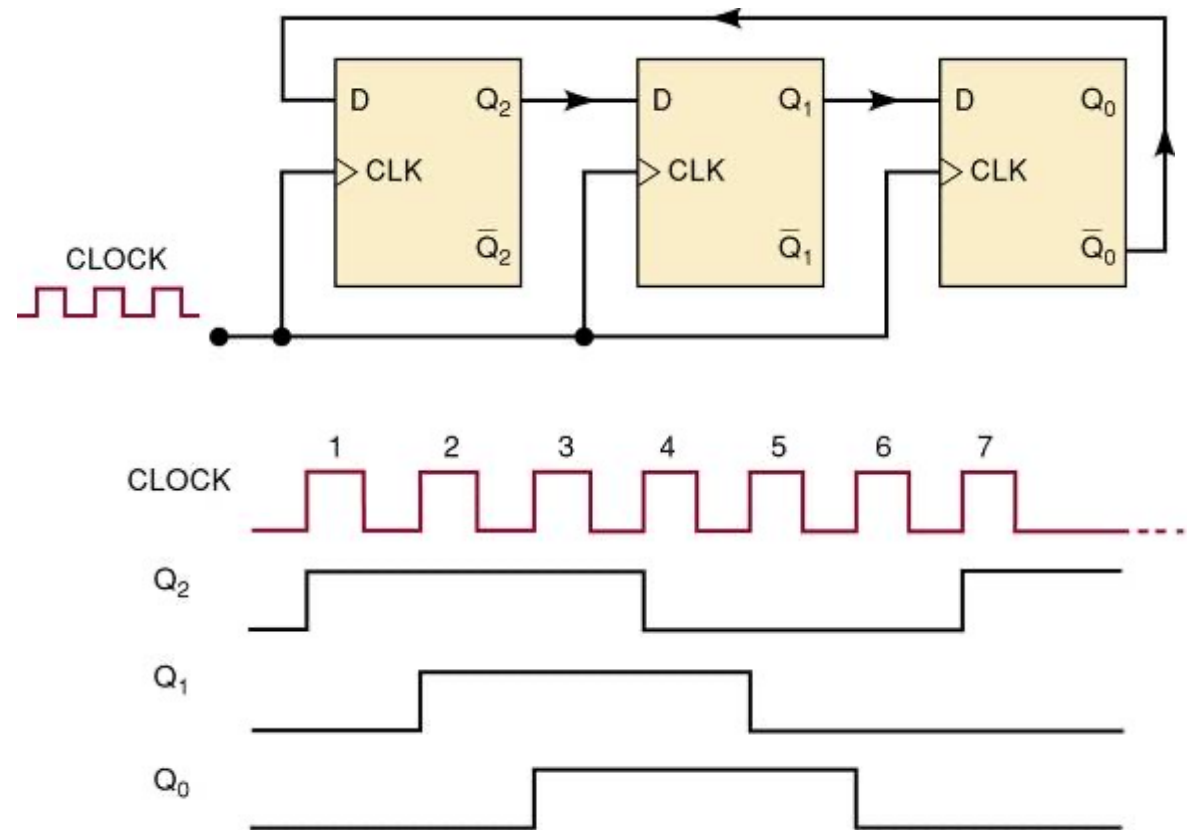

     7-17 Shift Register Counters

- For a given MOD number, a Johnson counter requires only half the FFs a ring counter requires.
 - It requires decoding gates—a ring counter does not.
- A Johnson counter uses one logic gate to decode for each count.
 - Each gate requires only two inputs, regardless of the number of FFs in the counter.



| Q_2 | Q_1 | Q_0 | Active gate |
|-------|-------|-------|-------------|
| 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 2 |
| 1 | 1 | 1 | 3 |
| 0 | 1 | 1 | 4 |
| 0 | 0 | 1 | 5 |

7-17 Shift Register Counters

- Very few ring counters or Johnson counters are available as ICs.
 - It is relatively simple to wire a shift-register IC as either a ring counter or a Johnson counter.
- Some of the CMOS Johnson-counter ICs include the complete decoding circuitry on the same chip as the counter.
 - (74HC4017, 74HC4022)

7-18 Troubleshooting


- Flip-flops, counters, and registers are the major components in sequential logic system.
 - Sequential systems suffer from the same types of failures as do combinational systems.
 - Open circuits, shorts, internal IC faults, etc.
- Basic troubleshooting procedures still apply.
 - Observe system operation.
 - Use analytical reasoning to determine possible causes.
 - Use test equipment to isolate the exact fault.

7-20 HDL Registers

- HDL techniques use bit arrays to describe register data & transfer the data in parallel or serial format.
- **Concatenation**—grouping together in a specific sequence—of desired set of data bits can be used to describe data movement for serial shifting.

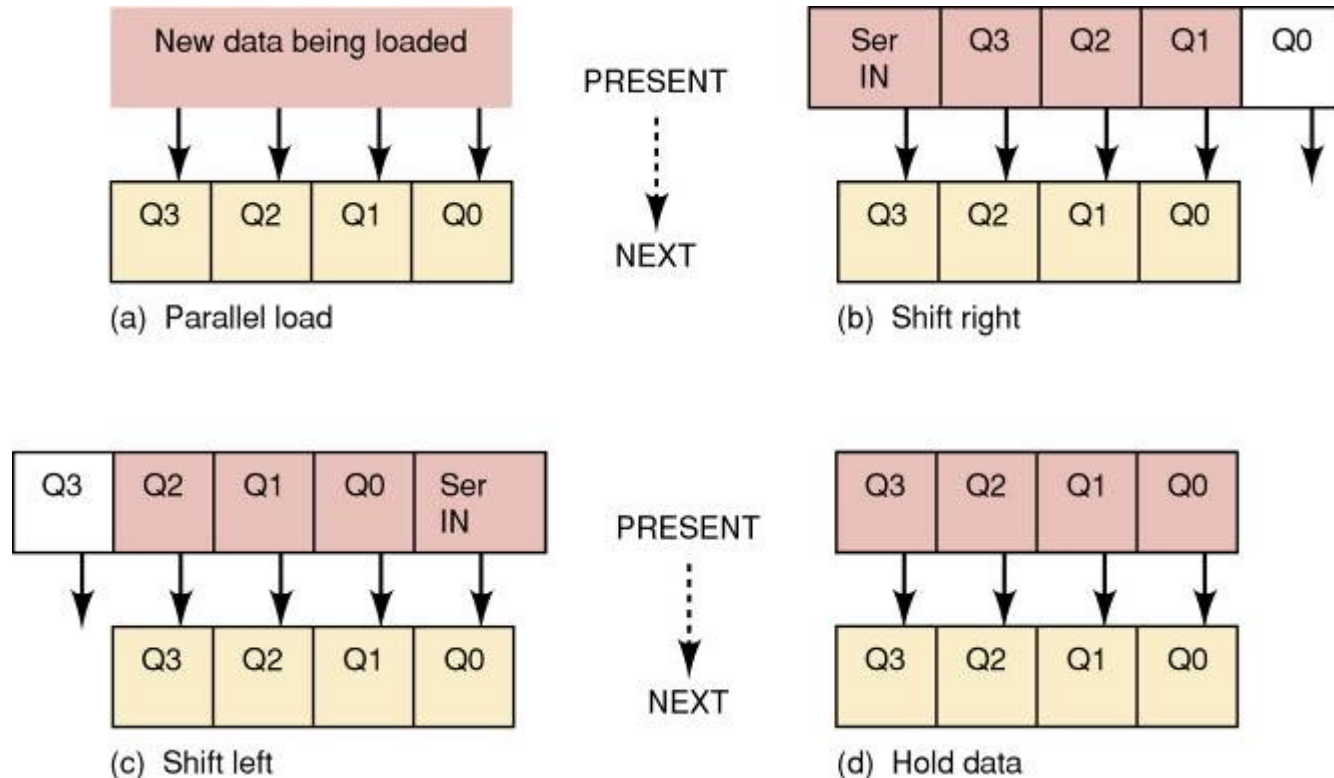7-20 HDL Registers

Four flip-flops performing transfer operations of parallel load, shift right, shift left, and hold data.



Bits are transferred synchronously, which means they all move simultaneously on a single clock edge.

7-21 HDL Ring Counters

- A ring counter is a shift register that circulates a single active logic level through all its FFs.
 - Modulus is equal to the number of FFS in the register.
 - There are always many unused and invalid states.
- With planning, we can ensure the counter reaches the desired sequence—no matter the initial state.
 - Regardless of the state to which the counter initializes, it eventually fills with zeros.
 - At which time, logic shifts in a HIGH to start the ring sequence.

7-21 HDL Ring Counters

- In the AHDL code shown, lines 11 & 12 control the serial input using the strategy just described.
 - The (==) operator evaluates whether the expressions on each side are equal or not.

```
1  SUBDESIGN fig7_92
2  (
3      clk          :INPUT;
4      q[3..0]      :OUTPUT;
5  )
6  VARIABLE
7      ff[3..0]     :DFF;
8      ser_in       :NODE;
9  BEGIN
10     ff[].clk = clk;
11     IF ff[3..1].q == B"000" THEN ser_in = VCC;  -- self start
12     ELSE ser_in = GND;
13     END IF;
14     ff[3..0].d = (ser_in, ff[3..1].q);          -- shift right
15     q[] = ff[].q;
16 END;
```


- The concept of a counter can be applied to implement a **digital one-shot** using HDL.
 - A *nonretriggerable* one-shot ignores the trigger input pulse output is still active.
 - A *retriggerable* one-shot starts a pulse in response to a trigger.
 - Internal pulse timer restarts each time a subsequent trigger edge occurs *before* the pulse is complete.

END

ELEVENTH EDITION

Digital Systems

Principles and Applications

Ronald J. Tocci

Monroe Community College

Neal S. Widmer

Purdue University

Gregory L. Moss

Purdue University

PEARSON