

Computer Architecture and Organization

INSTRUCTOR: YAN-TSUNG PENG

DEPT. OF COMPUTER SCIENCE, NCCU

The Structure of a CPU

From a Single-cycle Processor

$$\begin{aligned}\text{CPU Time} &= \frac{\text{Seconds}}{\text{Program}} \\ &= \frac{\text{Instructions}}{\text{Program}} \times \frac{\text{Clock cycles}}{\text{Instruction}} \times \frac{\text{Seconds}}{\text{Clock cycle}}\end{aligned}$$

IC CPI Clock cycle time

CPU performance factors

- Instruction count
 - Determined by ISA and compiler
- CPI and Cycle time
 - Determined by CPU hardware

Introduction

- We will be examining an implementation that includes a subset of the core MIPS instructions:
 - Memory-reference instructions: lw, sw
 - Arithmetic-logical instructions: add, sub, AND, OR, slt
 - Branch instructions: beq, j
- These will illustrate the key principles used in creating a datapath and designing the control.


Instruction Execution

- For every instruction, the first two steps are identical
 1. PC \rightarrow instruction memory, fetch instruction
 2. From the instruction: Register numbers \rightarrow register file, read registers
- Depending on instruction class
 - Use ALU to calculate
 - Arithmetic result
 - Memory address for load/store
 - Branch target address
 - Access data memory for load/store
 - PC \leftarrow target address or PC + 4


Instruction Execution

- General steps (not all the steps needed for every instruction):
 1. Start with fetching the instruction from memory
 2. Read registers (Register numbers)
 3. ALU
 4. Access data memory
 5. Write registers ($PC \leftarrow PC + 4$)


Processor Overview

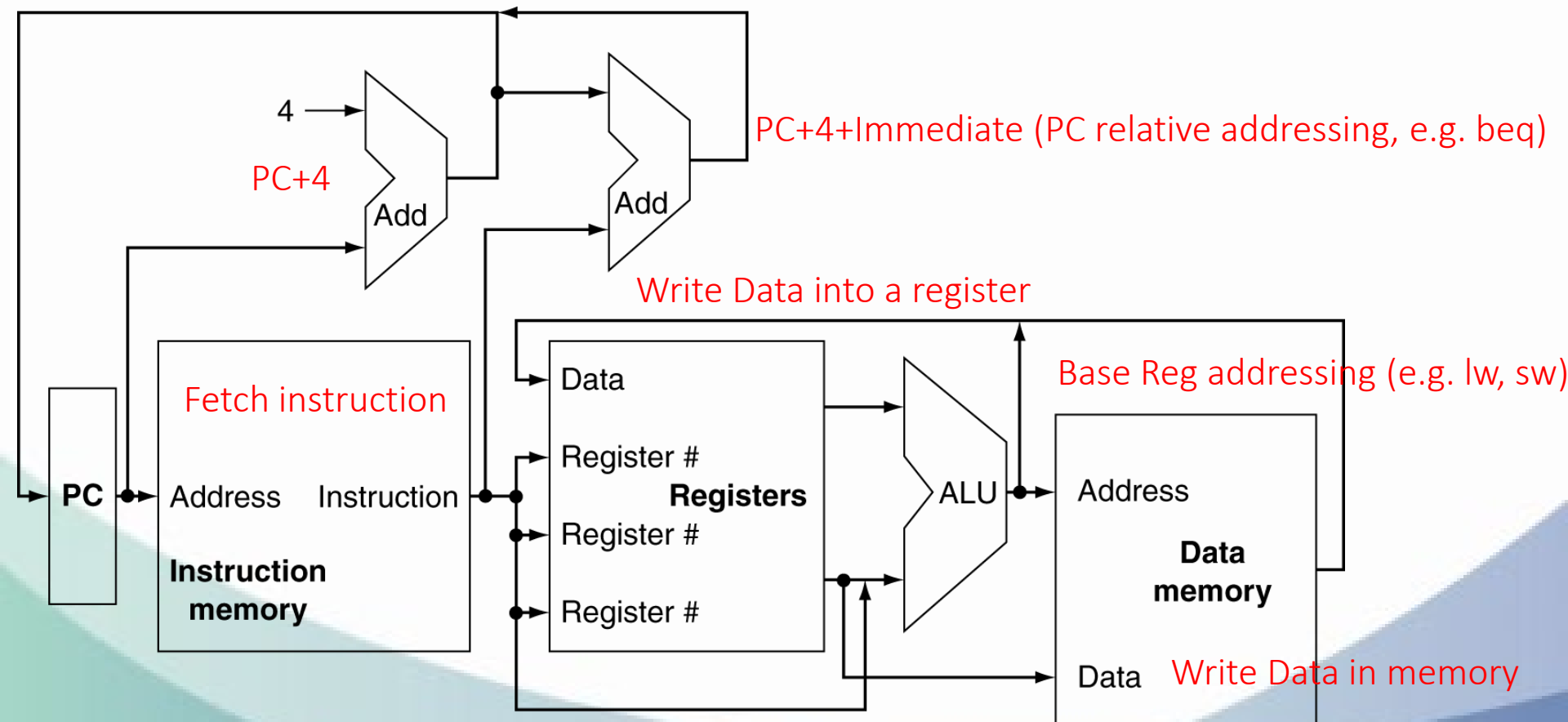


Processor Overview

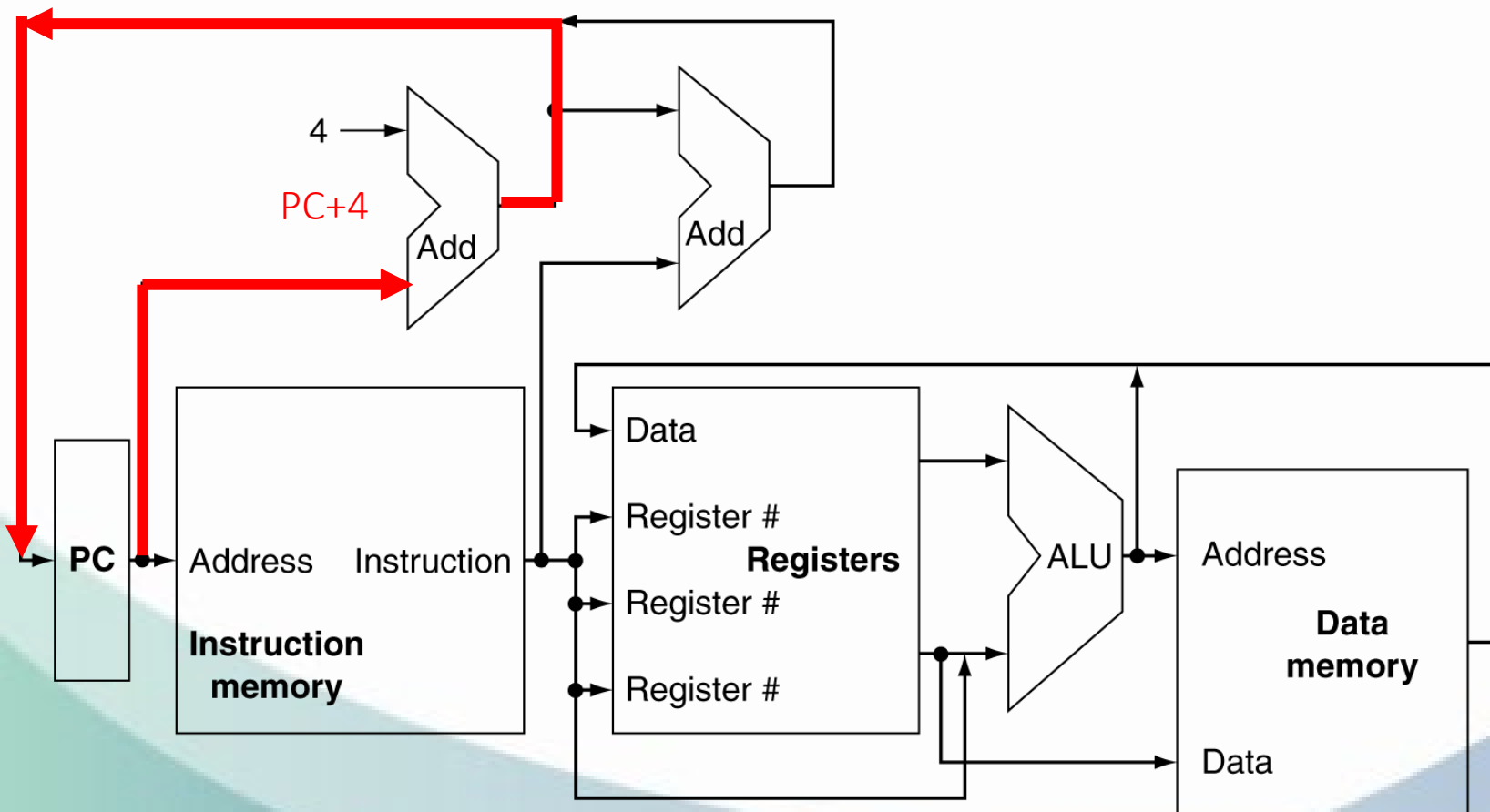

Processor Overview

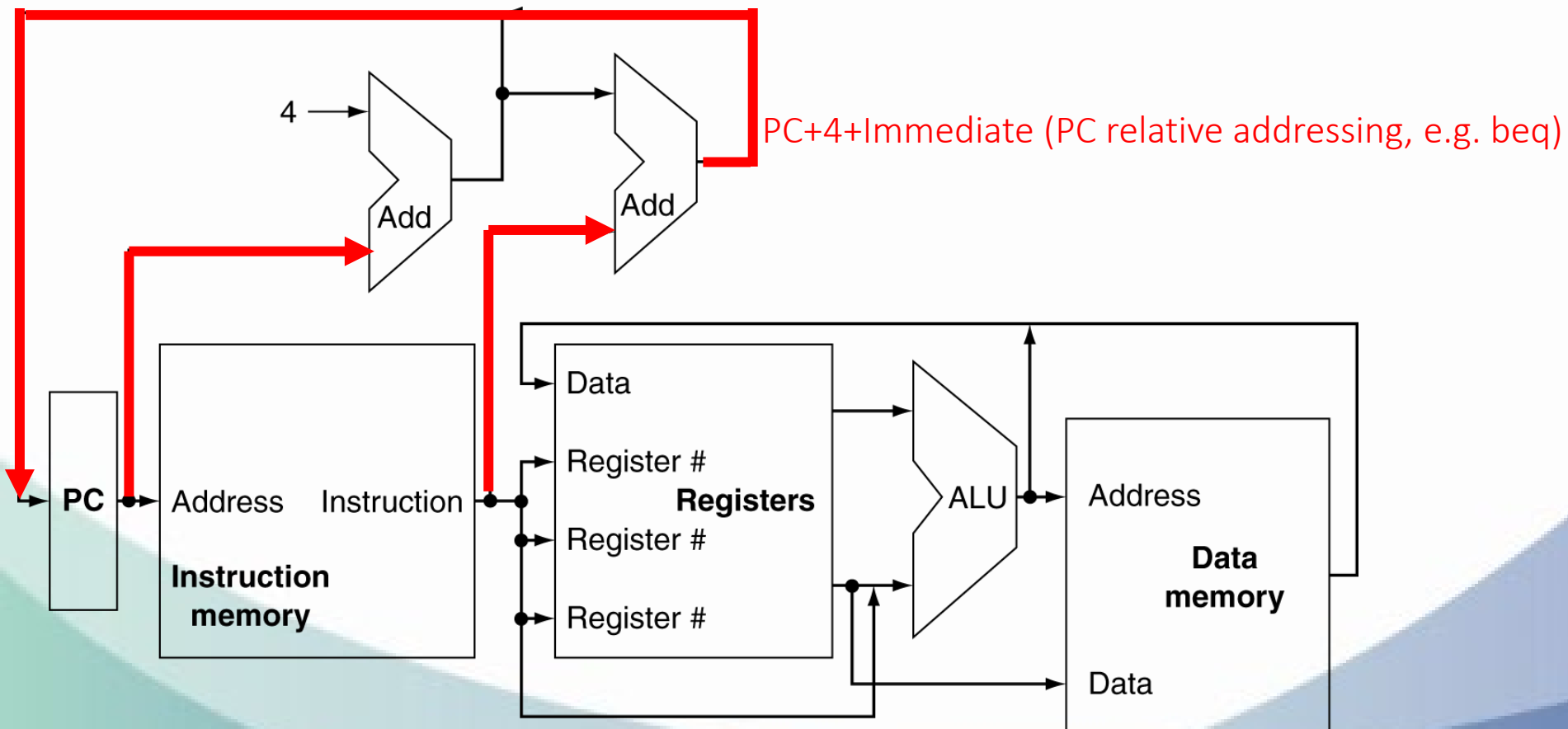

Processor Overview

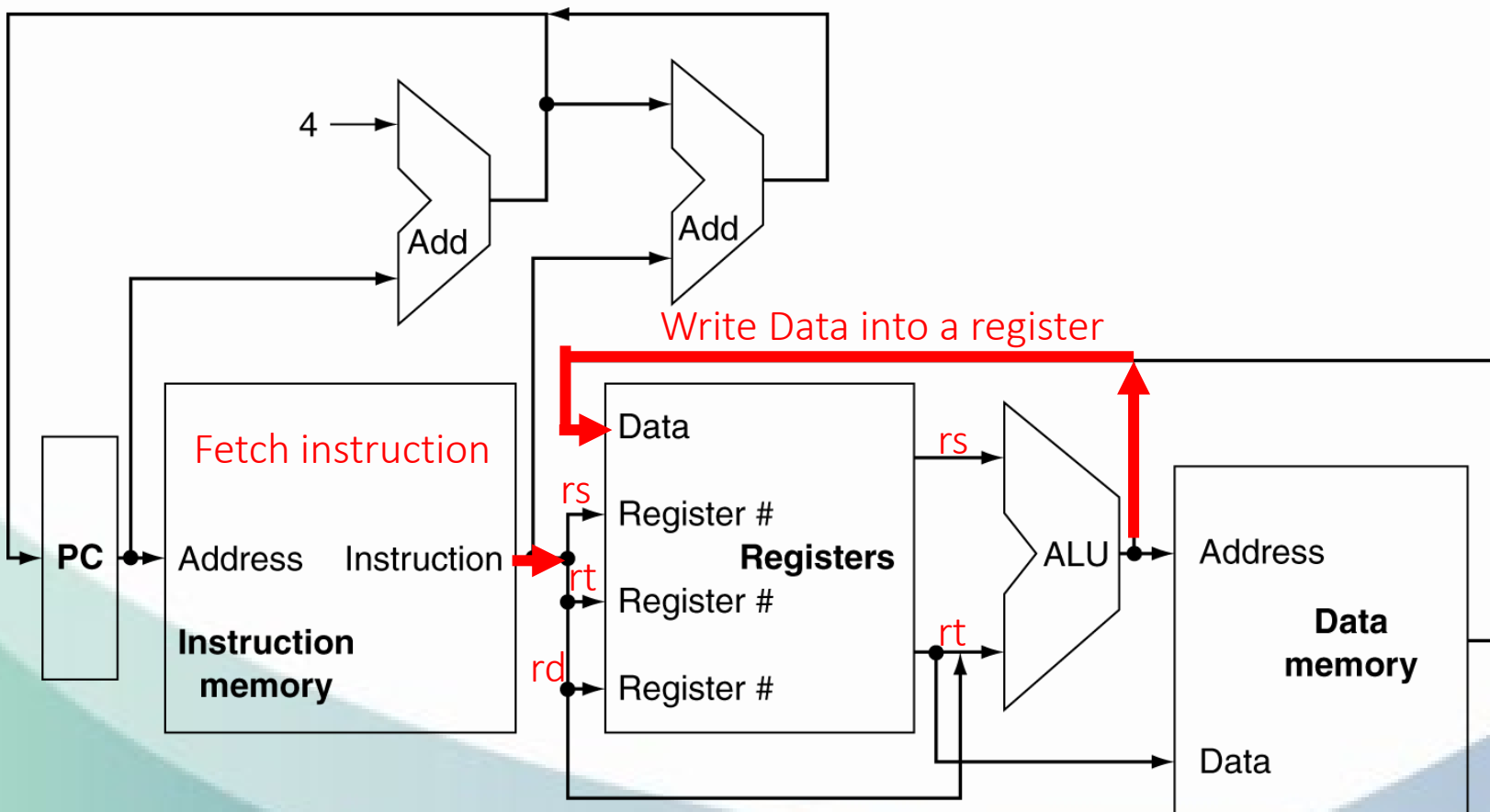


Logic Design Basics

- Information encoded in binary
 - Low voltage = 0, High voltage = 1
 - One wire per bit
 - Multi-bit data encoded on multi-wire buses
- Combinational element
 - Operate on data
 - Output is a function of input
- State (sequential) elements
 - Store information

Combinational Logic


■ AND-gate

- $Y = A \& B$

 


■ Adder

- $Y = A + B$

 


■ Multiplexer

- $Y = S ? I_1 : I_0$

 



■ Arithmetic/Logic Unit

- $Y = F(A, B)$

 

Sequential Logic

  
- Register: stores data in a circuit
 - Uses a clock signal to determine when to update the stored value
 - Edge-triggered: update when Clk changes from 0 to 1



Sequential Elements

■ Register with write control

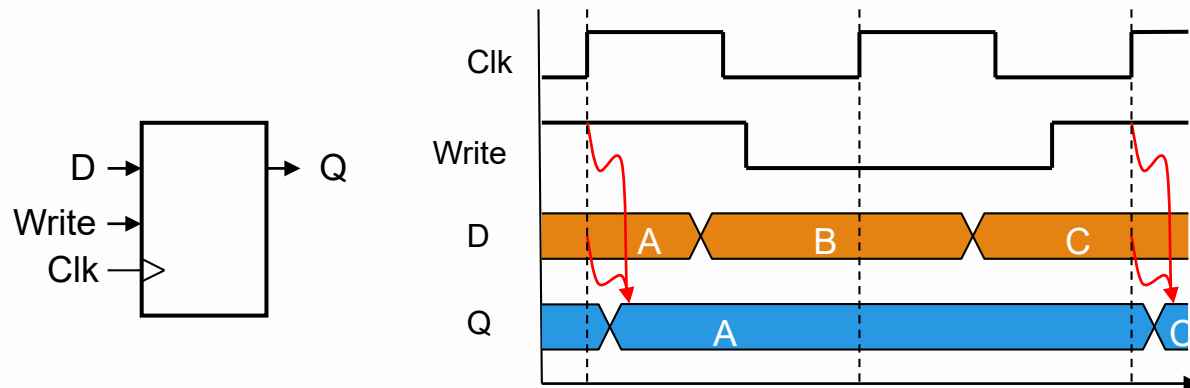- Only updates on clock edge when write control input is 1
- Used when stored value is required later




- Setup time: the time span when the input signal needs to keep stable before the rising/falling) clock edge
- Hold time: the time span when the input signal needs to keep stable after the rising/falling clock edge to prevent the signal from being overwritten by another signal


Clocking Methodology

- Combinational logic transforms data during clock cycles
 - Between clock edges
 - Input from state elements, output to state element
 - Longest delay determines clock period

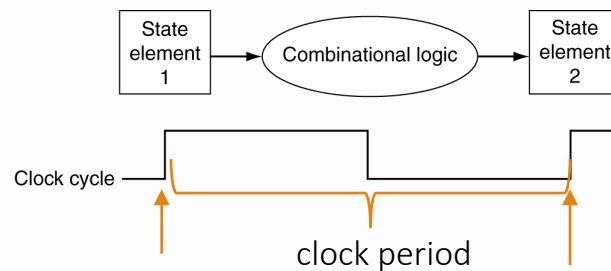
A signal has to be transformed from S1 to S2 through C




rising edge-triggered

 

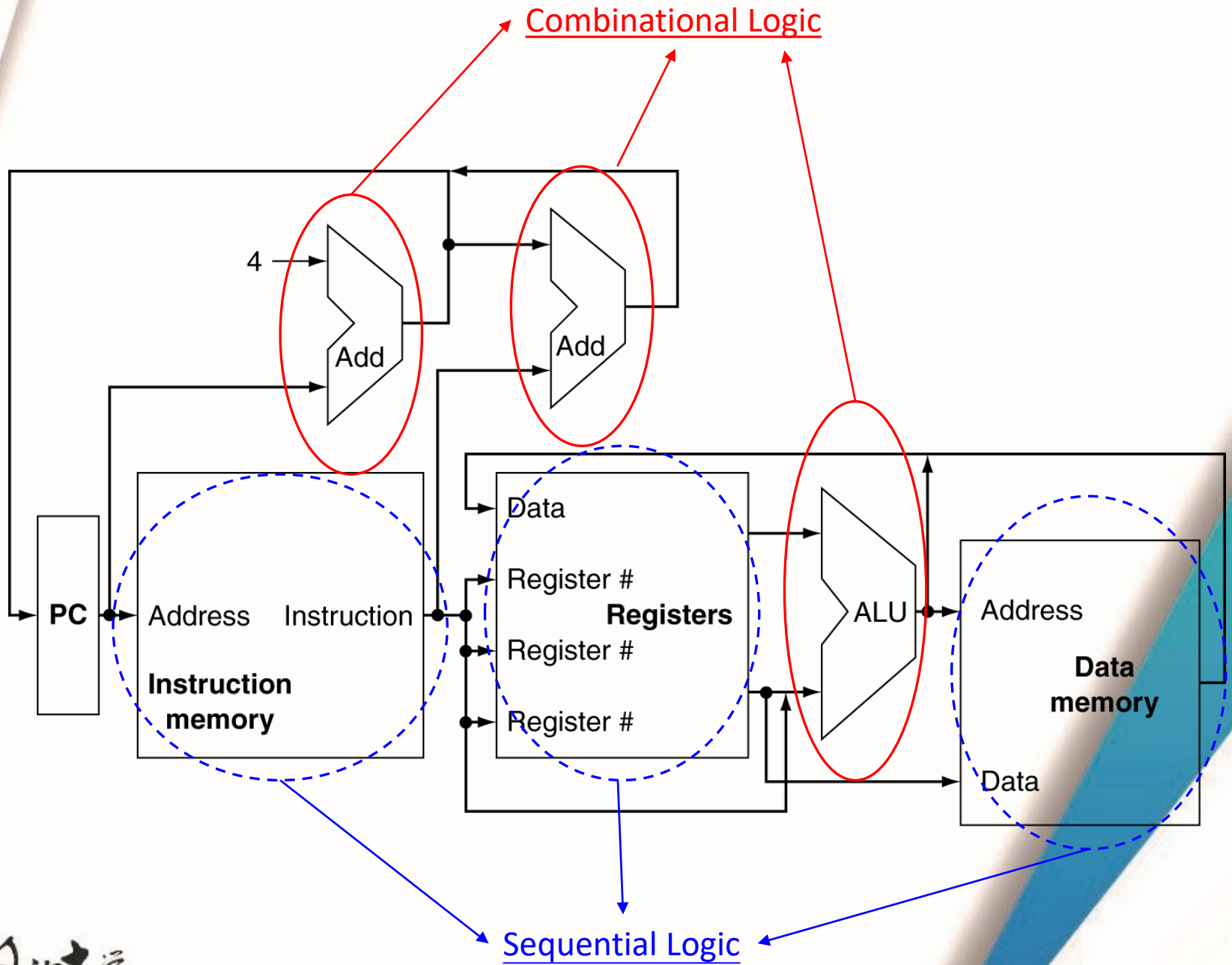State will be x2 upon the next rising edge.
Before that, it will still be x1.




Multiplexers

 


$$O = \begin{cases} I_0 & \text{if } sel = 0 \\ I_1 & \text{if } sel = 1 \end{cases}$$

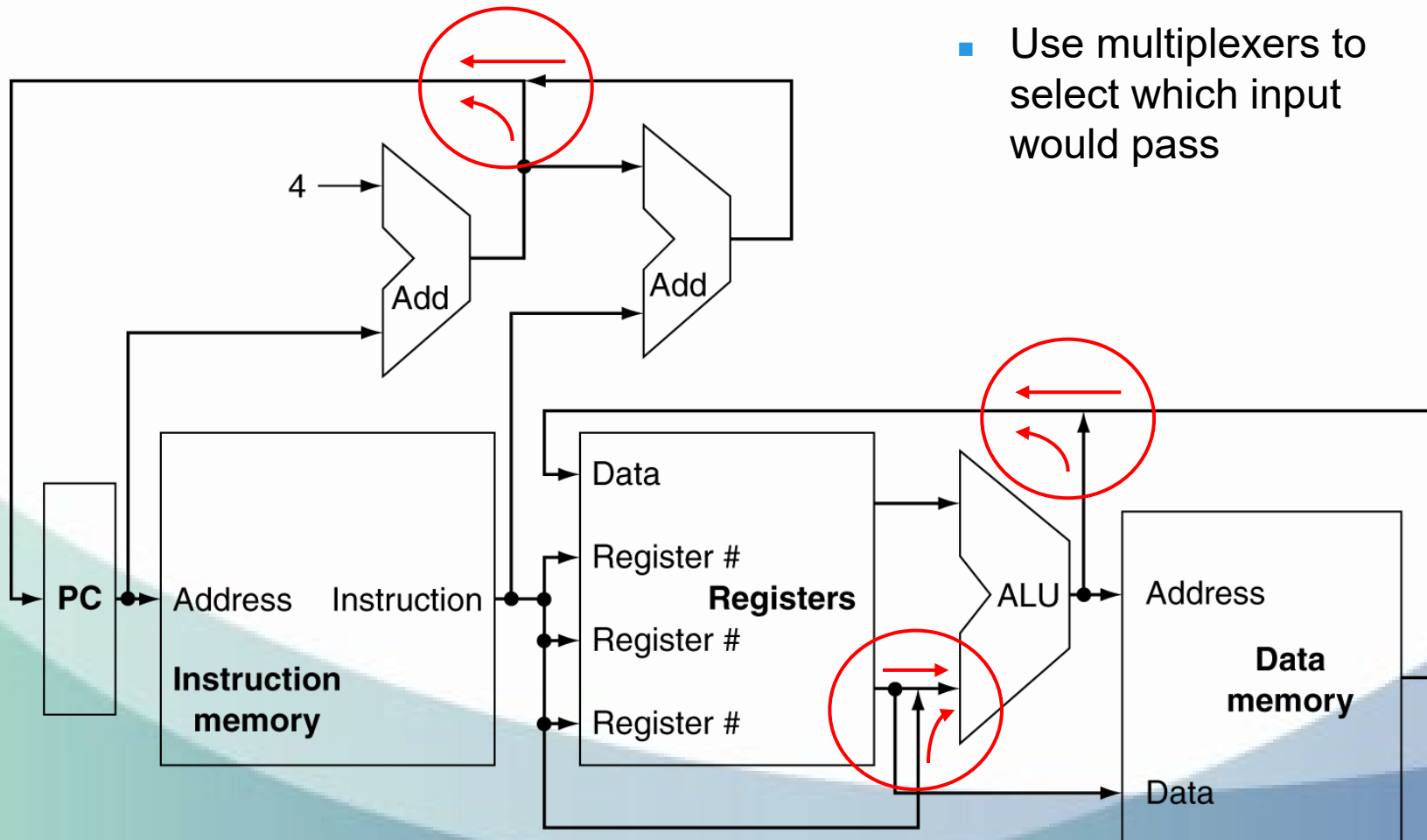
- Use multiplexers to select which input would pass




Control Unit

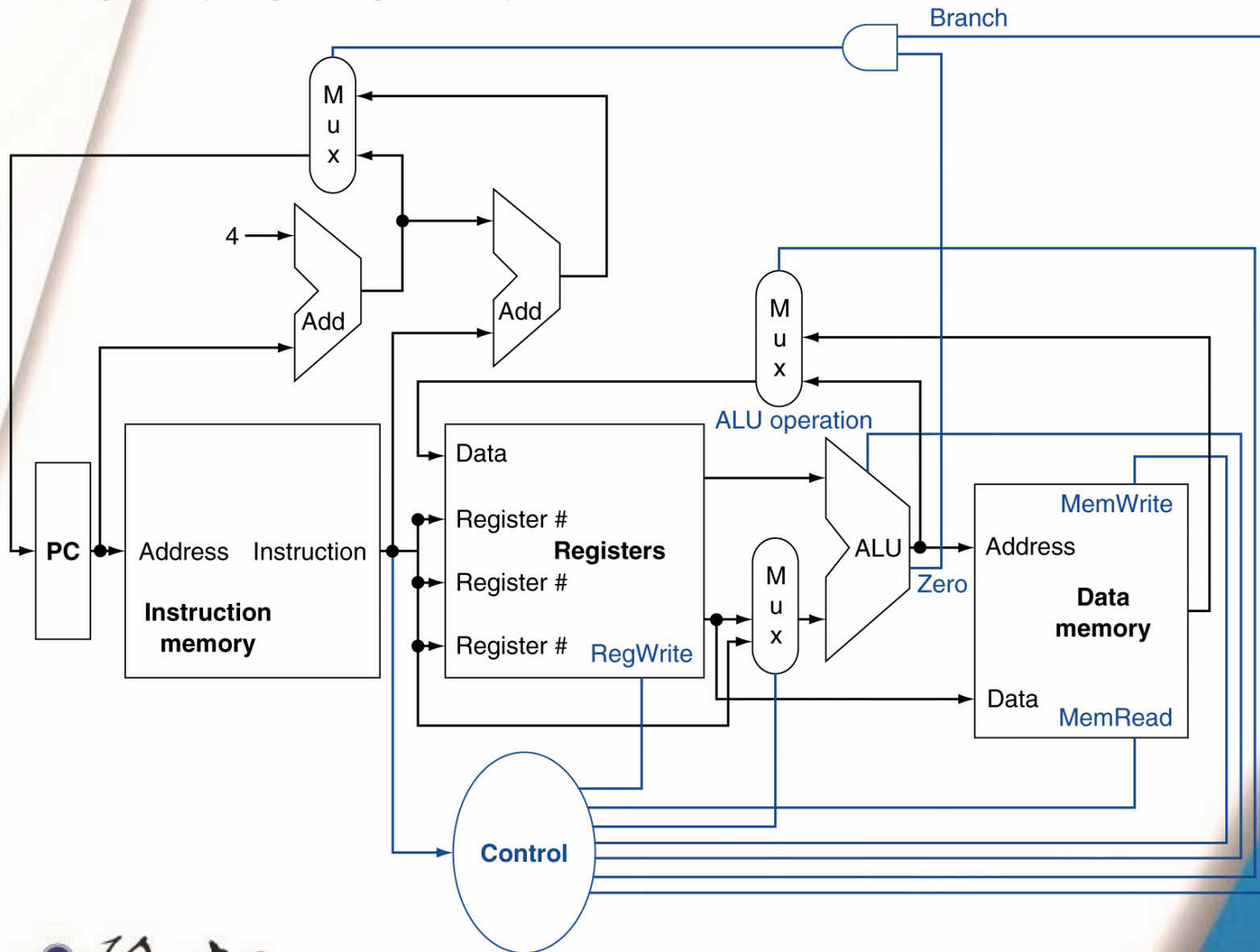

Control - ADD

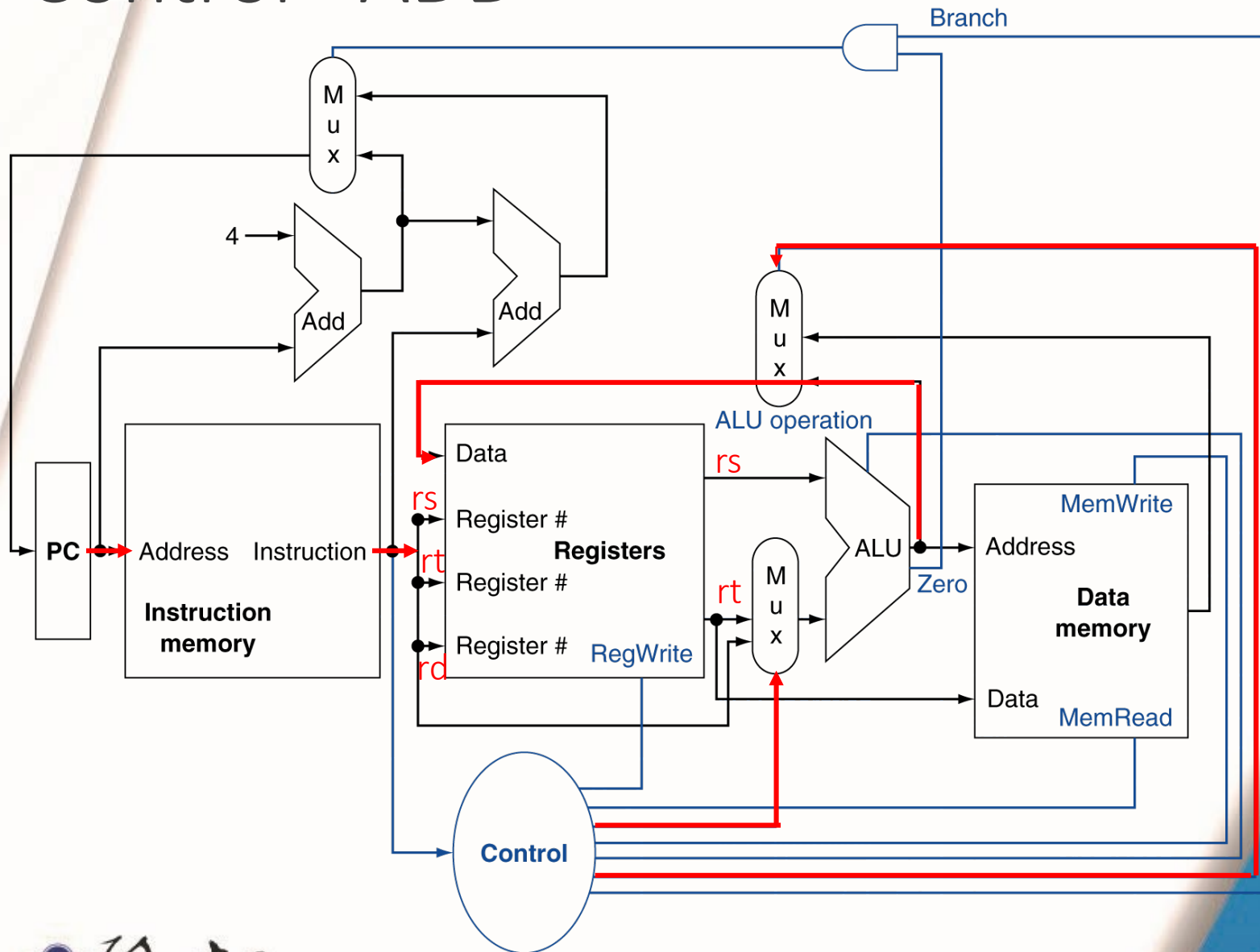

Control-Beq

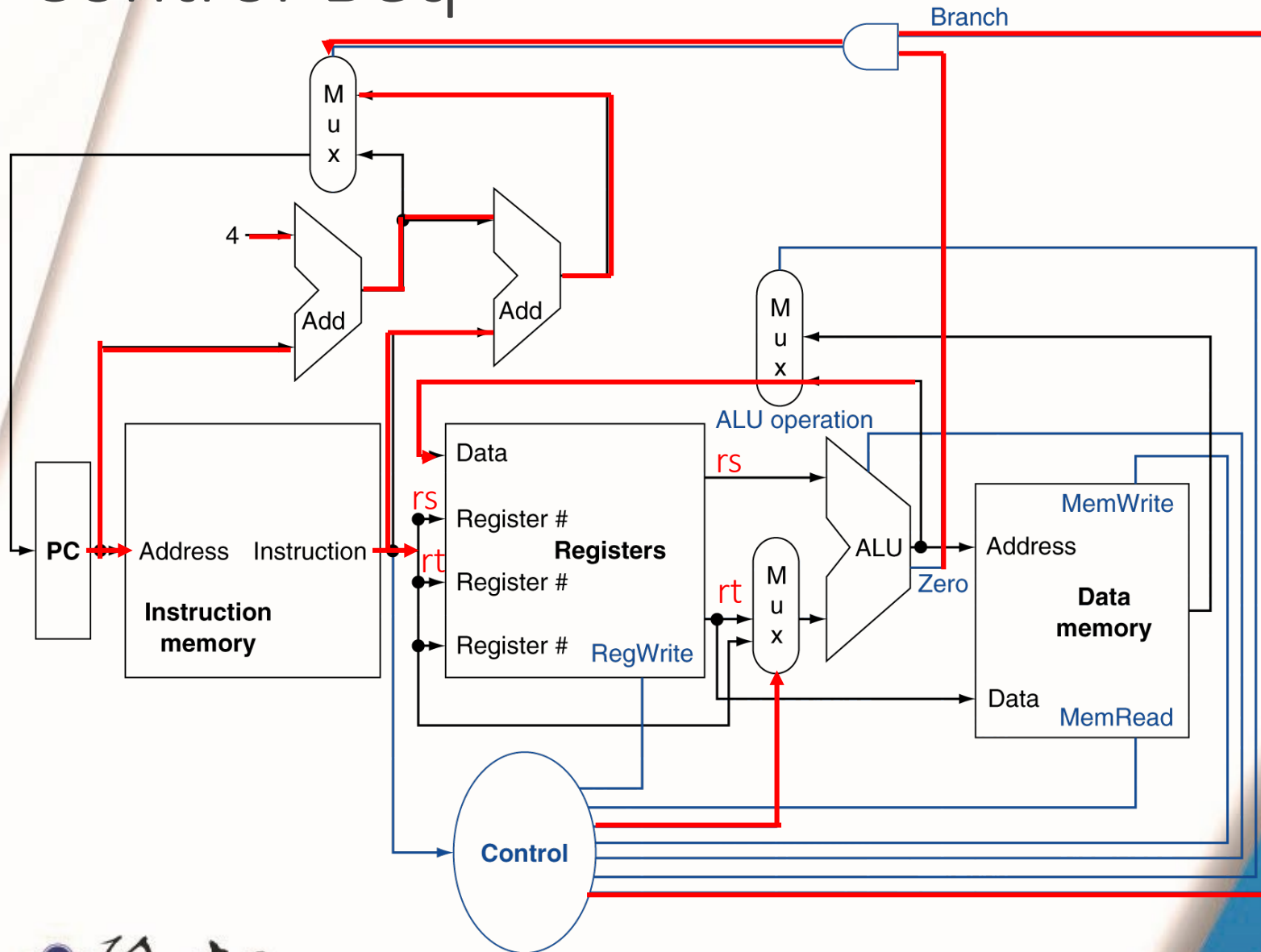

Instruction Review

■ R-type

- add, sub, or, slt

op	rs	rt	rd	shamt	funct
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

■ I-type

- lw, sw
- addi
- beq

op	rs	rt	constant or address
6 bits	5 bits	5 bits	16 bits

Imm16

■ J-type:

- j

op	address
6 bits	26 bits

Addr26

- Analyze instructions, including fields, addressing modes, for a CPU design

Instruction Review

■ R-type

- add rd, rs, rt
- sub rd, rs, rt
- and rd, rs, rt
- or rd, rs, rt
- slt rd, rs, rt

op	rs	rt	rd	shamt	funct
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

Imm16

op	rs	rt	constant or address
6 bits	5 bits	5 bits	16 bits

■ I-type

- lw rt,rs,imm16
- sw rt,rs,imm16
- addi rt,rs,imm16
- beq rs,rt,imm16

Addr26

op	address
6 bits	26 bits

■ J-type:

- j tar_address

Data Transfer in Memory and Register

$IR \leftarrow \text{Mem}[PC]$

$rs \leftarrow IR[25:21]$ $rt \leftarrow IR[20:16]$ $rd \leftarrow IR[15:11]$ $\text{Imm16} \leftarrow IR[15:0]$ $\text{Addr26} \leftarrow IR[25:0]$

add/sub: $R[rd] \leftarrow R[rs] \pm R[rt]$

lw: $R[rt] \leftarrow \text{Mem}[R[rs] + \text{sign_ext}[\text{Imm16}]]$

sw: $\text{Mem}[R[rs] + \text{sign_ext}[\text{Imm16}]] \leftarrow R[rt]$

addi: $R[rt] \leftarrow R[rs] + \text{sign_ext}[\text{Imm16}]$

beq: $PC \leftarrow \begin{cases} PC+4+(\text{sign_ext}[\text{Imm16}] \ll 2), & \text{if } R[rs] == R[rt] \\ PC+4, & \text{otherwise.} \end{cases}$

j: $PC \leftarrow PC[31:28] \parallel \text{Addr26} \parallel 00$

($PC \leftarrow PC+4$)

Datapath for Instruction Execution

$I \leftarrow \text{Mem}[\text{PC}] \quad \text{PC} \leftarrow \text{PC} + 4$

add/sub: $R[\text{rd}] \leftarrow R[\text{rs}] \pm R[\text{rt}]$


lw: $R[\text{rt}] \leftarrow \text{Mem}[R[\text{rs}] + \text{sign_ext}[\text{Imm16}]]$

sw: $\text{Mem}[R[\text{rs}] + \text{sign_ext}[\text{Imm16}]] \leftarrow R[\text{rt}]$

addi: $R[\text{rt}] \leftarrow R[\text{rs}] + \text{sign_ext}[\text{Imm16}]$

beq: $\text{PC} \leftarrow \begin{cases} \text{PC} + 4 + (\text{sign_ext}[\text{Imm16}] \ll 2), & \text{if } R[\text{rs}] == R[\text{rt}] \\ \text{PC} + 4, & \text{otherwise.} \end{cases}$

 j: $\text{PC} \leftarrow \text{PC}[31:28] \parallel \text{Addr26} \parallel 00$




- A const added to PC
- Reg to Reg transfer
- Mem to Reg
- Reg to Mem
- Reg added to Reg
- An imm added to Reg
- Sign extension
- Concat with 00
- Concat with PC

Building a Processor

1. Analyze datapath & check which datapath elements each instruction needs
 - Datapath must have storage elements (register or memory)
2. Select datapath elements, which include a unit used to operate on or hold data in the CPU, and establish clocking methodology
 - Register file, ALUs, adder, memories
3. Need Program counter (PC)
 - The register having the address of the instruction in the program being executed
4. Analyze each instruction to design the control unit


Instruction Fetch

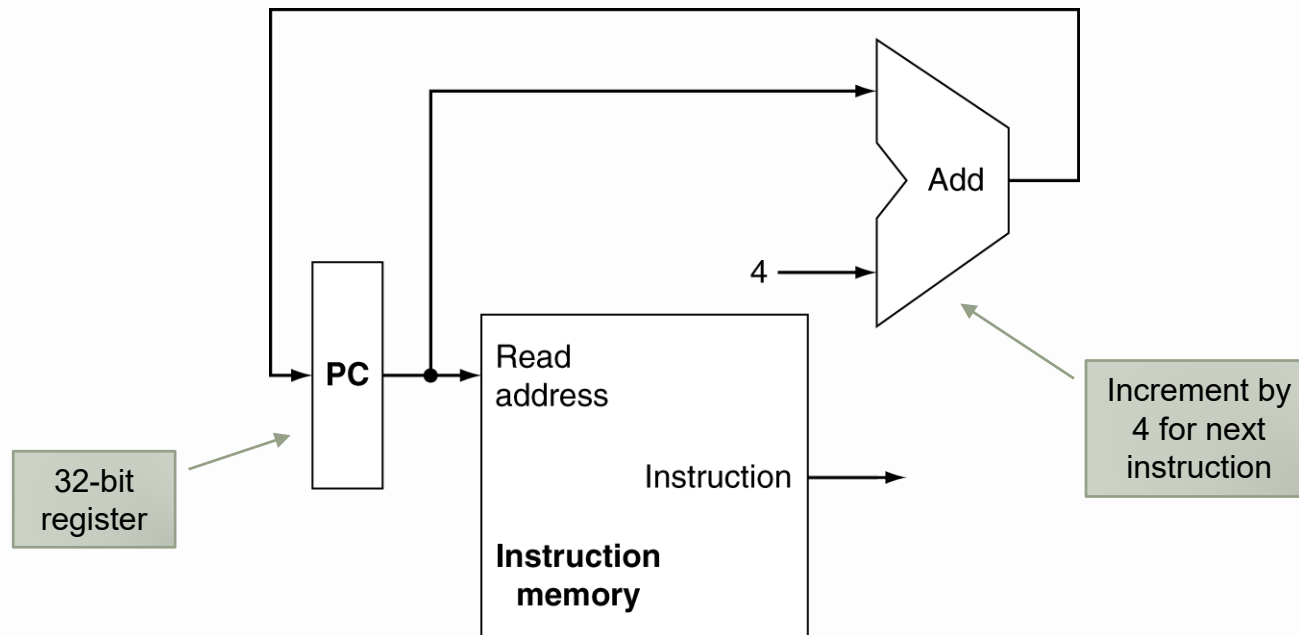

- When Branch and Jump: PC would be assigned to a specified address (Mux)


Instruction Fetch (IF)

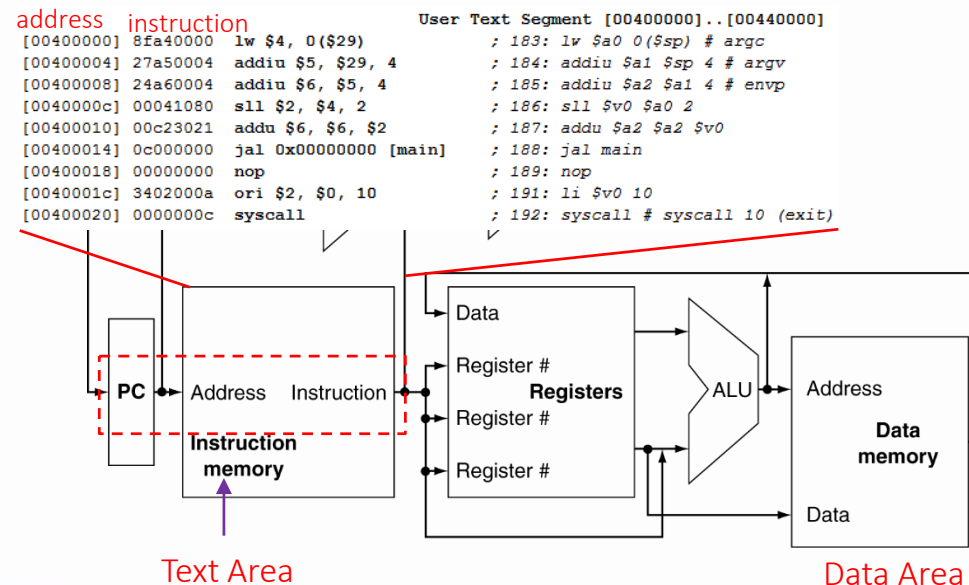- Send PC to the instruction memory to fetch the instruction




Register File

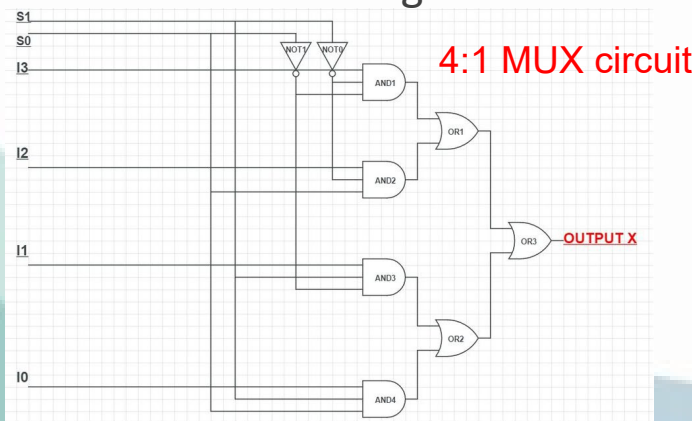- Stacking multiple registers to construct a register file
- Register can be made by D Flip Flops with N-bit input and output
- Write Enable:
 - 0: Read, and Data Out does not change




When "Read"

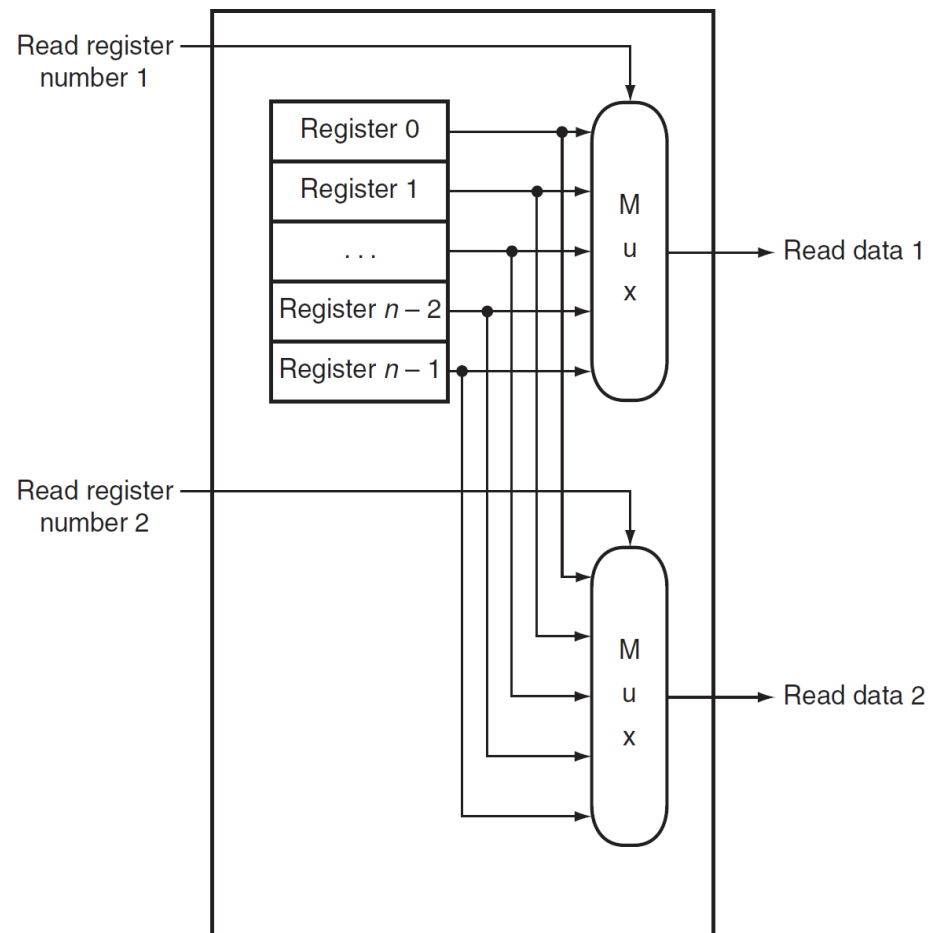

Register File


Write Enable:

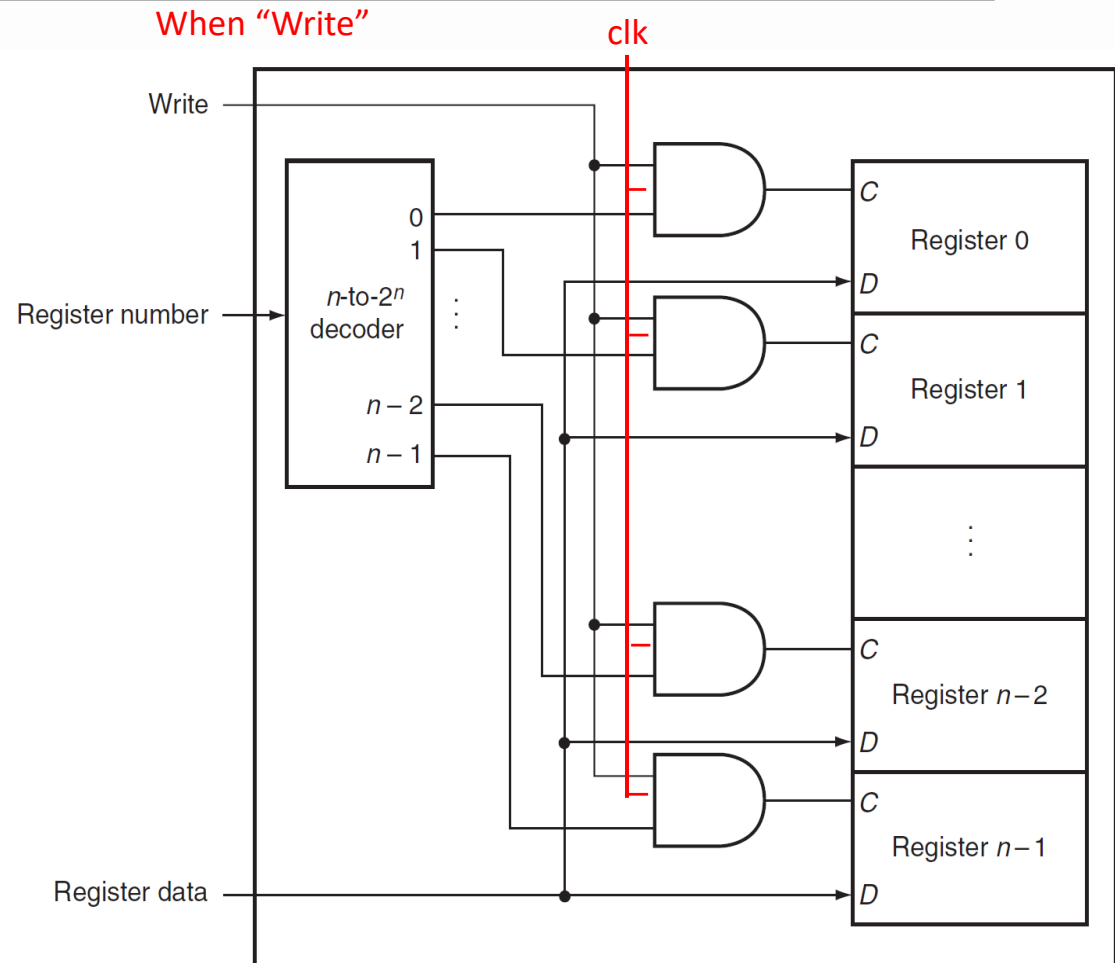- 0: Read, and Data Out does not change
- 1: Write, and Data Out becomes Data In



Instruction Decode (ID)

- Register numbers → read registers

 

For R-type instructions, it decodes rs and rt


Take **lw**, an I-type instruction as an example, it decodes rs (base reg)

Not yet touched **rd** of R-type instructions or **rt** of **lw** because it is in the “write back” stage (WB)

R-Format Instructions

■ After fetching the instruction, the CPU does

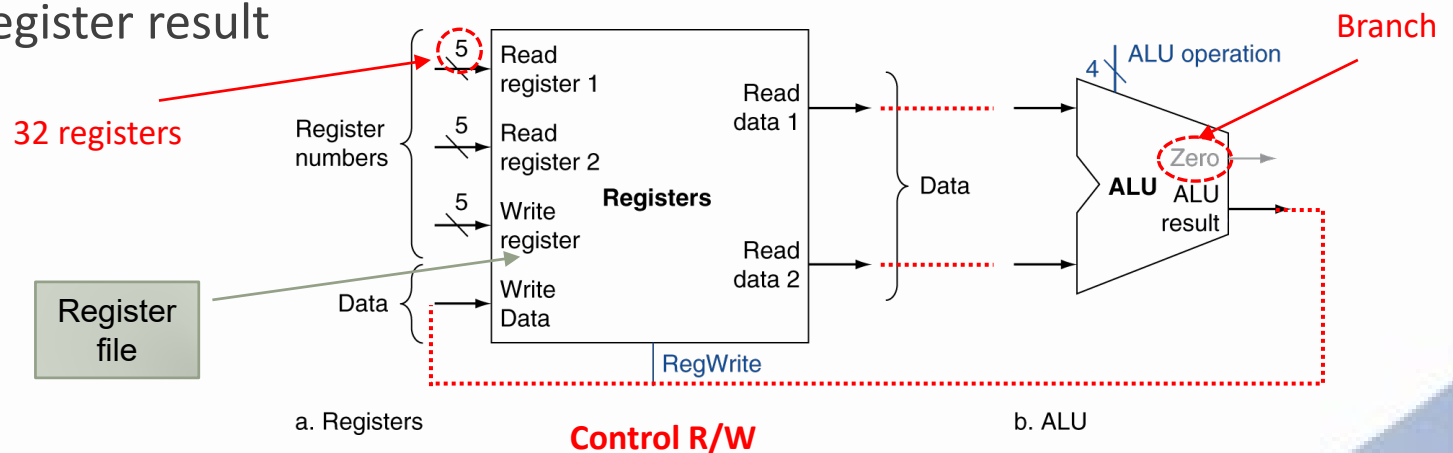1. Read two register operands
2. Perform arithmetic/logical operation (add, sub, and, or, and slt)
3. Write register result




Load/Store Instructions

lw: $R[rt] \leftarrow \text{Mem}[R[rs] + \text{sign_ext}[\text{Imm16}]]$

sw: $\text{Mem}[R[rs] + \text{sign_ext}[\text{Imm16}]] \leftarrow R[rt]$

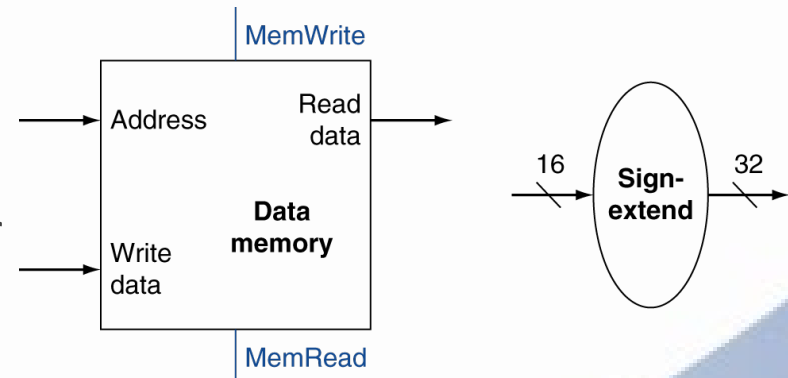- Read register operands
 - a source/destination register and the base register
- Calculate address using 16-bit offset
 - Use ALU, but sign-extend offset
 - $\text{sign_extend}(\text{offset_value}) + R[rs]$
- Load: Read memory and update register
- Store: Write register value to memory



a. Data memory unit


b. Sign extension unit

Load/Store Instructions

op	rs	rt	constant or address
6 bits	5 bits	5 bits	16 bits

lw: $R[rt] \leftarrow \text{Mem}[R[rs] + \text{sign_ext}[\text{Imm16}]]$

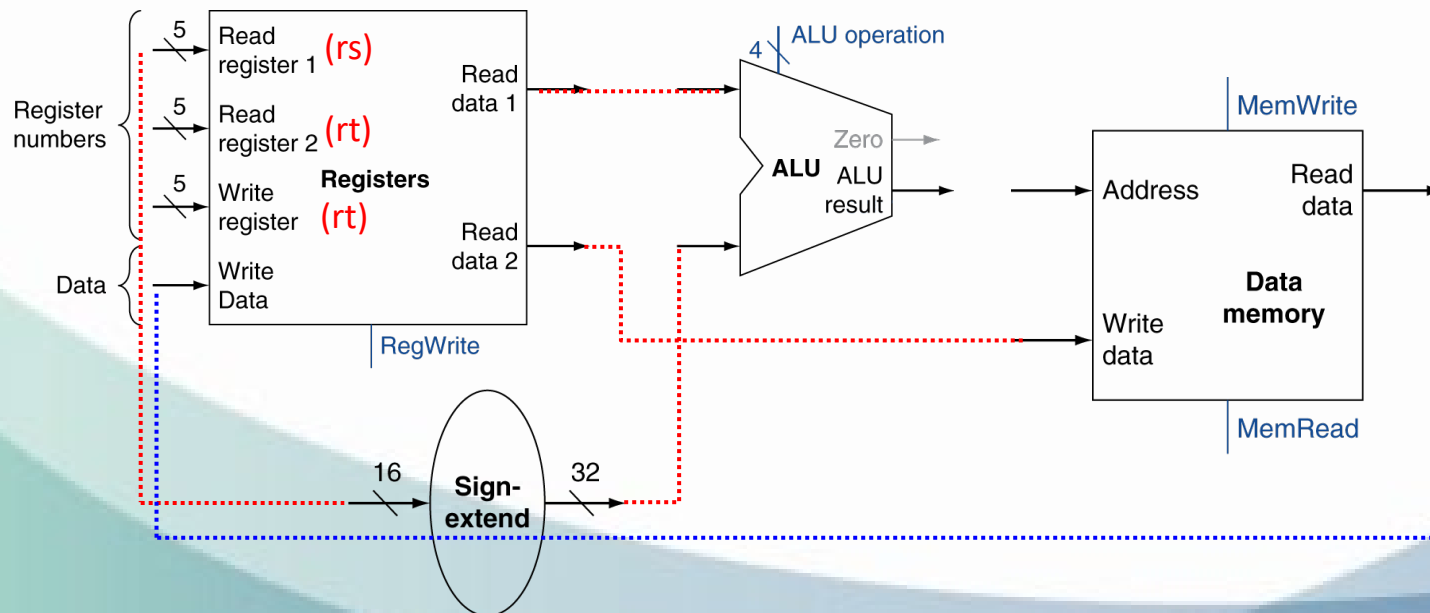sw: $\text{Mem}[R[rs] + \text{sign_ext}[\text{Imm16}]] \leftarrow R[rt]$



Branch Instructions

$$\text{beq: } PC \leftarrow \begin{cases} PC+4+(\text{sign_ext}[\text{Imm16}] \ll 2), & \text{if } R[\text{rs}] == R[\text{rt}] \\ PC+4, & \text{otherwise.} \end{cases}$$

- Read two register operands and one offset


- two registers compared for equality
- a 16-bit offset for **branch target address**
 - Left shifted sign-extended offset + (PC+4)

- Compare two register operands


- Subtract and check Zero signal (ALU)

- Calculate target address

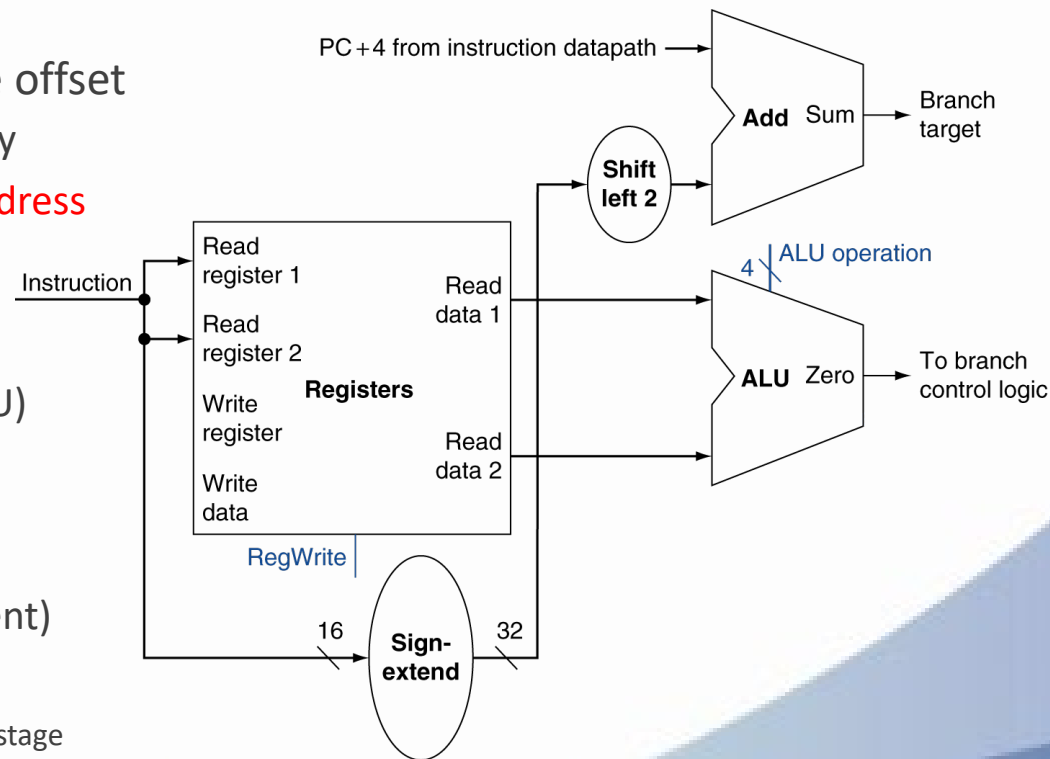
- Sign-extend the 16-bit offset
- Shift left 2 places (word displacement)
- Add to PC + 4
 - Already calculated in the "Instruction Fetch" stage



Instruction Decode


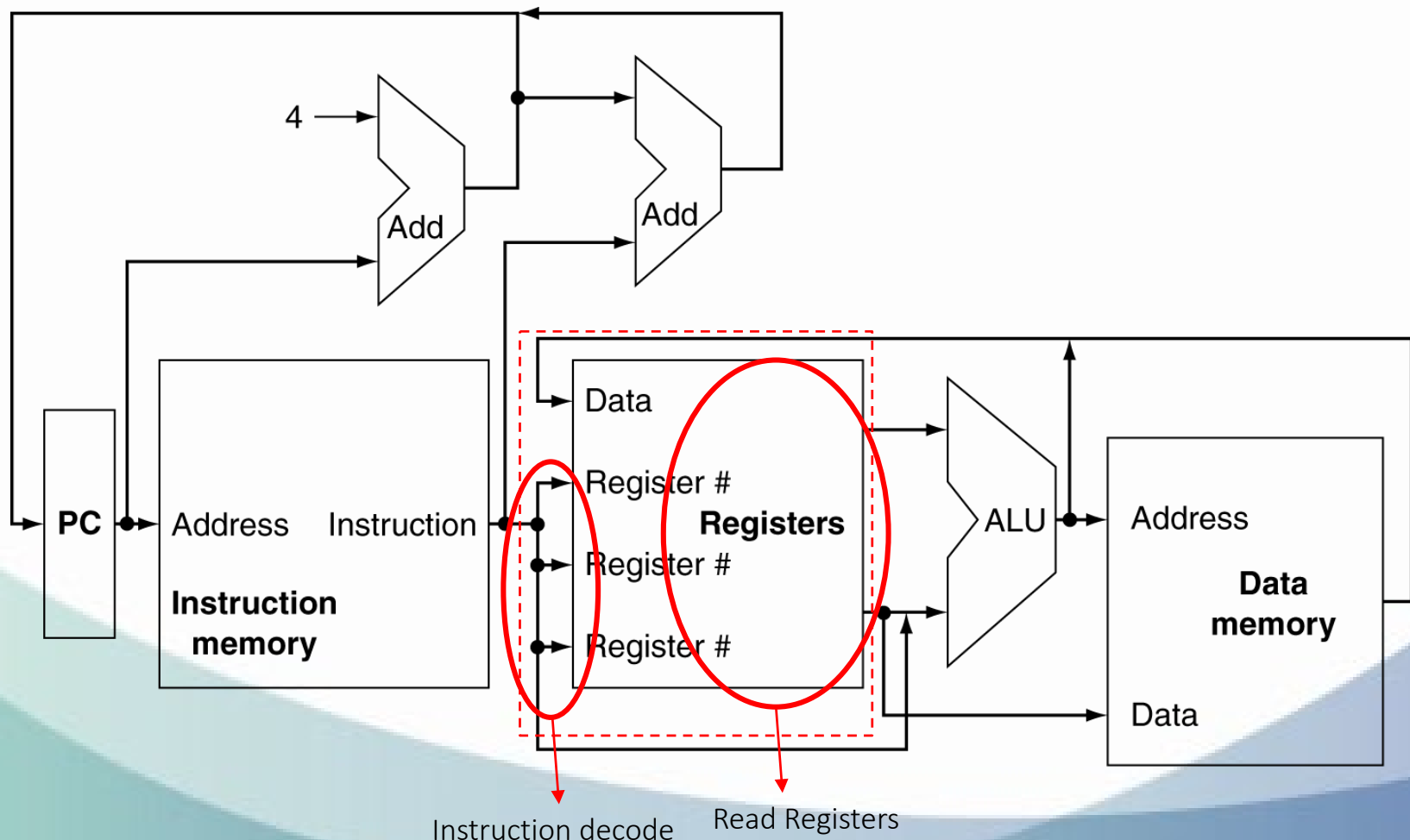


Execution (ALU)

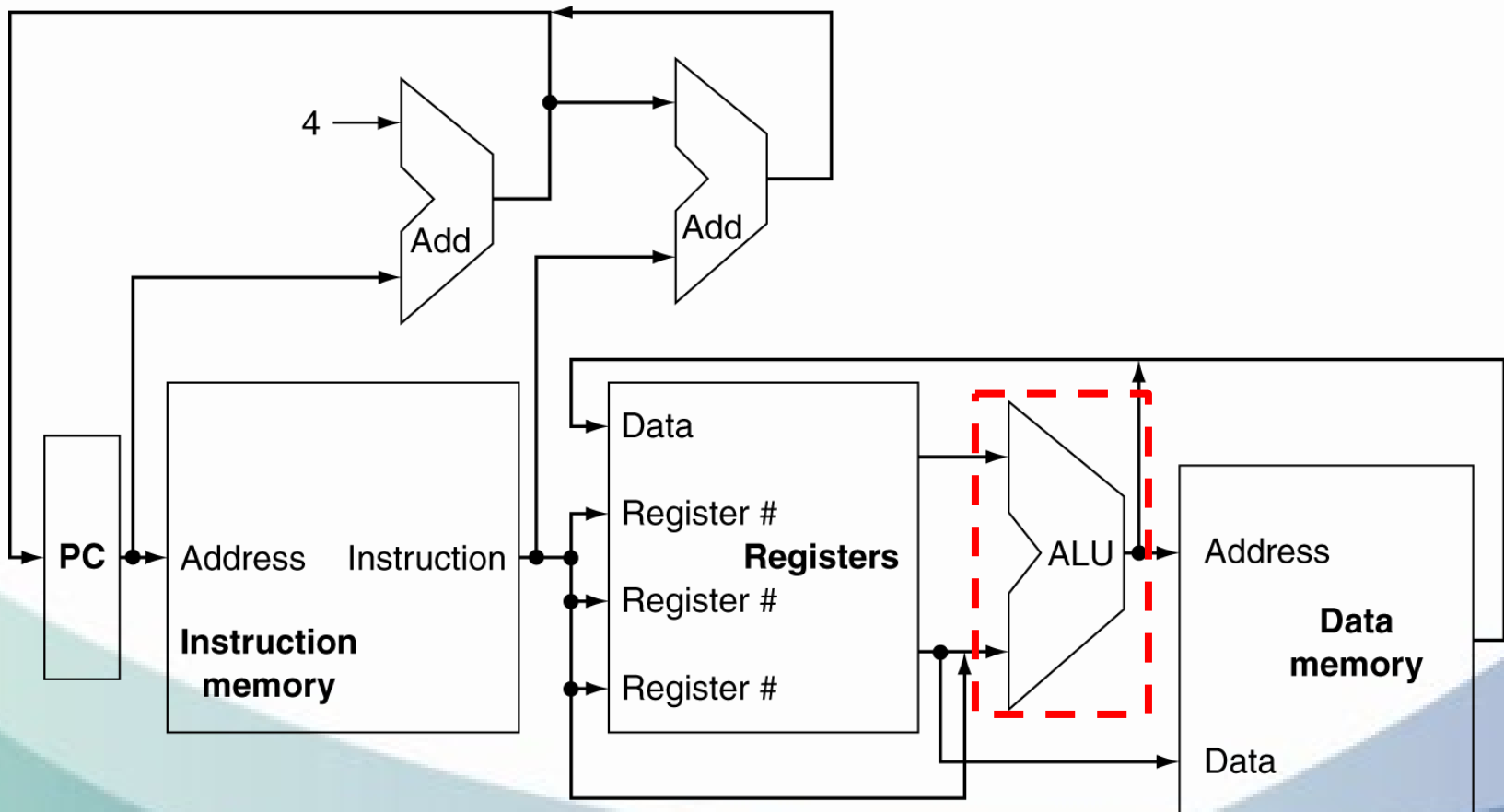


Execution (ALU)

  - Arithmetic operations (R-type)
- Memory address calculation for load/store
 - `lw $s2, 28($s1)`
 - $A = \$s1, B = 28$
- Branch condition
 - `beq $s1, $s2, Exit`
 - $\$s1 - \$s2 \text{ (rs-rt==0?)}$



Store Memory

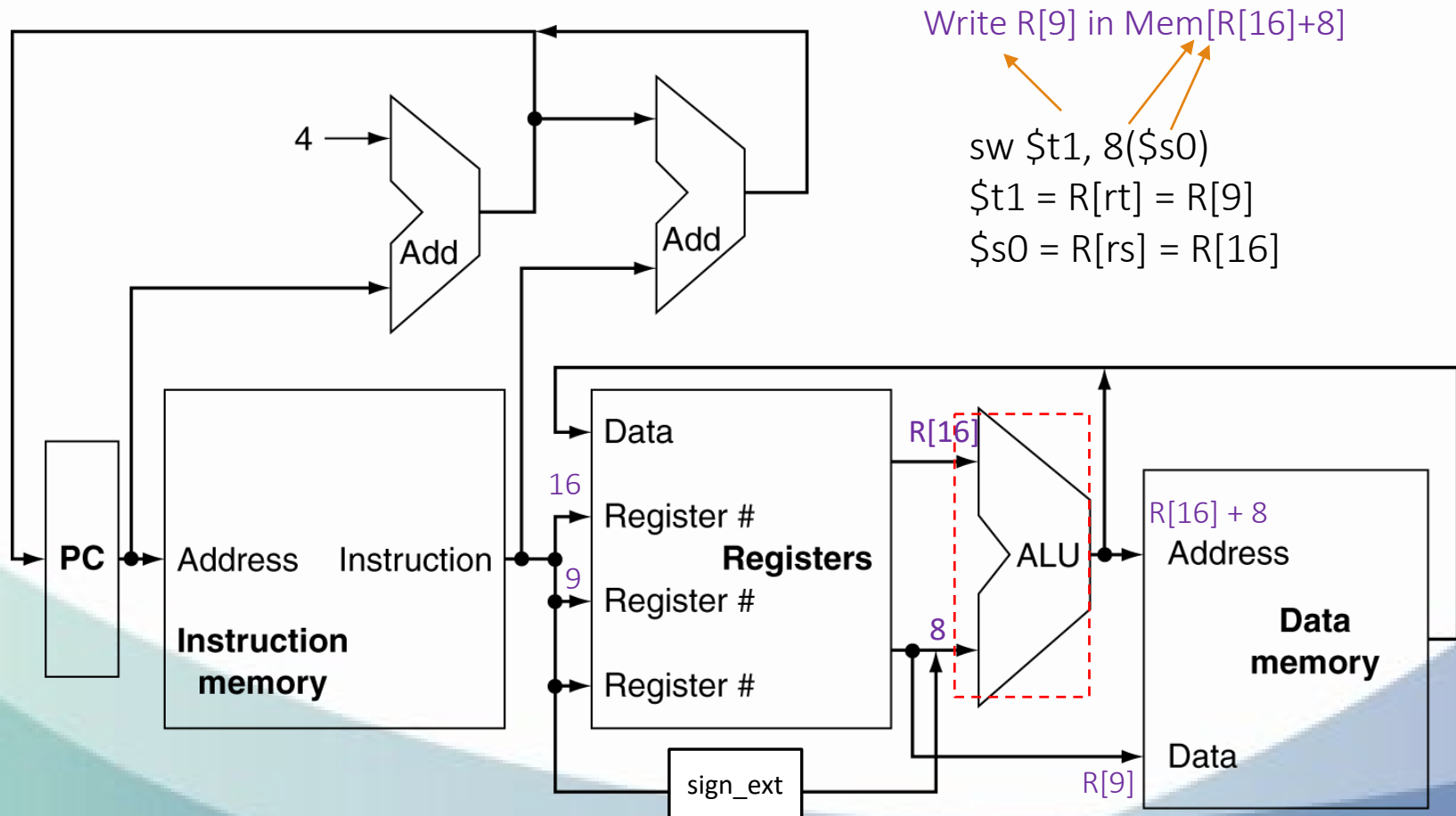

Write Back to Register

- Reg to Reg (R-type) or Mem to Reg (lw)
 - Write ALU result back to R[rd] (for R-type)
 - Write memory data to R[rt] (for lw)

