

PEARSON



# Chapter 5 – Flip-Flops and Related Devices

ELEVENTH EDITION

## Digital Systems

### Principles and Applications

**Ronald J. Tocci**

Monroe Community College

**Neal S. Widmer**

Purdue University

**Gregory L. Moss**

Purdue University


PEARSON

## Chapter 5 Objectives

- *Selected areas covered in this chapter:*
  - Constructing/analyzing operation of latch flip-flops made from NAND or NOR gates.
  - Differences of synchronous/asynchronous systems.
  - Major differences between parallel & serial transfers.
  - Operation of edge-triggered flip-flops.
  - Typical characteristics of Schmitt triggers.
  - Effects of clock skew on synchronous circuits.
  - Troubleshoot various types of flip-flop circuits.
  - Sequential circuits with PLDs using schematic entry.
  - Logic primitives, components & libraries in HDL code.
  - Structural level circuits from components.

 
## Chapter 5 Introduction

- Block diagram of a general digital system that combines combinational logic gates with memory devices.


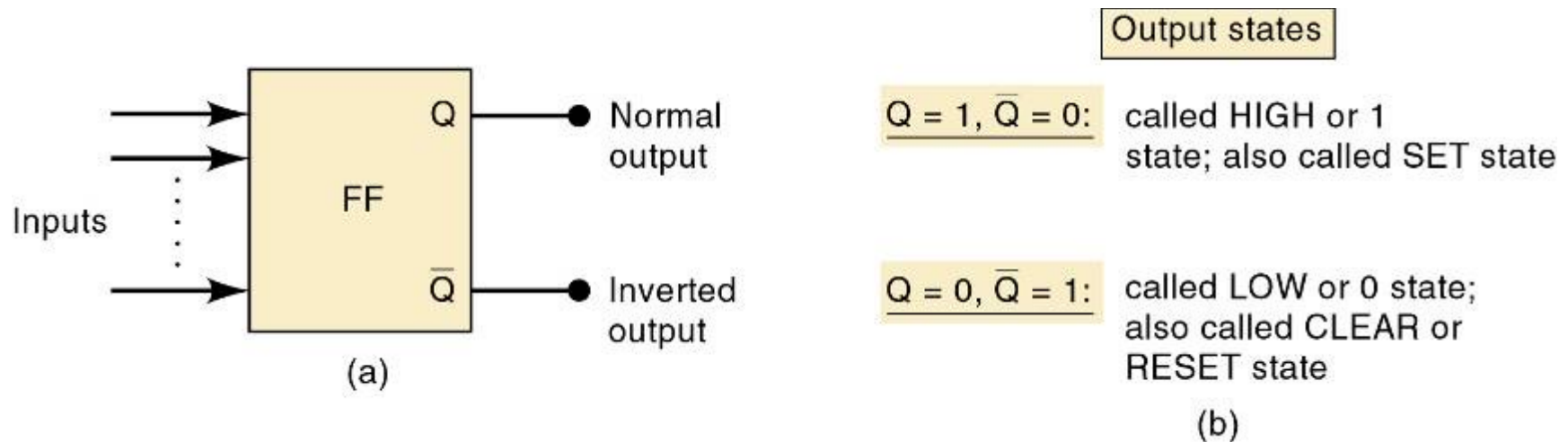
## Chapter 5 Introduction



- The most important memory element is the **flip-flop (FF)**—made up of an assembly of logic gates.



The flip-flop is known by other names, including *latch* and *bistable multivibrator*.

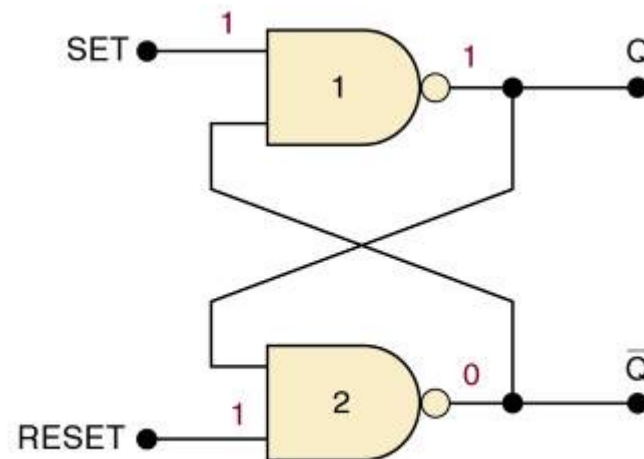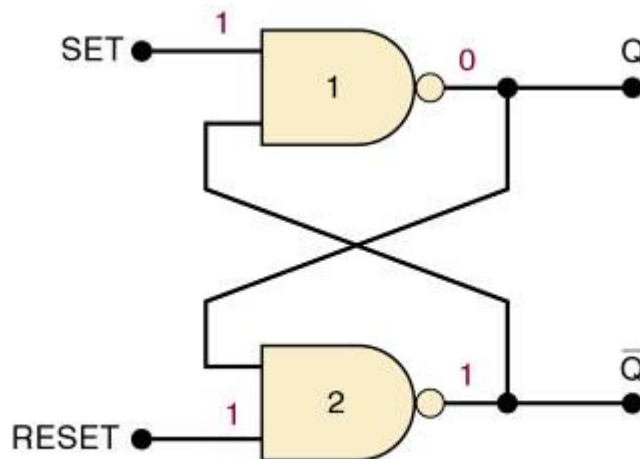
## 5-1 NAND Gate Latch

- The **NAND** gate latch or simply latch is a basic FF.
  - Inputs are *SET* and *CLEAR (RESET)*.
- Inputs are active-LOW—output will change when the input is pulsed LOW.
  - When the latch is set:  $Q = 1$  and  $\bar{Q} = 0$
  - When the latch is clear or reset:  $Q = 0$  and  $\bar{Q} = 1$


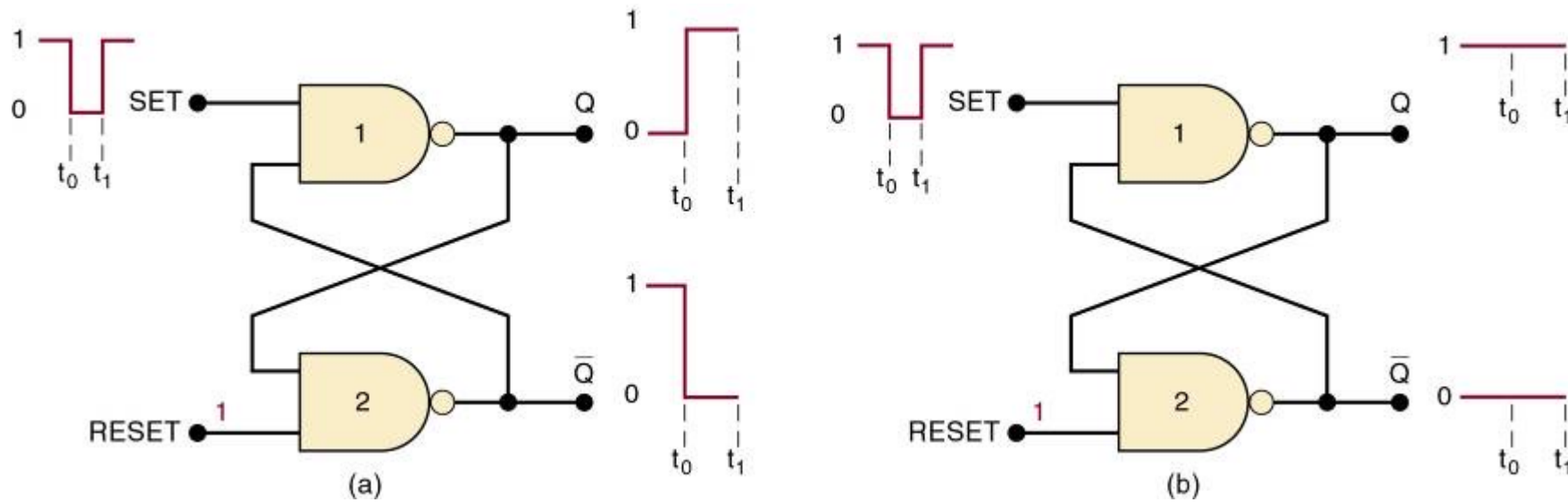
## 5-1 NAND Gate Latch – Setting the Latch (FF)

- Pulsing the SET input to the 0 state...
  - (a)  $Q = 0$  prior to SET pulse.
  - (b)  $Q = 1$  prior to SET pulse.





**In both cases,  $Q$  ends up HIGH.**


  
## 5-1 NAND Gate Latch – Resetting the Latch (FF)

- Pulsing RESET LOW when...
  - (a)  $Q = 0$  prior to the RESET pulse.
  - (b)  $Q = 1$  prior to the RESET pulse.




**In each case,  $Q$  ends up LOW.**


 
## 5-1 NAND Gate Latch – Alternate Representations

**NAND** latch equivalent representations  
and simplified block diagram.




## 5-1 NAND Gate Latch - Summary

- Summary of the **NAND** latch:
  - **SET = 1, RESET = 1**—Normal resting state, outputs remain in state they were in prior to input.
  - **SET = 0, RESET = 1**—Output will go to  $Q = 1$  and remains there, even after SET returns HIGH.
    - Called *setting* the latch.
  - **SET = 0, RESET = 0**—Will produce  $Q = 0$  LOW and remains there, even after RESET returns HIGH.
    - Called *clearing* or *resetting* the latch.
  - **SET = 0, RESET = 0**—Tries to set and clear the latch at the same time, and produces  $Q = \bar{Q} = 1$ .
    - Output is unpredictable, and this input condition should not be used.

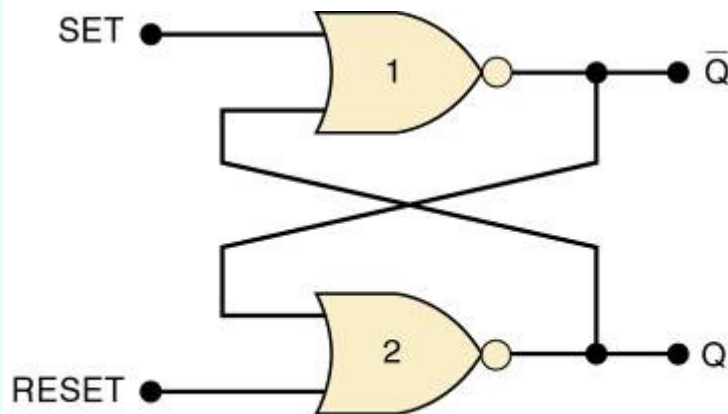
## 5-2 NOR Gate Latch

- Two cross-coupled **NOR** gates can be used as a **NOR** gate latch—similar to the **NAND** latch.
  - The **Q** and  $\bar{Q}$  outputs are reversed.



Set	Reset	Output
0	0	No change
1	0	$Q = 1$
0	1	$Q = 0$
1	1	Invalid*

\*Produces  $Q = \bar{Q} = 0$ .

 

The SET and RESET inputs are active-HIGH.  
Output will change when the input is pulsed HIGH.


## 5-1 NOR Gate Latch - Summary

- Summary of the **NOR** latch:
  - **SET = 0, RESET = 0**—Normal resting state, No effect on output state.
  - **SET = 1, RESET = 0**—will always set  $Q = 1$ , where it remains even after SET returns to 0.
  - **SET = 0, RESET = 1**—will always clear  $Q = 0$ , where it remains even after RESET returns to 0.
  - **SET = 1, RESET = 1**—Tries to set and reset the latch at the same time, and produces  $Q = \bar{Q} = 0$ .
    - Output is unpredictable, and this input condition should not be used.

- When power is applied, it is not possible to predict the starting state of a flip-flop's output.
  - If SET and RESET inputs are in their inactive state.
- To start a latch or FF in a particular state, it must be *placed* in that state by momentarily activating the SET or RESET input, at the start of operation.
  - Often achieved by application of a pulse to the appropriate input.

## 5-3 Troubleshooting Case Study

Switch Position	$\overline{\text{SET}}$ (Z1-1)	$\overline{\text{RESET}}$ (Z1-5)	$Q$ (Z1-3)	$\overline{Q}$ (Z1-6)	$X_A$ (Z2-3)	$X_B$ (Z2-6)
A	LOW	HIGH	LOW	HIGH	LOW	Pulses
B	HIGH	LOW	LOW	HIGH	LOW	Pulses

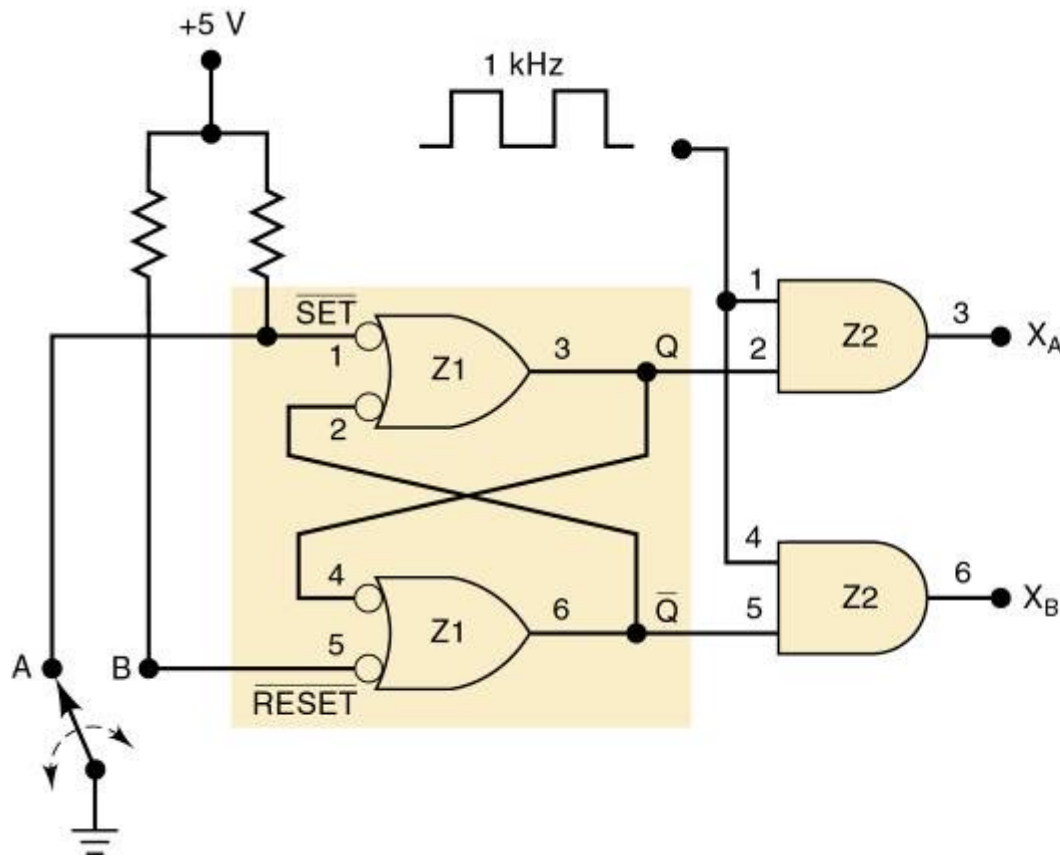

**Troubleshoot the circuit.**

Switch position	$X_A$	$X_B$
A	Pulses	LOW
B	LOW	Pulses

## 5-3 Troubleshooting Case Study


Switch Position	$\overline{\text{SET}}$ (Z1-1)	$\overline{\text{RESET}}$ (Z1-5)	$Q$ (Z1-3)	$\overline{Q}$ (Z1-6)	$X_A$ (Z2-3)	$X_B$ (Z2-6)
A	LOW	HIGH	LOW	HIGH	LOW	Pulses
B	HIGH	LOW	LOW	HIGH	LOW	Pulses

- There are several possibilities:
  - An internal open connection at Z1-1, which would prevent  $Q$  from responding to the input.
  - An internal component failure in NAND gate Z1 that prevents it from responding properly.
  - $Q$  output is stuck LOW, which could be caused by:
    - Z1-3 internally shorted to ground
    - Z1-4 internally shorted to ground
    - Z2-2 internally shorted to ground
    - The  $Q$  node externally shorted to ground



## 5-4 Digital Pulses

 
**Signals that switch between active and inactive states are called pulse waveforms.**



**A positive pulse has an active-HIGH level.**

## 5-4 Digital Pulses

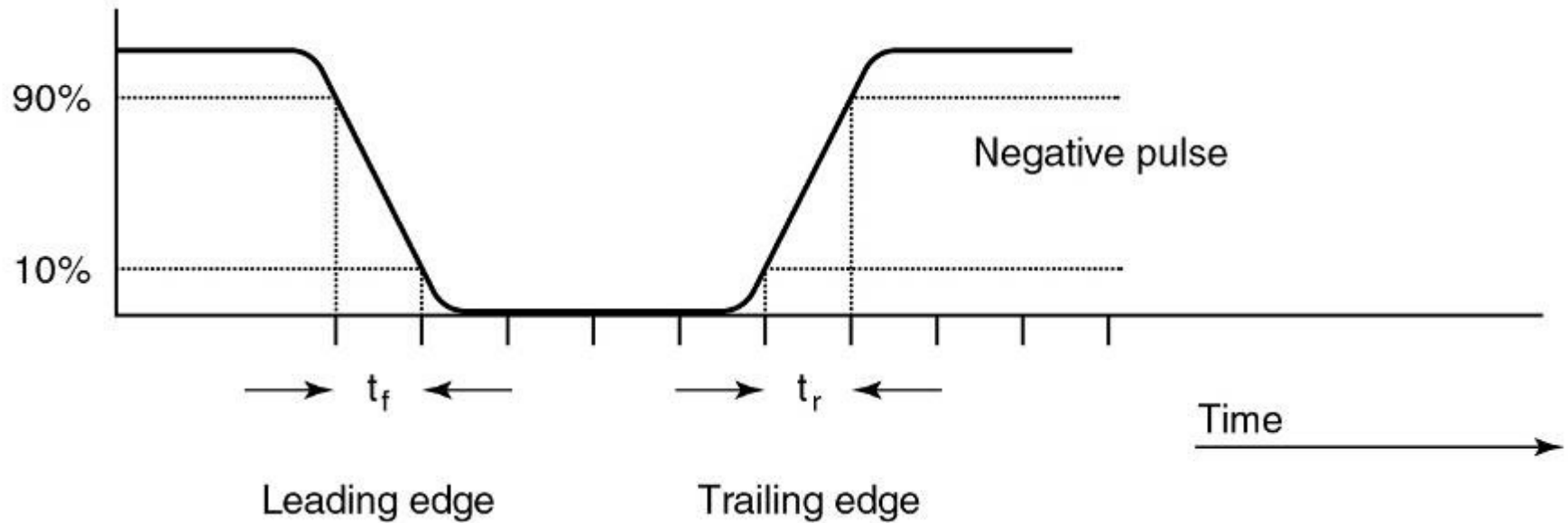
**Signals that switch between active and inactive states are called pulse waveforms.**



**A negative pulse has an active-LOW level.**
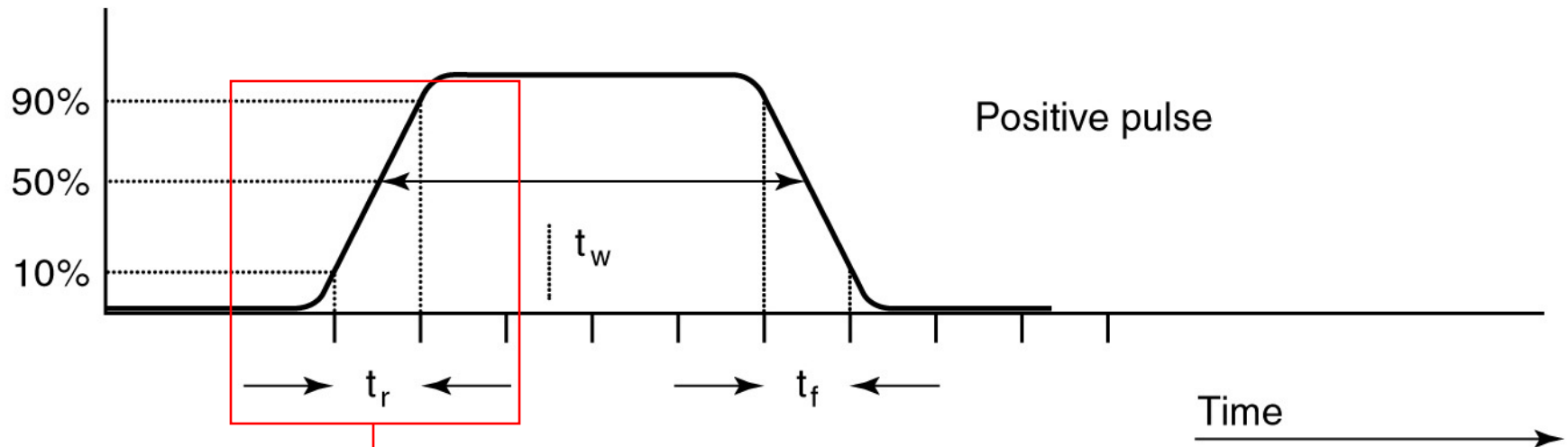
## 5-4 Digital Pulses


- In actual circuits it takes time for a pulse waveform to change from one level to the other.
  - Transition from LOW to HIGH on a positive pulse is called *rise time* ( $t_r$ ).



**Measured between the 10% and 90% points  
on the *leading edge* of the voltage waveform.**
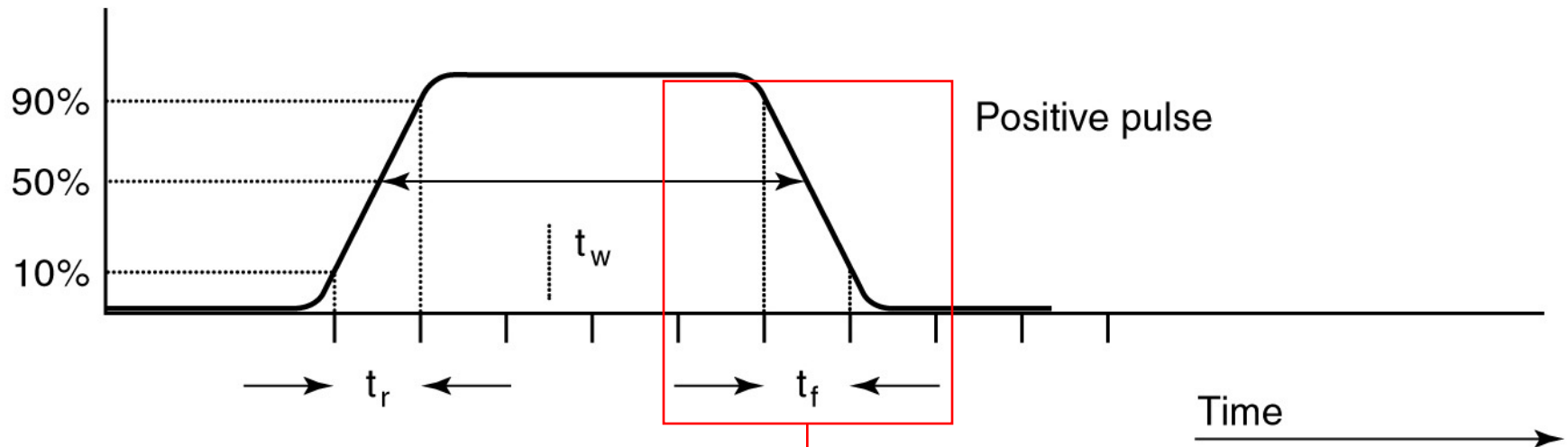
## 5-4 Digital Pulses


- In actual circuits it takes time for a pulse waveform to change from one level to the other.
  - Transition from HIGH to LOW on a positive pulse is called *fall time* ( $t_f$ ).



**Measured between the 90% and 10% points on the *trailing edge* of the voltage waveform.**
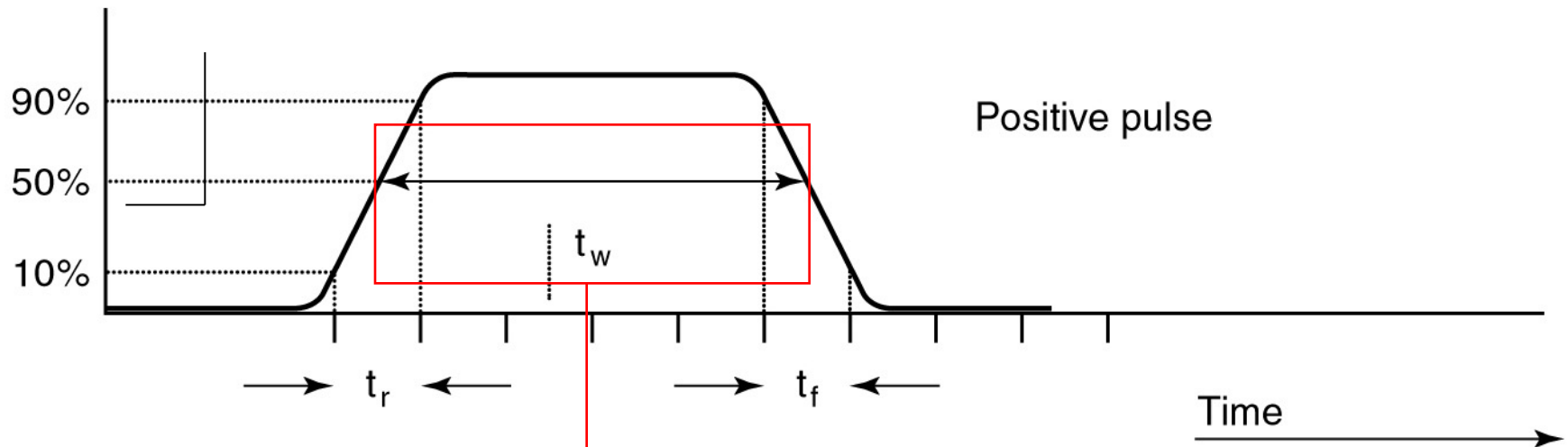
## 5-4 Digital Pulses

- In actual circuits it takes time for a pulse waveform to change from one level to the other.
  - A pulse also has a *duration*—width—( $t_w$ ).



The time between the points when the leading and trailing edges are at 50% of the HIGH level voltage.


## ● 5-5 Clock Signals and Clocked Flip-Flops

- Digital systems can operate either *asynchronously* or *synchronously*.
  - **Asynchronous system**—outputs can change state at any time the input(s) change.
  - **Synchronous system**—output can change state only at a specific time in the clock cycle.

## 5-5 Clock Signals and Clocked Flip-Flops

- The clock signal is a rectangular pulse train or square wave.
  - Positive going transition (PGT)—clock pulse goes from 0 to 1.
  - Negative going transition (NGT)—clock pulse goes from 1 to 0.

Transitions are also called *edges*.

 




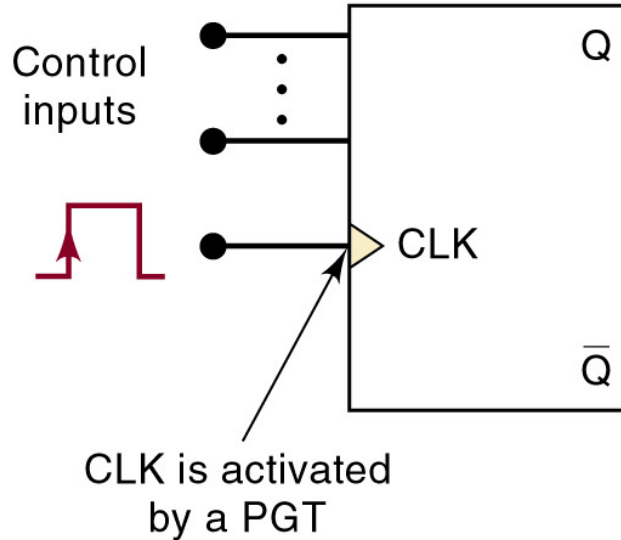
## 5-5 Clock Signals and Clocked Flip-Flops

- Clocked FFs change state on one or the other clock transitions.
  - Clock inputs are labeled CLK, CK, or CP.

A small triangle at the CLK input indicates that the input is activated with a PGT.





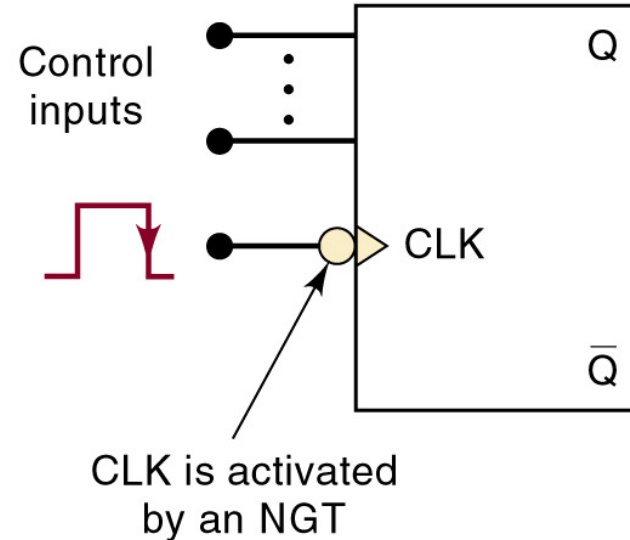A bubble and a triangle indicates that the CLK input is activated with a NGT.



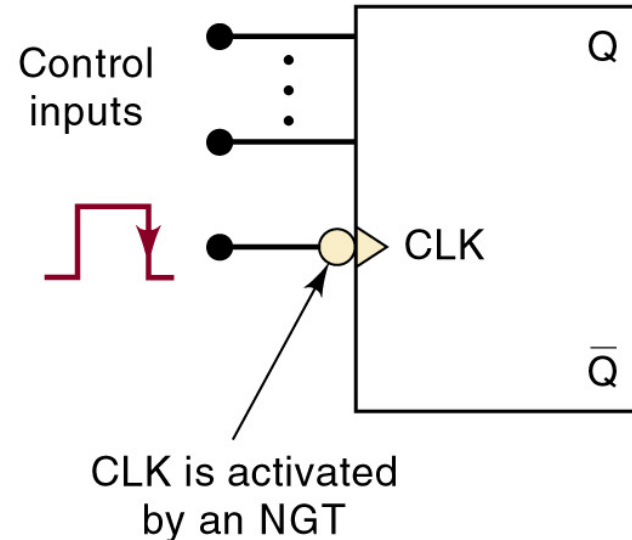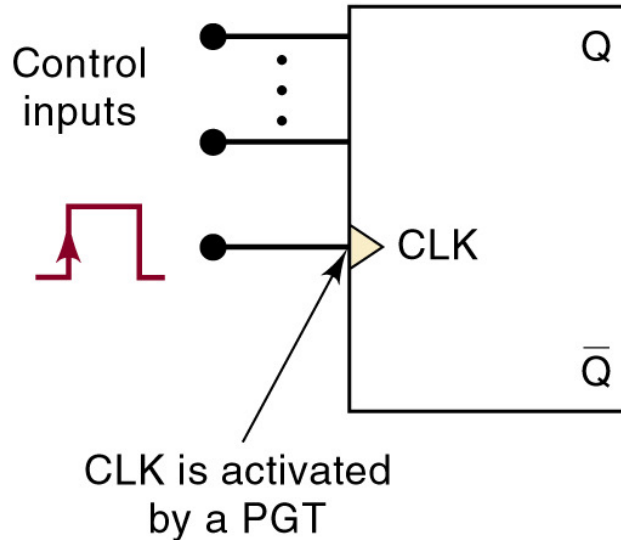
## 5-5 Clock Signals and Clocked Flip-Flops

- Control inputs have an effect on the output only at the active clock transition (NGT or PGT)—also called synchronous control inputs.
  - The control inputs get the outputs ready to change, but the change is not triggered until the CLK edge.



 
## 5-5 Clock Signals and Clocked Flip-Flops

- *Setup time* ( $t_s$ ) is the minimum time interval before the active CLK transition that the control input must be kept at the proper level.


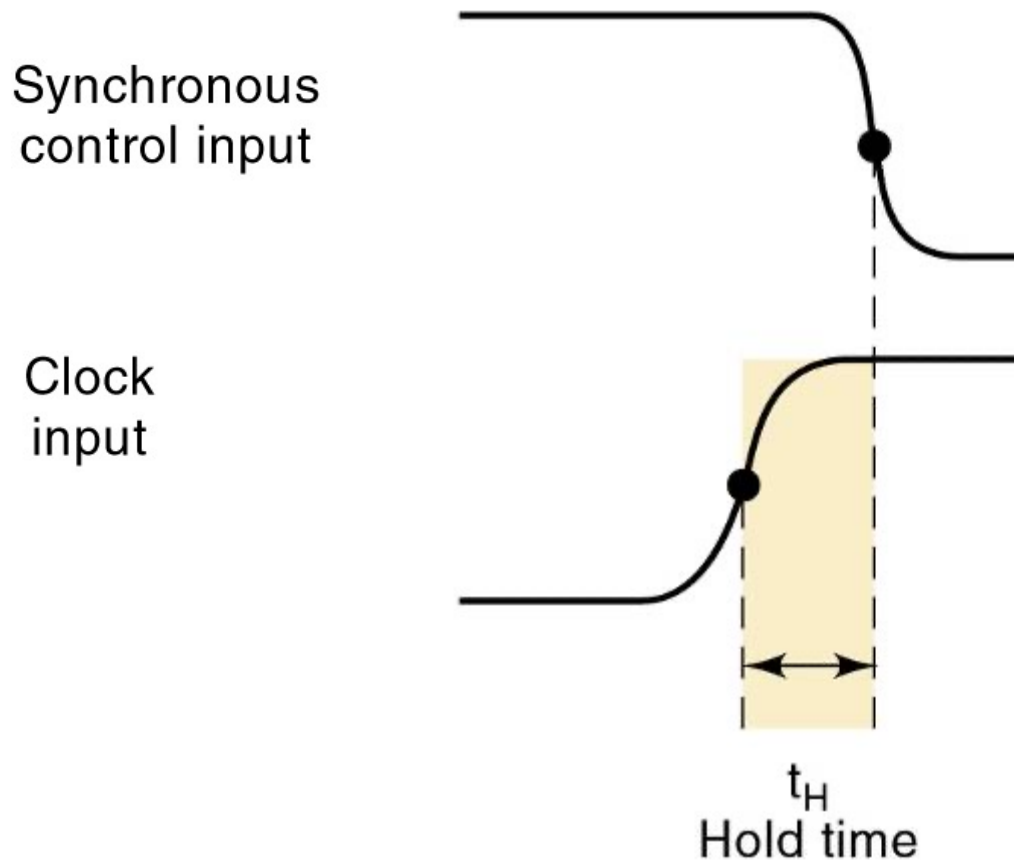
## 5-5 Clock Signals and Clocked Flip-Flops

- *Hold time* ( $t_H$ ) is the time following the active transition of the CLK, during which the control input must be kept at the proper level.




## 5-6 Clocked S-R Flip-Flop

- The  $S$  and  $R$  inputs are synchronous *control* inputs, which control the state the FF will go to when the clock pulse occurs.
  - The  $CLK$  input is the **trigger** input that causes the FF to change states according to the  $S$  and  $R$  inputs.
- SET-RESET (or SET-CLEAR) FF will change states at positive- or negative-going clock edges.

## 5-6 Clocked S-R Flip-Flop

 **A clocked S-R flip-flop triggered by the positive-going edge of the clock signal.**




Inputs			Output
S	R	CLK	Q
0	0	↑	$Q_0$ (no change)
1	0	↑	1
0	1	↑	0
1	1	↑	Ambiguous

$Q_0$  is output level prior to ↑ of CLK.  
↓ of CLK produces no change in Q.

The  $S$  and  $R$  inputs control the state of the FF in the same manner as described earlier for the **NOR** gate latch, but the FF does *not* respond to these inputs *until* the occurrence of the PGT of the clock signal.
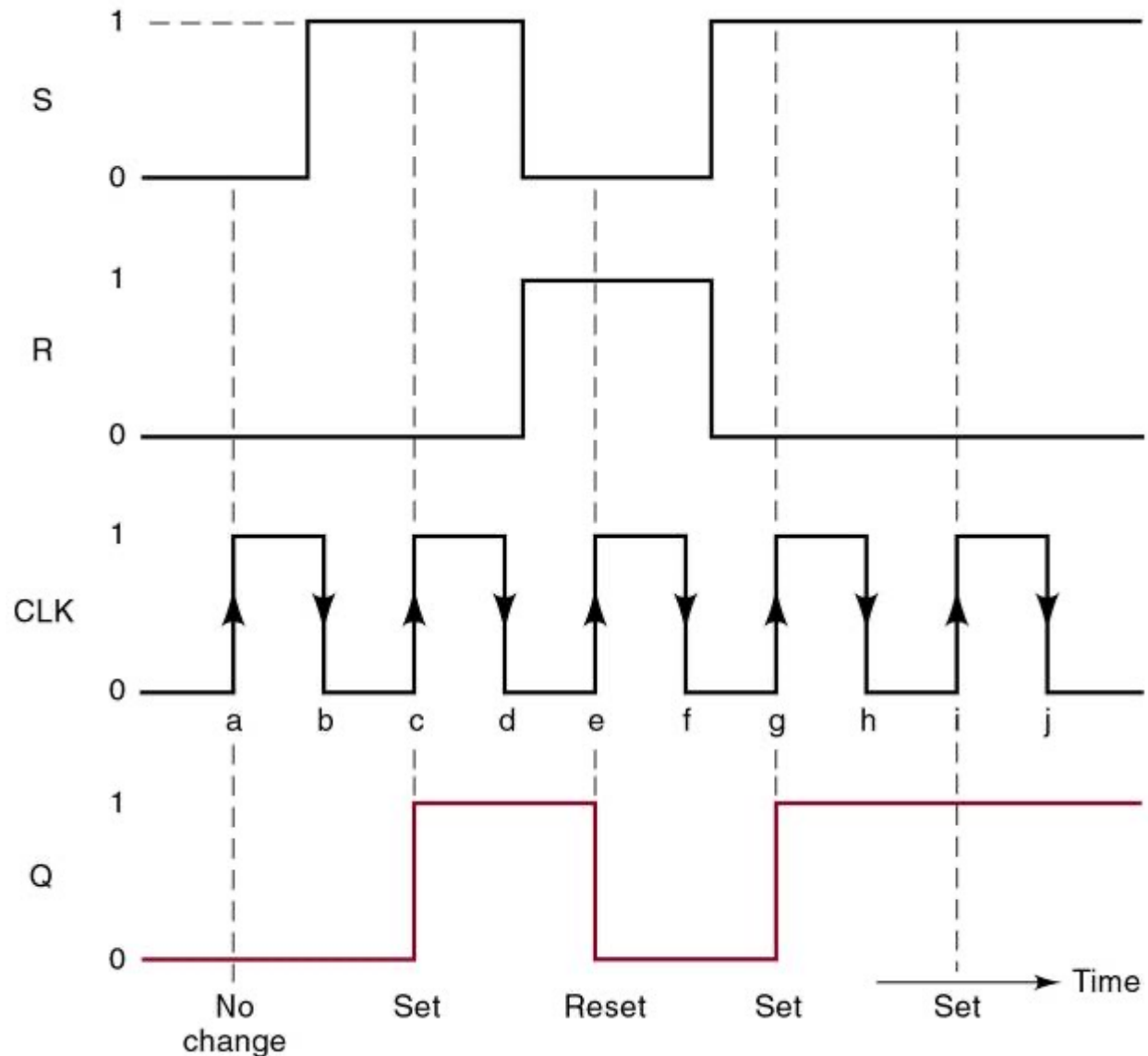
## 5-6 Clocked S-R Flip-Flop


Waveforms of the operation of a clocked S-R flip-flop triggered by the positive-going edge of a clock pulse.





## 5-6 Clocked S-R Flip-Flop

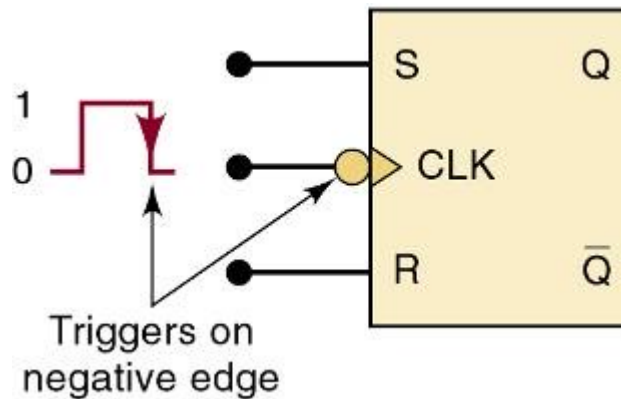
**A clocked S-R flip-flop triggered by the negative-going edge of the clock signal.**



Inputs			Output
S	R	CLK	Q
0	0	↓	$Q_0$ (no change)
1	0	↓	1
0	1	↓	0
1	1	↓	Ambiguous

Both positive-edge and negative-edge triggering FFs are used in digital systems.


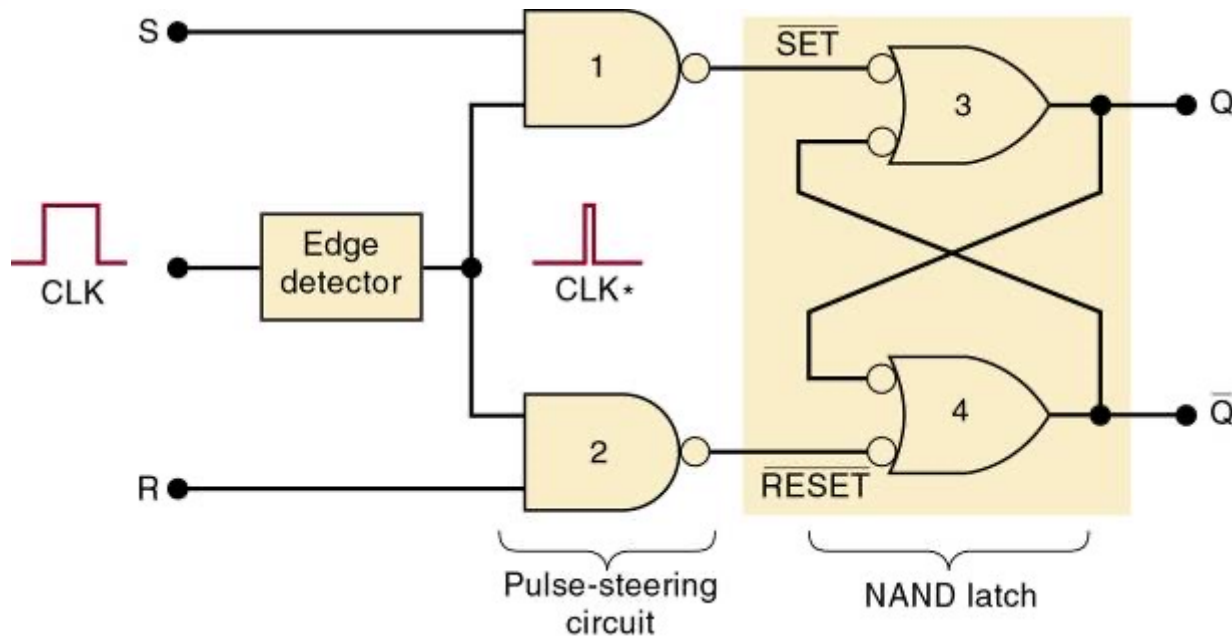
## 5-6 Clocked S-R Flip-Flop – Internal Circuitry





- An edge-triggered S-R flip-flop circuit features:
  - A basic **NAND** gate latch formed by **NAND-3** and **NAND-4**.
  - A **pulse-steering circuit** formed by **NAND-1** and **NAND-2**.
  - An **edge-detector circuit**.
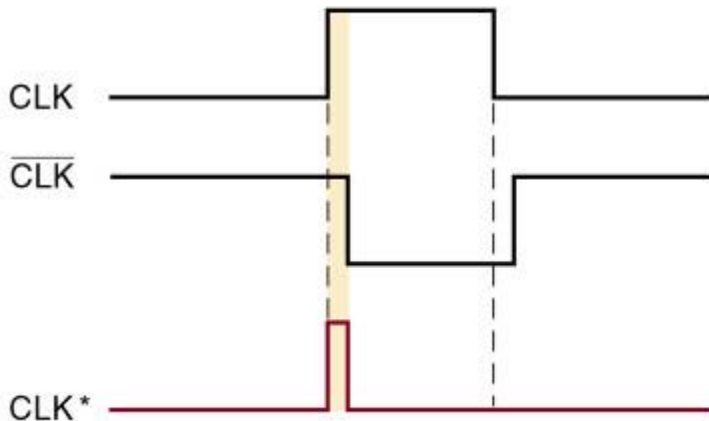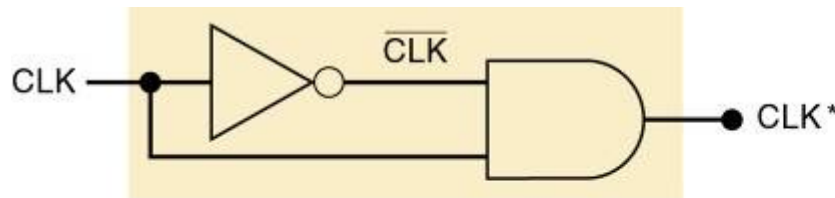
## 5-6 Clocked S-R Flip-Flop – Internal Circuitry

- Implementation of edge-detector circuits used in edge-triggered flip-flops:
  - (a) PGT; (b) NGT.



(a)

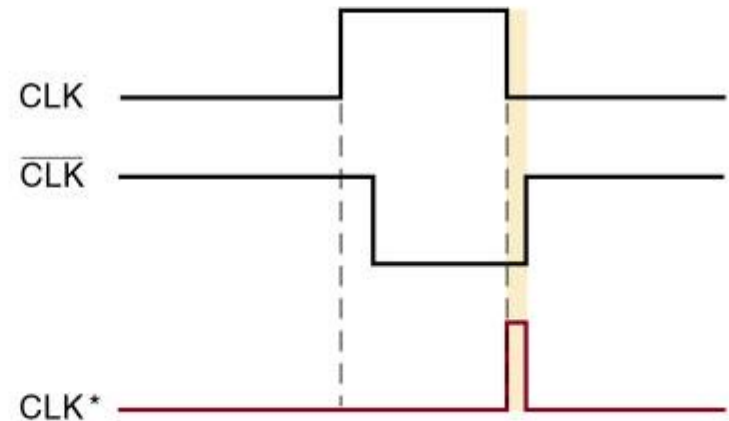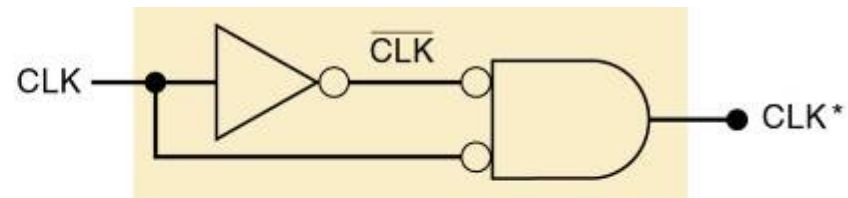

(b)


The duration of the  $\text{CLK}^*$  pulses is typically 2–5 ns.

## 5-7 Clocked J-K Flip-Flop


- Operates like the S-R FF.
  - J is SET, K is CLEAR.
- When J and K are both HIGH, output is toggled to the opposite state.
  - May be positive going or negative going clock trigger.
- Much more versatile than the S-R flip-flop, as it has no ambiguous states.
  - Has the ability to do everything the S-R FF does, plus operates in toggle mode.

## 5-7 Clocked J-K Flip-Flop

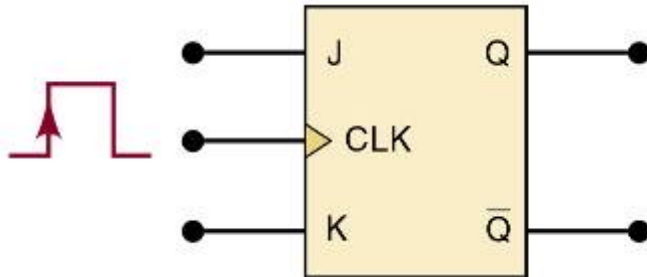**Clocked J-K flip-flop that responds only to the positive edge of the clock.**




J	K	CLK	Q
0	0	↑	$Q_0$ (no change)
1	0	↑	1
0	1	↑	0
1	1	↑	$\bar{Q}_0$ (toggles)

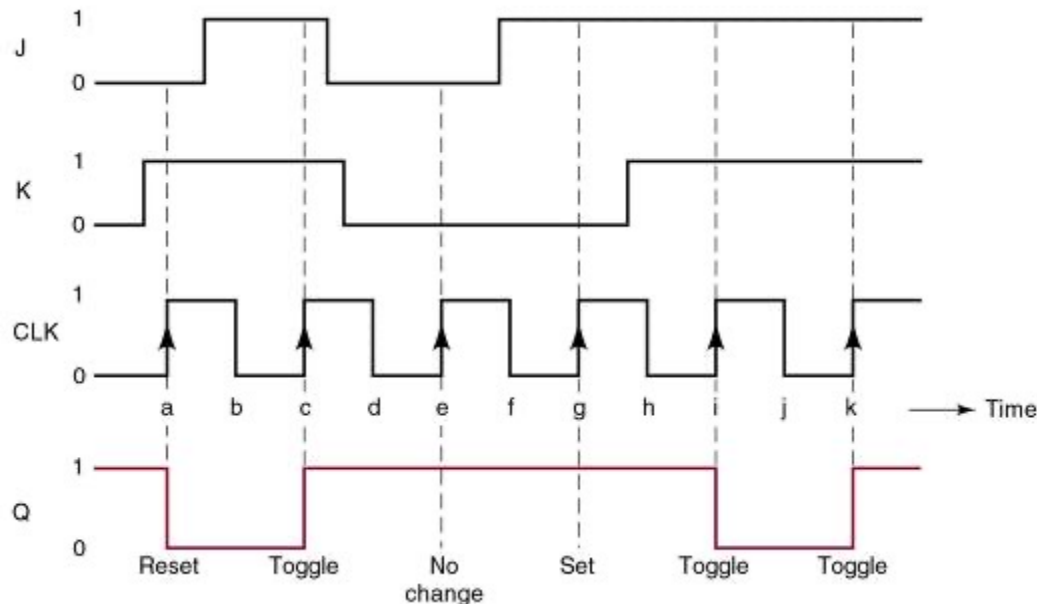

## 5-7 Clocked J-K Flip-Flop

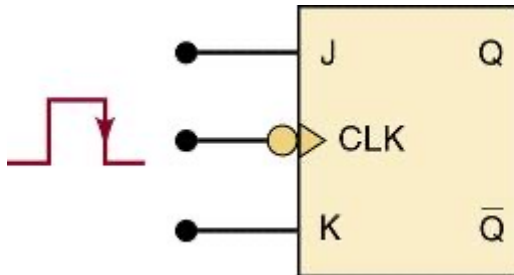
**Clocked J-K flip-flop that responds only to the negative edge of the clock.**



J	K	CLK	Q
0	0	↓	$Q_0$ (no change)
1	0	↓	1
0	1	↓	0
1	1	↓	$\overline{Q_0}$ (toggles)
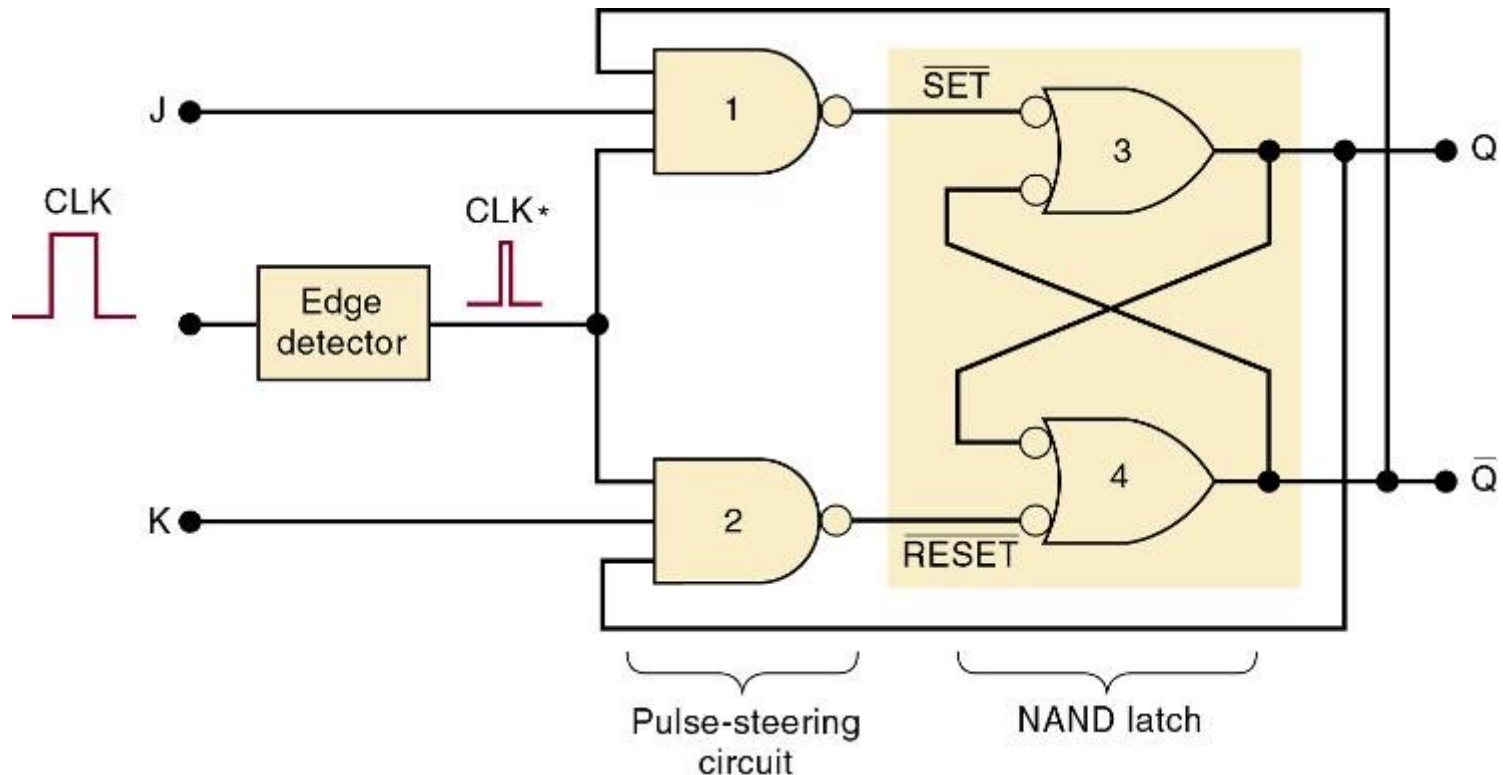
## 5-7 Clocked J-K Flip-Flop – Internal Circuitry

- The internal circuitry of an edge-triggered J-K flip-flop contains the same three sections as the edge-triggered S-R flip-flop.







## 5-8 Clocked D Flip-Flop

- One data input—output changes to the value of the input at either the positive- or negative-going clock trigger.
- May be implemented with a J-K FF by tying the J input to the K input through an inverter.
- Useful for parallel data transfer.

## 5-8 Clocked D Flip-Flop

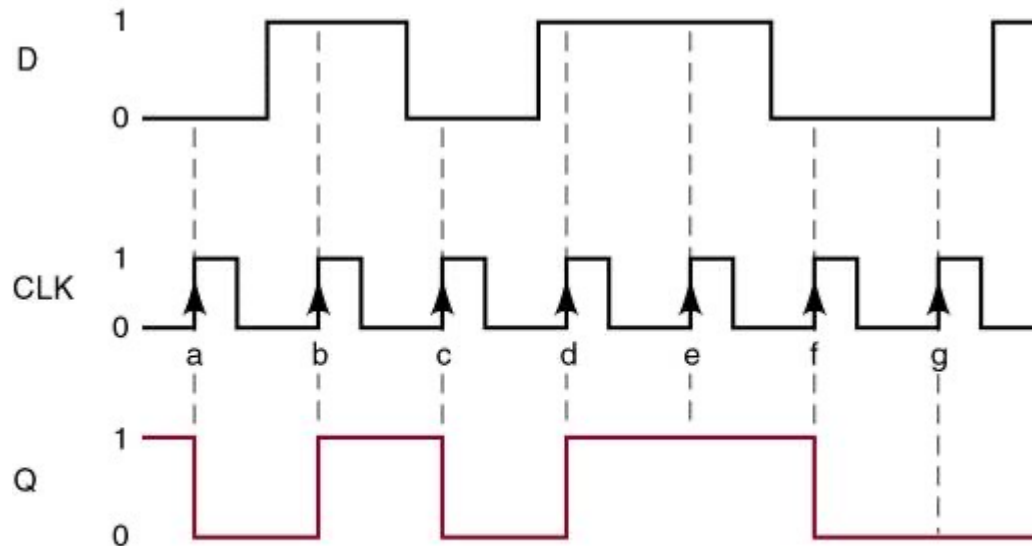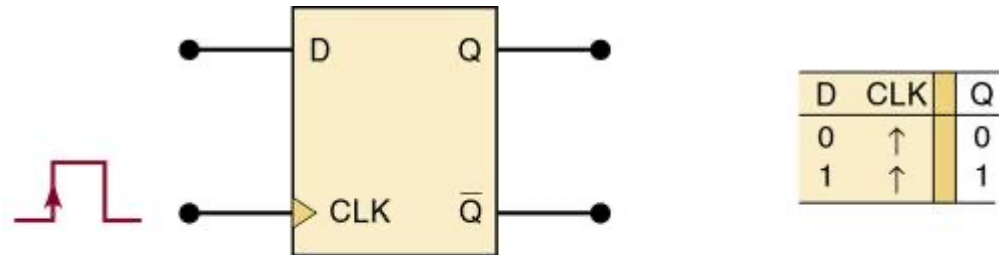
**D flip-flop that triggers only on positive-going transitions.**



## 5-8 Clocked D Flip-Flop - Implementation

- An edge-triggered D flip-flop is implemented by adding a single INVERTER to the edge-triggered J-K flip-flop.
  - The same can be done to convert a S-R flip-flop to a D flip-flop.

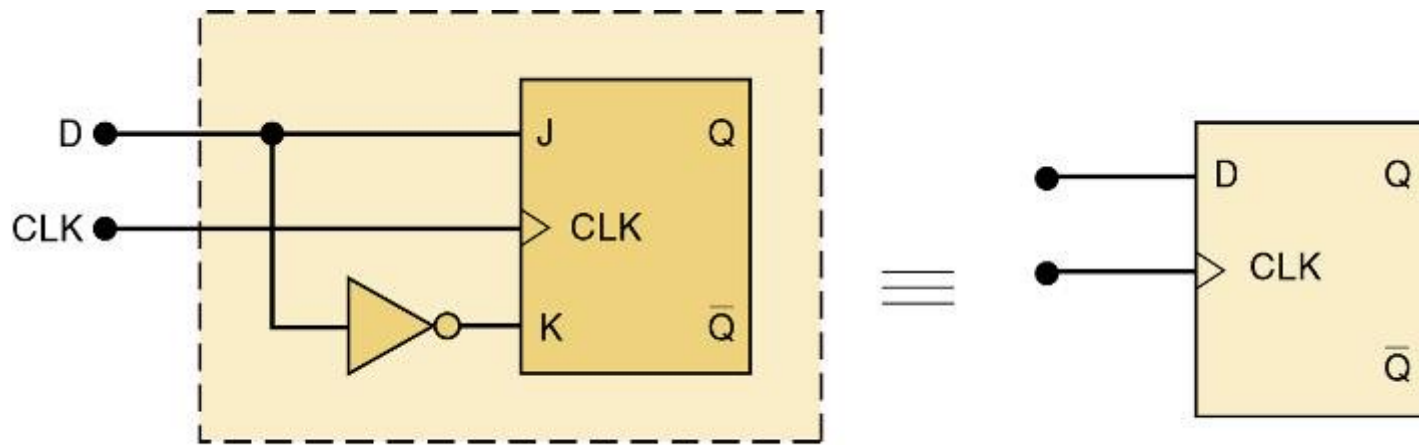
### Edge-triggered D flip-flop implementation from a J-K flip-flop.



## 5-8 Clocked D Flip-Flop – Parallel Data Transfer

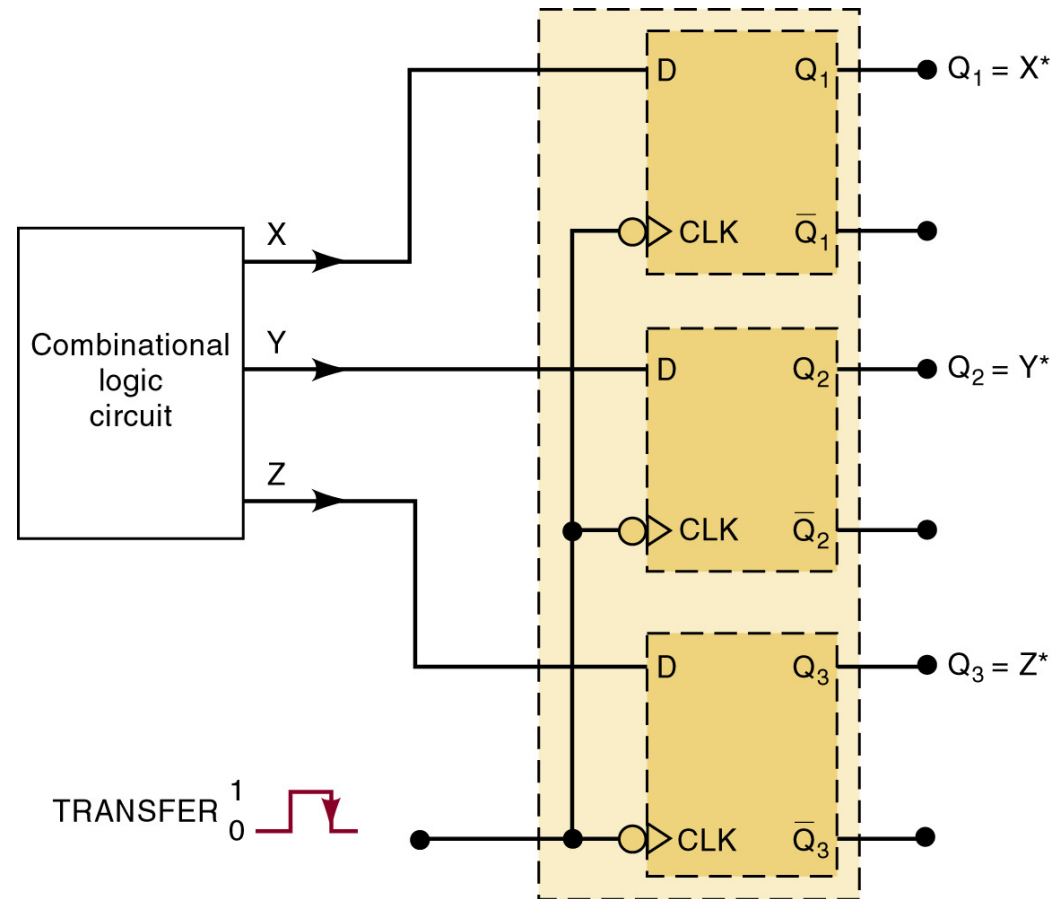**Outputs  $X$ ,  $Y$ ,  $Z$  are to be transferred to FFs  $Q_1$ ,  $Q_2$ , and  $Q_3$  for storage.**

Using D flip-flops, levels present at  $X$ ,  $Y$  &  $Z$  will be transferred to  $Q_1$ ,  $Q_2$  &  $Q_3$ , upon application of a TRANSFER pulse to the common  $CLK$  inputs.




\*After occurrence of NGT
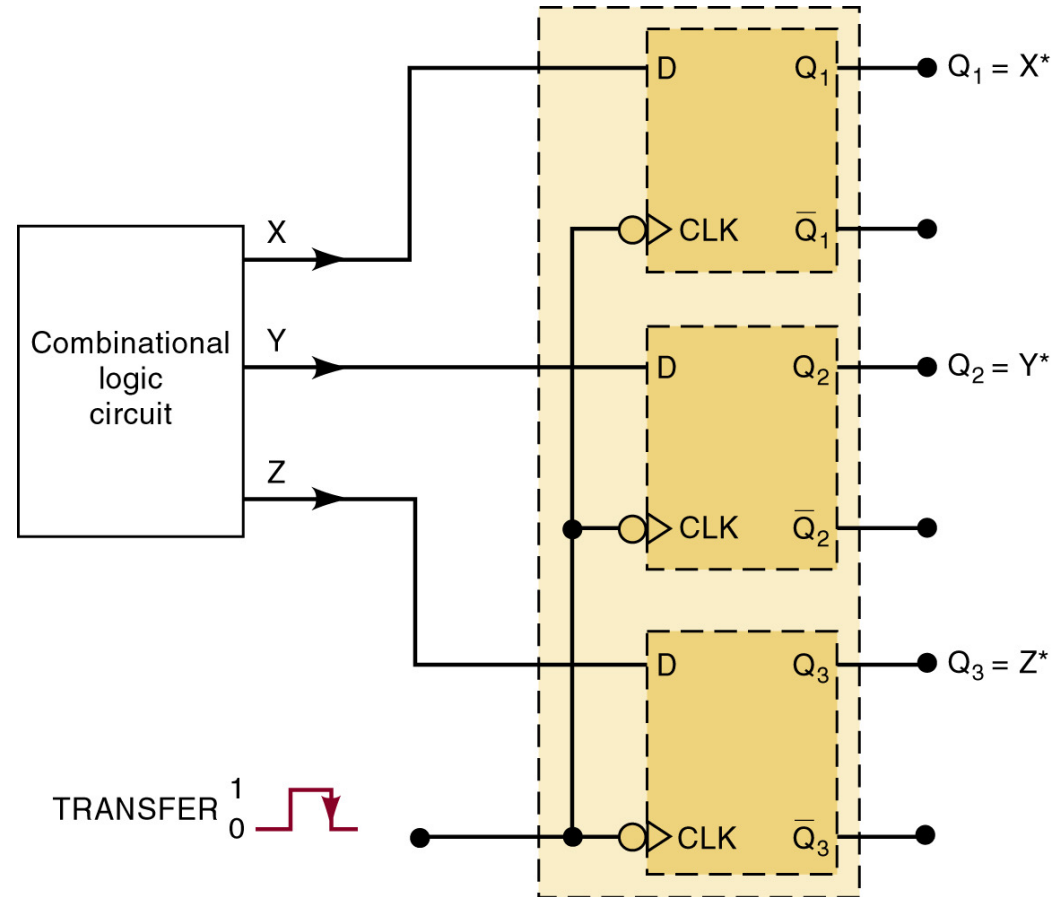
## 5-8 Clocked D Flip-Flop – Parallel Data Transfer

Outputs  $X$ ,  $Y$ ,  $Z$  are to be transferred to FFs  $Q_1$ ,  $Q_2$ , and  $Q_3$  for storage.

This is an example of **parallel data transfer** of binary data—the three bits  $X$ ,  $Y$  &  $Z$  are transferred *simultaneously*.




\*After occurrence of NGT

## 5-9 D Latch (Transparent Latch)

- The edge-triggered D flip-flop uses an edge-detector circuit to ensure the output responds to the *D* input *only* on active transition of the clock.
  - If this edge detector is not used, the resultant circuit operates as a **D latch**.


## 5-9 D Latch (Transparent Latch)
 
## D latch structure, function table, logic symbol.



Inputs		Output
EN	D	Q
0	X	Q <sub>0</sub> (no change)
1	0	0
1	1	1

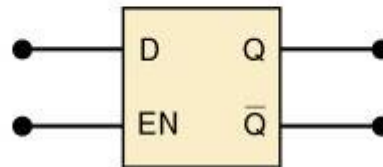"X" indicates "don't care."  
Q<sub>0</sub> is state Q just  
prior to EN going LOW.



## 5-9 D Latch (Transparent Latch)

- The circuit contains the **NAND** latch and the steering **NAND** gates 1 and 2 *without* the edge-detector circuit.
- The common input to the steering gates is called an *enable* input (abbreviated *EN*)—rather than a clock input.
  - Its effect on the  $Q$  and  $\bar{Q}$  outputs is not restricted to occurring only on its transitions




## 5-10 Asynchronous Inputs

- Inputs that depend on the clock are synchronous.
- Most clocked FFs have asynchronous inputs that do not depend on the clock.
  - Labels PRE & CLR are used for asynchronous inputs.
- Active-LOW asynchronous inputs will have a bar over the labels and inversion bubbles.
- If the asynchronous inputs are not used they will be tied to their inactive state.

## 5-10 Asynchronous Inputs
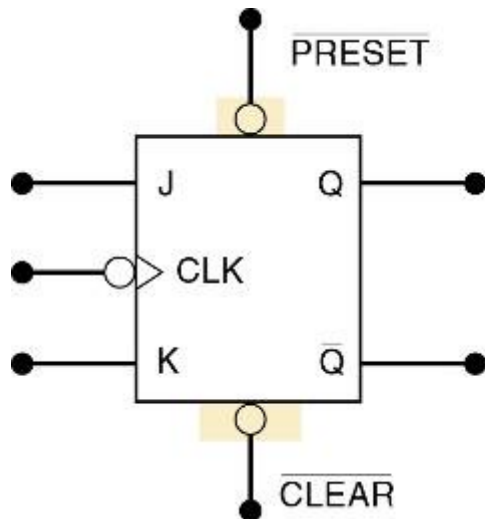
### Clocked J-K flip-flop with asynchronous inputs.




J	K	Clk	$\overline{\text{PRE}}$	$\overline{\text{CLR}}$	Q
0	0	↓	1	1	Q (no change)
0	1	↓	1	1	0 (Synch reset)
1	0	↓	1	1	1 (Synch set)
1	1	↓	1	1	$\bar{Q}$ (Synch toggle)
x	x	x	1	1	Q (no change)
x	x	x	1	0	0 (asynch clear)
x	x	x	0	1	1 (asynch preset)
x	x	x	0	0	(Invalid)

## 5-10 Asynchronous Inputs - Designations


- IC manufacturers do not agree on nomenclature for asynchronous inputs.
  - The most common designations are *PRE* (PRESET) and *CLR* (CLEAR).
    - Clearly distinguished from synchronous SET & RESET.
  - Labels such as *S-D* (direct SET) and *R-D* (direct RESET) are also used.
 
## 5-10 Asynchronous Inputs

A J-K FF that responds to a NGT on its clock input and has active-LOW asynchronous inputs.



Point	Operation
a	Synchronous toggle on NGT of CLK
b	Asynchronous set on $\overline{PRE} = 0$
c	Synchronous toggle
d	Synchronous toggle
e	Asynchronous clear on $\overline{CLR} = 0$
f	$\overline{CLR}$ overrides the NGT of CLK
g	Synchronous toggle

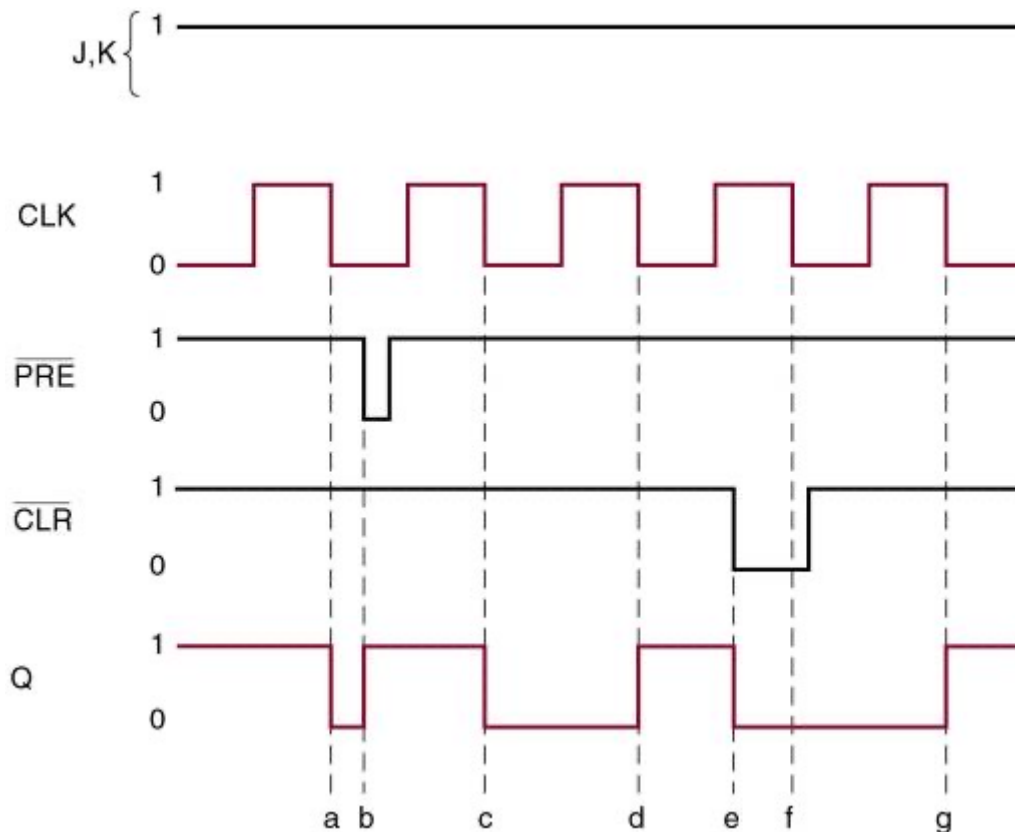


## 5-11 Flip-Flop Timing Considerations - Parameters

- Important timing parameters:
  - Setup and hold times
  - **Propagation delay**—time for a signal at the input to be shown at the output. ( $t_{PLH}$  and  $t_{PHL}$ )
  - **Maximum clocking frequency**—Highest clock frequency that will give a reliable output. ( $f_{MAX}$ )
  - **Clock pulse HIGH and LOW times**—minimum clock-time between HIGH/LOW changes. (  $t_W(L)$ ;  $t_W(H)$  )
  - **Asynchronous Active Pulse Width**—time the clock must HIGH before going LOW, and LOW before going HIGH.
  - **Clock transition times**—maximum time for clock transitions,
    - Less than 50 ns for TTL ; 200 ns for CMOS

## 5-11 Flip-Flop Timing Considerations - Parameters

### FF propagation delays.

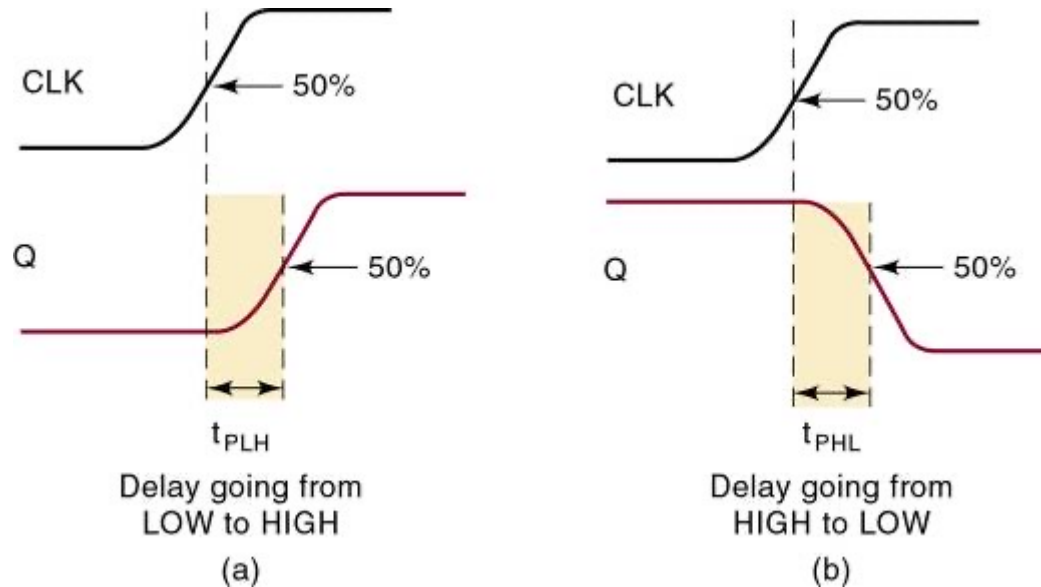

### Clock Pulse HIGH and LOW and Asynch pulse width.



## 5-11 Flip-Flop Timing Considerations – Actual IC Values

7474	Dual edge-triggered D flip-flop (standard TTL)
74LS112	Dual edge-triggered J-K flip-flop (low-power Schottky TTL)
74C74	Dual edge-triggered D flip-flop (metal-gate CMOS)
74HC112	Dual edge-triggered J-K flip-flop (high-speed CMOS)

Timing values for FFs from manufacturer data books.

All of the listed values are *minimum* values, except propagation delays, which are *maximum* values.

		TTL		CMOS	
		7474	74LS112	74C74	74HC112
$t_S$		20 ns	20 ns	60 ns	25 ns
$t_H$		5	0	0	0
$t_{PHL}$	from <i>CLK</i> to <i>Q</i>	40	24	200	31
$t_{PLH}$	from <i>CLK</i> to <i>Q</i>	25	16	200	31
$t_{PHL}$	from <i>CLR</i> to <i>Q</i>	40	24	225	41
$t_{PLH}$	from <i>PRE</i> to <i>Q</i>	25	16	225	41
$t_{W(L)}$	<i>CLK</i> LOW time	37	15	100	25
$t_{W(H)}$	<i>CLK</i> HIGH time	30	20	100	25
$t_{W(L)}$	at <i>PRE</i> or <i>CLR</i>	30	15	60	25
$f_{MAX}$	in MHz	15	30	5	20

## 5-12 Potential Timing Problems in FF Circuits



- When the output of one FF is connected to the input of another FF and both are triggered by the same clock, there is a *potential* timing problem.
  - Propagation delay may cause unpredictable outputs.
- Edge-triggered FFs have hold time requirements 5 ns or less—most have  $t_H = 0$ .
  - They have *no* hold time requirement.

**Assume the FF hold time requirement is short enough to respond reliably according to the following rule:**

**Flip-Flop output will go to a state determined by logic levels present at its synchronous control inputs just prior to the active clock transition.**


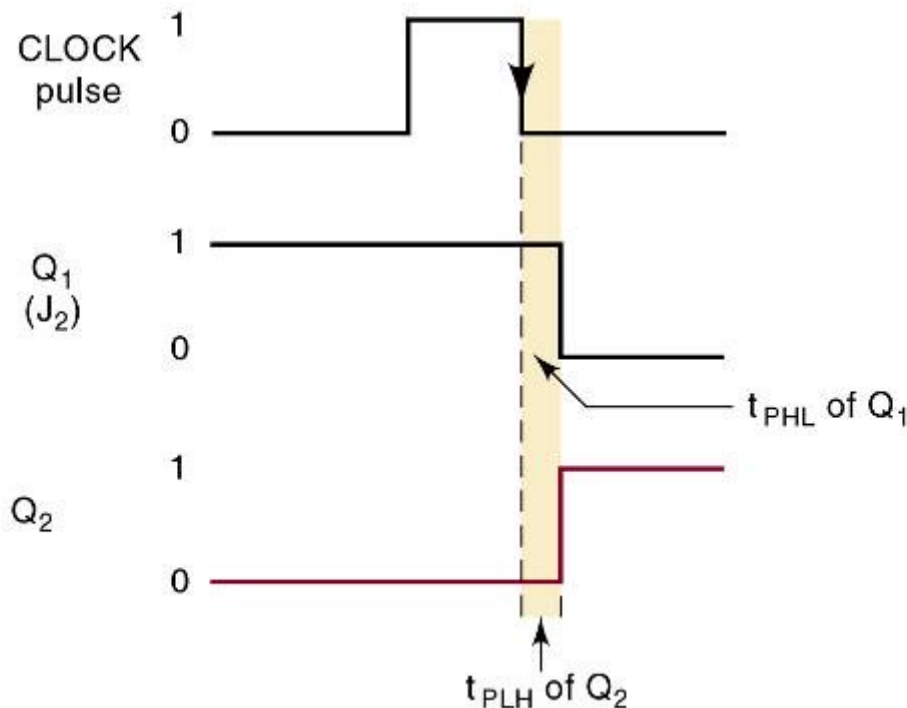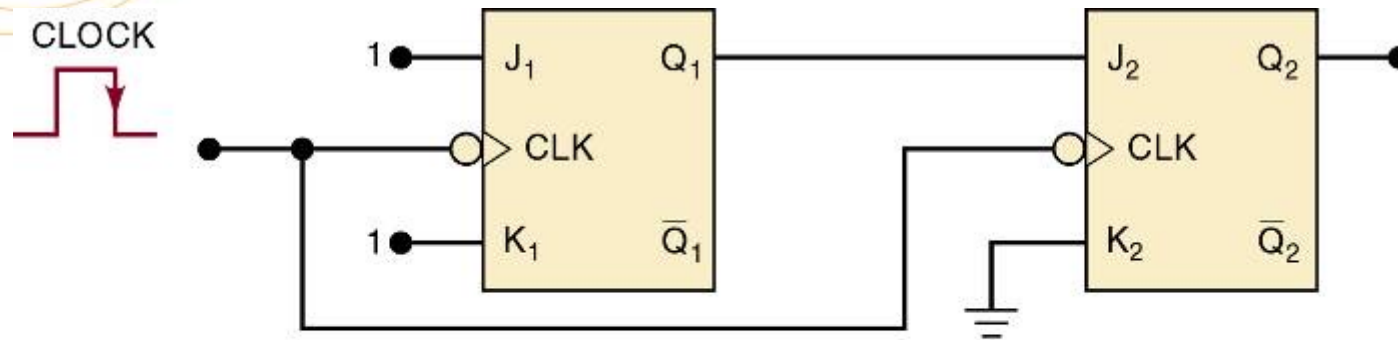
## 5-12 Potential Timing Problems in FF Circuits



Q<sub>2</sub> will respond properly to the level present at Q<sub>1</sub> prior to NGT of CLK—*provided* Q<sub>2</sub>'s hold time requirement,  $t_H$ , is *less* than Q<sub>1</sub>'s propagation delay.


## ● 5-13 Flip-Flop Applications

- Examples of applications:
  - Counting; Storing binary data
  - Transferring binary data between locations
- Many FF applications are categorized sequential.
  - Output follows a predetermined sequence of states.
 
## 5-14 Flip-Flop Synchronization



- Most systems are primarily synchronous in operation—in that changes depend on the clock.
- Asynchronous and synchronous operations are often combined—frequently through human input.
  - The random nature of asynchronous inputs *can* result in unpredictable results.

The asynchronous signal *A* can produce partial pulses at *X*.


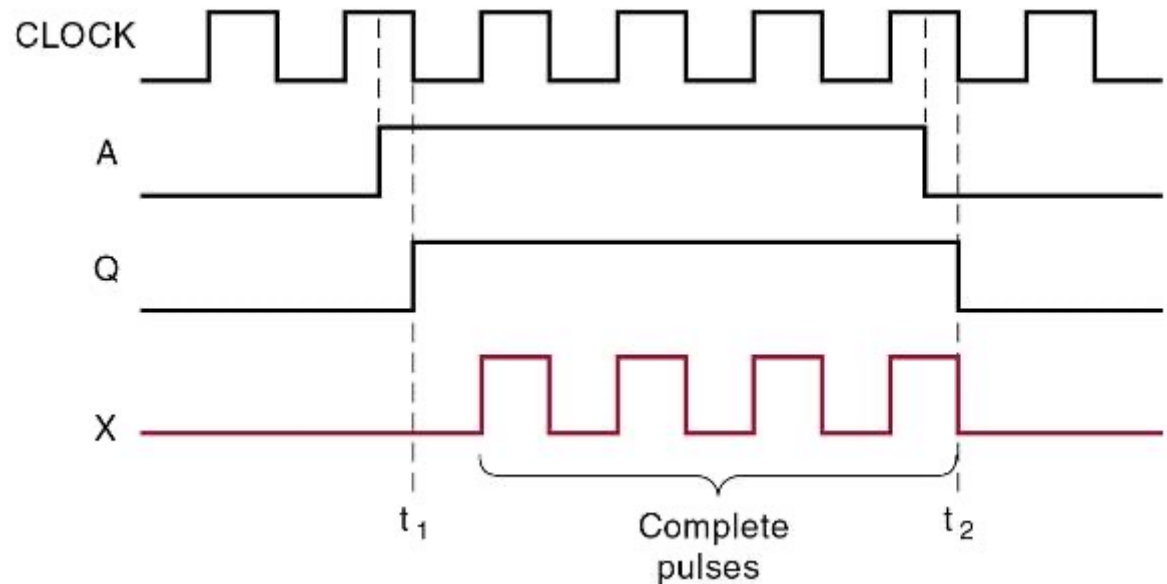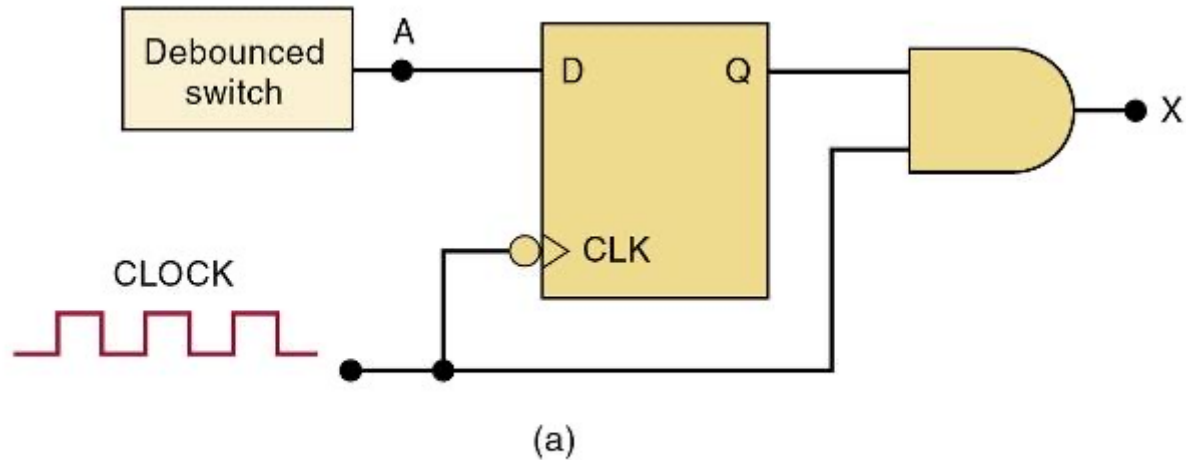
## 5-14 Flip-Flop Synchronization


An edge-triggered D flip-flop synchronizes the enabling of the **AND** gate to the NGTs of the clock.




## 5-15 Detecting an Input Sequence

- FFs provide features pure combinational logic gates do not—in many situations, output activates *only* when inputs activate in a *certain sequence*
  - This requires the storage characteristic of FFs.

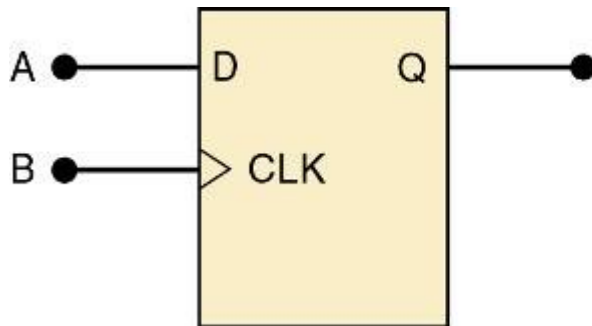
**Clocked D flip-flop used to respond to a particular *sequence* of inputs.**



 To work properly, A must go HIGH, prior to B, by *at least* an amount of time *equal* to FF setup time.



A goes HIGH before B

 


B goes HIGH before A

## 5-16 Data Storage and Transfer

- FFs are commonly used for storage and transfer of binary data.
  - Groups used for storage are **registers**.
- Data transfers take place when data is moved between registers or FFs.
  - *Synchronous* transfers take place at clock PGT/NGT.
  - *Asynchronous* transfers are controlled by PRE & CLR.

## 5-16 Data Storage and Transfer – Synchronous

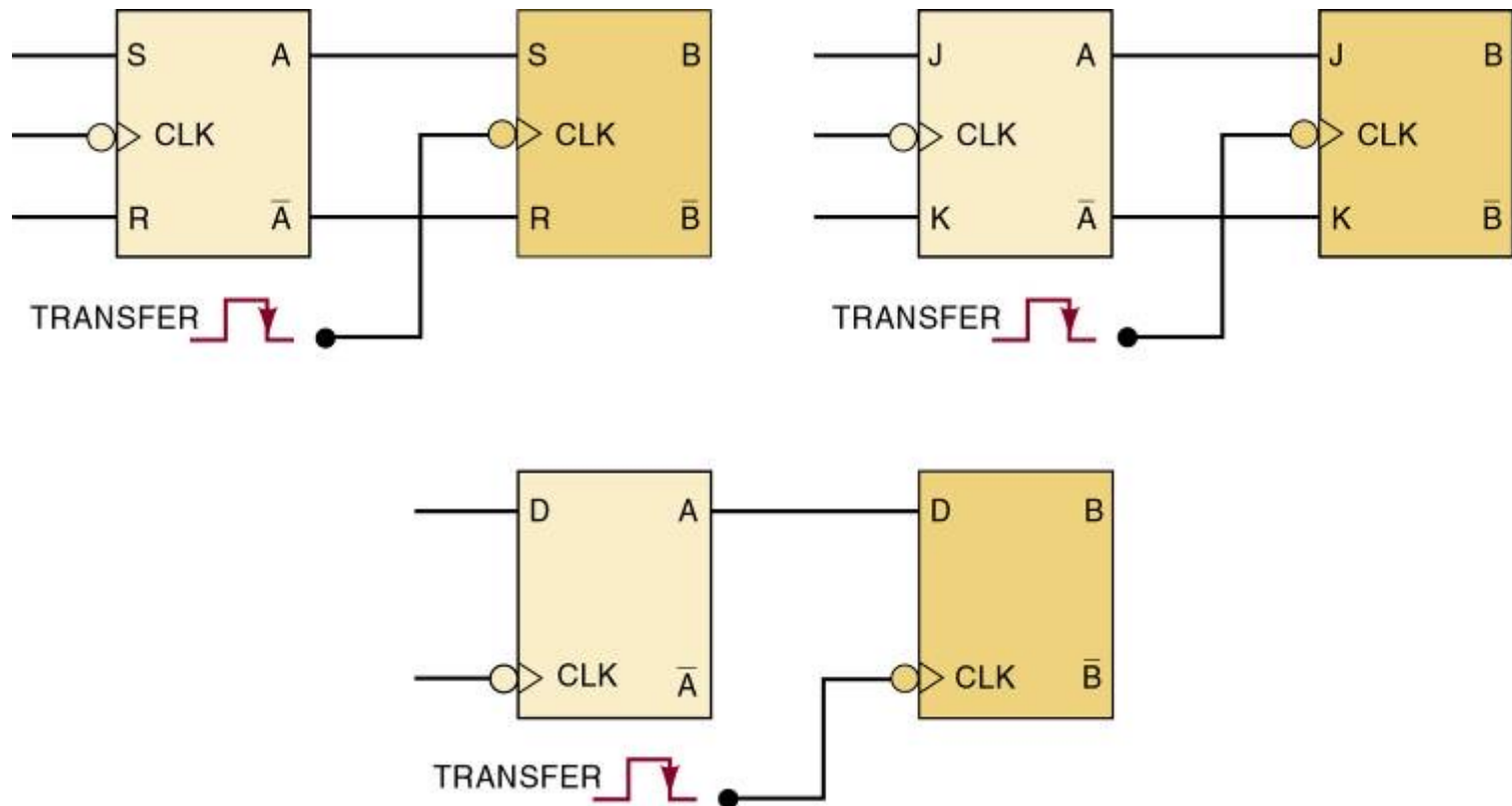
**Synchronous data transfer operation by various clocked FFs.**



**CLK inputs are used to perform the transfer.**

## 5-16 Data Storage and Transfer – Asynchronous

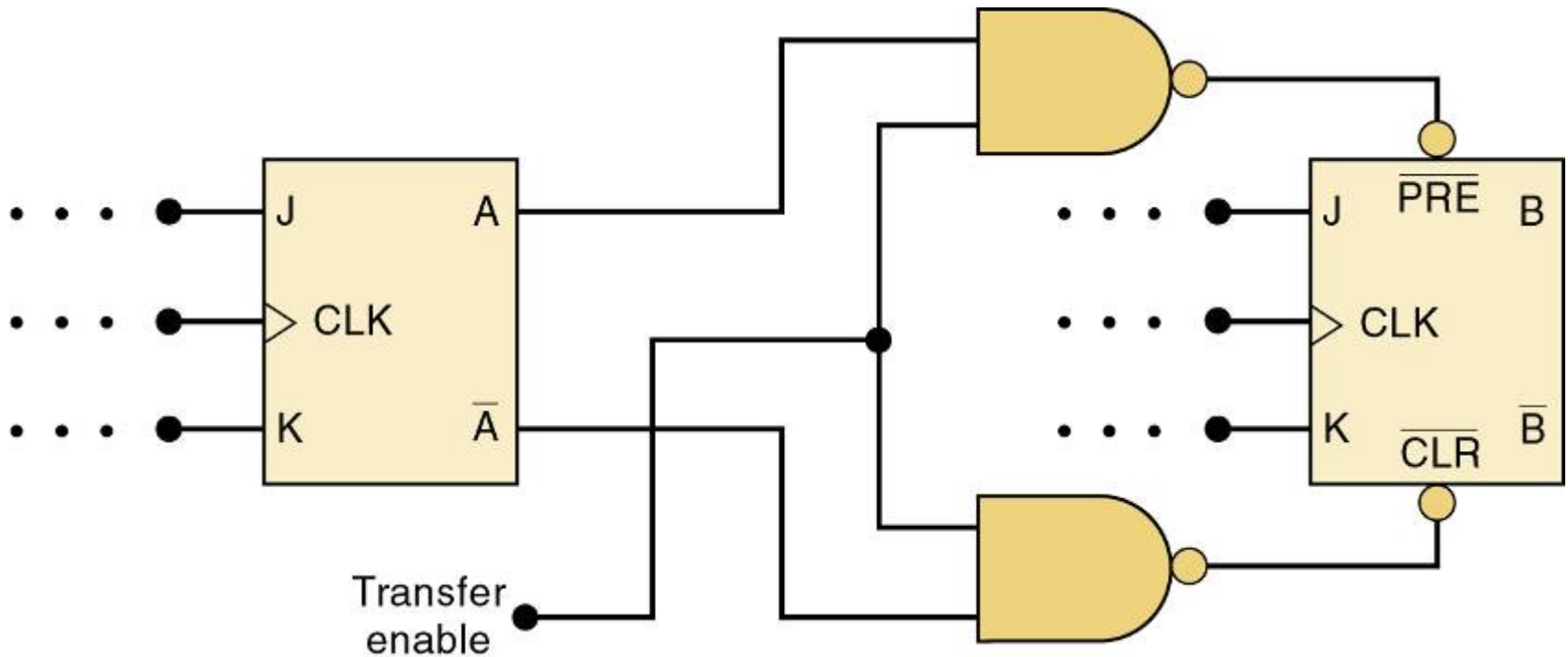**Asynchronous data transfer operation.**




***PRE and CLR inputs are used to perform the transfer.***


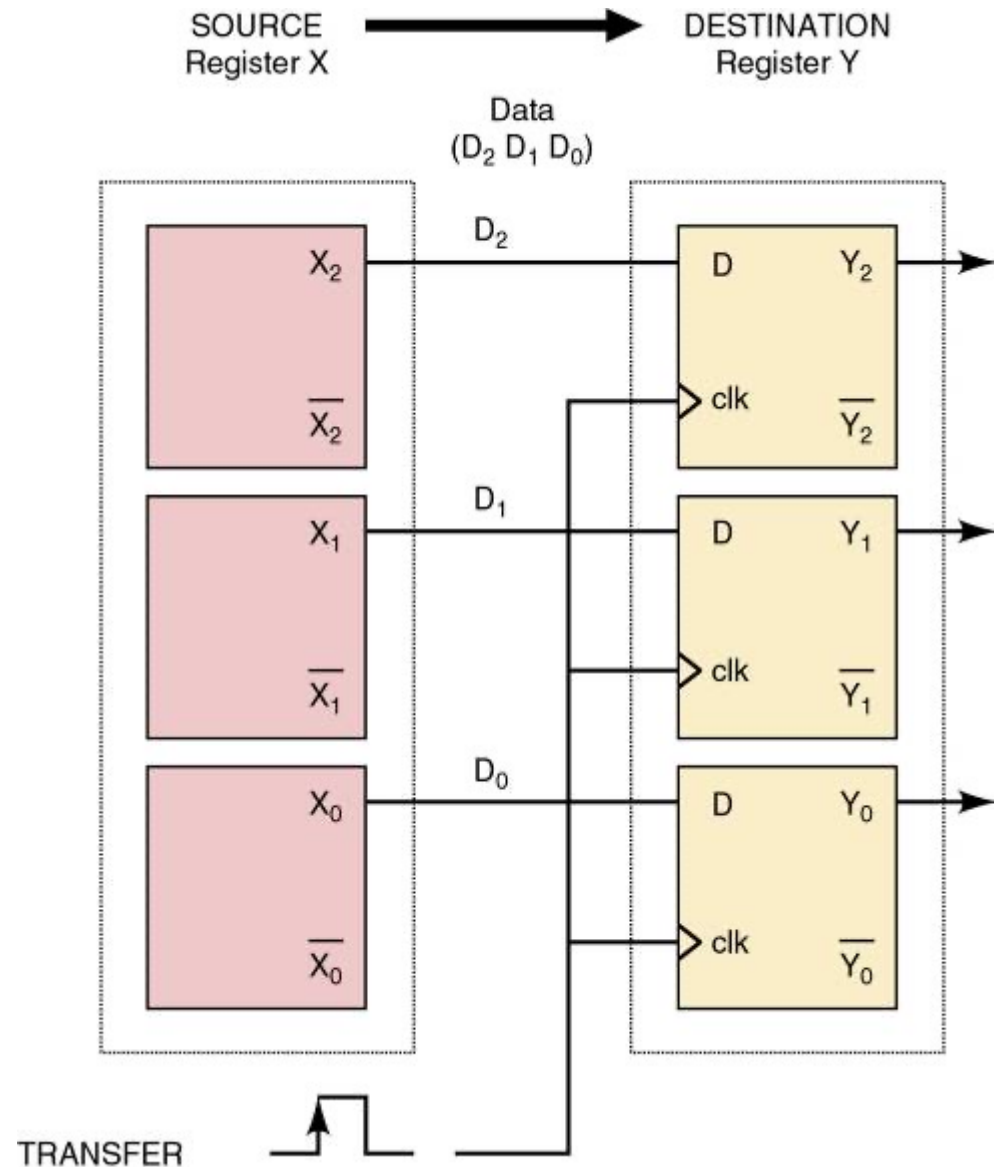
## 5-16 Data Storage and Transfer – Parallel

Transferring the bits of a register *simultaneously* is a *parallel* transfer.




## ● 5-17 Serial Data Transfer

- Transferring the bits of a register *a bit at a time* is a *serial* transfer.
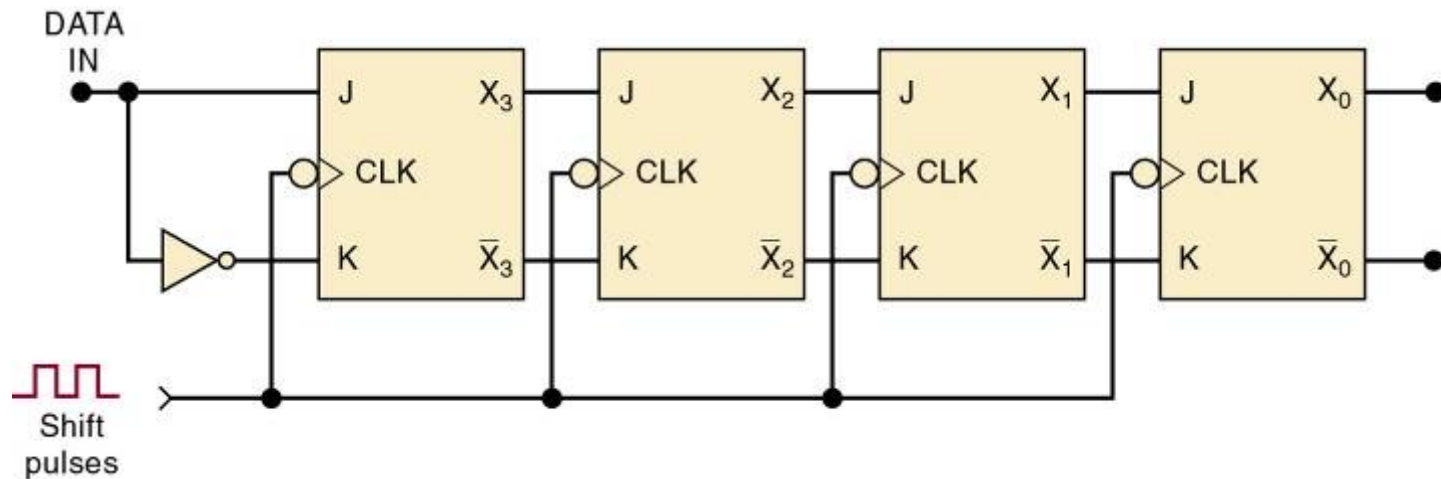
## 5-17 Serial Data Transfer – Shift Register

- A **shift register** is a group of FFs arranged so the binary numbers stored in the FFs are shifted from one FF to the next, for every clock pulse.




**J-K flip-flops operated as a four-bit shift register.**

## 5-17 Serial Data Transfer – Shift Register

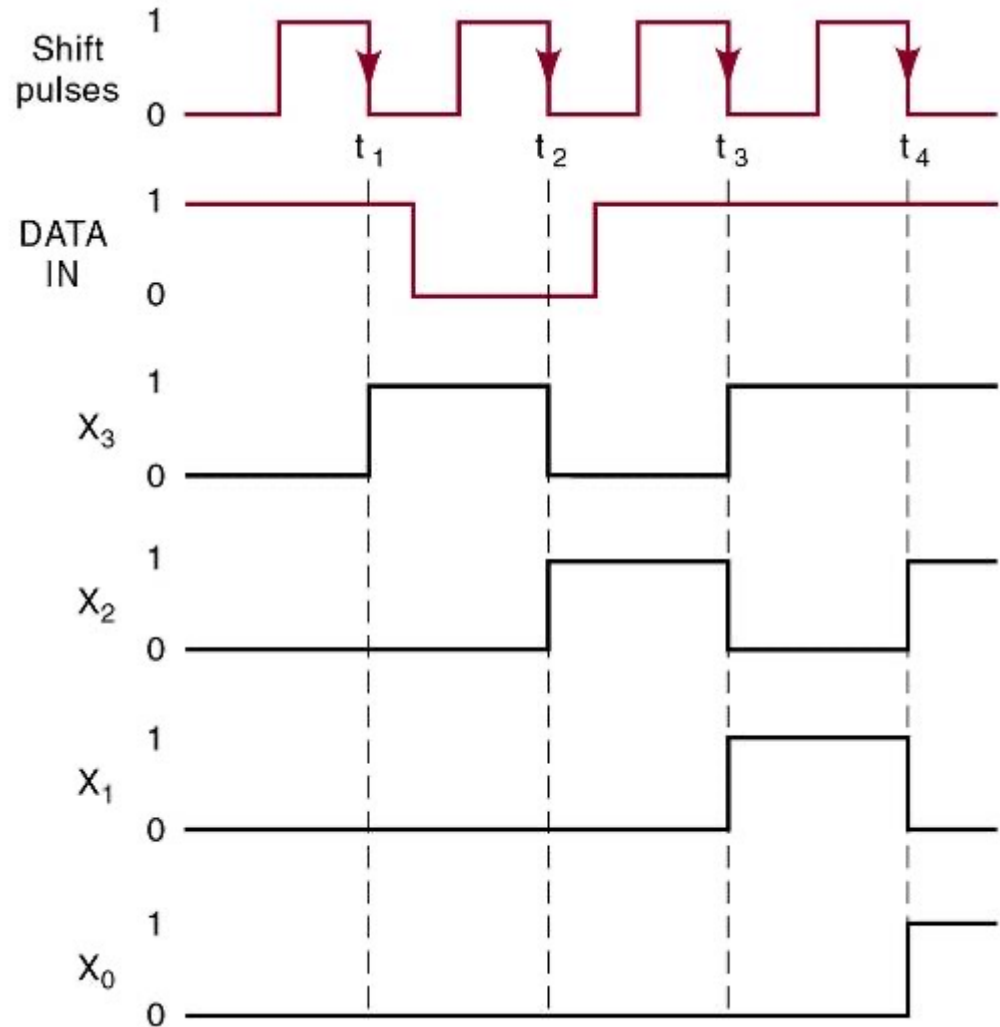**Input data are shifted left to right from FF to FF as shift pulses are applied.**


In this shift-register arrangement, it is necessary to have FFs with very small hold time requirements.

There are times when the  $J$ ,  $K$  inputs are changing at about the same time as the  $CLK$  transition.



## 5-17 Serial Data Transfer – Shift Register

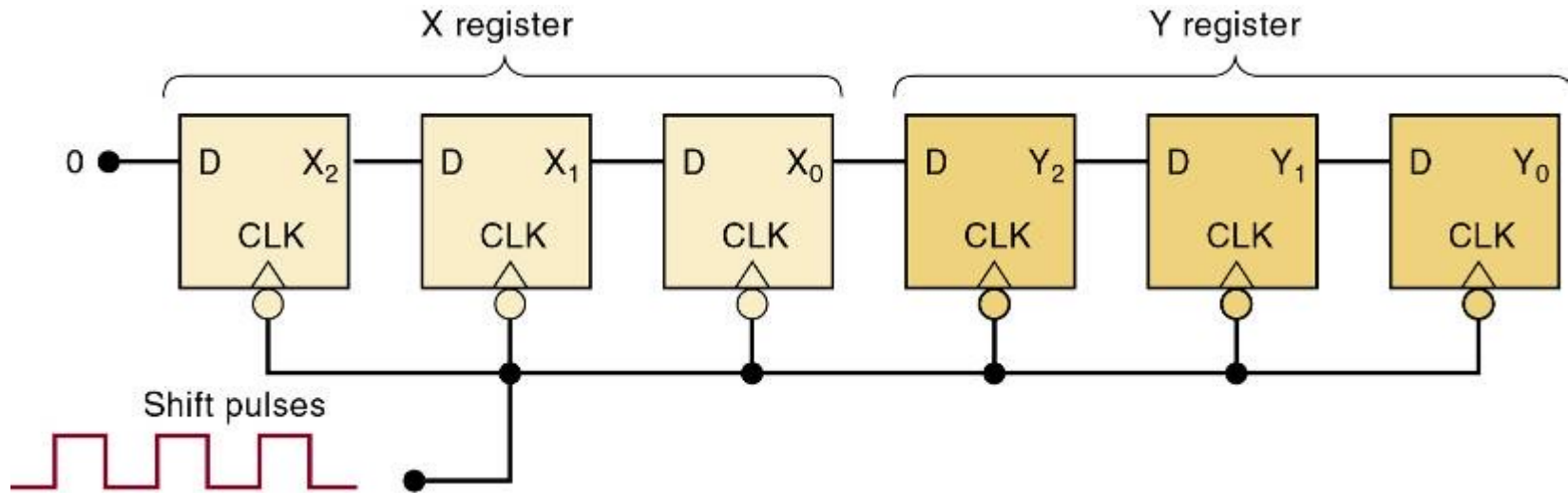**Two connected three-bit shift registers.**



**The contents of the X register will be serially transferred (shifted) into register Y.**

The D flip-flops in each shift register require fewer connections than J-K flip-flops.

## 5-17 Serial Data Transfer – Shift Register

**Two connected three-bit shift registers.**

**The complete transfer of the three bits of data requires three shift pulses.**

$X_2$	$X_1$	$X_0$	$Y_2$	$Y_1$	$Y_0$	
1	0	1	0	0	0	← Before pulses applied
0	1	0	1	0	0	
0	0	1	0	1	0	
0	0	0	1	0	1	

## 5-17 Serial Data Transfer – Shift Register

**Two connected three-bit shift registers.**


**On each pulse NGT, each FF takes on the value stored in the FF on its *left* prior to the pulse.**

$X_2$	$X_1$	$X_0$	$Y_2$	$Y_1$	$Y_0$	
1	0	1	0	0	0	← Before pulses applied
0	1	0	1	0	0	← After first pulse
0	0	1	0	1	0	
0	0	0	1	0	1	

## 5-17 Serial Data Transfer – Shift Register

**Two connected three-bit shift registers.**

 **On each pulse NGT, each FF takes on the value stored in the FF on its *left* prior to the pulse.**






## 5-17 Serial Data Transfer – Shift Register

**Two connected three-bit shift registers.**

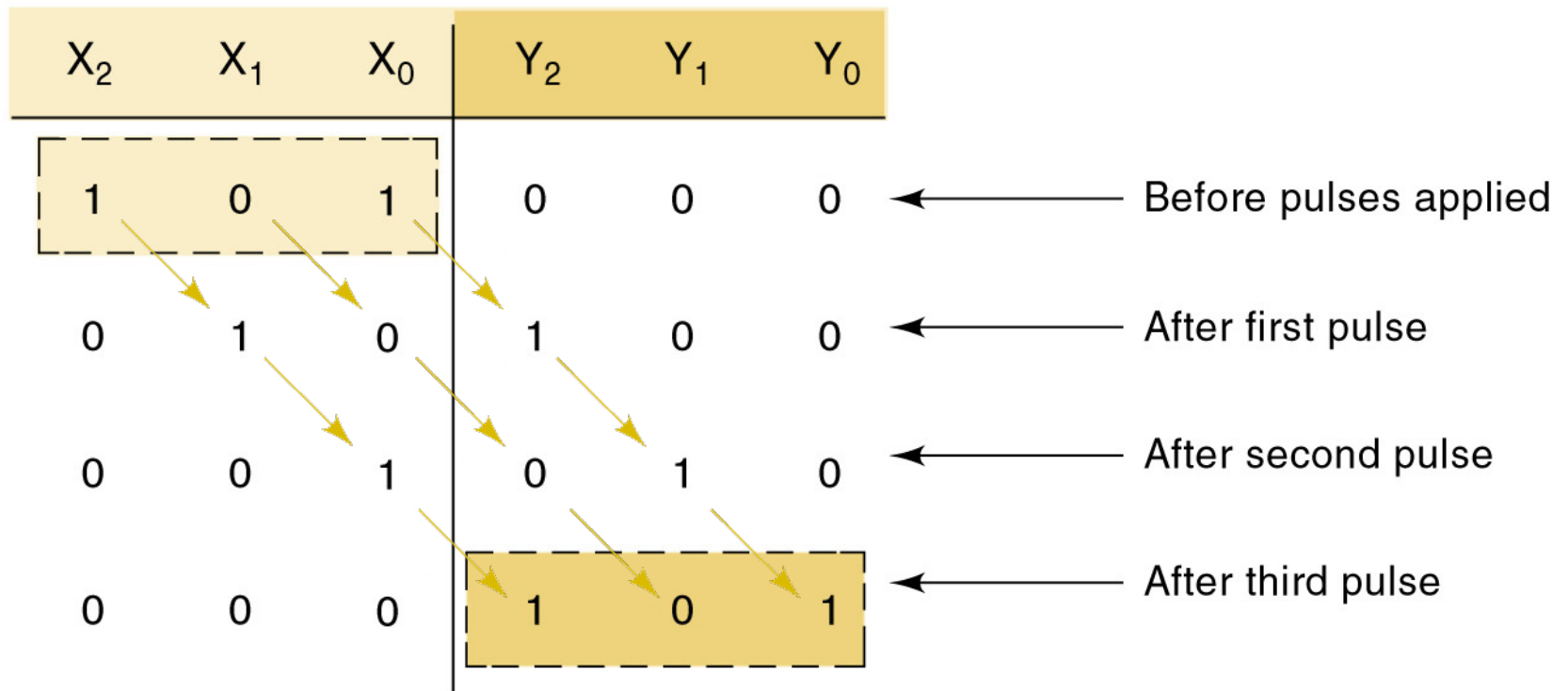**On each pulse NGT, each FF takes on the value stored in the FF on its *left* prior to the pulse.**



## 5-17 Serial Data Transfer – Shift Register

**Two connected three-bit shift registers.**

**After three pulses:**

- The 1 initially in  $X_2$  is in  $Y_2$ .**
- The 0 initially in  $X_1$  is in  $Y_1$ .**
- The 1 initially in  $X_0$  is in  $Y_0$ .**

$X_2$	$X_1$	$X_0$	$Y_2$	$Y_1$	$Y_0$
1	0	1	0	0	0
0	1	0	1	0	0
0	0	1	0	1	0
0	0	0	1	0	1

The 101 stored in the X register has now been shifted into the Y register.

The X register has lost its original data, and is at 000.

## 5-17 Serial Data Transfer vs. Parallel

- FFs in can just as easily be connected so that information shifts from *right* to *left*.
  - No general advantage of one direction over another.
    - Often dictated by the nature of the application.
- Parallel transfer requires more interconnections between sending & receiving registers than serial.
  - More critical when a greater number of bits of are being transferred.
- Often, a combination of types is used
  - Taking advantage of parallel transfer *speed* and serial transfer the *economy and simplicity* of serial transfer.



## 5-18 Frequency Division and Counting

**J-K flip-flops wired as a three-bit binary counter (MOD-8).**

Each FF divides the input frequency by 2.

Output frequency is 1/8 of the input (clock) frequency.

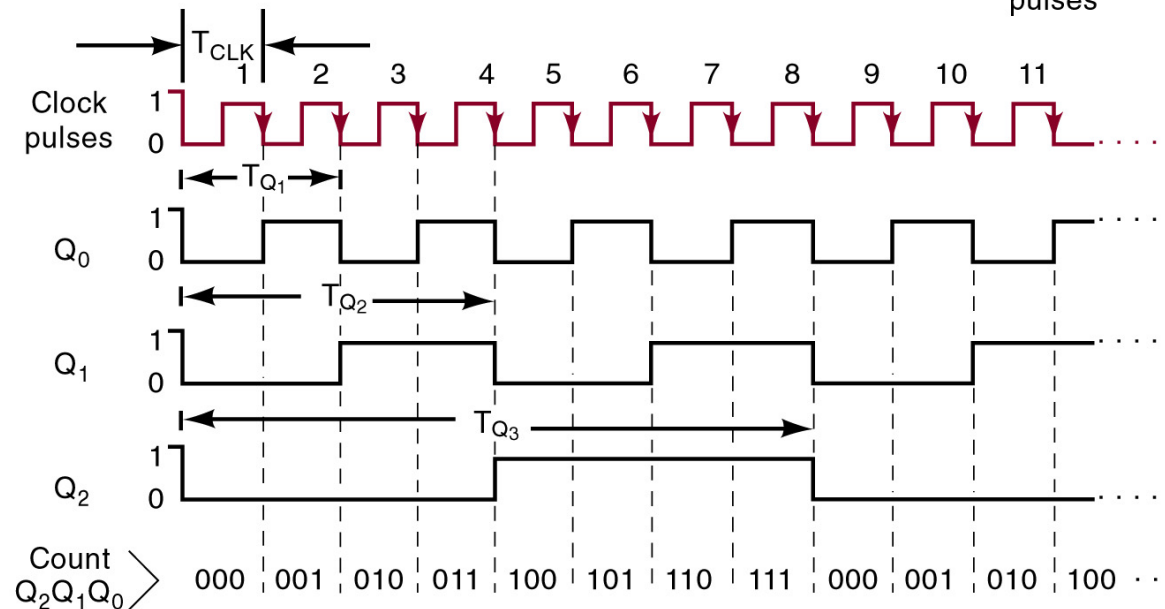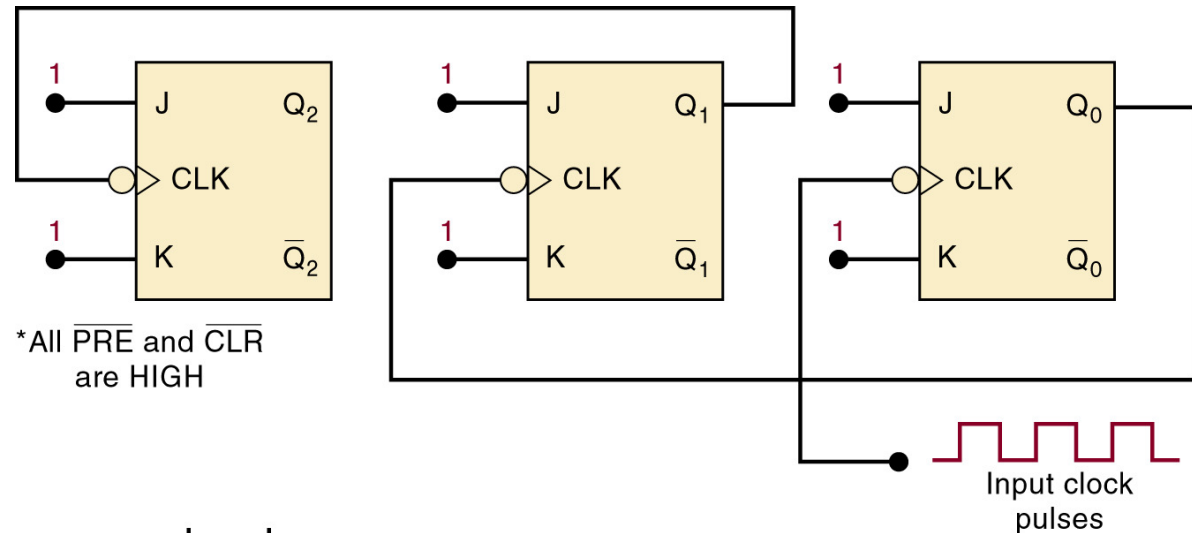A fourth FF would make the frequency 1/16 of the clock.





## 5-18 Frequency Division and Counting

**J-K flip-flops wired as a three-bit binary counter (MOD-8).**

This circuit also acts as a binary counter.

Outputs will count from 0002 to 1112 or 010 to 710.

 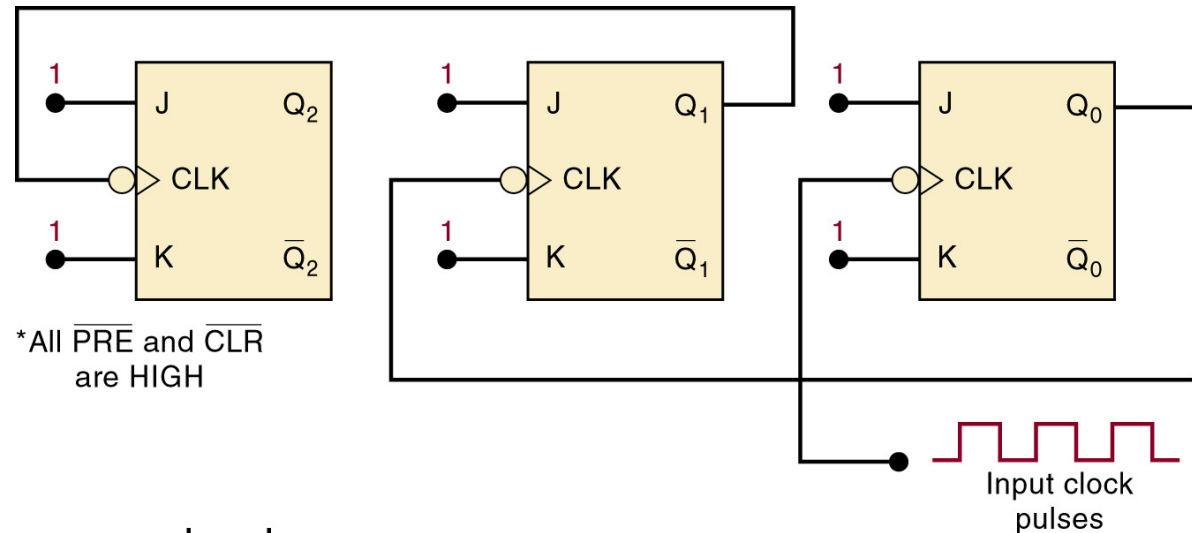The number of states possible in a counter is the modulus or MOD number.




## 5-18 Frequency Division and Counting

### A MOD-8 ( $2^3$ ) counter.

If another FF is added it would become a MOD-16 ( $2^4$ ) counter.

$2^2$	$2^1$	$2^0$	
$Q_2$	$Q_1$	$Q_0$	
0	0	0	Before applying clock pulses
0	0	1	After pulse #1
0	1	0	After pulse #2
0	1	1	After pulse #3
1	0	0	After pulse #4
1	0	1	After pulse #5
1	1	0	After pulse #6
1	1	1	After pulse #7
0	0	0	After pulse #8 recycles to 000
0	0	1	After pulse #9
0	1	0	After pulse #10
0	1	1	After pulse #11
.	.	.	.
.	.	.	.
.	.	.	.

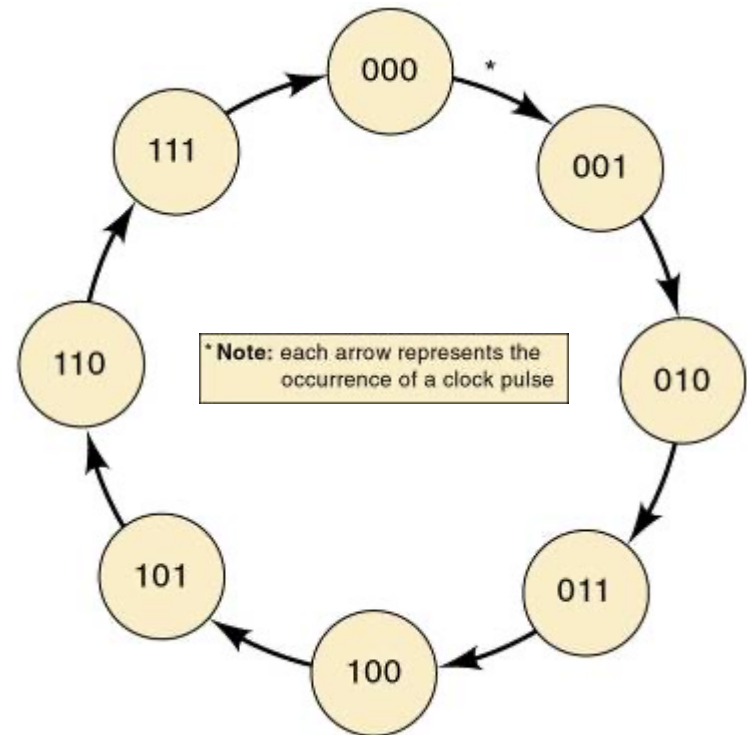


## ● 5-19 Microcomputer Application

- Microprocessor units (MPUs) perform many functions involving use of registers for data transfer and storage.
- MPUs may send data to external registers for many purposes, including:
  - Solenoid/relay control; Device positioning.
  - Motor starting & speed controls.

## 5-19 Microcomputer Application
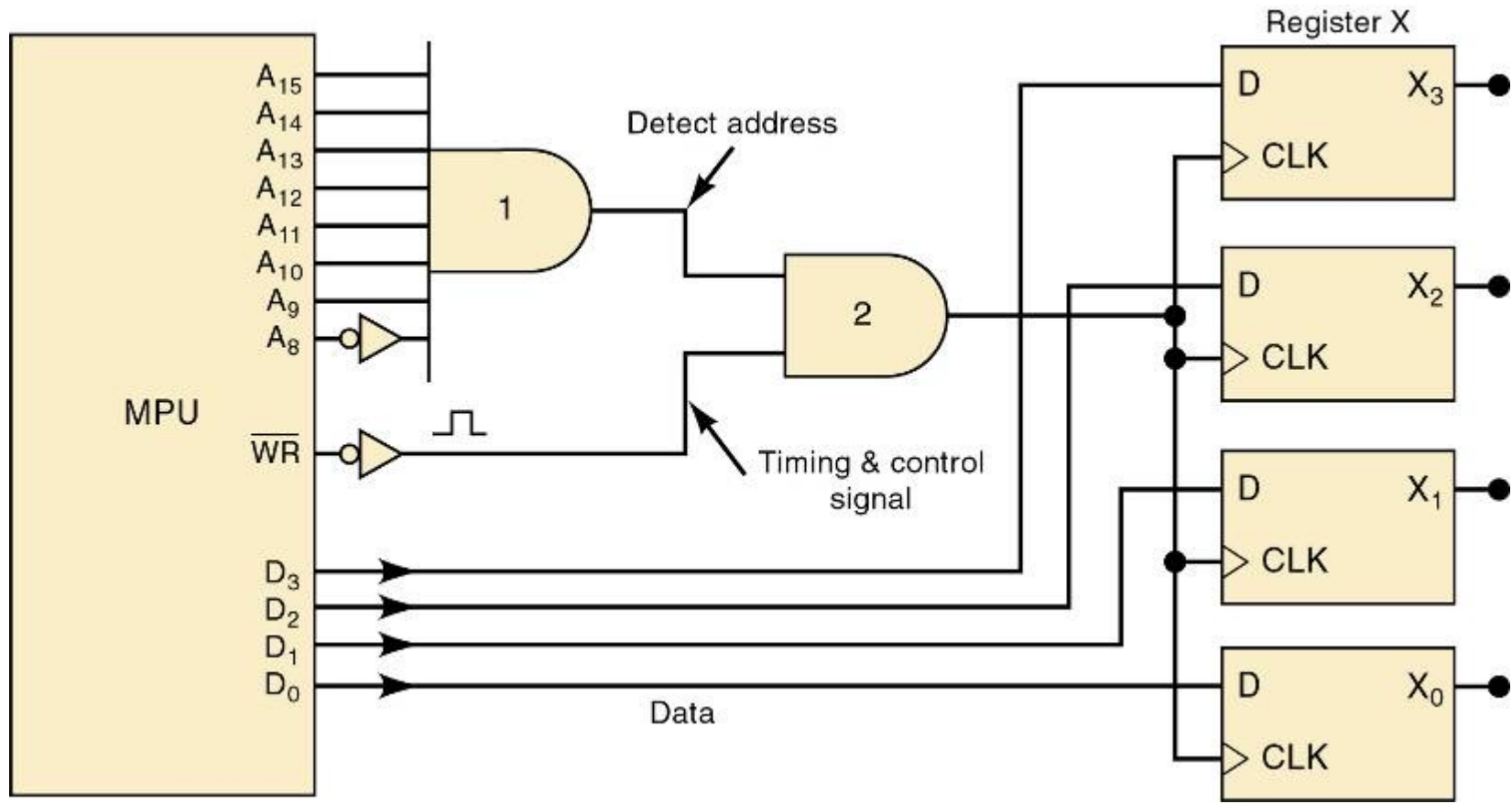
### Microprocessor transferring binary data to an external register.






## 5-20 Schmitt-Trigger Devices

- Not classified as a FF—but has a useful a memory characteristic in certain situations.
- Accepts slow changing signals and produces a signal that transitions quickly, oscillation-free.
- A Schmitt trigger device will not respond to input until it exceeds the positive- $(V_{T+})$  or negative- $(V_{T-})$  going threshold.
- Separation between the threshold levels means the device will “remember” the last threshold exceeded.
  - Until the input goes to the opposite threshold.


## 5-20 Schmitt-Trigger Devices
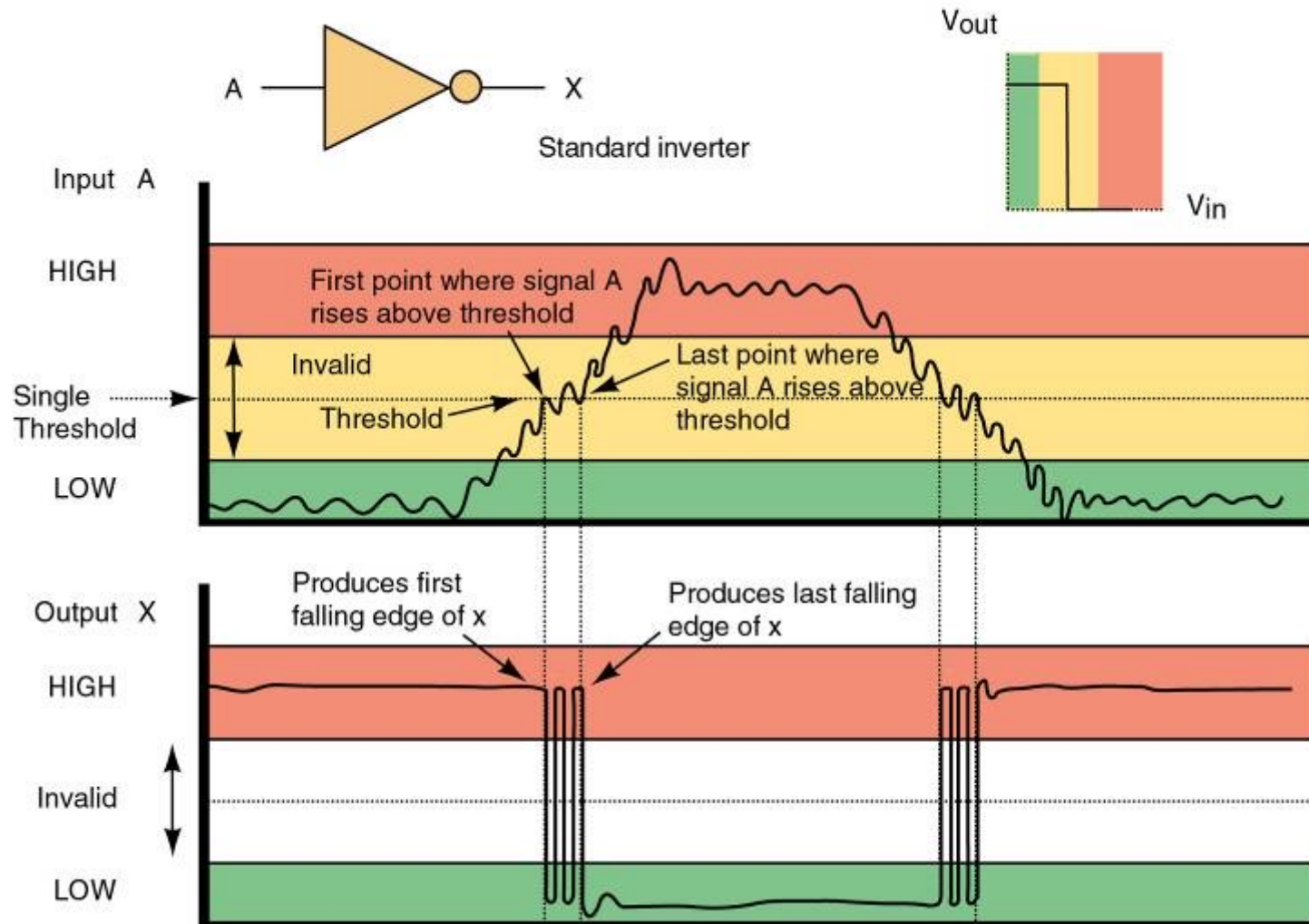
### Standard inverter response to slow noisy input.



## 5-20 Schmitt-Trigger Devices
 
### Schmitt-trigger response to slow noisy input.



## 5-21 One-shot (Monostable Multivibrator)


- Like the FF, the OS has two outputs,  $Q$  and  $\bar{Q}$ .
  - The inverse of each other.
- One shots are called monostable multivibrators because they have only one stable state.
  - Prone to triggering by noise.
- Changes from stable to quasi-stable state for a fixed time-period ( $t_p$ ).
  - Usually determined by an  $RC$  time constant from external components.

## ● 5-21 One-shot (Monostable Multivibrator)

- **Nonretriggerable** devices trigger & return to stable.
- **Retriggerable** devices can be triggered while in the quasi-stable state, to begin another pulse.

## 5-21 One-shot (Monostable Multivibrator)

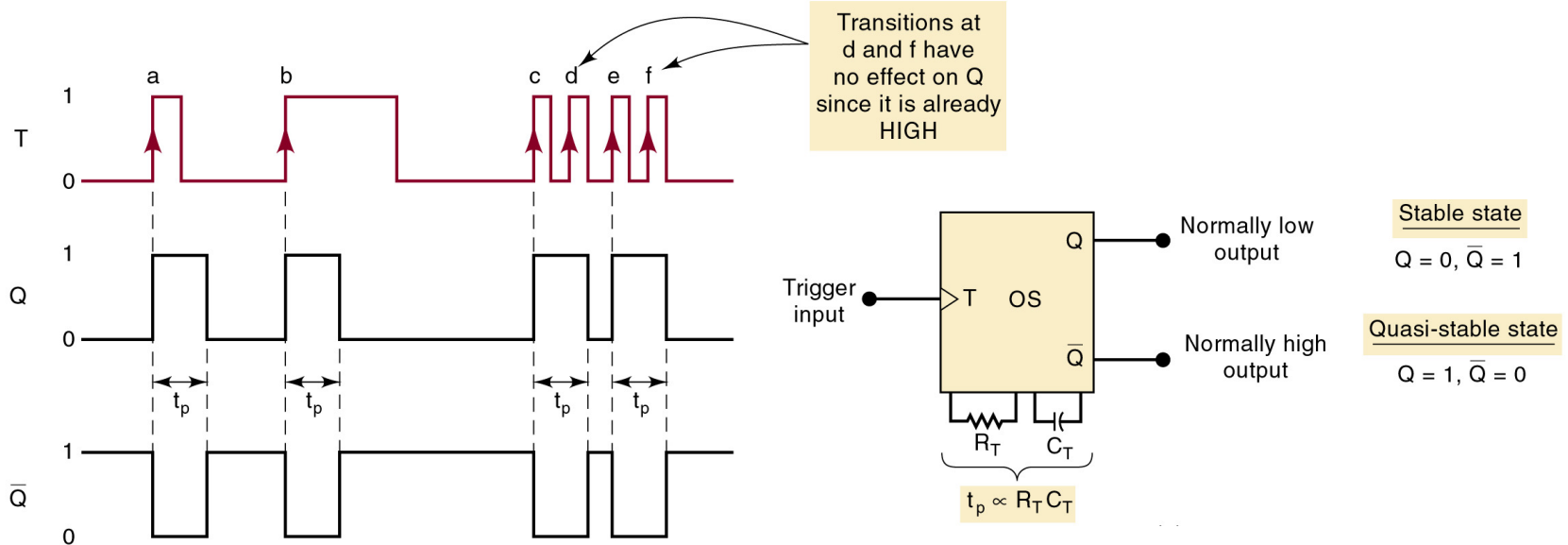
### OS symbol and typical waveforms for nonretriggerable operation.



**PGTs at points *a*, *b*, *c*, and *e* will trigger the OS to its quasi-stable state for a time  $t_p$ . After which it automatically returns to the stable state.**

## 5-21 One-shot (Monostable Multivibrator)

 
### OS symbol and typical waveforms for nonretriggerable operation.



**PGTs at points *d* and *f* have no effect on the OS because it has already been triggered quasi-stable. OS must return to the stable before it can be triggered.**

## 5-21 One-shot (Monostable Multivibrator)
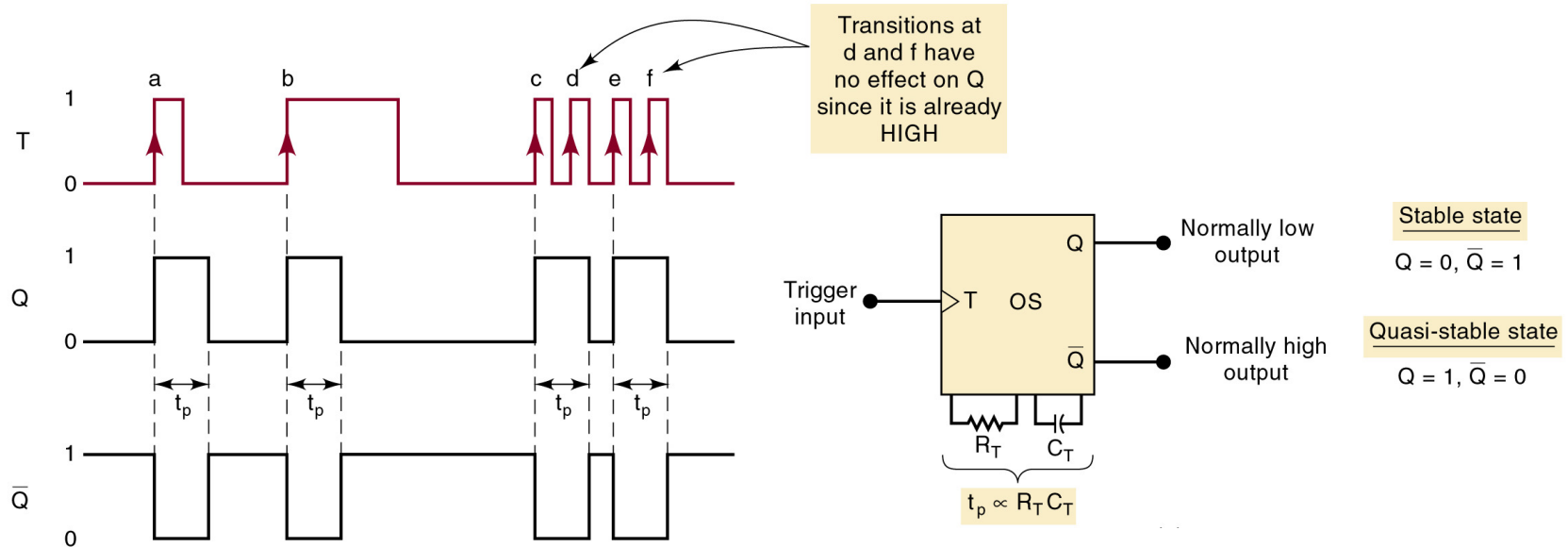
### OS symbol and typical waveforms for nonretriggerable operation.




**OS output-pulse duration is always the same, regardless of the duration of the input pulses.**

**Time  $t_p$  depends only on  $R_T$ ,  $C_T$  & internal OS circuitry.**




## 5-21 One-shot (Monostable Multivibrator)

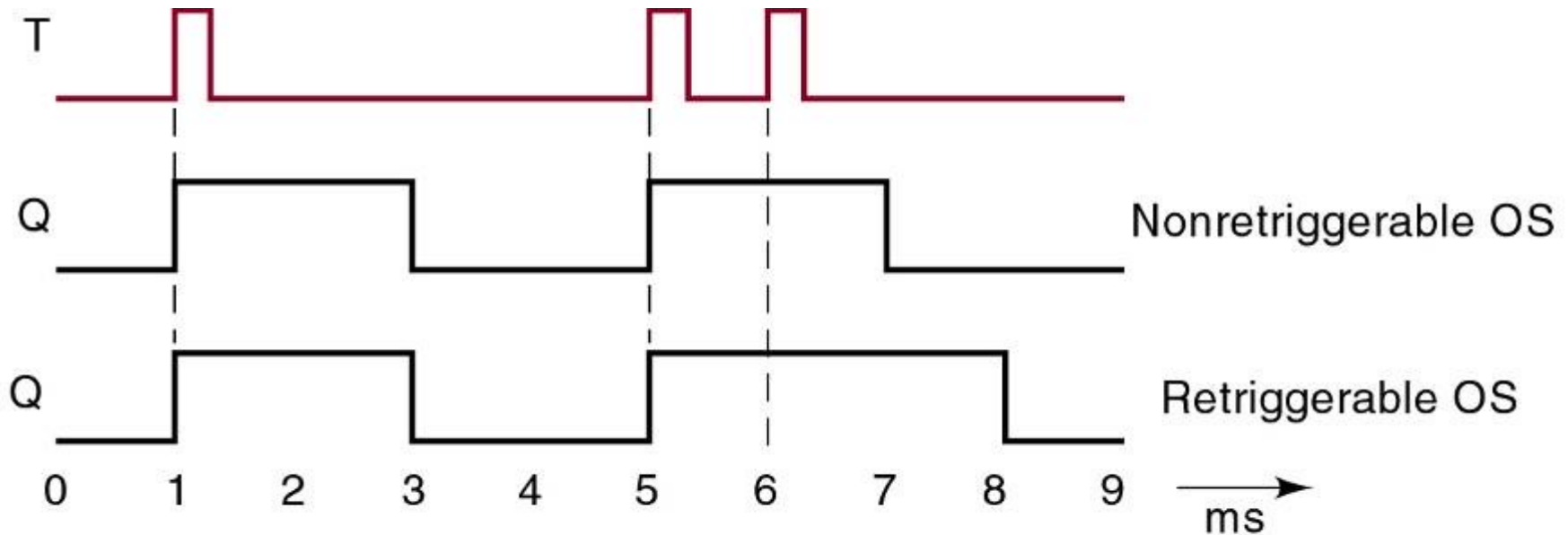**Comparison of nonretriggerable and retriggerable OS responses for  $t_p = 2\text{ms}$ .**



## 5-21 One-shot (Monostable Multivibrator)

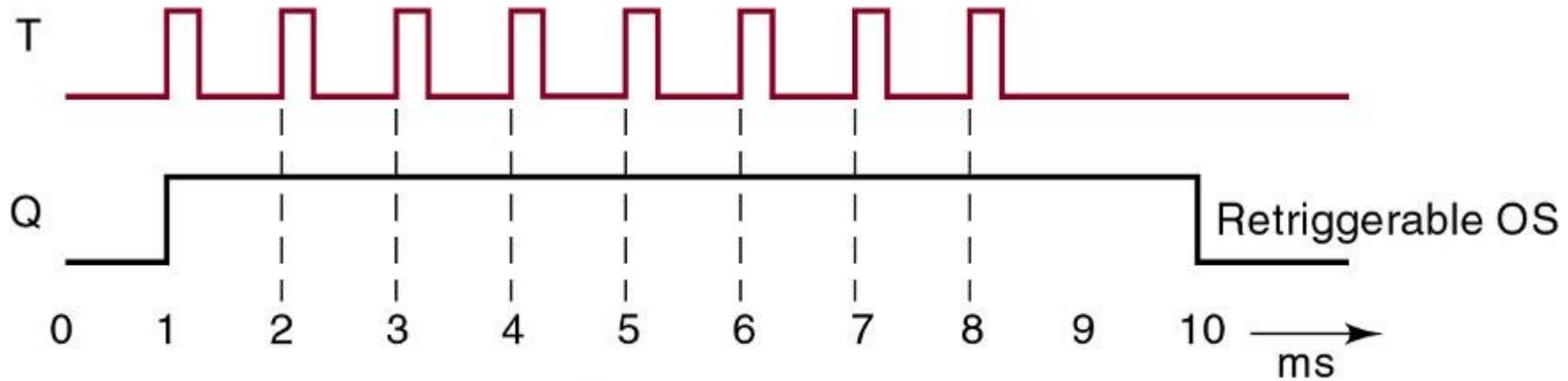**Retriggerable OS begins a new  $t_p$  interval each time it receives a trigger pulse.**




## 5-21 One-shot (Monostable Multivibrator)

### 74121 nonretriggerable one-shot IC.

Contains internal logic gates to allow inputs  $A_1$ ,  $A_2$ , and  $B$  to trigger OS.

Input  $B$  is a Schmitt-trigger—allowed to have slow transition times & still reliably trigger OS.

 Pins  $R_{INT}$ ,  $R_{EXT}/C_{INT}$ , and  $C_{EXT}$  connect to an external resistor & capacitor to achieve desired output pulse duration.




## 5-22 Clock Generator Circuits

- A third type multivibrator has no stable states—an **astable** or **free-running multivibrator**.
  - Astable or free-running multivibrators switch back and forth between two unstable states.
  - Useful for generating clock signals for synchronous circuits.
 
## 5-22 Clock Generator Circuits

**Schmitt-trigger oscillator using a 7414 INVERTER.**  
**A 7413 Schmitt-trigger NAND may also be used.**




IC	Frequency	
7414	$\approx 0.8/RC$	$(R \leq 500 \Omega)$
74LS14	$\approx 0.8/RC$	$(R \leq 2 \text{ k}\Omega)$
74HC14	$\approx 1.2/RC$	$(R \leq 10 \text{ M}\Omega)$

## 5-22 Clock Generator Circuits

- The **555 timer** IC is a TTL-compatible device that can operate in several different modes.
  - Output is a repetitive rectangular waveform that switches between two logic levels.
  - The time intervals at each logic level are determined by the  $R$  and  $C$  values.
- The heart of the 555 timer is two voltage comparators and an S-R latch.
  - The comparators produce a HIGH out when voltage on the (+) input is greater than on the (-) input.
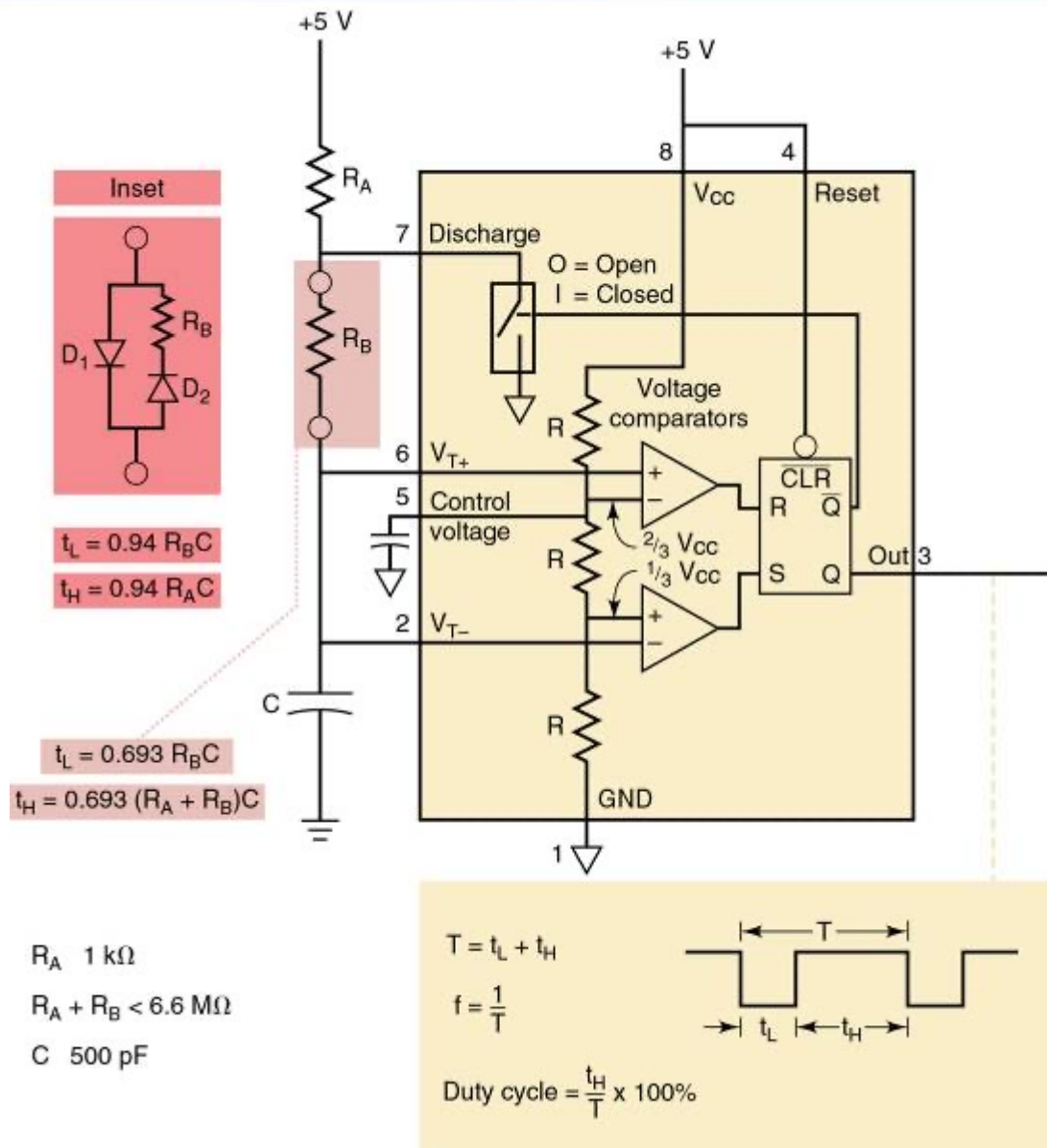
## 5-22 Clock Generator Circuits

**555 Timer IC used  
as an astable  
multivibrator.**



## 5-22 Clock Generator Circuits

- Crystal control may be used if a very stable clock is needed—used in microprocessor systems and microcomputers where accurate timing intervals are essential.



## 5-23 Troubleshooting Flip-Flop Circuits


- FFs are subject to the same faults that occur in combinational logic circuits.
  - Timing problems create some faults and symptoms that are not seen in combinational logic circuits.
- Unconnected or floating inputs are particularly susceptible spurious voltage fluctuations—*noise*.
- Given sufficient noise amplitude and duration, logic circuit output may change states in response.
  - In a logic gate, output will return to its original state when the noise signal subsides.
  - In a FF, output will remain in its new state due to its memory characteristic.

## ● 5-23 Troubleshooting Flip-Flop Circuits

- Clock skew occurs when CLK signals arrive at different FFs at different times.
  - The fault may be seen only intermittently, or may disappear during testing.

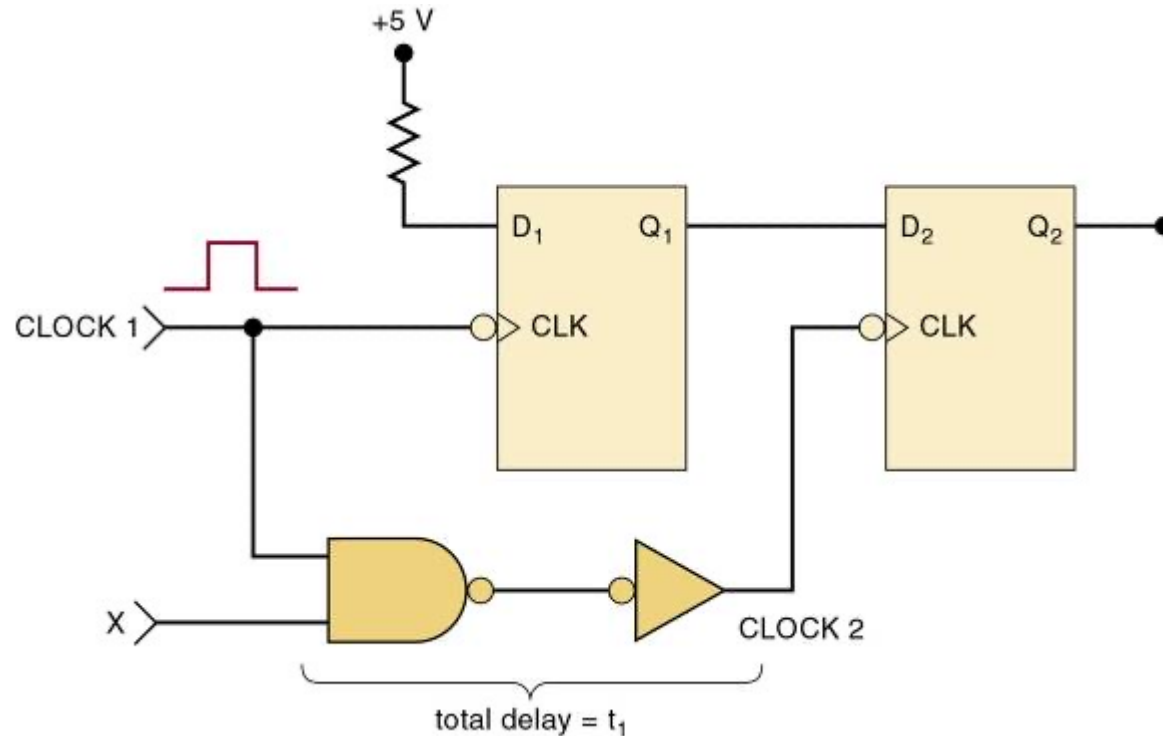
## 5-23 Troubleshooting Flip-Flop Circuits

Extra gating circuits can cause clock skew.



## 5-23 Troubleshooting Flip-Flop Circuits

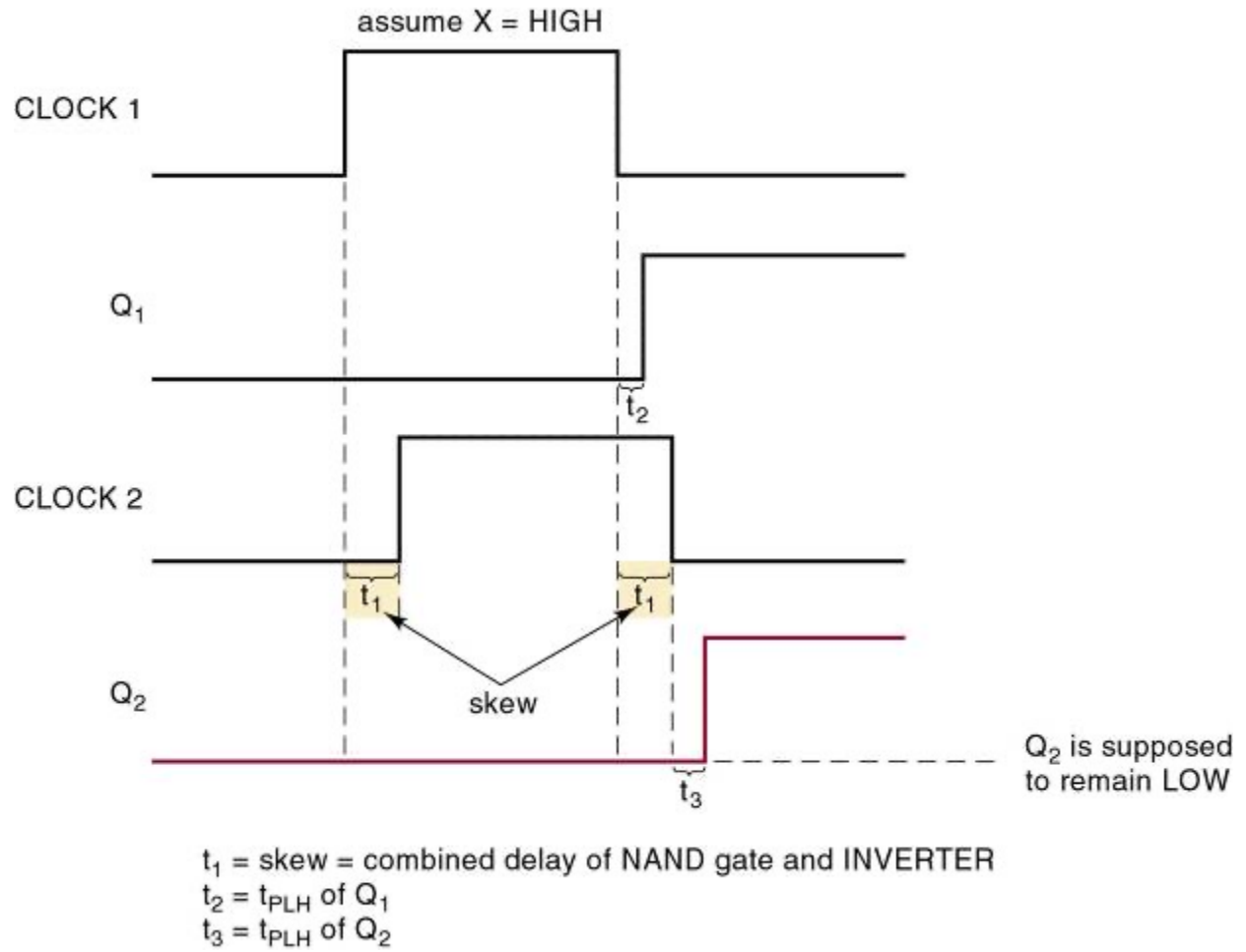**Extra gating circuits can cause clock skew.**




## 5-24 Sequential Circuits In PLDs Using Schematic Entry


- Altera's Quartus II development system software allows designers to describe the desired circuit using schematics.
  - The megafunction library contains high-level modules that can be used to create logic designs.
- The Quartus II simulator can be used to verify the sequential circuits by schematic capture before you program a PLD.
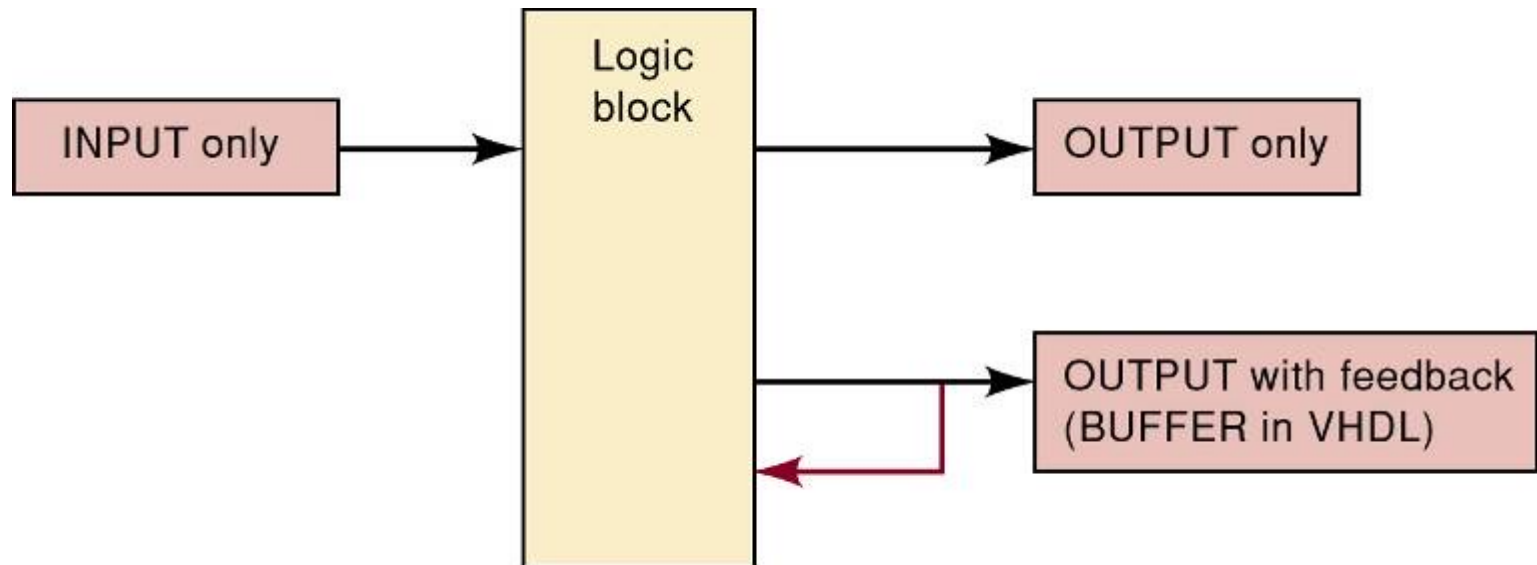
## 5-25 Sequential Circuits Using HDL

- Most PLDs have the ability to feed back the output signal to the input circuitry—to accommodate latching action.
  - The port bit is an output with feedback.


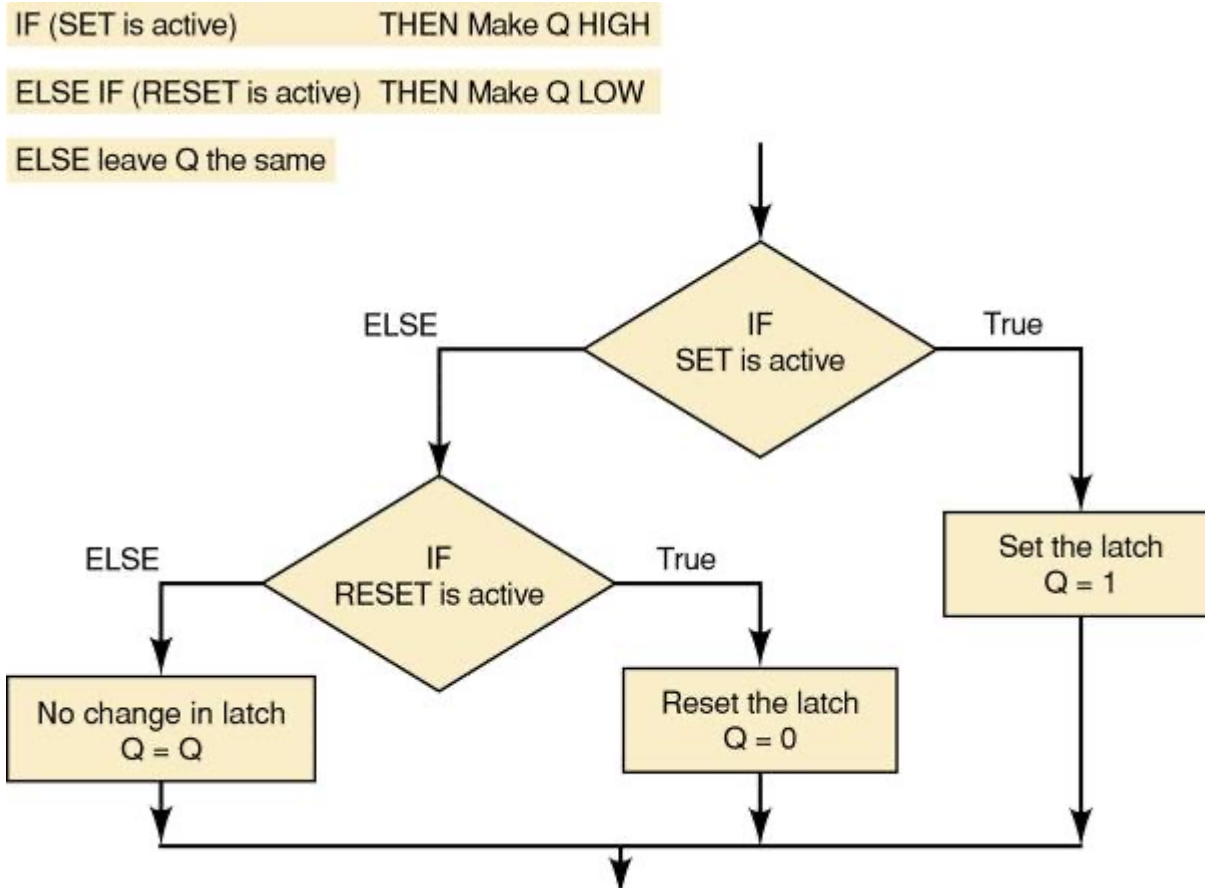
# The logic of a behavioral description of an S-R latch.



## 5-25 Sequential Circuits Using HDL


- Sequential circuits that feed output value back to inputs, may possibly create an unstable system.
  - A change in the output state might be fed back to the inputs, which changes the output state again, which feeds back to the inputs, which changes the output back again....
- It is very important to make sure no combination of inputs & outputs can make this undesirable oscillation undesirable happen.


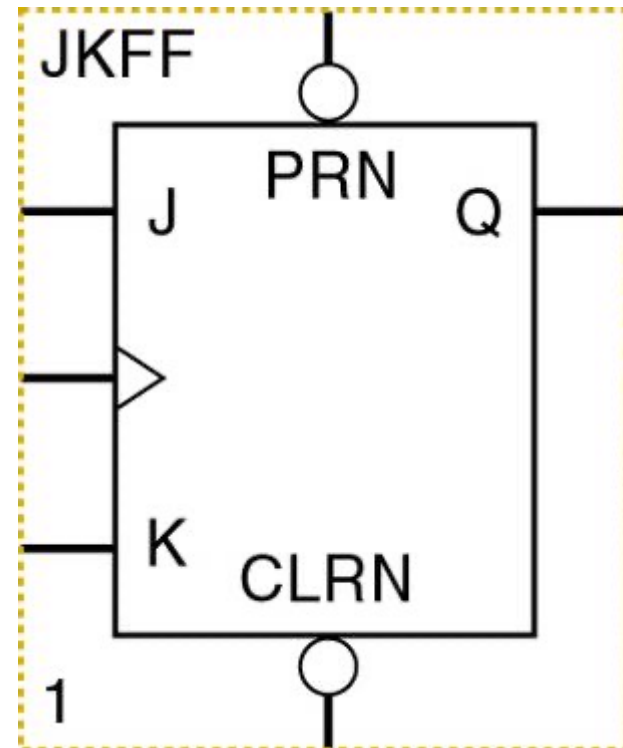
## 5-26 Edge Triggered Devices


- Edge-triggered device output respond to the inputs when the clock input sees an “edge.”
  - An edge is a transition from HIGH to LOW, or vice versa—and is often referred to as an **event**.

The J-K flip-flop is a standard building block of clocked (sequential) logic circuits known as a **logic primitive**.



## 5-27 HDL Circuits with Multiple Components

### A three-bit binary counter.

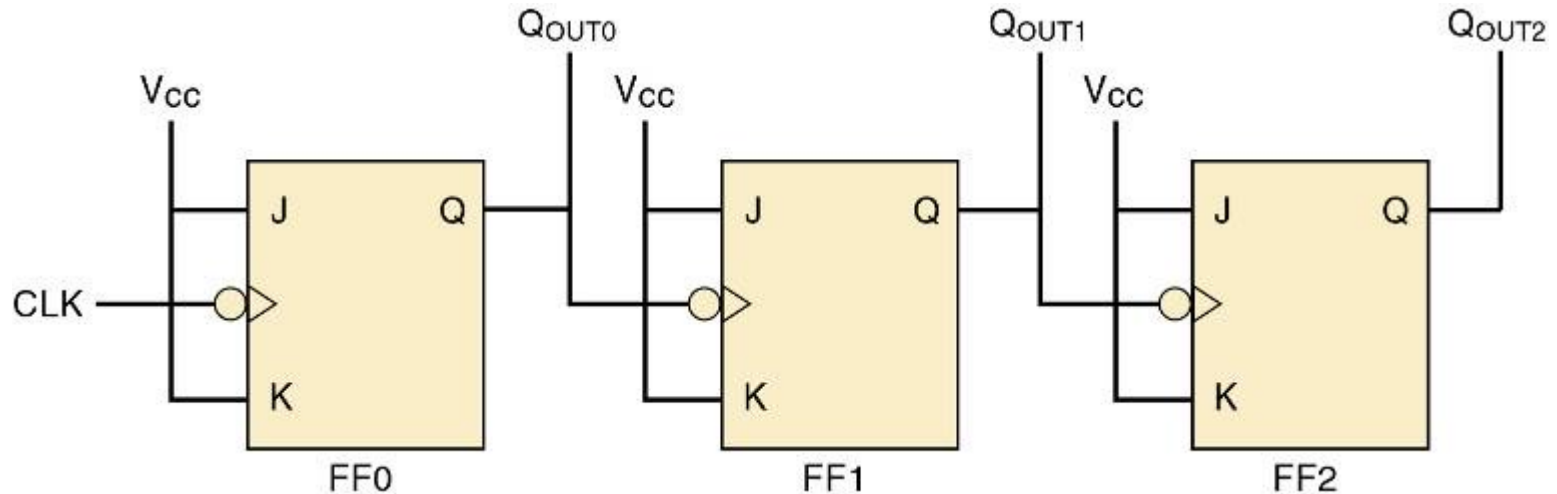

**These logic symbols are negative edge-triggered.**

**These flip-flops do not have asynchronous inputs prn or clrn.**

# END

ELEVENTH EDITION

# Digital Systems

## Principles and Applications

**Ronald J. Tocci**

Monroe Community College

**Neal S. Widmer**

Purdue University

**Gregory L. Moss**

Purdue University

PEARSON