

Methods of analysis of resistive circuits


Large scale circuits by 1 st order linear equations

Algorithm to analyze circuit using computers

Node voltage analysis

1. Unknowns are node voltage (n-1)
2. Express current as function of node voltage
3. Apply KCL to all nodes except reference (n-1)

① Resistors + independent current source

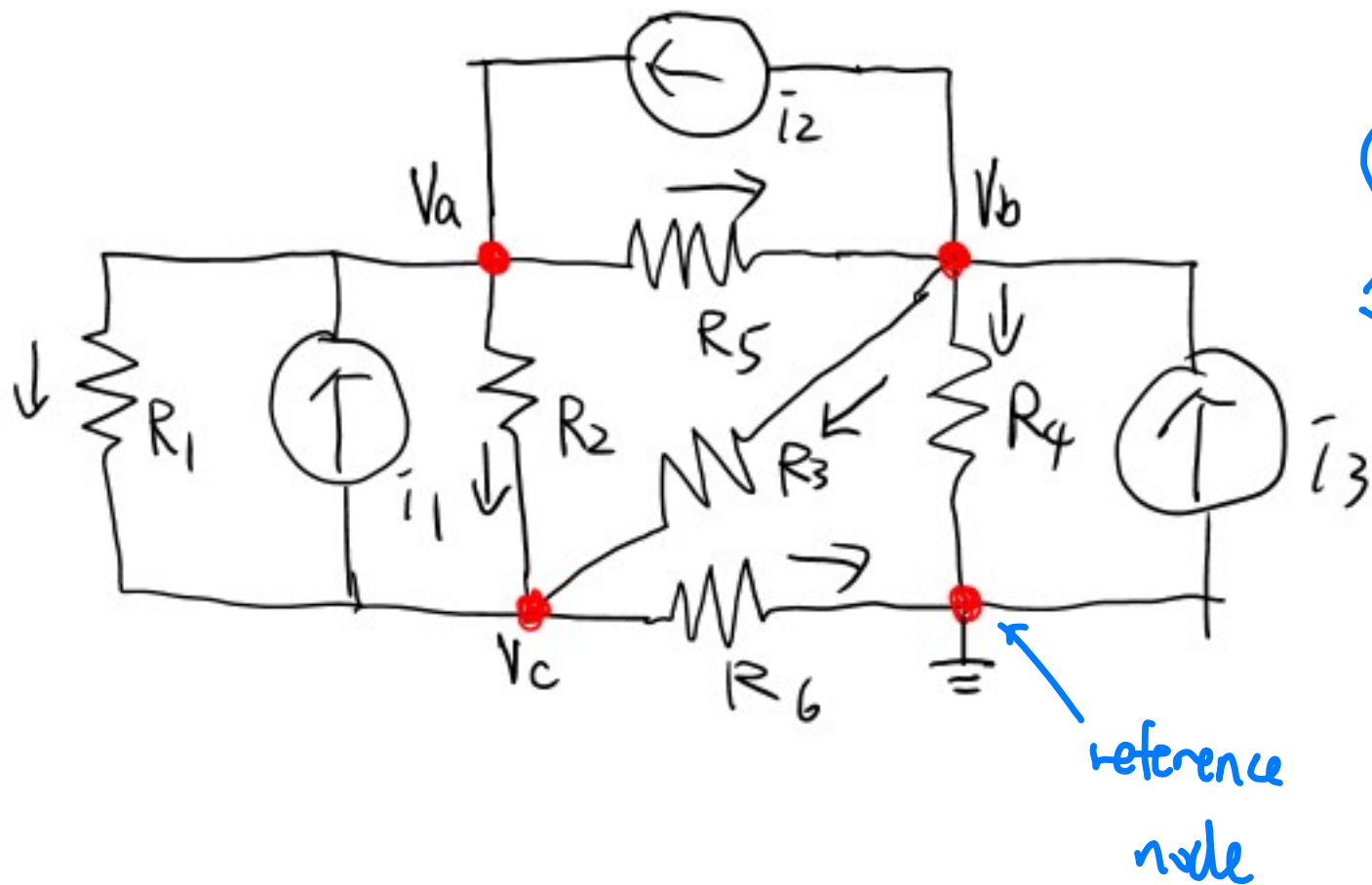

$$\text{node a: } -\frac{V_a - V_c}{R_1} + \bar{i}_1 - \frac{V_a - V_b}{R_2} + \bar{i}_2 - \frac{V_a - V_b}{R_5} = 0$$

$$\text{node b: } -\bar{i}_2 + \frac{V_a - V_b}{R_5} - \frac{V_b - V_c}{R_3} - \frac{V_b}{R_4} + \bar{i}_3 = 0$$

$$\text{node c: } \frac{V_a - V_c}{R_1} - \bar{i}_1 + \frac{V_a - V_c}{R_2} + \frac{V_b - V_c}{R_3} - \frac{V_c}{R_6} = 0$$

$$\text{node a: } -\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_5}\right)V_a + \frac{1}{R_5}V_b + \left(\frac{1}{R_1} + \frac{1}{R_2}\right)V_c = -\bar{i}_1 - \bar{i}_2$$

$$\text{b: } \frac{1}{R_5}V_a - \left(\frac{1}{R_5} + \frac{1}{R_3} + \frac{1}{R_4}\right)V_b + \frac{1}{R_3}V_c = \bar{i}_2 - \bar{i}_3$$

$$\text{c: } \left(\frac{1}{R_1} + \frac{1}{R_2}\right)V_a + \frac{1}{R_3}V_b - \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_6}\right)V_c = \bar{i}_1$$


$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_5} & -\frac{1}{R_5} & -(\frac{1}{R_1} + \frac{1}{R_2}) \\ \frac{1}{R_5} & -(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5}) & \frac{1}{R_3} \\ \frac{1}{R_1} + \frac{1}{R_2} & \frac{1}{R_3} & -(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_6}) \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} \bar{I}_1 + \bar{I}_2 \\ \bar{I}_2 - \bar{I}_3 \\ \bar{I}_1 \end{bmatrix}$$

$$AV = b \Rightarrow V = A^{-1}b$$

$$\bar{I}_1 = 1A, \bar{I}_2 = 2A, \bar{I}_3 = 3A, \quad R_1 = R_5 = 5\Omega, \quad R_2 = R_6 = 2\Omega, \quad R_3 = 10\Omega, \quad R_4 = 4\Omega$$

$$A = \begin{bmatrix} 0.9 & -0.2 & -0.7 \\ 0.2 & -0.55 & 0.1 \\ 0.7 & -0.1 & -1.3 \end{bmatrix} \quad b = \begin{bmatrix} 3 \\ -1 \\ 1 \end{bmatrix} \quad V = \begin{bmatrix} 7.16 \\ 5.05 \\ 3.47 \end{bmatrix}$$

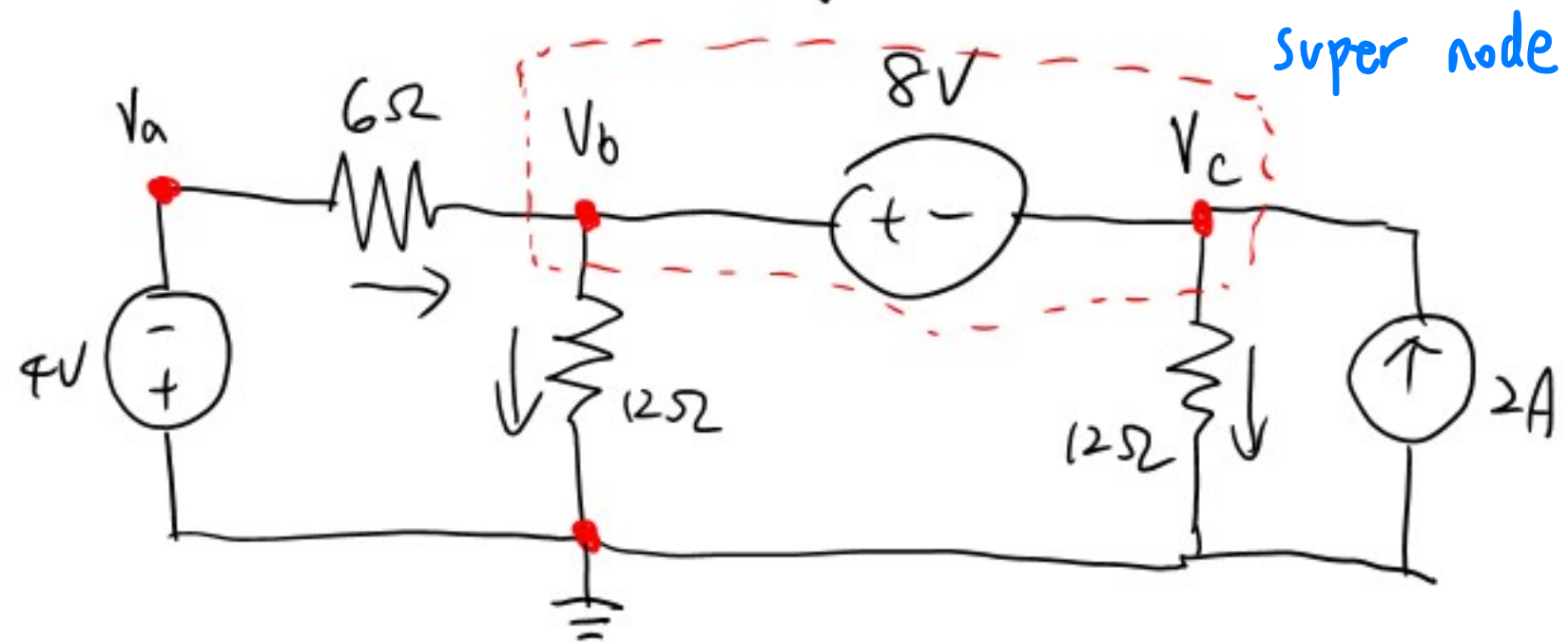② Resistor + independent "voltage" source



node a : $V_a = -4V$

node b : current in the ind. voltage source cannot be expressed by node voltage


node b, c. combine as "super node" (view as the same node)

$$\frac{V_a - V_b}{6} - \frac{V_b}{12} - \frac{V_c}{12} + 2 = 0 \Rightarrow V_b = 6V, V_c = -2V$$
$$V_b - V_c = 8$$

$$V = IR$$

$$\Rightarrow I = \frac{V}{R}$$

③ Resistor + dependent source

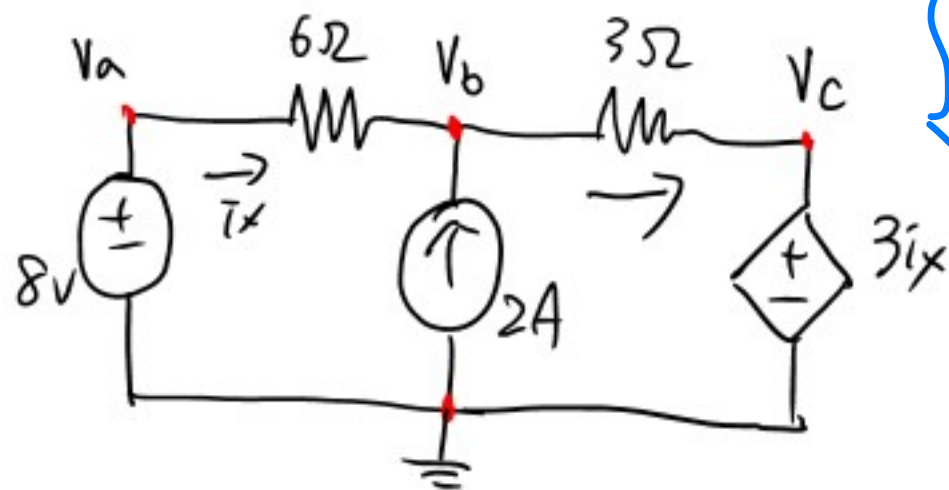

node a, $V_a = 8V$

node b, $\frac{V_a - V_b}{6} + 2 - \frac{V_b - V_c}{3} = 0$

node c, $V_c = 3i_x = 3 \cdot \frac{V_a - V_b}{6}$

$$V_a + 0V_b + 0V_c = 8$$

$$\frac{1}{6}V_a - \frac{1}{2}V_b + \frac{1}{3}V_c = -2$$

$$\frac{1}{2}V_a - \frac{1}{2}V_b - V_c = 0$$

$$A = \begin{bmatrix} 1 & 0 & 0 \\ \frac{1}{6} & -\frac{1}{2} & \frac{1}{3} \\ \frac{1}{2} & -\frac{1}{2} & -1 \end{bmatrix}$$



$$b = \begin{bmatrix} 8 \\ -2 \\ 0 \end{bmatrix}$$

$$V = \begin{bmatrix} 8 \\ 1 \\ -2 \end{bmatrix}$$

Mesh current analysis

1. Unknowns is mesh current (I)
2. Express voltage of each branch as function of mesh current
3. Apply KVL to all meshes (I)

mesh = independent loop

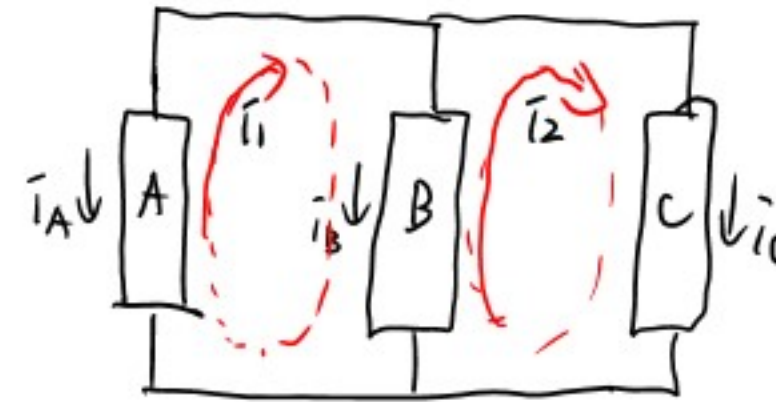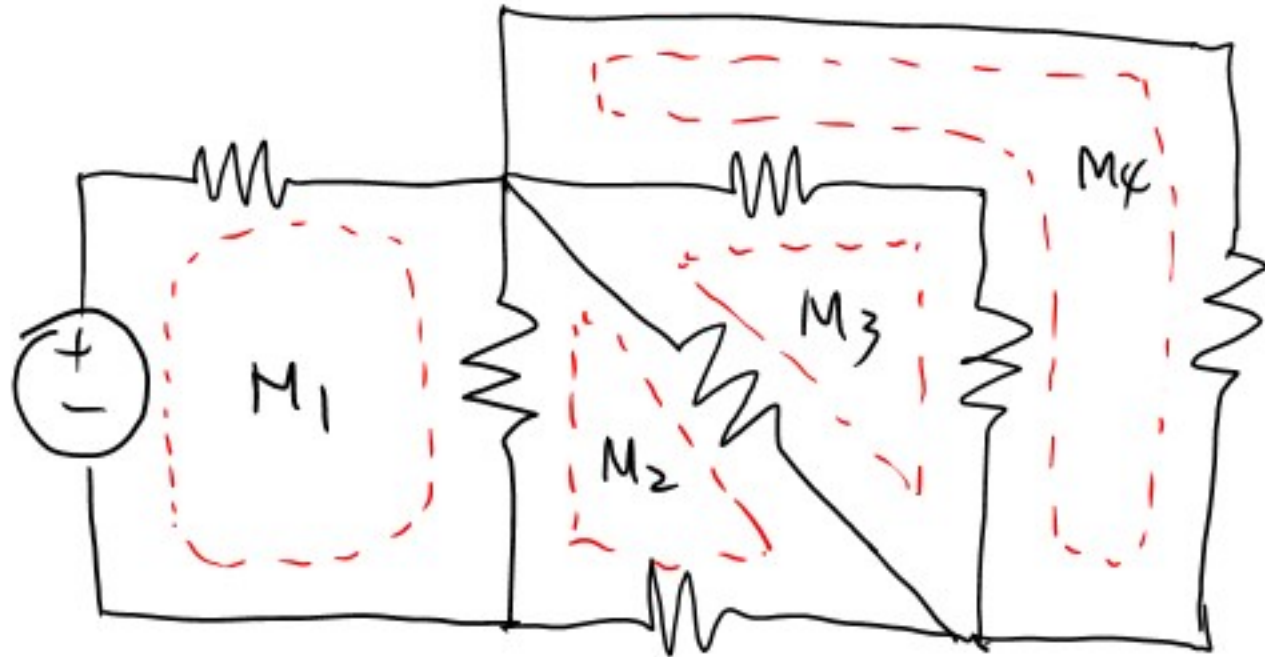


mesh current, \bar{i}_1, \bar{i}_2

$$\bar{i}_A = -\bar{i}_1$$

$$\bar{i}_B = \bar{i}_1 - \bar{i}_2$$

$$\bar{i}_C = \bar{i}_2$$

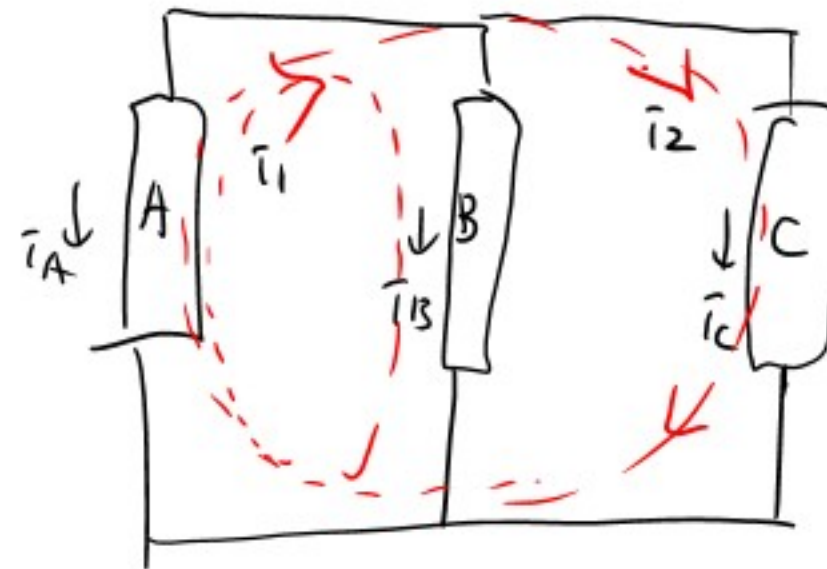


mesh current, \bar{i}_1, \bar{i}_2

$$\bar{i}_A = -\bar{i}_1 - \bar{i}_2$$

$$\bar{i}_B = \bar{i}_1$$

$$\bar{i}_C = \bar{i}_2$$

resistor + voltage source ... ②

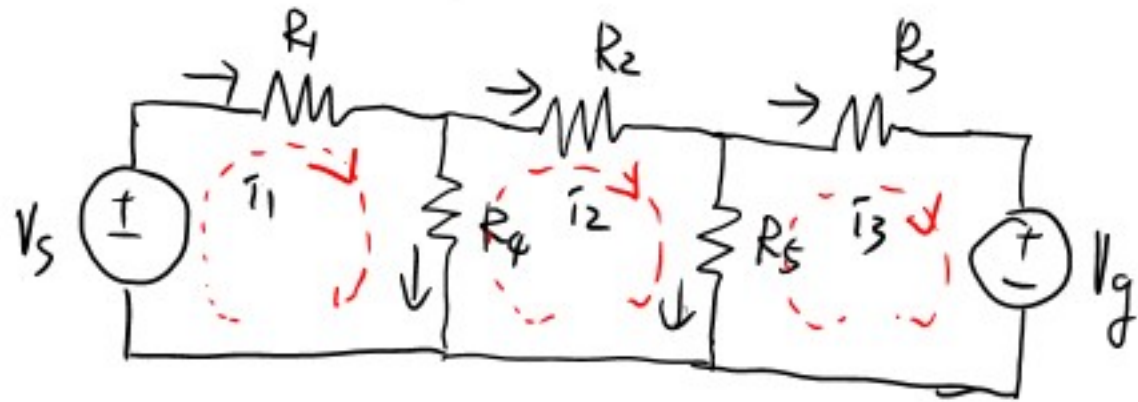

$$\begin{cases} \text{mesh 1: } +V_s - \bar{i}_1 R_1 - (\bar{i}_1 - \bar{i}_2) R_4 = 0 \\ \text{mesh 2: } (\bar{i}_1 - \bar{i}_2) R_4 - \bar{i}_2 R_2 - (\bar{i}_2 - \bar{i}_3) R_5 = 0 \\ \text{mesh 3: } (\bar{i}_2 - \bar{i}_3) R_5 - \bar{i}_3 R_3 - V_g = 0 \end{cases}$$


$$\begin{cases} (R_1 + R_4) \bar{i}_1 - R_4 \bar{i}_2 + 0 \bar{i}_3 = V_s \\ -R_4 \bar{i}_1 + (R_2 + R_4 + R_5) \bar{i}_2 - R_5 \bar{i}_3 = 0 \\ 0 \bar{i}_1 - R_5 \bar{i}_2 + (R_3 + R_5) \bar{i}_3 = -V_g \end{cases}$$

$$A = \begin{bmatrix} R_1 + R_4 & -R_4 & 0 \\ -R_4 & R_2 + R_4 + R_5 & -R_5 \\ 0 & -R_5 & R_3 + R_5 \end{bmatrix} \quad b = \begin{bmatrix} V_s \\ 0 \\ -V_g \end{bmatrix}$$

$$\bar{i} = \begin{bmatrix} \bar{i}_1 \\ \bar{i}_2 \\ \bar{i}_3 \end{bmatrix}$$

$$\begin{aligned} \bar{i}_{R_1} &= \bar{i}_1 & \bar{i}_{R_4} &= \bar{i}_1 - \bar{i}_2 \\ \bar{i}_{R_2} &= \bar{i}_2 & \bar{i}_{R_5} &= \bar{i}_2 - \bar{i}_3 \\ \bar{i}_{R_3} &= \bar{i}_3 \end{aligned}$$

resistor + independent current source

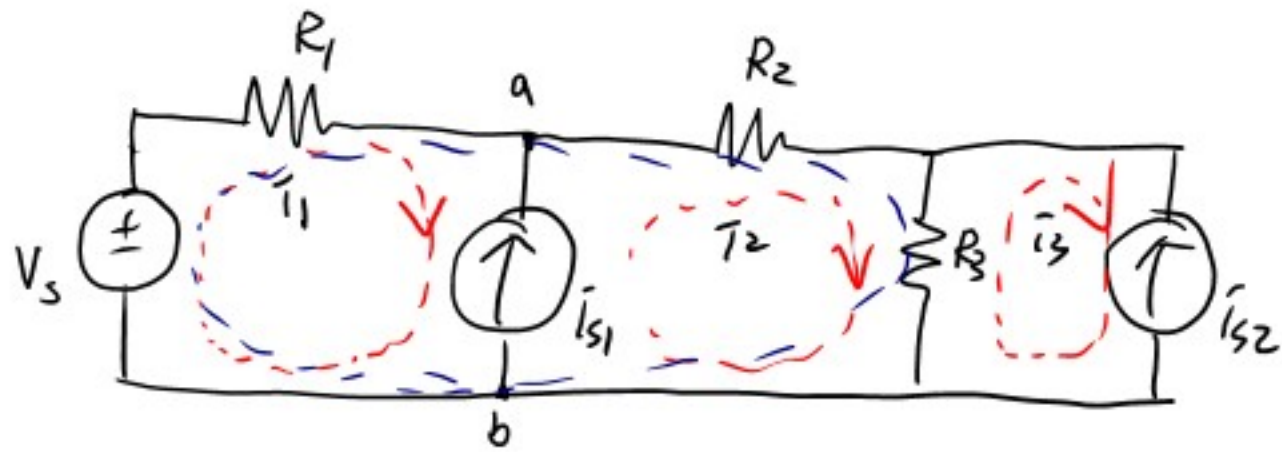

$$\text{mesh 1: } +V_s - i_1 R_1 - V_{ab} = 0 \quad \text{--- (1)}$$

$$\underline{-i_1 + i_2 = -i_{s1}}$$

$$\text{mesh 2: } \underline{V_{ab}} - i_2 R_2 - (i_2 - i_3) R_3 = 0 \quad \text{--- (2)}$$

$$\text{mesh 3: } i_3 = -i_{s2}$$

Super mesh combine two meshes containing current source

$$\text{mesh 1,2: } V_s - i_1 R_1 - i_2 R_2 - (i_2 - i_3) R_3 = 0$$

$$-i_1 + i_2 = -i_{s1}$$

$$\text{mesh 3: } i_3 = -i_{s2}$$


Case 1: current source on branch of only one mesh

Case 2: current source is a common branch to two meshes

sol: assume voltage across current source as an unknown

sol: create supermesh containing two meshes

resistor with dependent source

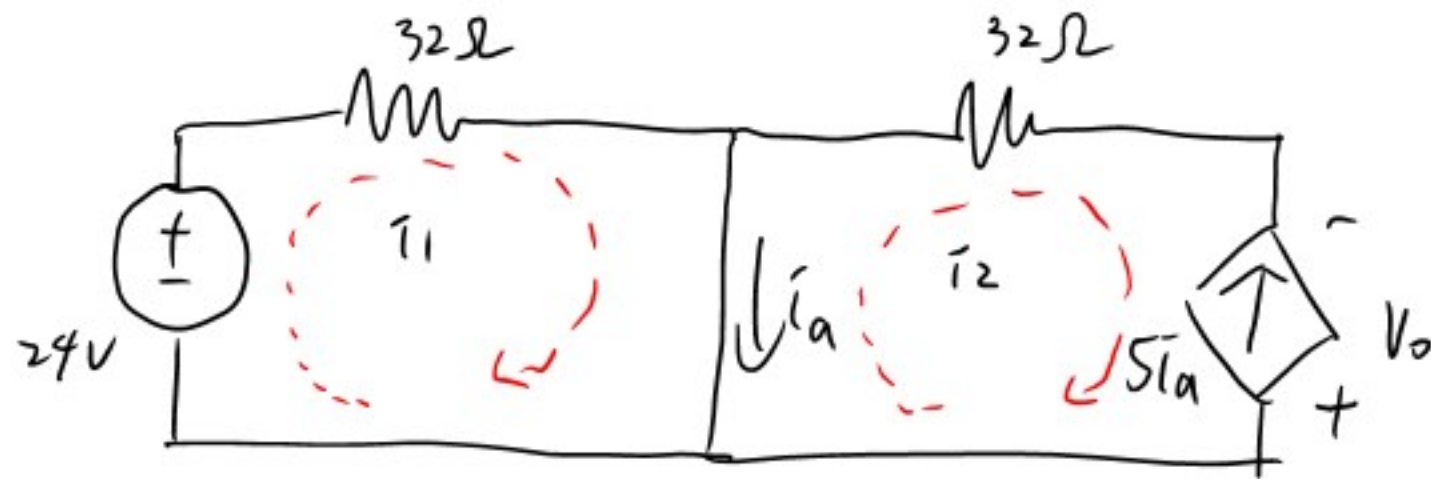

$$V_o = ?$$

$$\bar{i}_1, \bar{i}_2, V_o$$

$$\begin{cases} 24 - 32\bar{i}_1 = 0 \\ -32\bar{i}_2 + V_o = 0 \\ 5\bar{i}_a = -\bar{i}_2 = 5(\bar{i}_1 - \bar{i}_2) \end{cases}$$

$$V = IR.$$

$$\bar{i}_1 = \frac{24}{32} = \frac{3}{4} A$$

$$5\bar{i}_1 - 4\bar{i}_2 = 0 \Rightarrow \bar{i}_2 = \frac{5}{4}\bar{i}_1 = \frac{5}{4} \cdot \frac{3}{4} = \frac{15}{16} A$$

$$V_o = 32\bar{i}_2 = 32 \cdot \frac{15}{16} = 30 V$$

mesh or node?

- mesh is easier for voltage source
 - node is easier for current source
-) avoid super nodes & meshes

-
- use the one with fewer equations (meshes and nodes)
 - consider what information is required, if current is of interest, mesh is easier
- ↓ voltage & current sources