

Lab 06: Oscillator

【目的】

Build oscillator using op amps and reactive elements

【原理】

Lead lag network

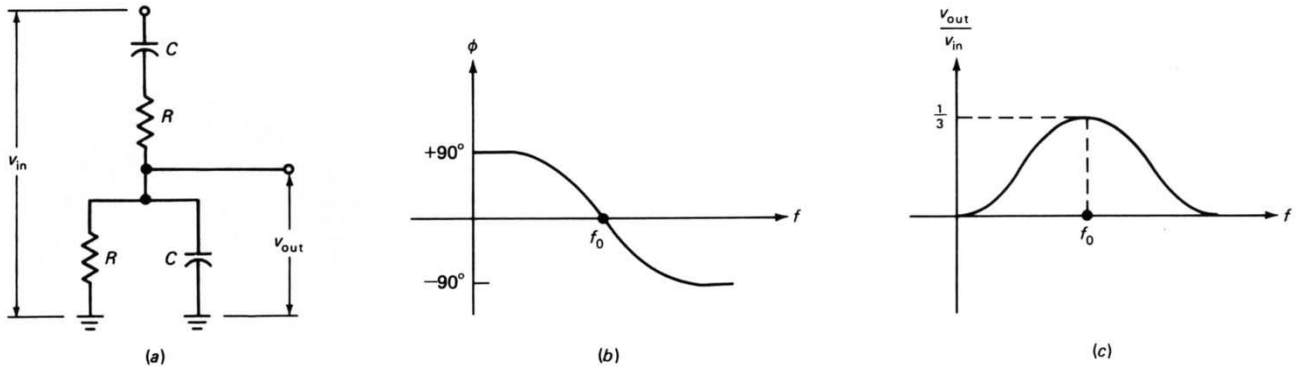


Fig. 38-1. Lead-lag network. (a) Circuit; (b) phase shift; (c) voltage gain.

$$f_0 = \frac{1}{2\pi RC} \quad A(f_0) = \frac{1}{3}$$

Twin-T filter

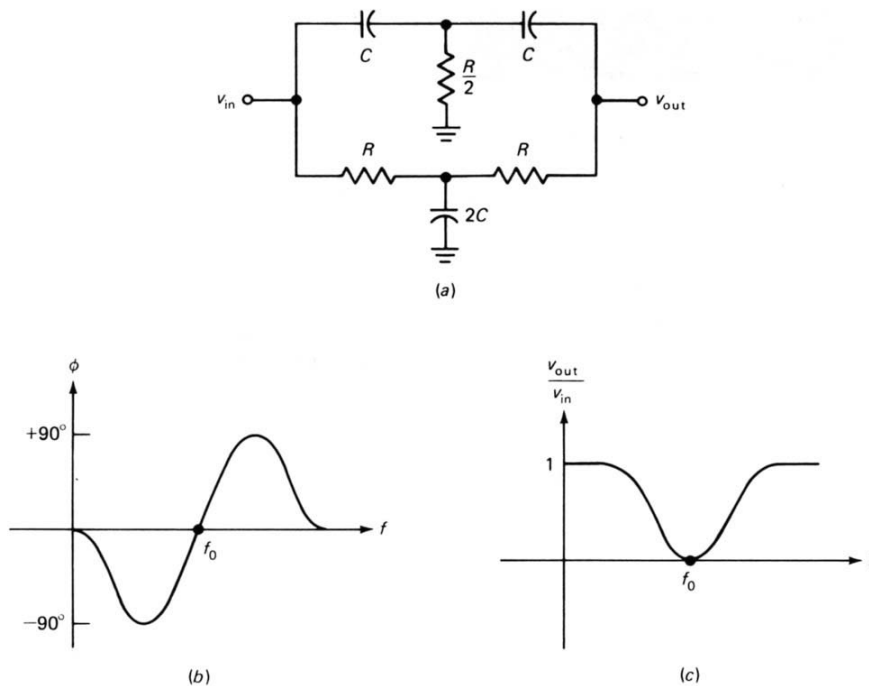


Fig. 38-3. Twin-T filter. (a) Circuit; (b) phase shift; (c) voltage gain.

$$f_0 = \frac{1}{2\pi RC} \quad A(f_0) \approx 0$$

【儀器】

示波器、電源供應器、電阻($100\ \Omega$, $220\ \Omega$, $1\text{K}\ \Omega$ x2, $10\text{K}\ \Omega$)、電容($0.1\ \mu\text{F}$ x2, $0.2\ \mu\text{F}$)、OPAMP (ua741C)、可變電阻($1\text{K}\ \Omega$)

【步驟】

Wien-Bridge Oscillator

1. Connect the circuit and calculate the theoretical oscillation frequency (f_0) based on lead-lag network.
2. Adjust R_2 to get as large a sine wave v_{out} as possible without excessive clipping or distortion (roughly 15 V p-p)
3. Measure and record the output frequency
4. Measure and record the phase angle between v_{in} (pin3) and v_{out} (pin6)

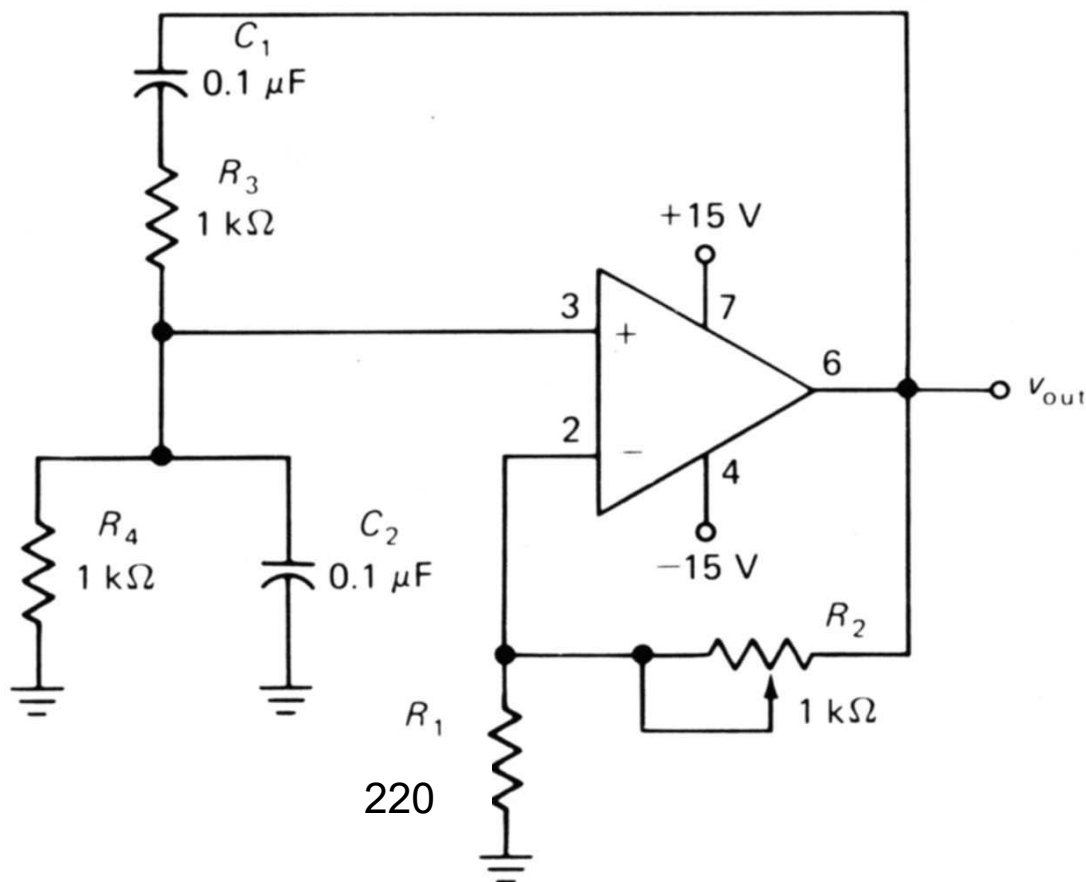


Fig. 38–5. Experimental Wien-bridge oscillator.

Twin-T Oscillator

1. Connect the circuit and calculate the theoretical oscillation frequency (f_0) based on lead-lag network.
2. Adjust R_2 to get as large a sine wave v_{out} as possible without excessive clipping or distortion (roughly 15 V p-p)
3. Measure and record the output frequency
4. Measure and record the phase angle between v_{in} (pin3) and v_{out} (pin6)

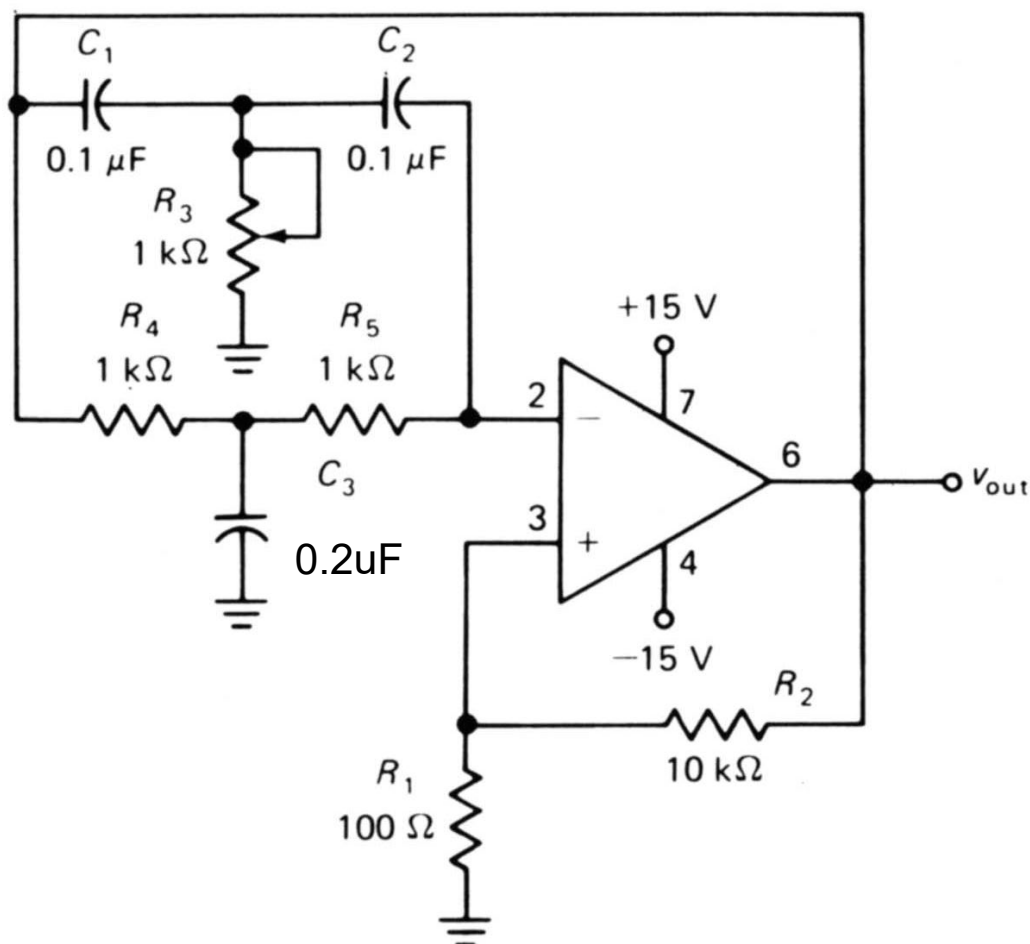


Fig. 38–6. Experimental twin-T oscillator.

【問題與討論】

1. Compare the measured frequency and theoretical values. Are they different? If yes, why?
2. If we want the wien-bridge oscillator to oscillate at 5 kHz, what component can we change to accomplish it?
3. If the capacitors in the twin-T oscillator are constant, what are the required values of resistors to get an oscillation frequency of 10 kHz?

【補充】

紀錄表格 (畫波型，紀錄頻率)

f_0 (calc)	f_0 (meas)	ϕ^0 (Phase angle) pin3 and pin6
1592	1592	0