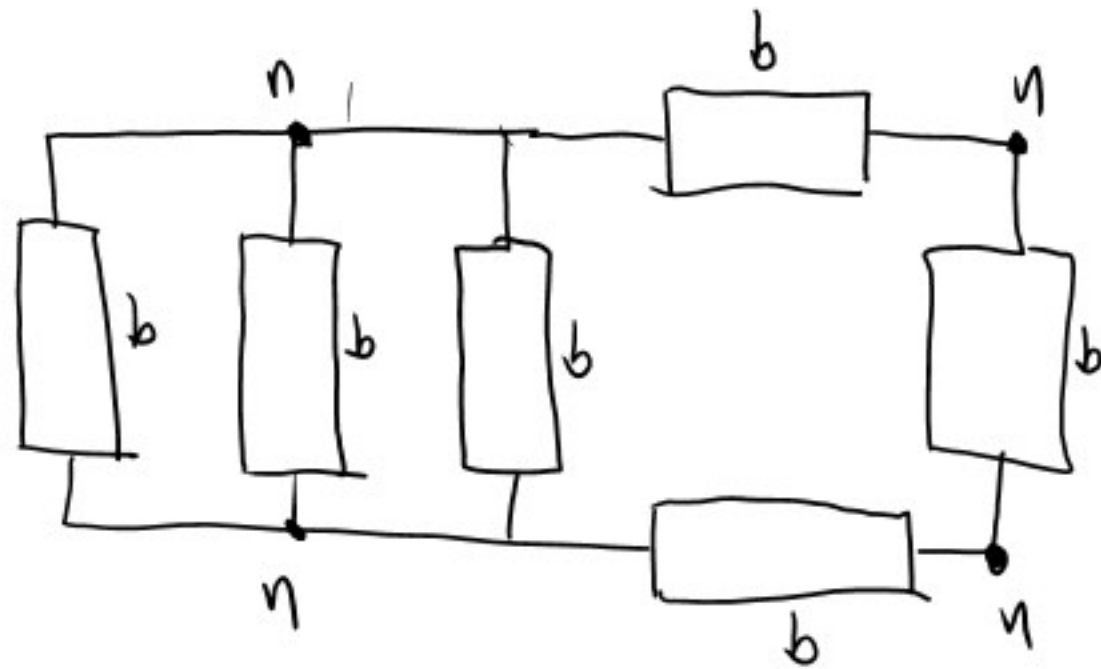


Electric circuit: a interconnection of circuit elements linked together in a closed loop



Network topology: node (n), branch (b), loop (l)

branch : a single element

node: point of connection between 2 or more branches

loop: a closed path
independent loop (mesh)

$$n=4, b=6, l=3, b=n+l-1$$

6 4 3

mobile carrier in electric circuit

charge: Q (electron)

current $I = \frac{dQ}{dt}$

I or $i(t)$

voltage $V = \frac{dW}{dQ}$

V or $v(t)$

power. $P = \frac{dW}{dt} = VI$

I changes
w.r.t. time


D.C.

$$i = 2A \quad i = -2A$$

$$V = 4V = V_a - V_b$$

$$V = -4V = V_a - V_b$$

$$\Rightarrow V_b - V_a = 4V$$

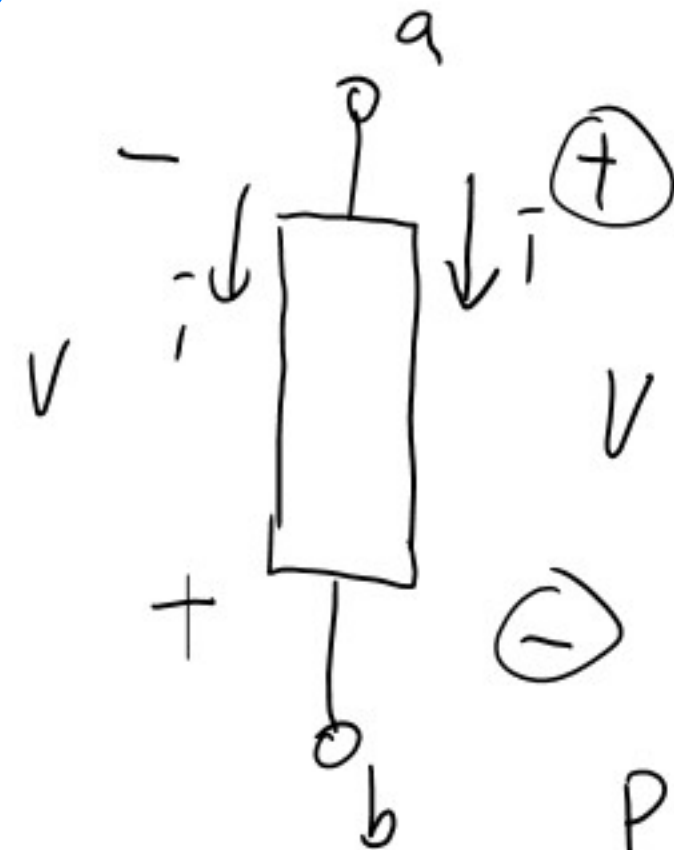

$$V = V_a - V_b$$

$$P = V \cdot i$$

power absorbed by the element.

$P = V \cdot i$
power supplied
by the element

the sign indicates the current direction /
which end has the higher potential /
a circuit element supplies or absorbs energy

Kirchhoff's law:

current law (KCL) = the algebraic sum of the current into a "node" is zero


$$\sum_{n=1}^N \bar{I}_n = 0$$

conservation of charge

voltage law (KVL) = the algebraic sum of the voltage around a loop is zero

$$\sum_{n=1}^N V_n = 0$$

conservation of energy


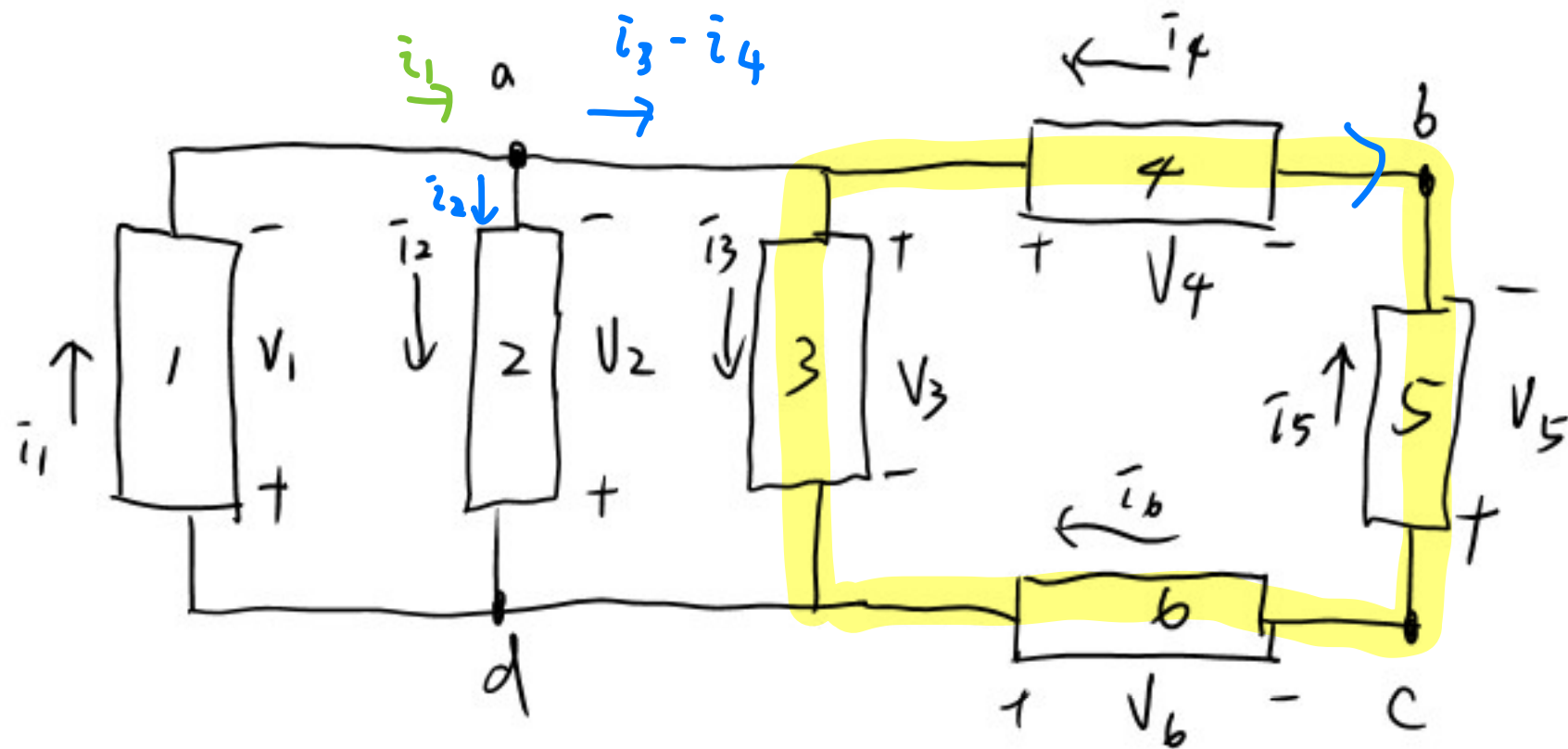


KCL: node a = $\underline{i_1} - \underline{i_2} - \underline{i_3} + i_4 = 0$

KVL: loop 4-5-6-3 = $-V_4 + V_5 + V_6 + V_3 = 0$

passive element (absorb energy) : resistor, capacitor.

1. resistor 電阻 (R) ohm law Ω

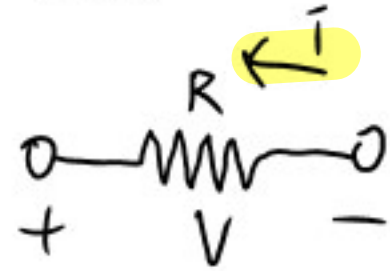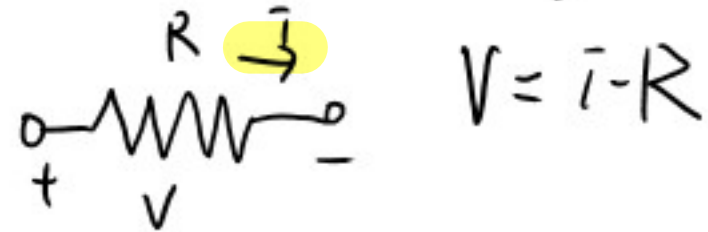


$$R = \rho \frac{L}{A}$$

resistivity ρ (green arrow pointing to ρ)
length L (green arrow pointing to L)
cross sectional area A (green arrow pointing to A)

$$V = -I \cdot R$$



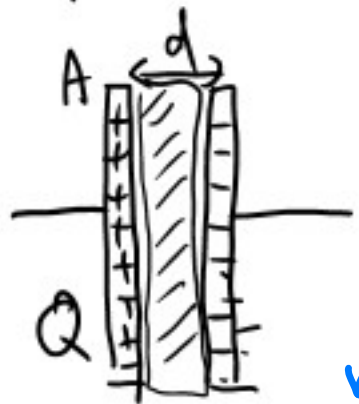2. capacitor 電容 (C), energy storage $\sim E$




$$C = \epsilon \cdot \frac{A}{d}$$

$$Q = C V$$

$$I(t) = C \cdot \frac{dV(t)}{dt}$$

parallel plates

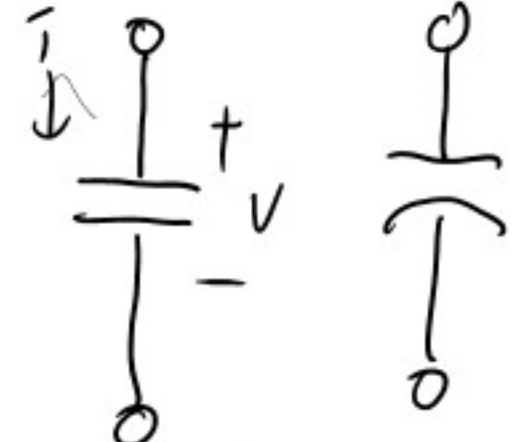

$$I = C \cdot \frac{dV}{dt}$$

note:

1. voltage change (charging, discharging) $dV(t)/dt$
2. In DC, act as open circuit ($i=0$)
3. in AC, act as resistor with values varying as frequency
4. actual capacitor has high resistivity (over Mohm)
5. in electric circuit, C is in $\mu F \sim pF$

10^{-6} 10^{-12}


mega ohm
(10^6)

not perfectly linear, only upon
a specific I interval

capacitor 1. internal property in transistor

2. widely used in the design of amplifier and filter.

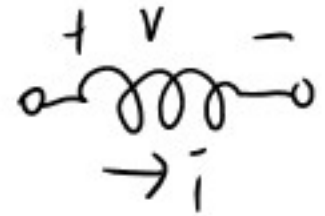3. Inductor (energy storage)  store energy as magnetic field B



$$V(t) = L \frac{di(t)}{dt}$$

in general, not used in electronic circuit for its size


nonlinear element

diode

transistor



operational amplifier (OPAMP)

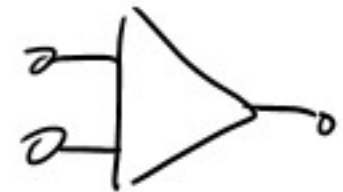


linear


nonlinear

relationship bw V and I?

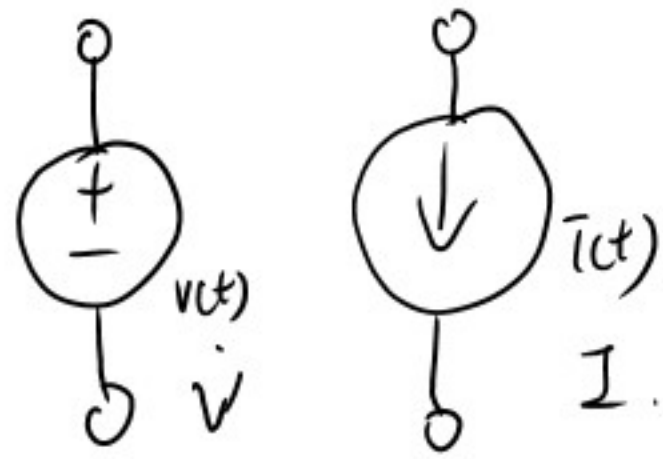active element (supply energy) = independent or dependent voltage or current source





ind.

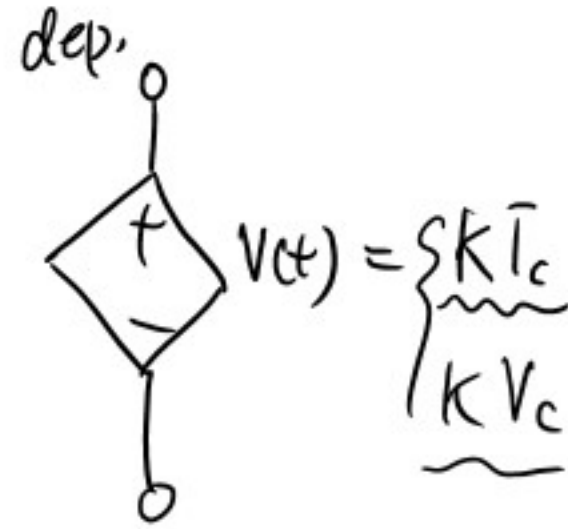





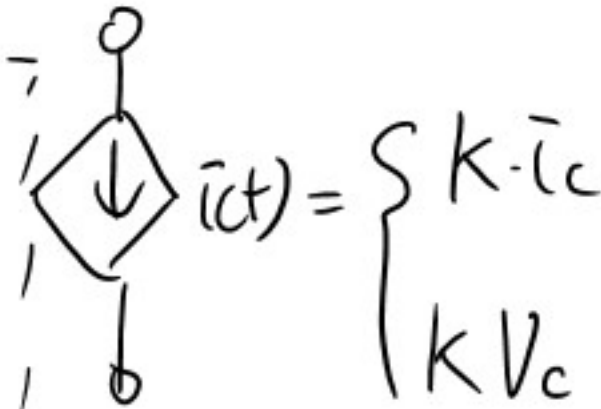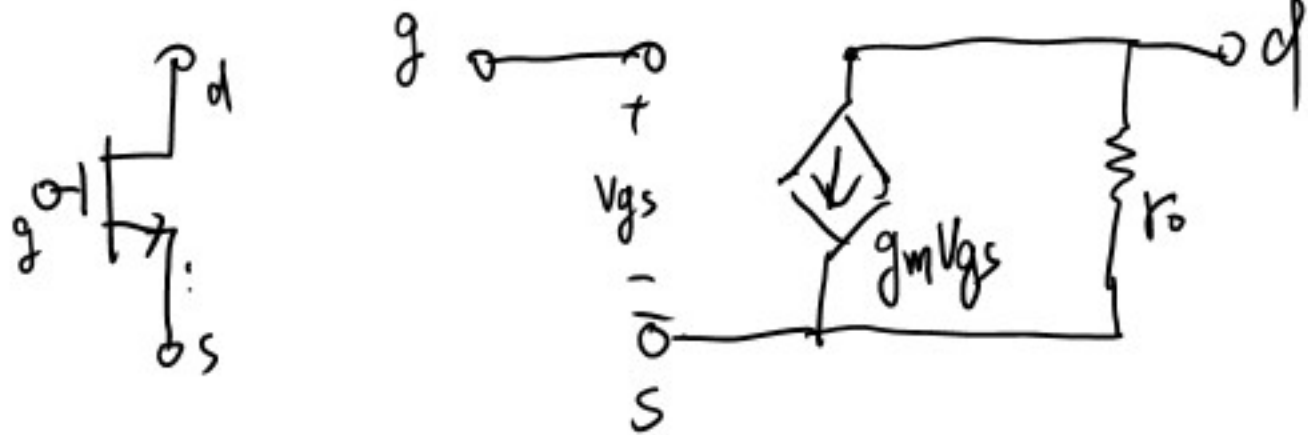


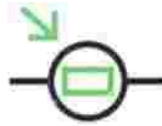







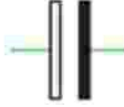















current controlled voltage source (CCVS)
voltage controlled voltage source (VCVS)

circuit model of a transistor

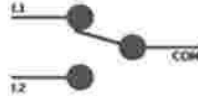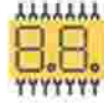


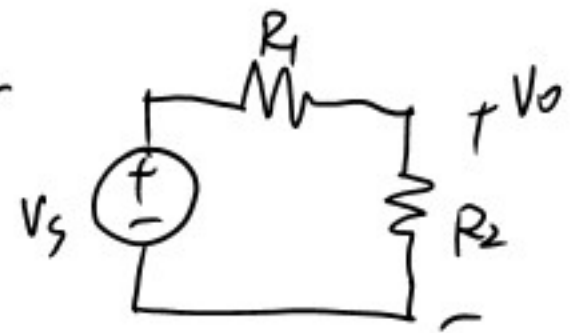
ACTIVE


PASSIVE

Transistor			Resistor		
Diode			LDR		
LED			Thermistor		
Photodiode			Capacitor		
Integrated Circuit		-	Inductor		
Operational Amplifier			Switch		
Seven Segment Display			Variable Resistor		
Battery			Transformer		

series,  $R_{eq} = R_1 + R_2$

parallel  $R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$ $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$




voltage divider  $V_o = \frac{R_1}{R_1 + R_2} V_s$ $R_1 = 1\Omega, R_2 = 3\Omega, V_o = \frac{3}{3+1} V_s = \frac{3}{4} V_s$

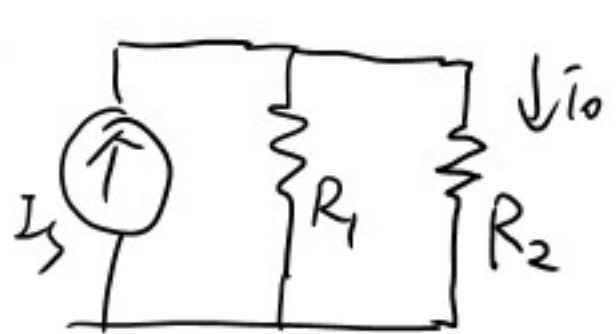current divider  $I_o = \frac{R_1}{R_1 + R_2} I_s$ $I_o = \frac{1}{4} I_s$




equivalent capacitor?



source

voltage in series

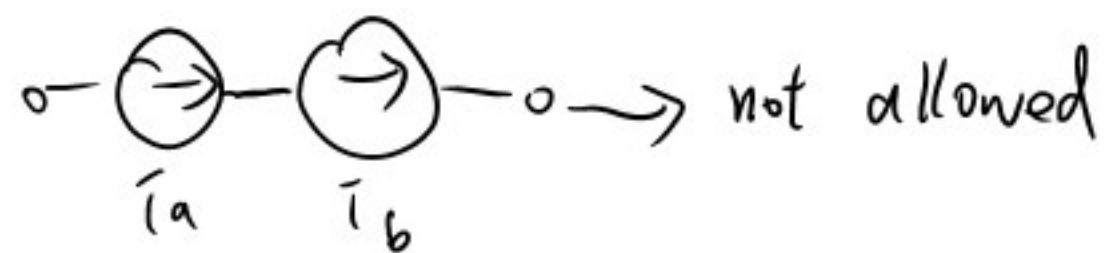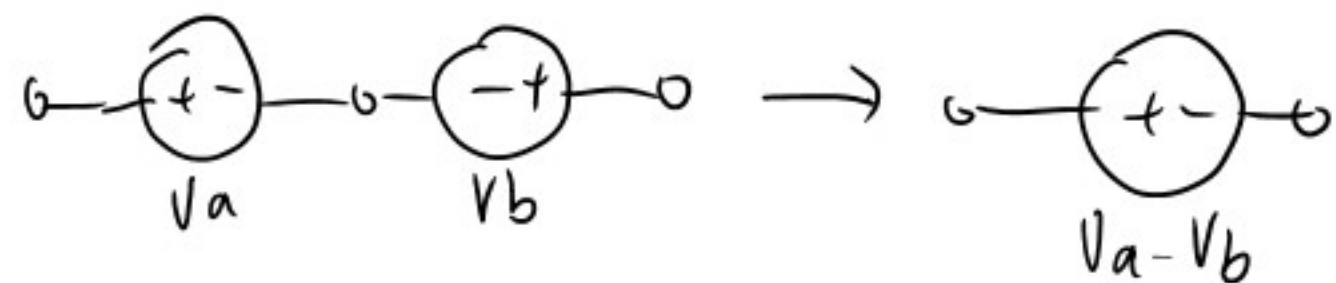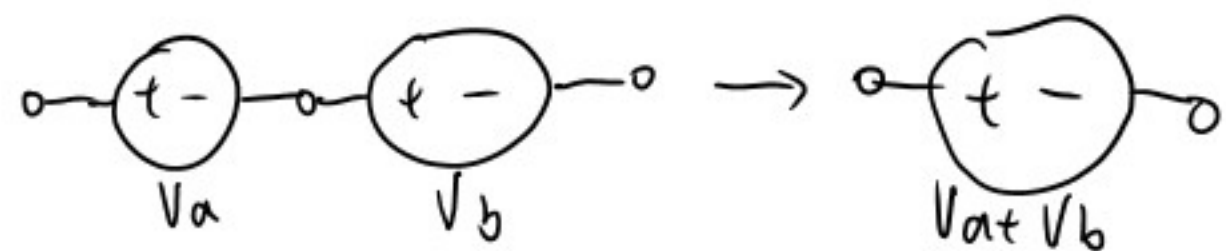

current source in parallel

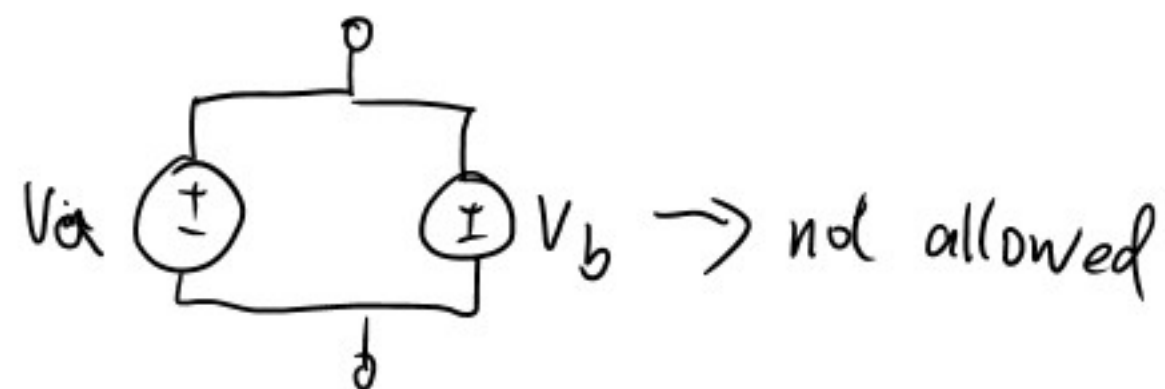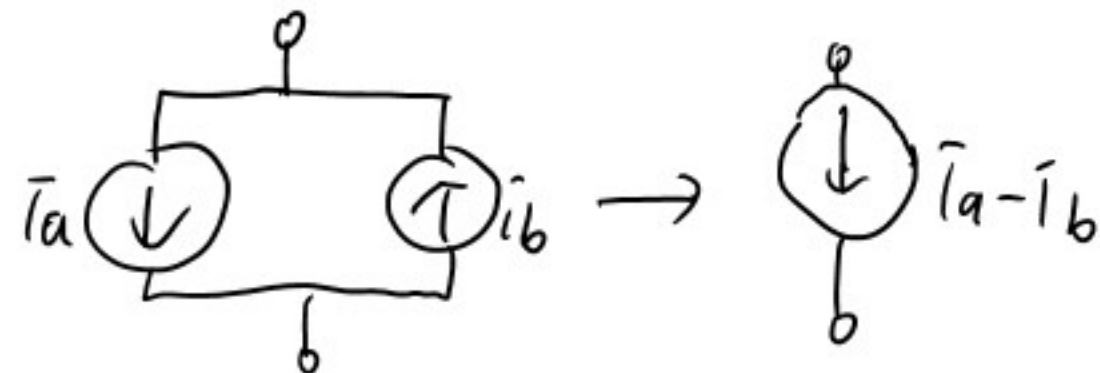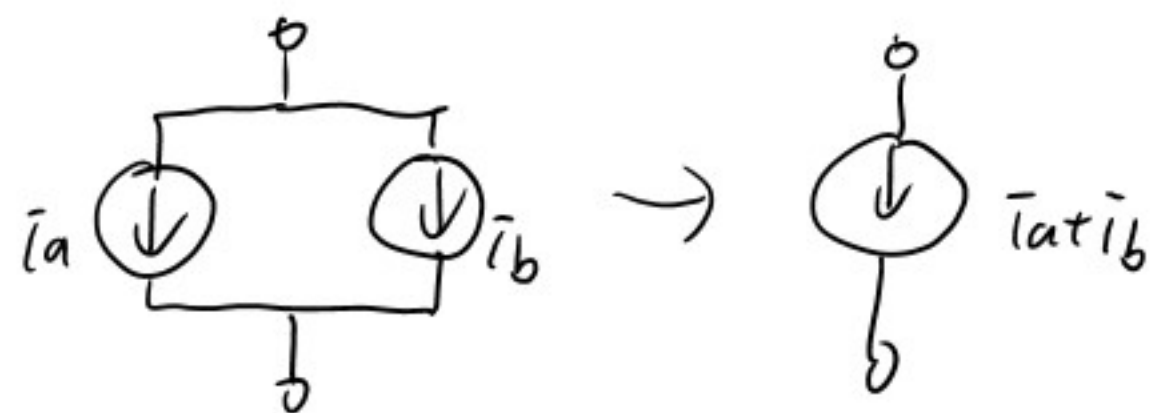

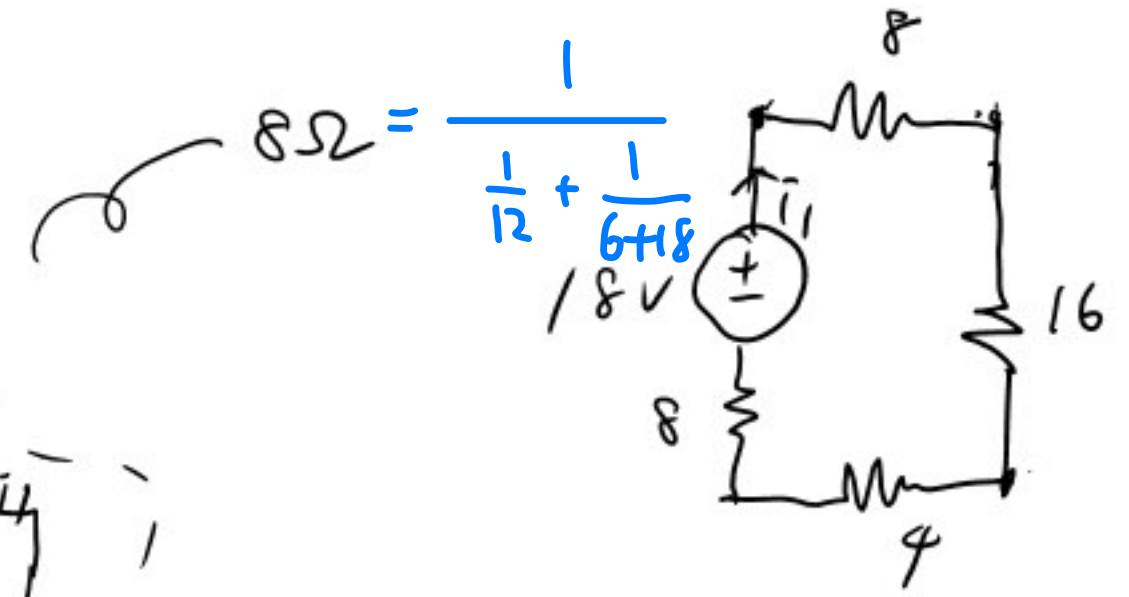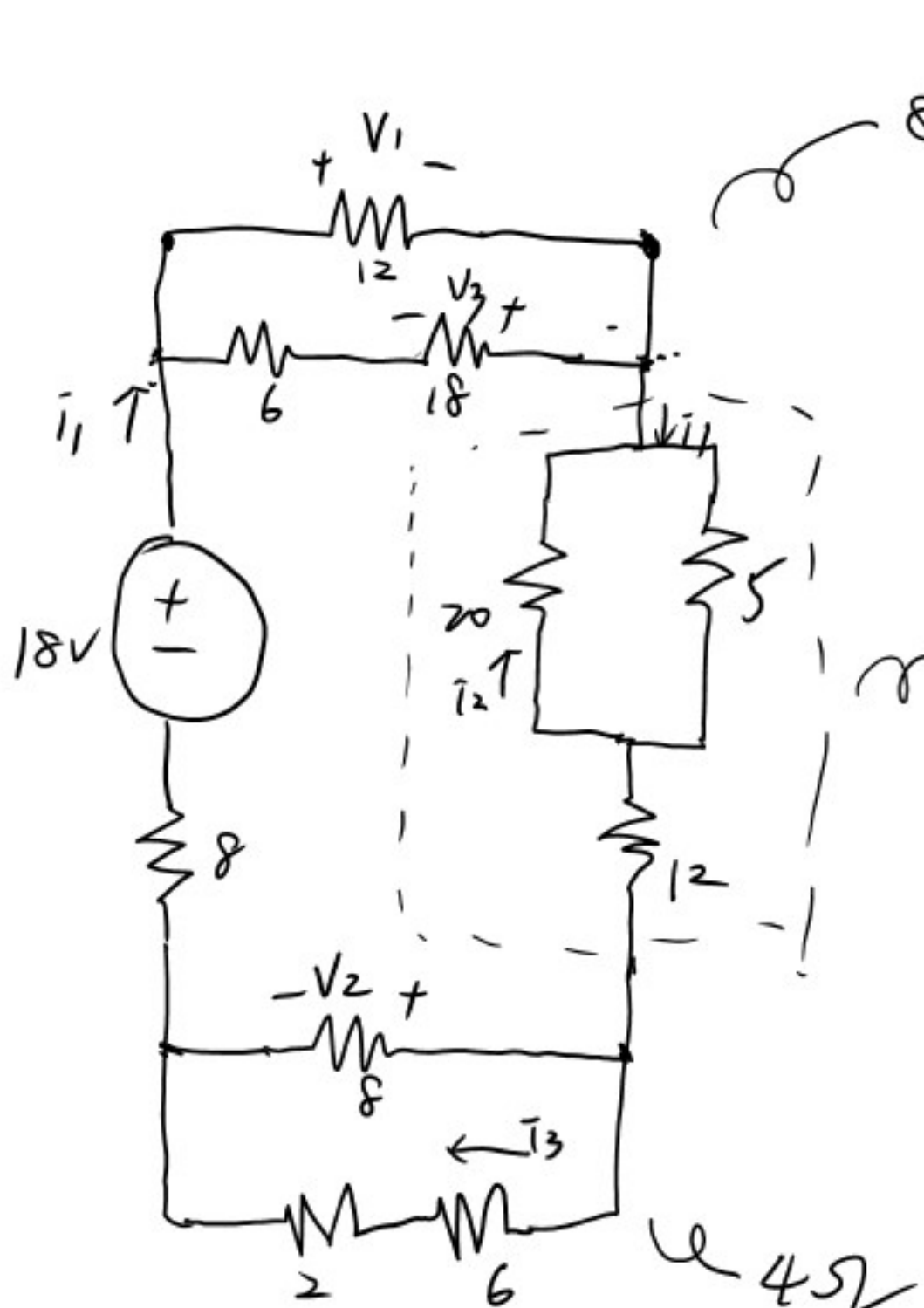

$$\bar{I}_1 = \frac{18}{8+16+8+4} = \frac{18}{36} = 0.5A \quad (\text{Ohm's Law})$$

$$V_1 = 18 \cdot \frac{8}{8+16+8+8} = 4V$$

$$16\Omega = \frac{1}{\frac{1}{2} + \frac{1}{5}} + 12$$

$$V_2 = 18 \cdot \frac{4}{8+16+8+8} = 2V$$

$$\bar{I}_2 = (-\bar{I}_1) \cdot \frac{5}{20+5} = -0.1A$$

$$V_3 = \frac{18}{6+18} (-V_1) = \frac{18}{24} (-4) = -3V$$

$$\bar{I}_3 = \bar{I}_1 \cdot \frac{8}{8+8} = 0.25A$$

$$4\Omega = \frac{1}{\frac{1}{8} + \frac{1}{2+6}}$$