

# Δ time response of AC signal

## ② energy storage element

capacitor	inductor		
symbol		C	L
i-V	$\bar{i} = C \cdot \frac{dv}{dt}$	in steady state (DC)	open
power	$P_c = C \cdot V \frac{dv}{dt}$	series	$\frac{C_1 C_2}{C_1 + C_2}$
energy	$W_c = \frac{1}{2} C V^2$	parallel	$C_1 + C_2$
Instantaneous change (AC)	$\bar{i}$		

In AC analysis, we need determine the initial condition when switch change at " $t_0$ "

1. Analyze DC circuit that exist before  $t_0$  ( $t < t_0$ )

2. Analyze capacitor voltage, inductor current change as AC source after  $t_0$  ( $t > t_0$ )

= highest derivative of voltage or current  
in the circuit's differential equation

### ⊙ Response of RC circuit



• Circuit that contains capacitors can be represented by differential equations, and the order of the circuit is usually equal to the number of capacitors (and inductors)

• time response of the circuit, means the change of output for an input change varies with respect to time

• Complete response = Transient response + steady-state response  
(natural response) (forced response)

• note, in electrical engineering or signal process, sometimes "transient" is used for "complete response".

PSPice

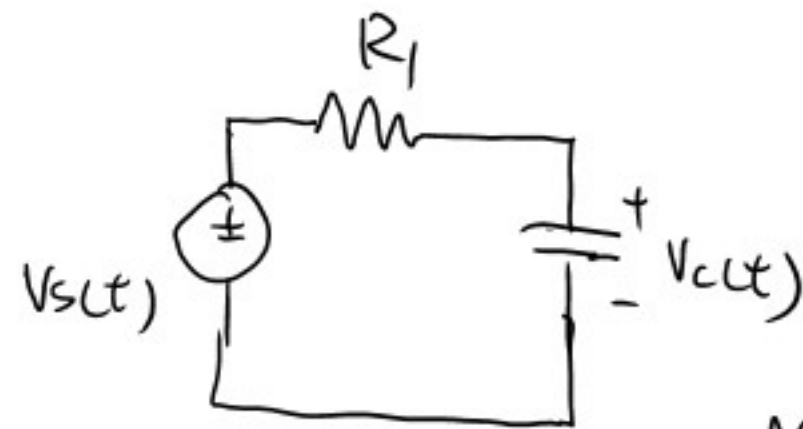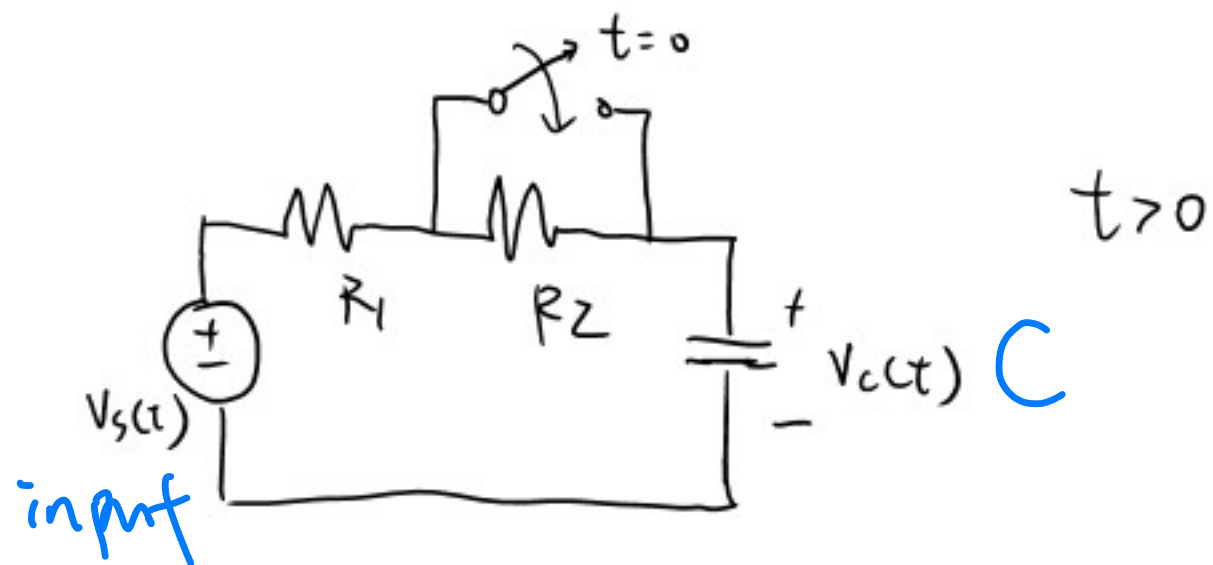


$$V_s(t) = A \cos(1000 \cdot t + \theta) \quad \omega = 1000 \text{ rad/s}$$

$$V_c(t) = B \cos(1000 \cdot t + \phi_1) \quad (t < 0)$$

$$B = A \cdot \frac{\omega C}{\sqrt{(R_1 + R_2)^2 + \omega^2 C^2}}$$
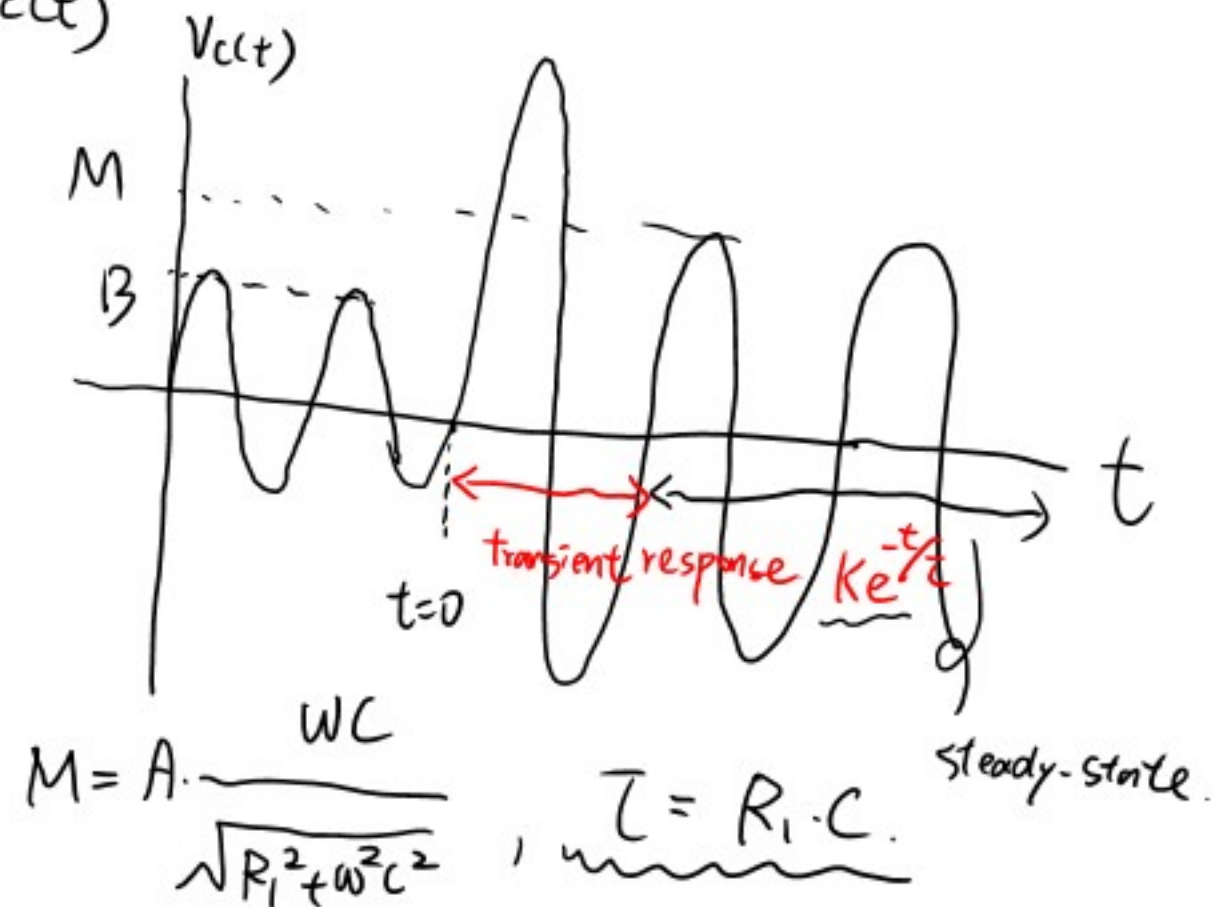
$$V_c(t) = \underbrace{k \cdot e^{-t/\tau}}_{\text{transient response}} + \underbrace{M \cdot \cos(1000 \cdot t + \phi_2)}_{\text{steady-state response}} \quad (t > 0)$$



## Stability


$$\left\{ \begin{array}{l} \tau > 0, \quad x_n(t) = k e^{-t/\tau} \rightarrow 0, \text{ as } t \rightarrow \infty \Rightarrow \text{stable.} \\ \tau < 0, \quad x_n(t) = k e^{-t/\tau} \rightarrow \infty, \text{ as } t \rightarrow \infty \Rightarrow \text{unstable} \end{array} \right.$$

↗ transient decays to 0  
↘ transient grows unbounded


- Steady-state response depends on the input, which contains the information of the input.
- In unstable circuit, information is lost because transient response is too large.



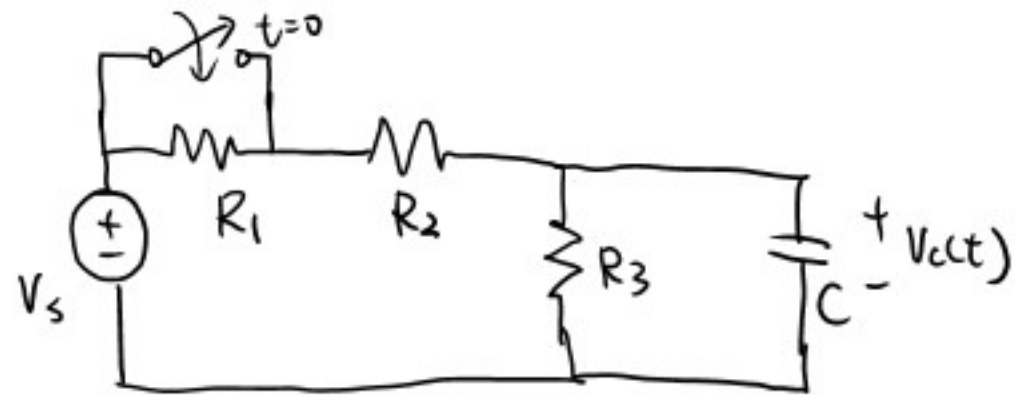② 1st order RC circuit to a constant input


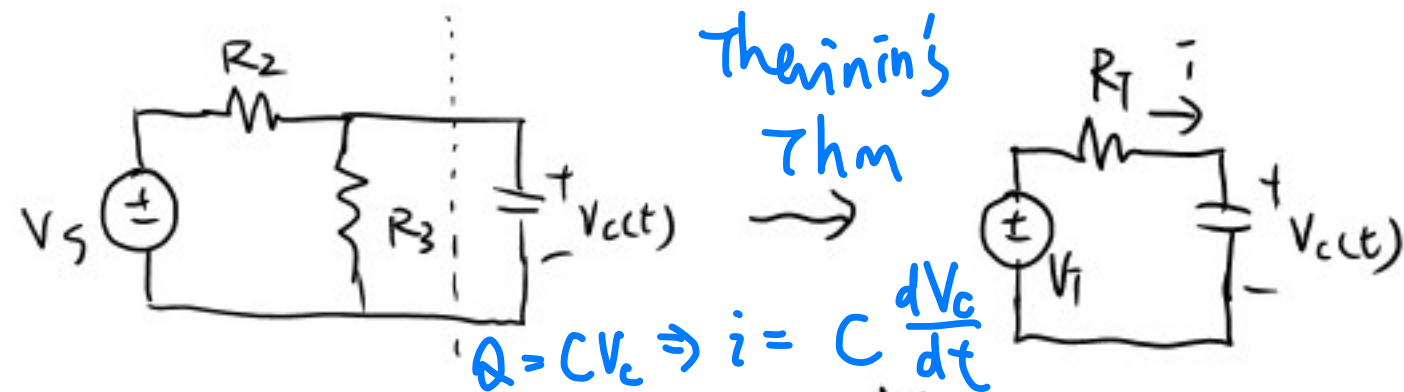
$$t=0, V_c = V_s \cdot \frac{R_3}{R_1 + R_2 + R_3} = V_c(0)$$



$$V_T = V_s \cdot \frac{R_3}{R_2 + R_3}$$

$$R_T = R_2 \parallel R_3 = \frac{R_2 R_3}{R_2 + R_3}$$

$$V_T = I \cdot R_T + V_c(t) = R_T \cdot C \cdot \frac{dV_c}{dt} + V_c \Rightarrow \frac{dV_c}{dt} + \frac{V_c}{R_T \cdot C} = \frac{V_T}{R_T \cdot C} \quad \left( R_T C = \tau \quad \frac{V_T}{R_T \cdot C} = K \right) \text{ let}$$

$$\frac{dV_c}{dt} + \frac{1}{\tau} \cdot V_c = K \rightarrow \frac{dV_c}{dt} = \frac{K\tau - V_c}{\tau} \rightarrow \int \frac{1}{K\tau - V_c} dV_c = \int \frac{1}{\tau} dt \rightarrow \ln(K\tau - V_c) = -\frac{t}{\tau} + T_0$$

$$\underline{V_c(t) = e^{-\frac{t}{\tau}} e^{T_0} + K\tau = A \cdot e^{-\frac{t}{\tau}} + K\tau}$$

solve differential equation

$$V_c(t) = A e^{-t/\tau} + kZ.$$

$$\left\{ \begin{array}{l} t=0, \quad V_c(0) = A + kZ \rightarrow A = V_c(0) - kZ \\ t=\infty, (t > 3\tau) \quad V_c(\infty) = kZ \end{array} \right.$$


$$V_c(t) = (V_c(0) - kZ) e^{-t/\tau} + kZ = \underbrace{V_c(\infty)}_{\text{steady-state}} + \underbrace{(V_c(0) - V_c(\infty)) e^{-t/\tau}}_{\text{transient}}, \quad \tau = R_T \cdot C.$$


Ex.  $V_s = 12V, R_1 = 10k\Omega, R_2 = 30k\Omega, R_3 = 60k\Omega, C = 2\mu F$

$$V_c(0) = 12 \cdot \frac{60}{10+30+60} = 7.2V, \quad \tau = R_T \cdot C = \frac{R_2 \cdot R_3}{R_2 + R_3} \cdot C = \frac{30(60)}{30+60} \times 10^3 \times 2 \times 10^{-6} = 40 \times 10^{-3} = \underline{40ms}$$

$$V_c(\infty) = k \cdot Z = V_1 = \frac{60}{30+60} \cdot 12 = 8V$$
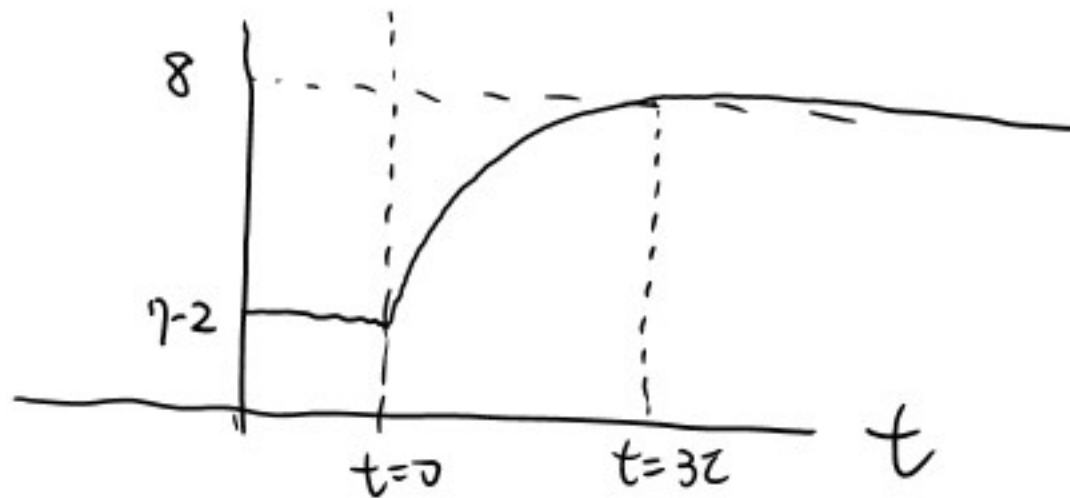
$$\begin{aligned} V_c(t) &= 8 + (7.2 - 8) e^{-t/40ms} \\ &= 8 - 0.8 e^{-t/0.04} (V) \end{aligned}$$



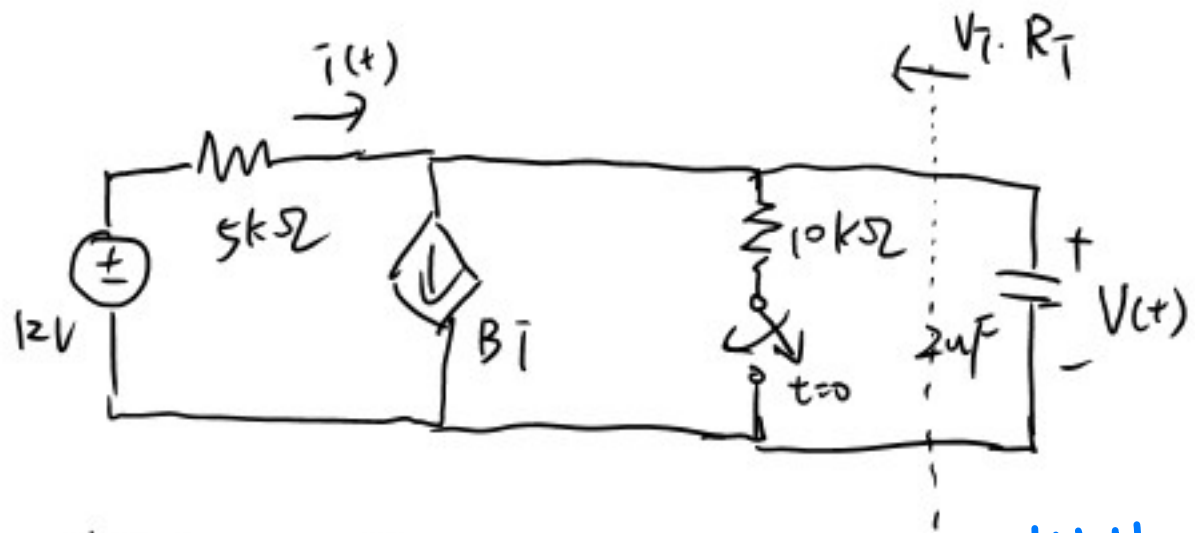


Design  $B$  so that the circuit is stable with  $\tau = 20\text{ms}$

$$V(0) = 12\text{V}$$


$t > 0$

KVL

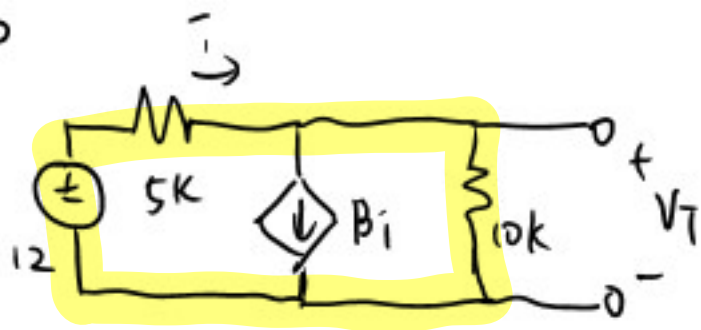

$$12 = 5\bar{i} + 10(\bar{i} - B\bar{i}) \rightarrow \bar{i} = \frac{12}{15 - 10B} \quad , \quad V_T = 10(\bar{i} - B\bar{i}) = \frac{120(1-B)}{15-10B} = \frac{24(1-B)}{3-2B}$$


KCL

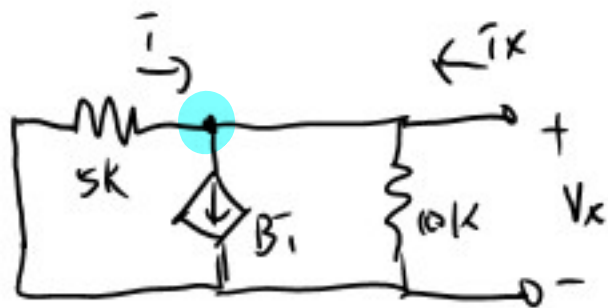

$$V_x = -5\bar{i} \rightarrow \bar{i} = -\frac{V_x}{5}$$

$$\bar{i} + \bar{i}_x = \frac{V_x}{10} + B\bar{i} \rightarrow \bar{i}_x = \frac{V_x}{10} + (B-1)\bar{i} = \frac{V_x}{10} + (B-1)\frac{-V_x}{5} = V_x \cdot \frac{3-2B}{10}$$
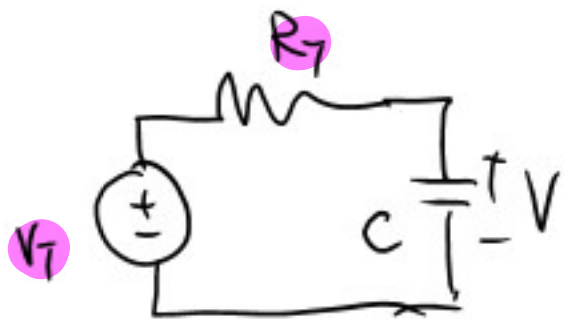
$$R_T = \frac{V_x}{\bar{i}_x} = \frac{10}{3-2B} \text{ (k}\Omega\text{)}$$



$$\tau = R_T \cdot C > 0 \rightarrow \frac{10}{3-2B} \cdot C > 0 \rightarrow 3-2B > 0 \rightarrow B < 1.5 \quad (\text{stable})$$

$$\tau = 20\text{ms} = \frac{10}{3-2B} \cdot C = \frac{10 \times 10^{-3}}{3-2B} \cdot 2 \times 10^{-6} \rightarrow B = 1$$

(steady state  $v(\infty)$ )

$$V_T = \frac{24(1-B)}{3-2B} = 0 = V(\infty), \quad \tau = 20 \text{ ms}$$

the circuit is stable when  $\tau = 20 \text{ ms}$

$$v(t) = 0 + \underbrace{(12 - 0)}_{V_C(\infty)} \cdot e^{-\frac{t}{\tau}} = 12 e^{-\frac{t}{0.02}} \text{ (V)}$$


$$V = IR \Rightarrow I = \frac{V}{R}$$

$$i(t) = \frac{12 - v(t)}{5} = 2.4 - 2.4 e^{-\frac{t}{0.02}} \text{ (mA)}$$



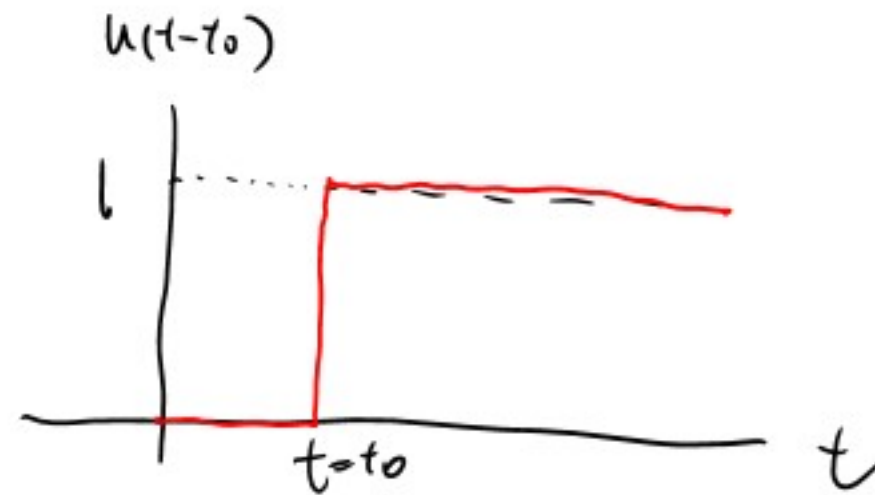
# ⑥ unit step response

$$u(t-t_0) = \begin{cases} 0 & t < t_0 \\ 1 & t > t_0 \end{cases}$$



$$V_s(t) = A + B u(t-t_0)$$

For switch  $t_0 = 0$

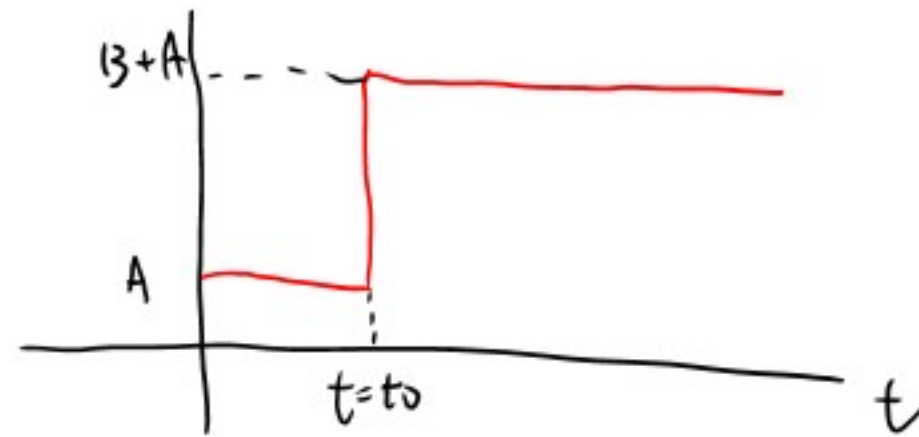

pulse source

$$V_s(t) = V_0 u(t-t_0) - V_0 u(t-t_1)$$

