

## Current and Resistance

- V** 7. The quantity of charge  $q$  (in coulombs) that has passed through a surface of area  $2.00 \text{ cm}^2$  varies with time according to the equation  $q = 4t^3 + 5t + 6$ , where  $t$  is in seconds. (a) What is the instantaneous current through the surface at  $t = 1.00 \text{ s}$ ? (b) What is the value of the current density?

- Q|C** 34. Lightbulb A is marked “25 W 120 V,” and lightbulb B is marked “100 W 120 V.” These labels mean that each lightbulb has its respective power delivered to it when it is connected to a constant 120-V source. (a) Find the resistance of each lightbulb. (b) During what time interval does  $1.00 \text{ C}$  pass into lightbulb A? (c) Is this charge different upon its exit versus its entry into the lightbulb? Explain. (d) In what time interval does  $1.00 \text{ J}$  pass into lightbulb A? (e) By what mechanisms does this energy enter and exit the lightbulb? Explain. (f) Find the cost of running lightbulb A continuously for 30.0 days, assuming the electric company sells its product at \$0.110 per kWh.

$$7. \quad (a) \quad i(t) = \frac{dq(t)}{dt} = \frac{d(4t^3 + 5t + 6)}{dt}$$

$$= 12t^2 + 5$$


$$i(1) = 17 \text{ (A)} \quad \#$$

$$(b) \quad J = \frac{I}{A} = \frac{17}{2 \times 10^{-4}} = 8.5 \times 10^4 \text{ (A/m}^2\text{)} \quad \#$$

34.



25W, 120V

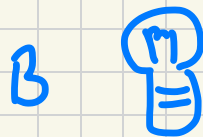

100W, 120V

$$P = IV = I^2 R = \frac{V^2}{R}$$

$$(a) \quad R = \frac{V^2}{P}$$

$$\left\{ \begin{array}{l} R_A = \frac{(120)^2}{25} = 576 \text{ (}\Omega\text{)} \\ R_B = \frac{(120)^2}{100} = 144 \text{ (}\Omega\text{)} \quad \# \end{array} \right.$$

$$\begin{aligned}
 (b) \quad I &= \frac{\Delta Q}{\Delta t} \Rightarrow \Delta t = \frac{\Delta Q}{I} \\
 \Rightarrow \Delta t &= \frac{V \cdot \Delta Q}{P} \quad \leftarrow \quad P = IV \Rightarrow \frac{1}{I} = \frac{V}{P} \\
 &= \frac{120 \cdot 1}{25} \approx 4.8 \text{ (s)} \quad \#
 \end{aligned}$$

(c) No (Conservation of charge)


$$(d) \quad P = \frac{W}{\Delta t} \Rightarrow \Delta t = \frac{W}{P} = \frac{1}{25} = 0.04 \text{ (s)}$$

(e)  $\left\{ \begin{array}{l} \text{enter : electrical energy} \\ \text{exit : thermal energy and radiation} \end{array} \right.$


$$\begin{aligned}
 (f) \quad \text{cost} &= 0.11 \times (0.025 \times 30 \times 24) \\
 &= \$ 19.8 \quad \#
 \end{aligned}$$

## DC Circuit

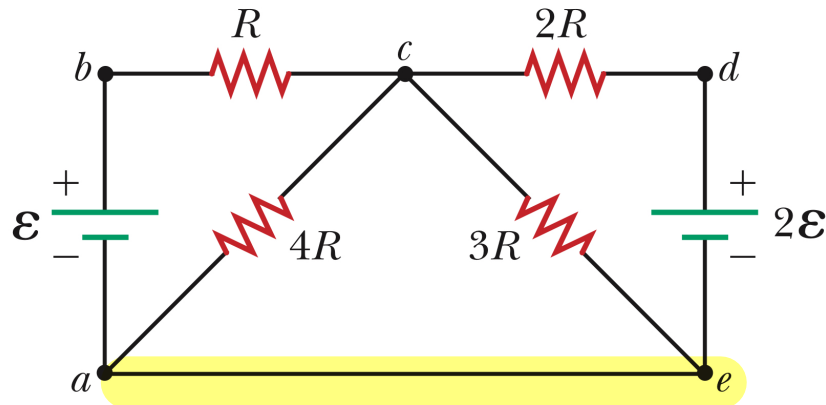
19. Taking  $R = 1.00 \text{ k}\Omega$  and  $\mathcal{E} = 250 \text{ V}$  in Figure P27.19, determine the direction and magnitude of the current in the horizontal wire between  $a$  and  $e$ .



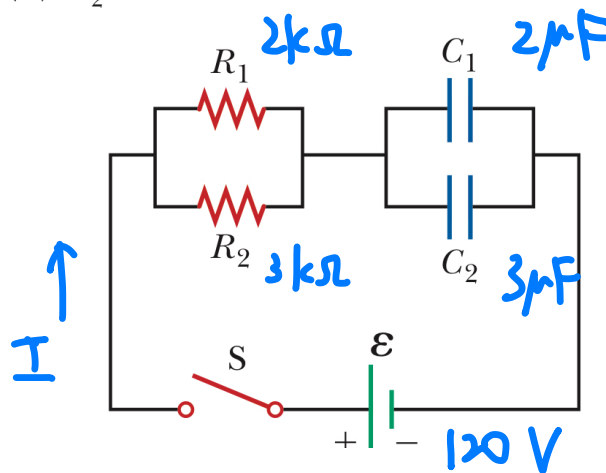41. The circuit in Figure P27.41 contains two resistors,  $R_1 = 2.00 \text{ k}\Omega$  and  $R_2 = 3.00 \text{ k}\Omega$ , and two capacitors,  $C_1 = 2.00 \mu\text{F}$  and  $C_2 = 3.00 \mu\text{F}$ , connected to a battery with emf  $\mathcal{E} = 120 \text{ V}$ . If there are no charges on the capacitors before switch  $S$  is closed, determine the charges on capacitors (a)  $C_1$  and (b)  $C_2$  as functions of time, after the switch is closed.



19.

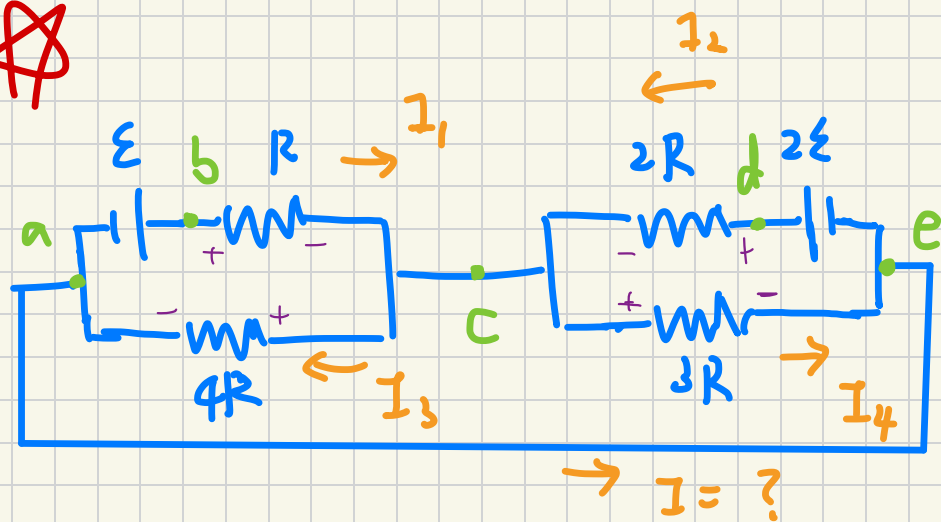

$$R = 1 \text{ k}\Omega$$

$$\mathcal{E} = 250 \text{ V}$$

① Loop 1:  $a \rightarrow b \rightarrow c \rightarrow a$

$$\mathcal{E} - I_1 R - I_3 (4R) = 0$$

$$\Rightarrow I_1 + 4I_3 = 250 \text{ (mA)}$$

② Loop 2:  $e \rightarrow d \rightarrow c \rightarrow e$

$$2\mathcal{E} - I_2 (2R) - I_4 (3R) = 0$$

$$\Rightarrow 2I_2 + 3I_4 = 500 \text{ (mA)}$$

③ Loop 3:  $c \rightarrow a \rightarrow e \rightarrow c$

$$I_3 (4R) - 4I_4 (3R) = 0$$

$$\Rightarrow 4I_3 - 3I_4 = 0$$

④ Node C:

$$I_1 + I_2 = I_3 + I_4$$

$$\begin{cases} I_1 + 4I_3 = 250 \\ 2I_2 + 3I_4 = 500 \\ 4I_3 = 3I_4 \\ I_1 + I_2 = I_3 + I_4 \end{cases} \Rightarrow \begin{cases} I_1 = 10 \\ I_2 = 130 \\ I_3 = 60 \\ I_4 = 80 \end{cases}$$


Node A:  $I_3 = I_1 + I_2$

$$\Rightarrow |I| = |I_1 - I_3| = 50 \text{ (mA)} \quad \#$$

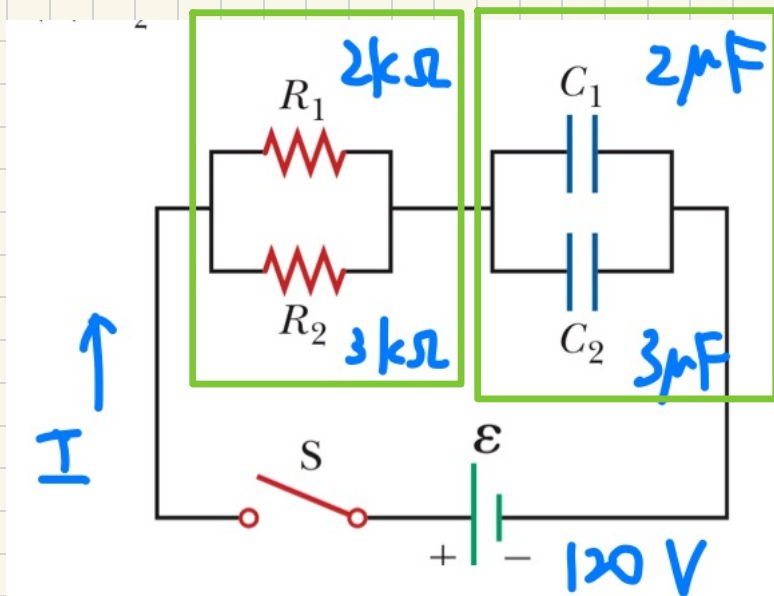41.  
~~\*~~

$$R_{eq} = \frac{1}{\frac{1}{2} + \frac{1}{3}} = 1.2 \text{ (k}\Omega\text{)}$$

$$Q = \frac{C}{\cancel{\Delta V}} \Rightarrow \begin{cases} Q \propto C \\ \Delta V = \frac{C}{Q} \end{cases}$$



An RC circuit w/

$$R = \frac{1}{\frac{1}{2} + \frac{1}{3}} = 1.2 \text{ (k}\Omega\text{)}$$

$$C = 2 + 3 = 5 \text{ (}\mu\text{F)}$$

$$V(t) = \varepsilon (1 - e^{-t/\tau_c})$$

$$= 120 [1 - e^{-t/(1.2 \times 10^3)(3 \times 10^{-9})}]$$

$$= 120 [1 - e^{-t/(6 \times 10^{-3})}]$$

$$\left( C = \frac{Q}{\Delta V} \Rightarrow Q = C \Delta V \right)$$

$$\left\{ \begin{array}{l} q_{c1} = (2 \times 10^{-6}) 120 [1 - e^{-t/(6 \times 10^{-3})}] \\ \quad = 2.4 \times 10^{-4} [1 - e^{-t/(6 \times 10^{-3})}] \\ q_{c2} = (3 \times 10^{-6}) 120 [1 - e^{-t/(6 \times 10^{-3})}] \\ \quad = 3.6 \times 10^{-4} [1 - e^{-t/(6 \times 10^{-3})}] \end{array} \right.$$

#