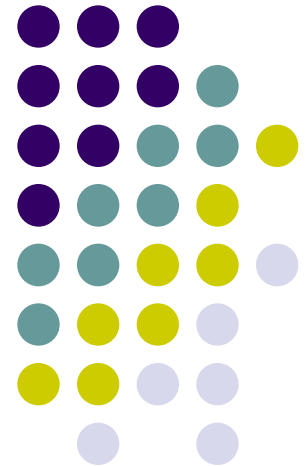


Counters and Registers

Wen-Hung Liao, Ph.D.





Objectives

- Understand several types of schemes used to decode different types of counters.
- Anticipate and eliminate the effects of decoding glitches.
- Compare the major differences between ring and Johnson counters.
- Analyze the operation of a frequency counter and of a digital clock.
- Recognize and understand the operation of various types of IC registers.



Synchronous Counter Design

- J-K flip-flop excitation table

Transition	Present State	Next State	J	K
0→0	0	0	0	X
0→1	0	1	1	X
1→0	1	0	X	1
1→1	1	1	X	0



Design Procedure


- Step1: Determine the desire number of bits (FFs) and the desired counting sequence.
- Step2: Draw the state transition diagram showing all possible states, including those that are not part of the desired counting sequence.
- Step 3: Use the state-transition diagram to set up a table that lists all PRESENT states and their NEXT states.




Design Procedure (cont'd)


- Step4: Add a column to the above table for each J and K input to produce a circuit excitation table.
- Step 5: Design the logic circuits to generate the levels required at each J and K input.
- Step 6: Implement the final expressions.

Example

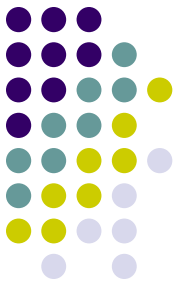

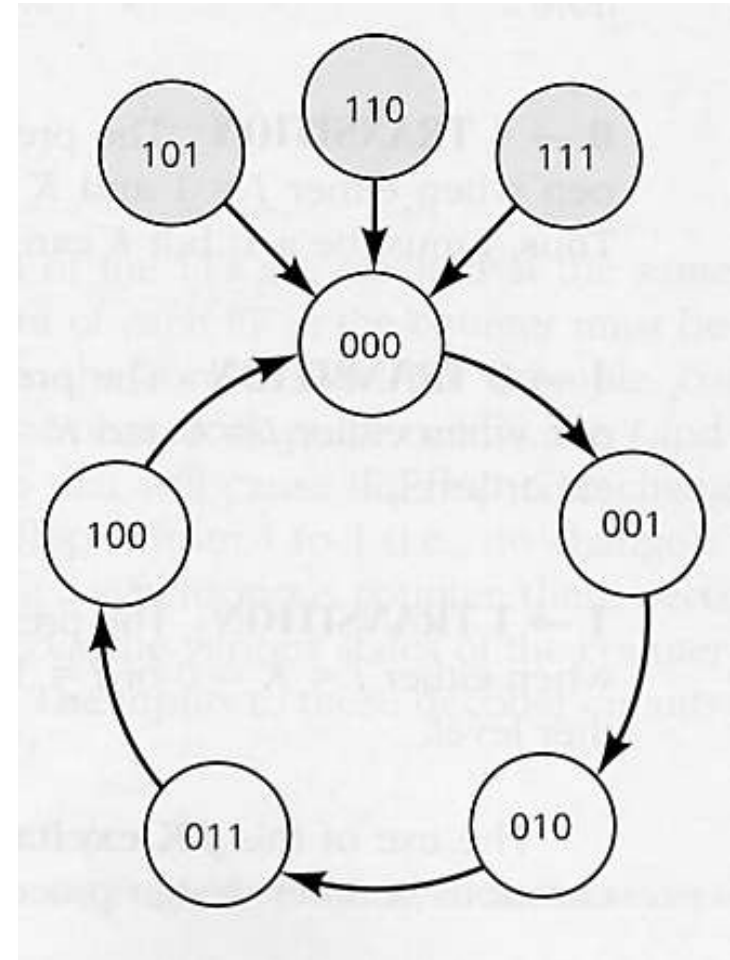
- MOD-5 synchronous counter
- $000 \rightarrow 001 \rightarrow 010 \rightarrow 011 \rightarrow 100 \rightarrow 000 \rightarrow \dots$
- State transition diagram



 

Present and Next States

	PRESENT State			NEXT State		
	<i>C</i>	<i>B</i>	<i>A</i>	<i>C</i>	<i>B</i>	<i>A</i>
line 1	0	0	0	0	0	1
2	0	0	1	0	1	0
3	0	1	0	0	1	1
4	0	1	1	1	0	0
5	1	0	0	0	0	0
6	1	0	1	0	0	0
7	1	1	0	0	0	0
8	1	1	1	0	0	0

 

Circuit Excitation Table


	PRESENT State			NEXT State								
	<i>C</i>	<i>B</i>	<i>A</i>	<i>C</i>	<i>B</i>	<i>A</i>	<i>J_C</i>	<i>K_C</i>	<i>J_B</i>	<i>K_B</i>	<i>J_A</i>	<i>K_A</i>
line 1	0	0	0	0	0	1	0	<i>x</i>	0	<i>x</i>	1	<i>x</i>
2	0	0	1	0	1	0	0	<i>x</i>	1	<i>x</i>	<i>x</i>	1
3	0	1	0	0	1	1	0	<i>x</i>	<i>x</i>	0	1	<i>x</i>
4	0	1	1	1	0	0	1	<i>x</i>	<i>x</i>	1	<i>x</i>	1
5	1	0	0	0	0	0	<i>x</i>	1	0	<i>x</i>	0	<i>x</i>
6	1	0	1	0	0	0	<i>x</i>	1	0	<i>x</i>	<i>x</i>	1
7	1	1	0	0	0	0	<i>x</i>	1	<i>x</i>	1	0	<i>x</i>
8	1	1	1	0	0	0	<i>x</i>	1	<i>x</i>	1	<i>x</i>	1

K-maps





- $J_A = C'$, $K_A = 1$ (Figure 7-34)

PRESENT			J_A
C	B	A	
0	0	0	1
0	0	1	x
0	1	0	1
0	1	1	x
1	0	0	0
1	0	1	x
1	1	0	0
1	1	1	x



(a)

 

(b)

    

Final Implementation

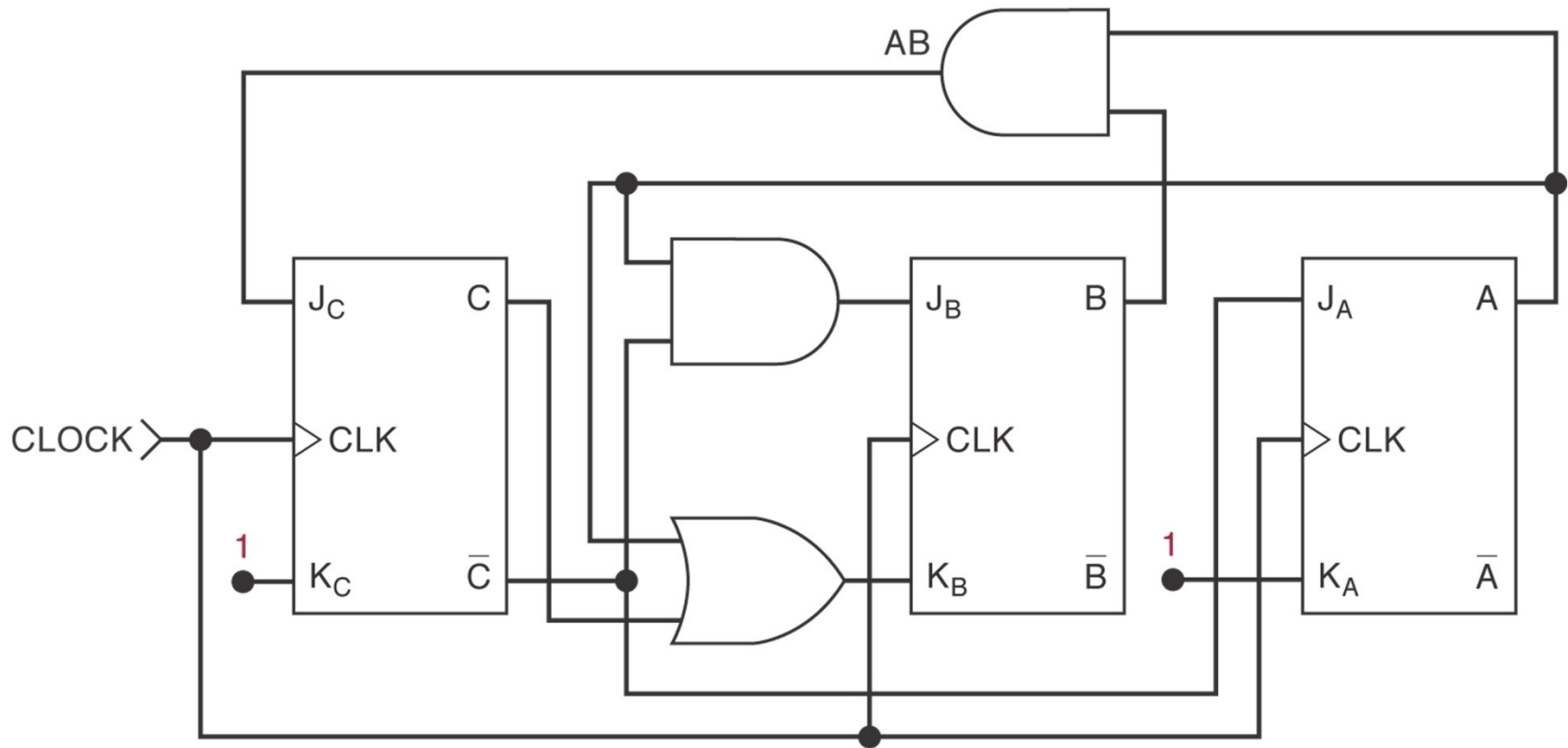
 





Step Motor Control

- A step motor is a motor that rotates in steps rather than in a continuous motion, typically 15 degrees per step.
- Used in positioning of read/write heads on magnetic tapes, in controlling print heads...
- [Figure 7.37](#): CW rotation and CCW rotation.
- Apply the design procedure to generate the circuit.

Step Motor Control (cont'd)


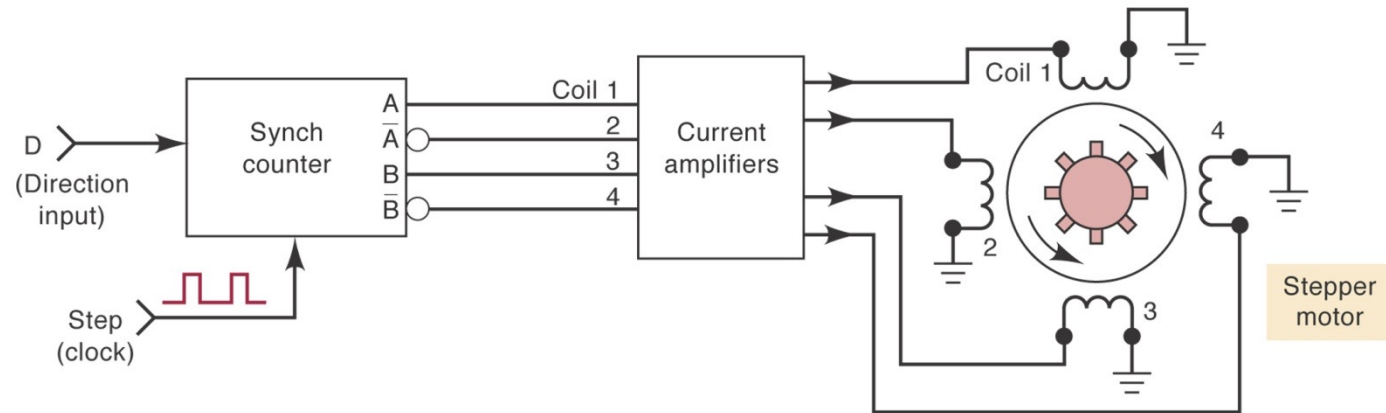
 


(a)


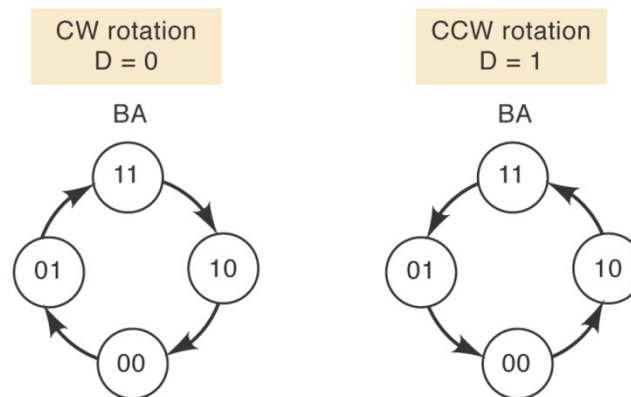


(b)

FIGURE 7-38 (a) K maps for J_B and K_B ; (b) K maps for J_A and K_A .

   

Final Implementation

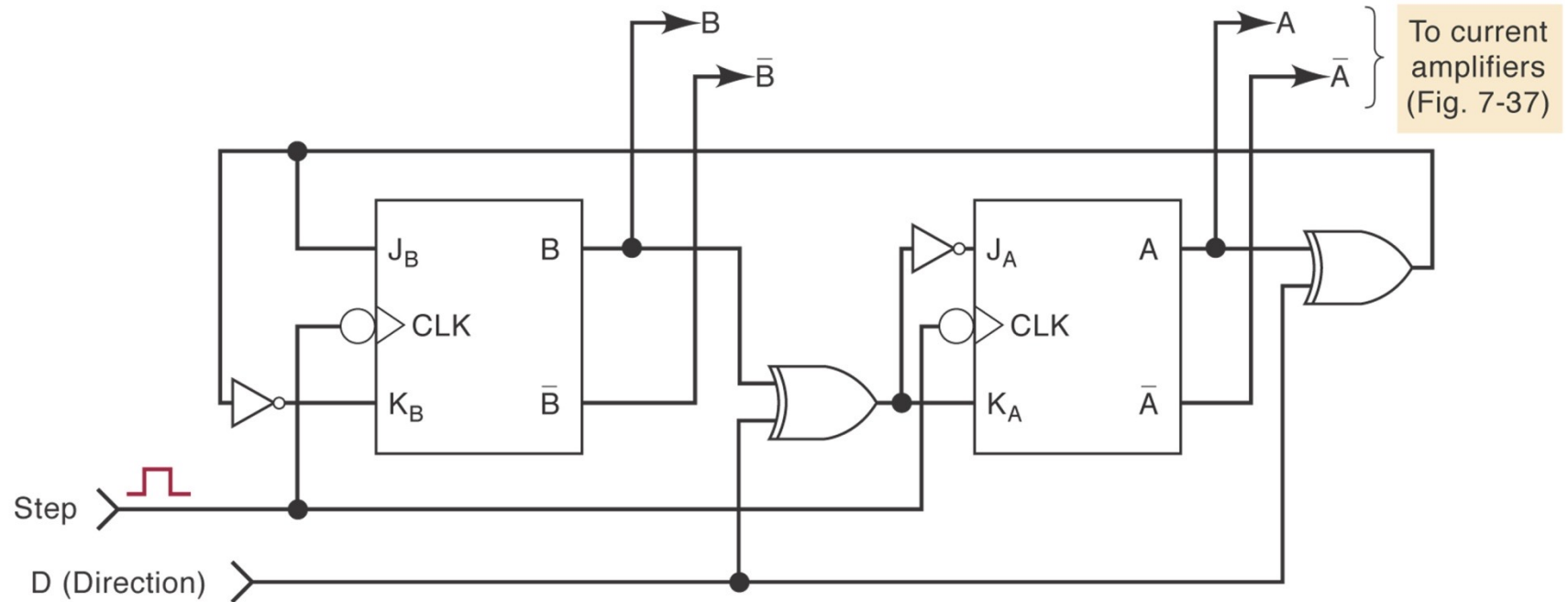
 




Shift-Register Counters

- Use feedback, output of last FF is connected back to the first FF in some way.
- Ring counter: circulating shift register.
- See [Figure 7-40](#).
- Why is it still a counter?

Four-Bit Ring Counter

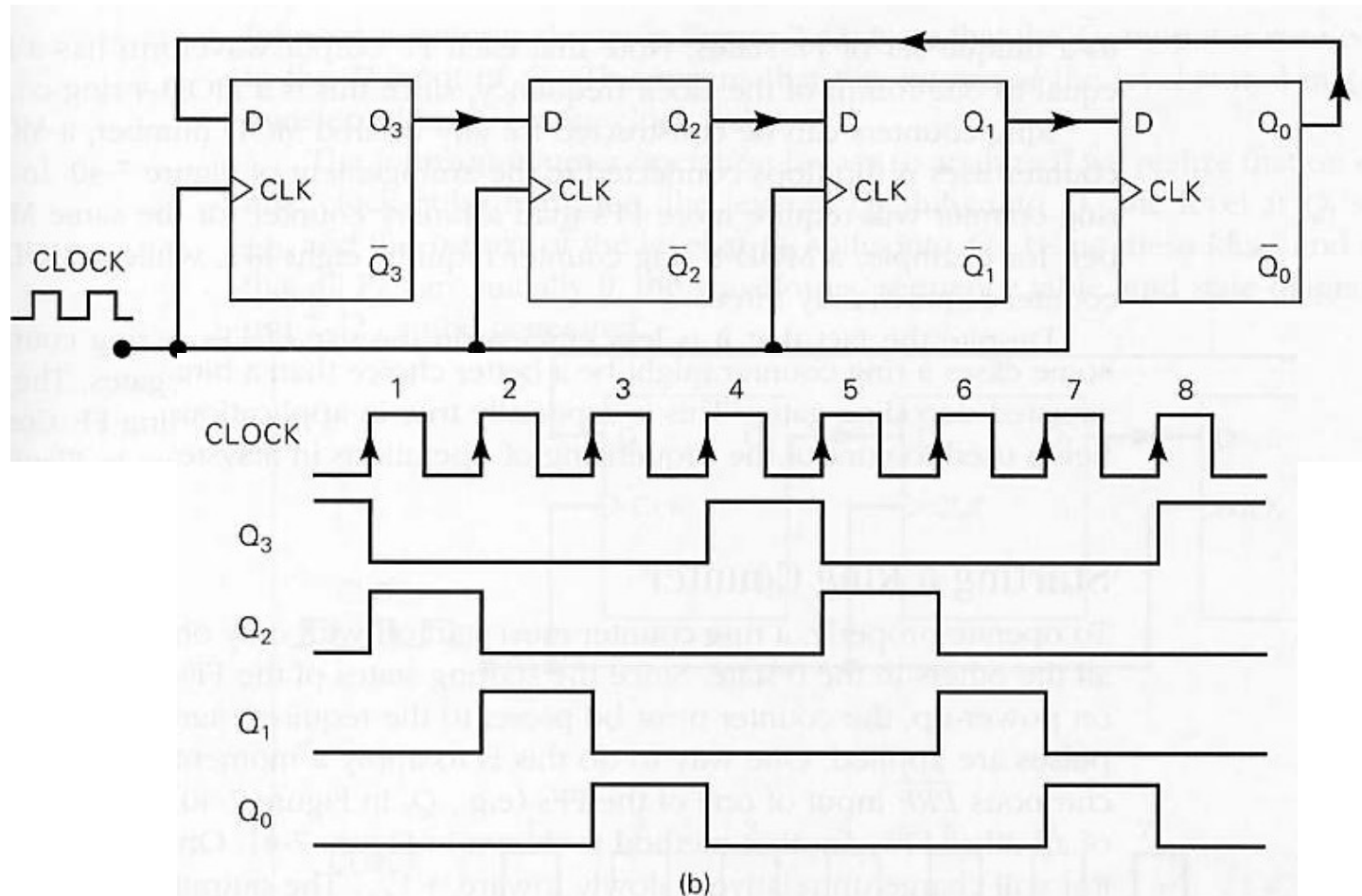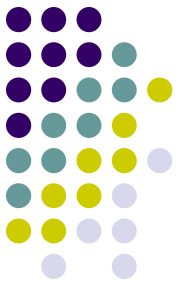




State Transition Diagram

- MOD-4 Counter
- Does not require decoding gates

Q ₃	Q ₂	Q ₁	Q ₀	CLOCK pulse
1	0	0	0	0
0	1	0	0	1
0	0	1	0	2
0	0	0	1	3
1	0	0	0	4
0	1	0	0	5
0	0	1	0	6
0	0	0	1	7
.
.

(c)

 

(d)



Starting a Ring Counter



- Start off with only one FF in the 1 state and all others in the 0 state.
- Use PRE and CLR inputs and Schmitt-trigger INVERTERS(page 261-262).




Johnson Counter

- Also known as the twisted-ring counter.
- Same as the ring counter except that the inverted output of the last FF is connected to the input of the first FF.
- Counting sequence:
 $000 \rightarrow 100 \rightarrow 110 \rightarrow 111 \rightarrow 011 \rightarrow 001 \rightarrow 000$
- A MOD-6 counter (twice the number of FFs)
- Needs decoding gates.
- [Figure 7-62](#)

MOD-6 Johnson Counter

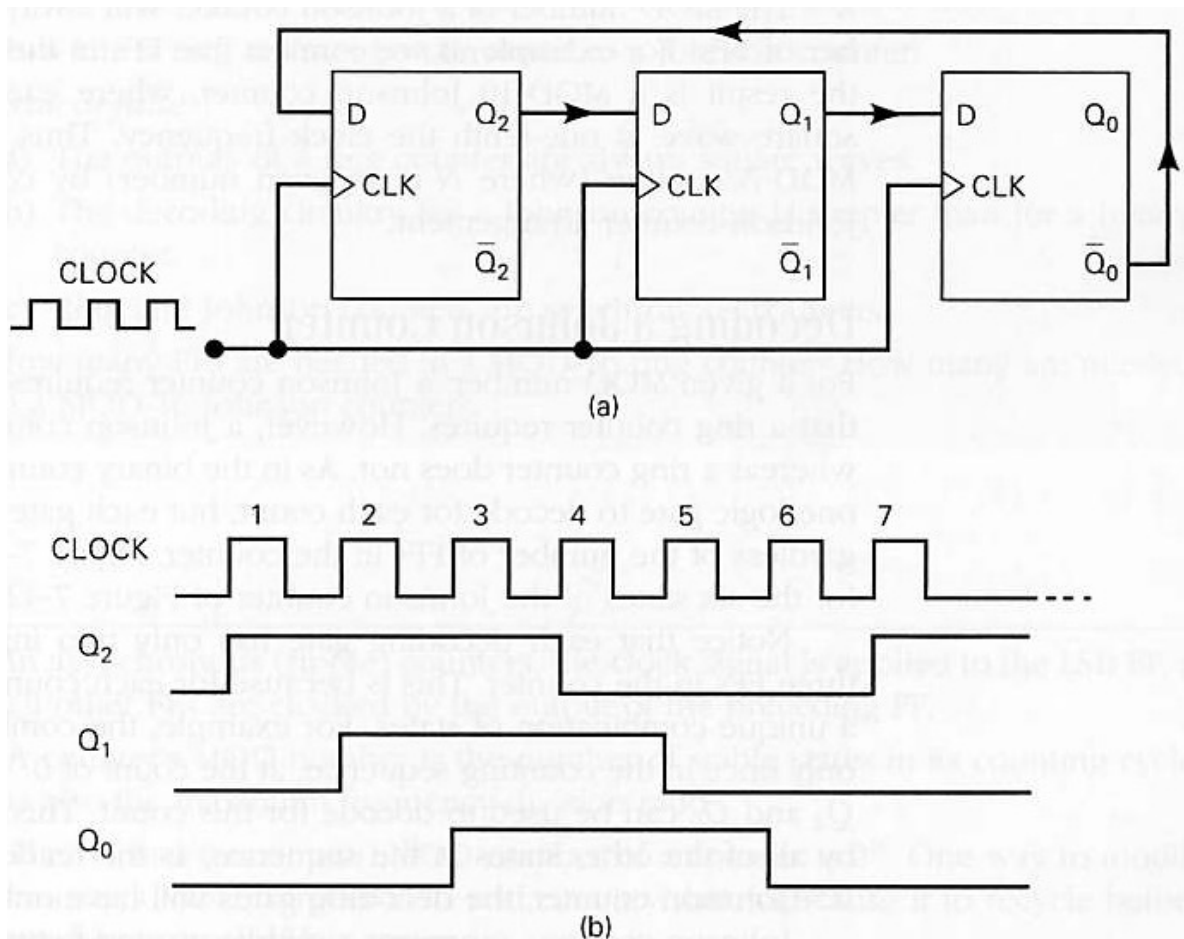 


State Transition Diagram

 

Q ₂	Q ₁	Q ₀	CLOCK pulse
0	0	0	0
1	0	0	1
1	1	0	2
1	1	1	3
0	1	1	4
0	0	1	5
0	0	0	6
1	0	0	7
1	1	0	8
.	.	.	.
.	.	.	.
.	.	.	.

(c)

 


(d)



Decoding a Johnson Counter

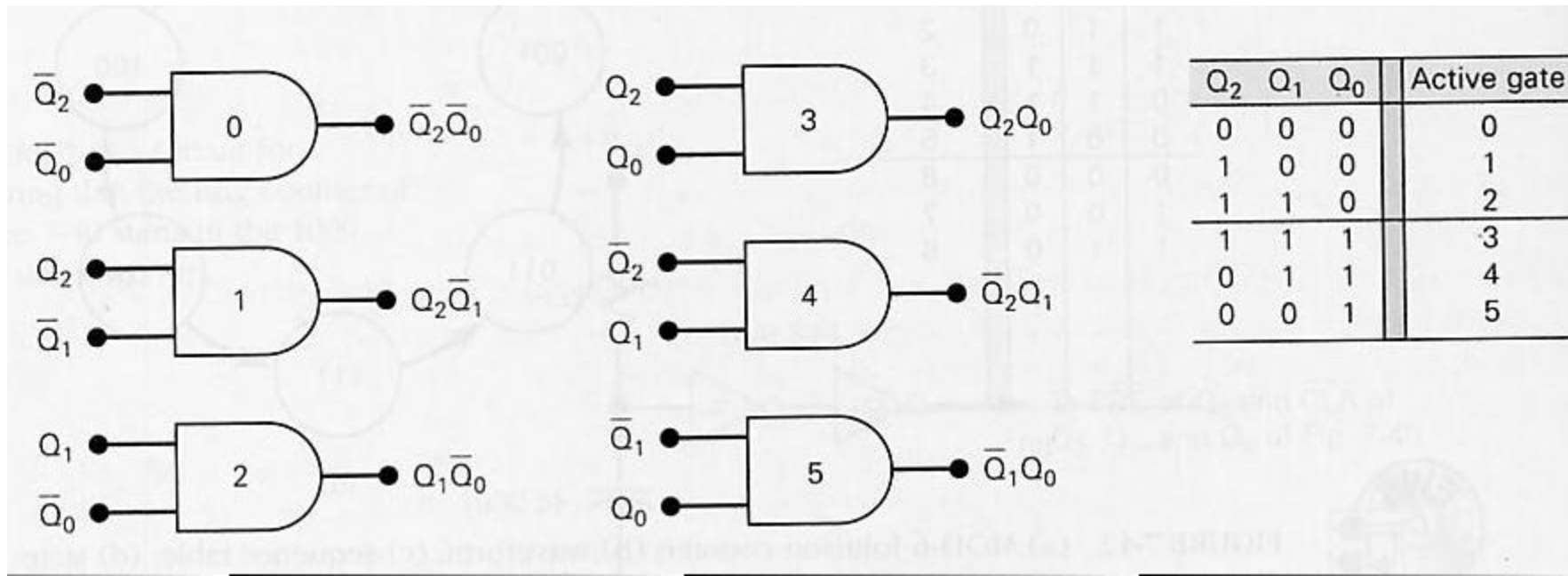- Each decoding has only two inputs.
- It can be shown that for any size Johnson counter, the decoding gates will have only two inputs.







Integrated-Circuit Registers

- Parallel in/Parallel Out: 74174 and 74178
- Serial in/Serial Out: 4731B
- Parallel in/Serial Out: 74165, 74LS165, 74HC165
- Serial in/Parallel Out: 74164, 74LS164, 74HC164

PIPO Register


 


(a)


 


(b)



74ALS174 Wired as a Shift Register

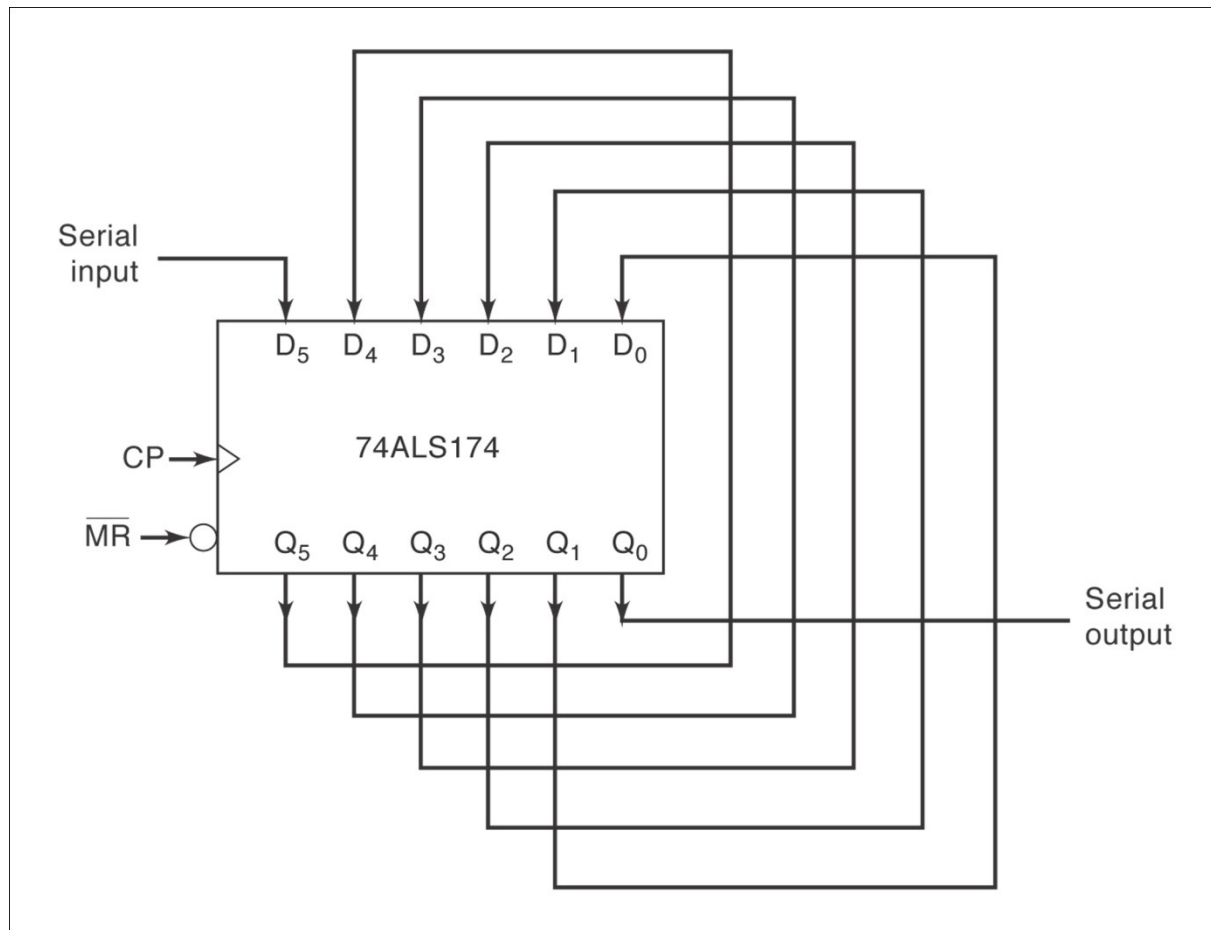 



SISO Register

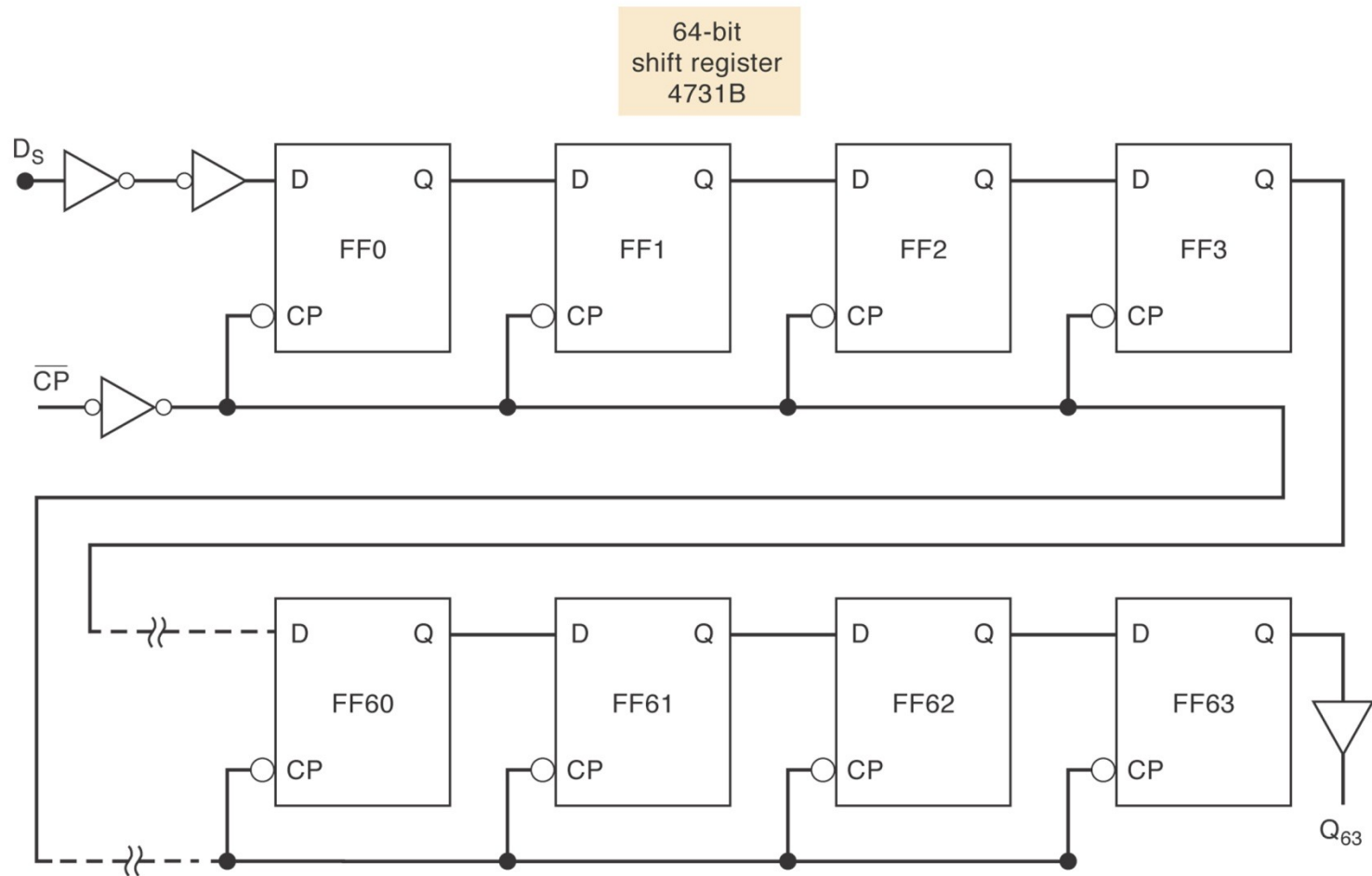 

Delay a Digital Signal

  

PISO Register

  

(a)


Function Table

Inputs			Operation
SH/LD	CP	CP INH	
L	X	X	Parallel load
H	H	X	No change
H	X	H	No change
H	⌄	L	Shifting
H	L	⌄	Shifting



H = high level
 L = low level
 X = immaterial
 ⌄ = PGT

(b)



SIPO Register

 

8-bit
shift register
74ALS164

 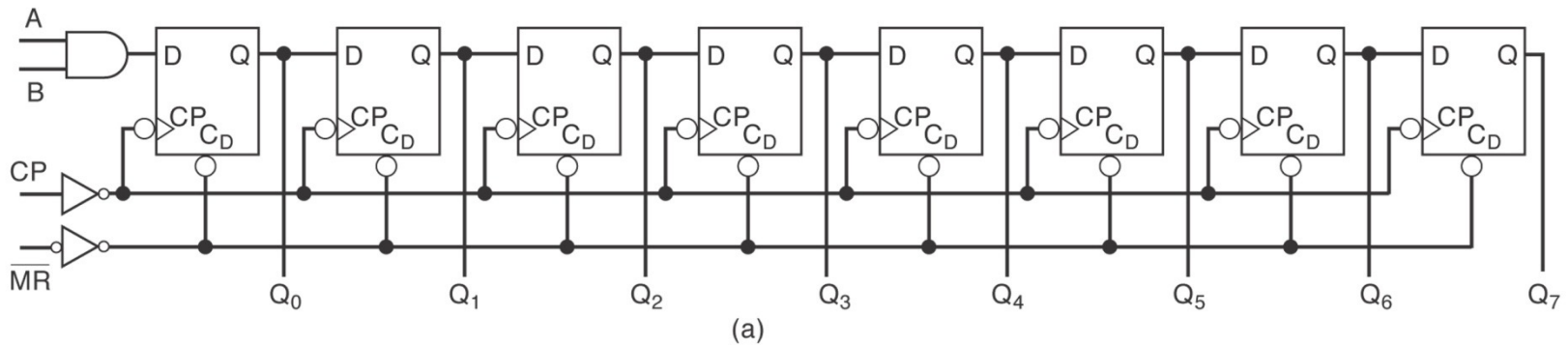

Example 7-23

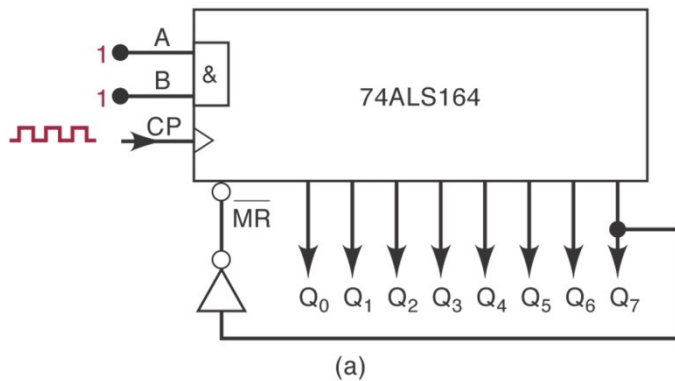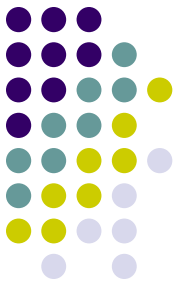

Input pulse number	Q ₀	Q ₁	Q ₂	Q ₃	Q ₄	Q ₅	Q ₆	Q ₇
0	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0
2	1	1	0	0	0	0	0	0
3	1	1	1	0	0	0	0	0
4	1	1	1	1	0	0	0	0
5	1	1	1	1	1	0	0	0
6	1	1	1	1	1	1	0	0
7	1	1	1	1	1	1	1	0
8	1	1	1	1	1	1	1	1

Temporary state

Recycles

(b)