

# system transfer function

△ Frequency response

circuit gain in frequency domain

$$H(\omega) = \frac{V_o(\omega)}{V_i(\omega)} = \frac{|V_o| \angle V_o}{|V_i| \angle V_i} = \frac{|V_o| e^{j\phi_o}}{|V_i| e^{j\phi_i}} = \left| \frac{V_o}{V_i} \right| e^{j(\phi_o - \phi_i)}$$


$V_o$  : output voltage  
 $V_i$  : input voltage

增益

$$\text{gain} = |H(\omega)| = \frac{|V_o|}{|V_i|}$$

phase shift.  $\angle H(\omega) = \angle V_o - \angle V_i$

ex.

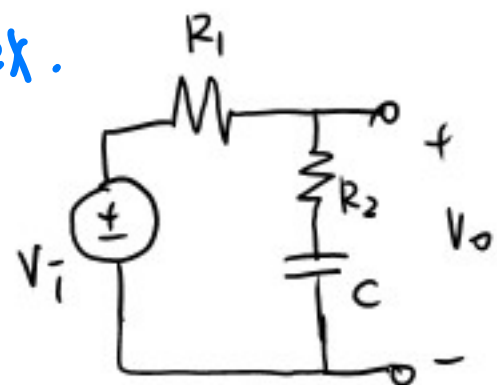

$$H(\omega) = \frac{V_o}{V_i} = \frac{R_2 + Z_C}{R_1 + R_2 + Z_C} = \frac{R_2 + \frac{1}{j\omega C}}{R_1 + R_2 + \frac{1}{j\omega C}} = \frac{1 + j\omega C R_2}{1 + j\omega C (R_1 + R_2)}$$

$$\text{gain} = |H(\omega)| = \frac{\sqrt{1 + \omega^2 C^2 R_2^2}}{\sqrt{1 + \omega^2 C^2 (R_1 + R_2)^2}}$$

phase shift =  $\angle H(\omega) = \tan^{-1}(\omega C R_2) - \tan^{-1}(\omega C (R_1 + R_2))$

$f \rightarrow 0$  (DC)  $\text{gain} \approx 1$ ,  $f \uparrow$  (高频)  $\omega^2 C^2 R_2^2 \gg 1 \rightarrow f \gg \frac{1}{2\pi C R_2}$   $\text{gain} \approx \frac{R_2}{R_1 + R_2} < 1$

$R_1 = 8k\Omega$ ,  $R_2 = 16k\Omega$ ,  $C = 0.23\mu F$ ,  $H(\omega) = \frac{1 + j\omega(3.68 \times 10^{-3})}{1 + j\omega(5.52 \times 10^{-3})}$

$f = 1000 \text{ Hz}$ ,  $\omega = 6280 \text{ rad/s}$   
gain = 0.67, phase =  $-0.8^\circ$

$$H(\omega) = \frac{1 + j\frac{\omega}{z}}{1 + j\frac{\omega}{p}}$$

$$1 + j = \sqrt{2} \angle 45^\circ$$

$$H(\omega) = \frac{(1 + j\frac{\omega}{z_1})(1 + j\frac{\omega}{z_2}) \dots}{(1 + j\frac{\omega}{p_1})(1 + j\frac{\omega}{p_2}) \dots}$$

$z$  is called zero of the circuit

- $\omega \ll z$  gain remains the same, phase shift  $\sim 0^\circ$
- $\omega \approx z$ , gain increase  $\sqrt{2}$  fold, phase shift increase  $45^\circ$
- $\omega \gg z$ , gain increase as  $\frac{\omega}{z}$ , phase shift increase  $90^\circ$

$$H(\omega) = \frac{1 + j\omega(3.68 \times 10^{-3})}{1 + j\omega(5.52 \times 10^{-3})}$$

$p$  is called pole of the circuit.

- $\omega \ll p$ , gain remain the same, phase shift  $\sim 0^\circ$
- $\omega \approx p$ , gain decrease  $\sqrt{2}$  fold, phase shift decrease  $45^\circ$
- $\omega \gg p$ , gain decrease as  $\frac{\omega}{p}$ , phase shift decrease  $90^\circ$

one zero at  $f_z = \frac{1}{2\pi(3.68 \times 10^{-3})} = \frac{271.14}{2\pi}$   
 $\approx 43.25 \text{ Hz}$

one pole at  $f_p = \frac{1}{2\pi(5.52 \times 10^{-3})} = \frac{181.16}{2\pi}$   
 $\approx 28.83 \text{ Hz}$

Bode plot: a chart of gain and phase shift versus frequency

gain is usually shown in decibels

frequency is usually shown in logarithm scale.

describes the frequency response

$$H(\omega) = \frac{1}{1 + j\frac{\omega}{\omega_0}} = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}} \angle \left[ -\tan^{-1}\left(\frac{\omega}{\omega_0}\right) \right]$$

$\omega_0$  is the pole.

$$20 \log_{10} |H(\omega)| = 20 \log_{10} \left( \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}} \right) = -20 \log_{10} \left( \sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2} \right) = -10 \log_{10} \left[ 1 + \left(\frac{\omega}{\omega_0}\right)^2 \right]$$


$$\left\{ \begin{array}{l} \omega \ll \omega_0, \quad 20 \log_{10} |H(\omega)| \approx 0 \text{ dB} \end{array} \right.$$

$$\left\{ \begin{array}{l} \omega \gg \omega_0, \quad 1 + \left(\frac{\omega}{\omega_0}\right)^2 \approx \left(\frac{\omega}{\omega_0}\right)^2 \quad 20 \log_{10} |H(\omega)| = -20 \log_{10} \left(\frac{\omega}{\omega_0}\right) = 20 \log_{10} \omega_0 - 20 \log_{10} \omega \end{array} \right.$$

$\omega$  increase 10 fold.  $\sim 20 \log_{10} |H(\omega)|$  decrease  $-20 \text{ dB}$   $[-20 \text{ dB/dec}]$



$\sim 2$  fold  $\sim 20 \log_{10} |H(\omega)|$  decrease  $-6 \text{ dB}$   $[-6 \text{ dB/oct}]$



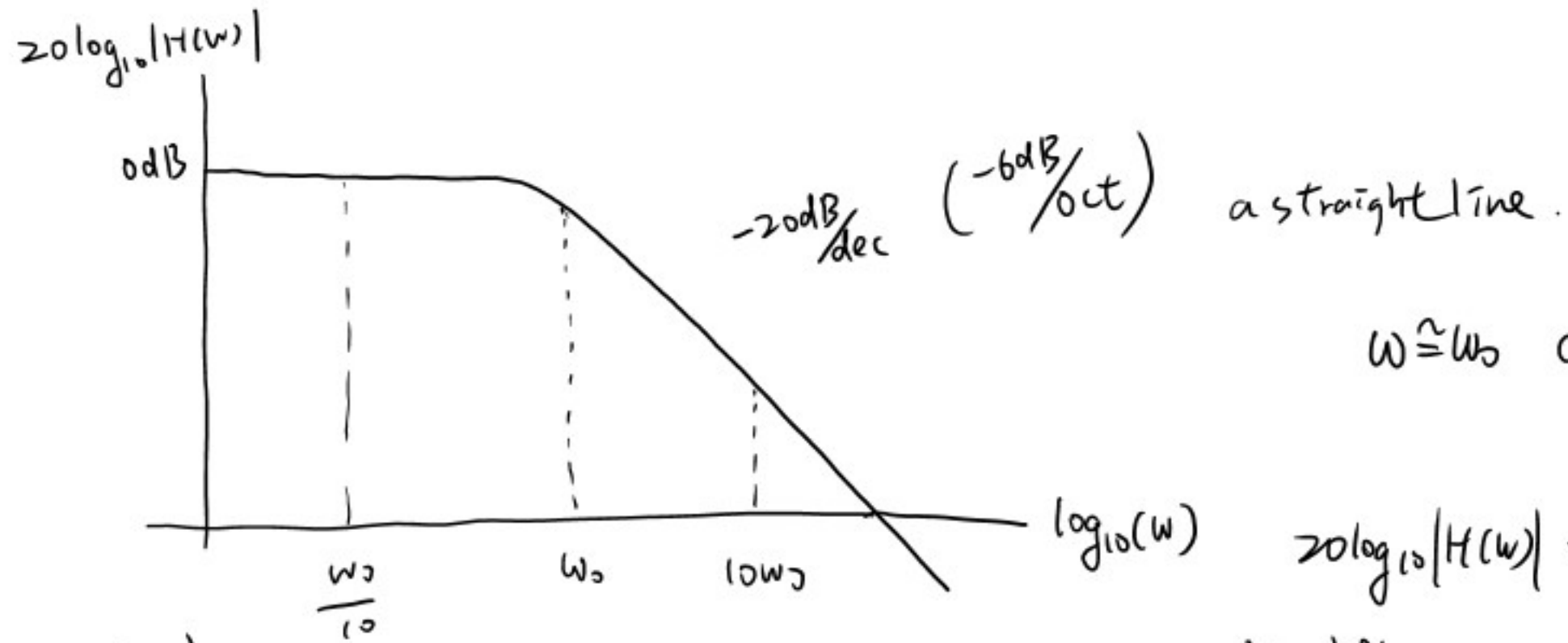

$w \approx w_0$  corner frequency (cut-off freq)  
 3 dB freq

$$20 \log_{10} |H(w)| = -10 \log_{10} \left[ 1 + \left( \frac{w}{w_0} \right)^2 \right] = -3 \text{ dB}$$

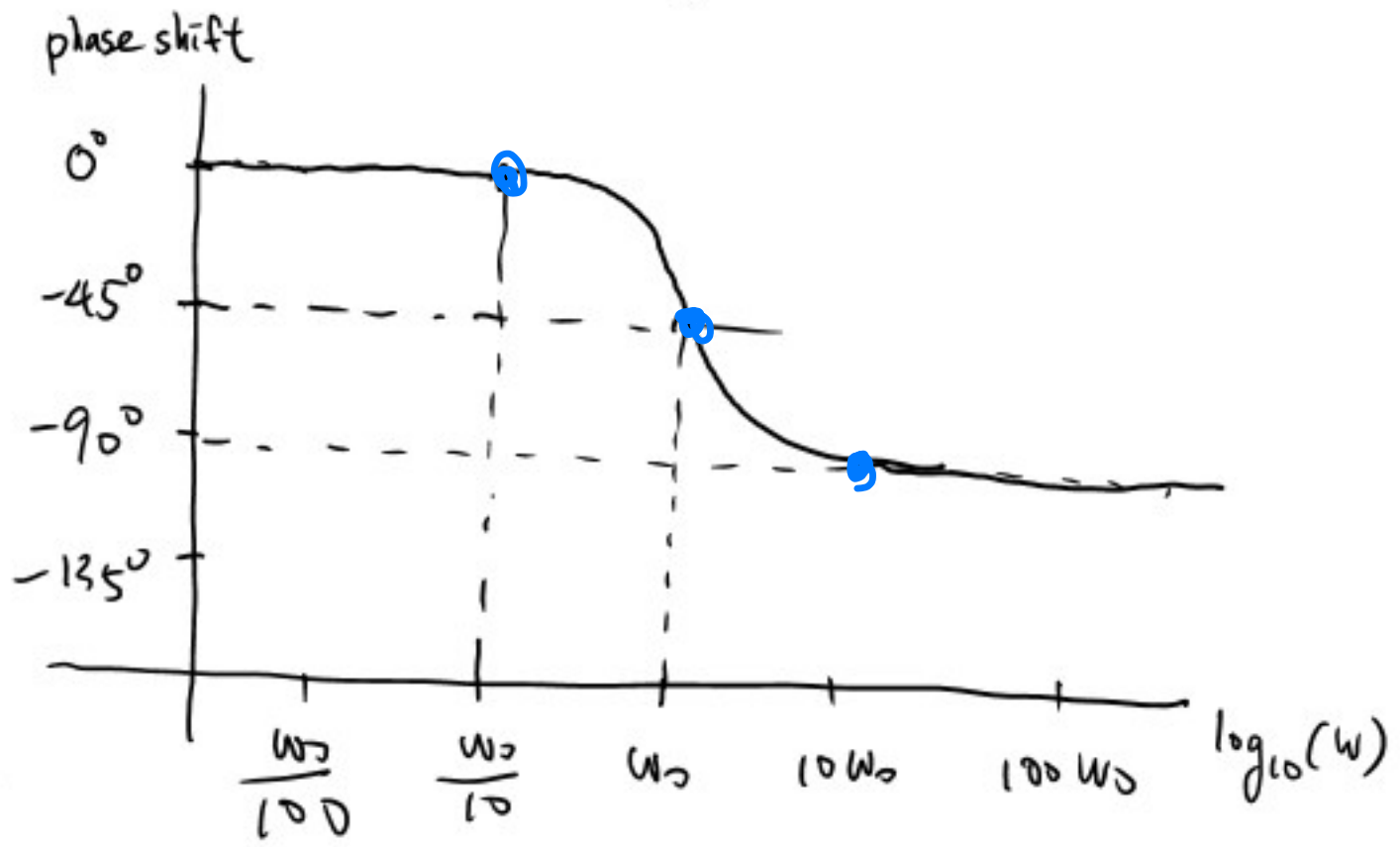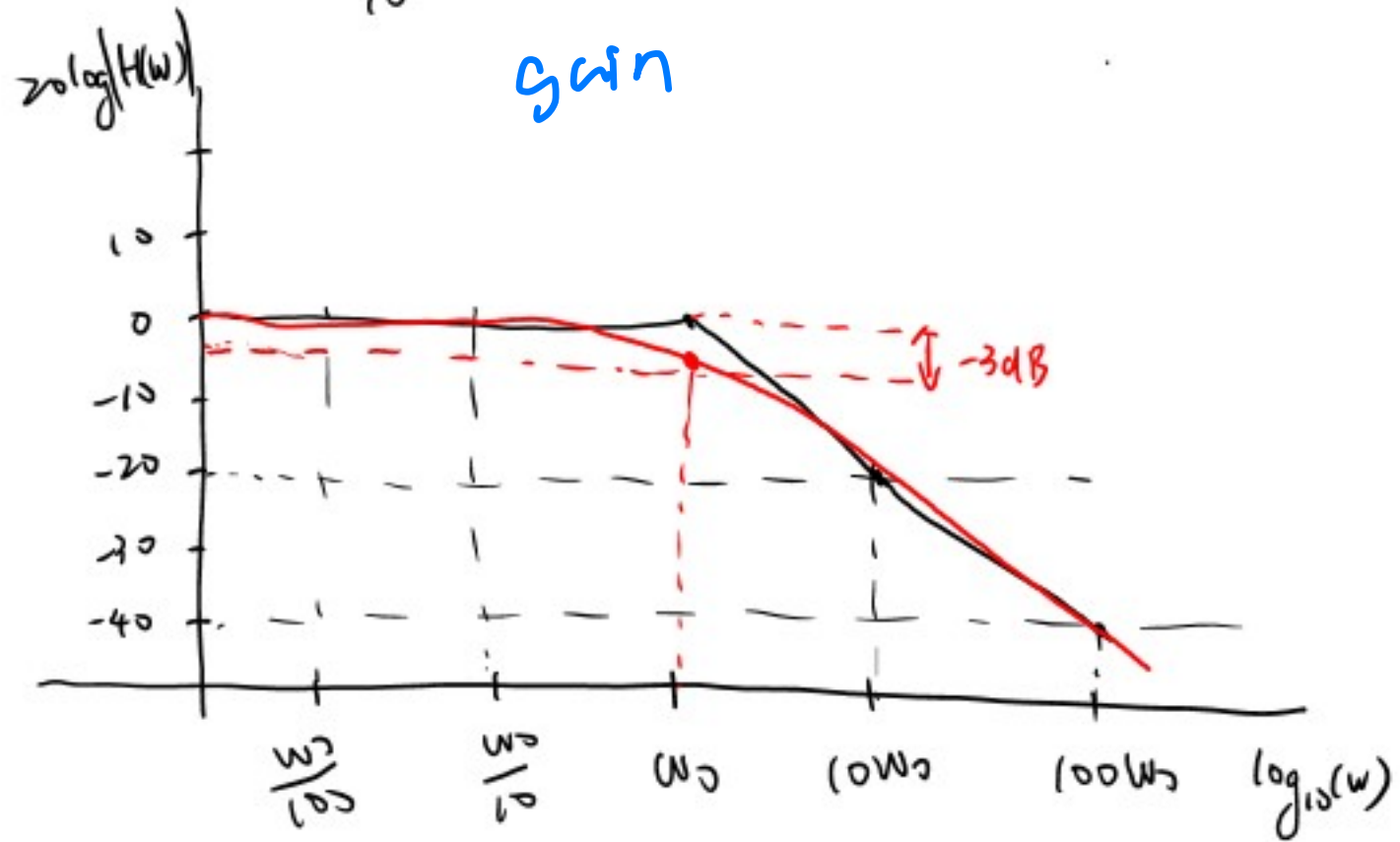

phase shift

ex 1.

$$H(\omega) = K \frac{j\omega}{1 + j\frac{\omega}{p}}$$

$$20 \log_{10} |H(\omega)| = 20 \log_{10} K + 20 \log_{10}(\omega) - 20 \log_{10} \sqrt{1 + \left(\frac{\omega}{p}\right)^2}$$

one pole,  $p$ , one zero at 0.



$\omega \ll p$   $20 \log_{10} K + 20 \log_{10} \omega$ , gain increase with slope  $+20 \text{ dB/dec}$  ( $+6 \text{ dB/oct}$ )

$\omega \gg p$   $20 \log_{10} K + 20 \log_{10} \omega - 20 \log_{10} \frac{\omega}{p} = 20 \log_{10} K + 20 \log_{10} \omega - 20 \log_{10} \omega + 20 \log_{10} p = 20 \log_{10}(K \cdot p)$ , a constant.

$\omega \approx p$   $20 \log_{10} K + 20 \log_{10} \omega - 20 \log_{10} \sqrt{2} = 20 \log_{10}(K \cdot p) - 3 \text{ dB}$

phase shift  $\angle H(\omega) = 90^\circ$   $\begin{cases} \omega \ll p & 90^\circ \\ \omega \gg p & 0^\circ \\ \omega \approx p & 45^\circ \end{cases}$

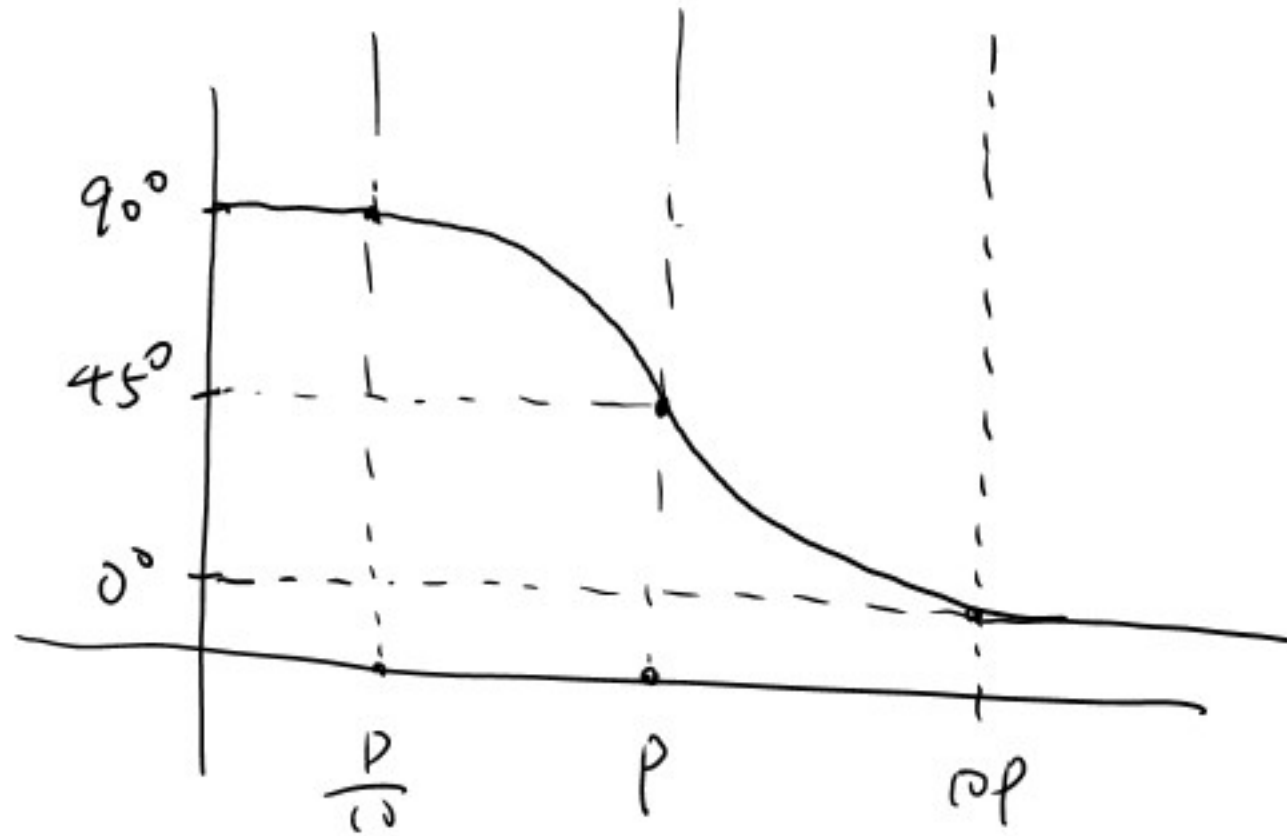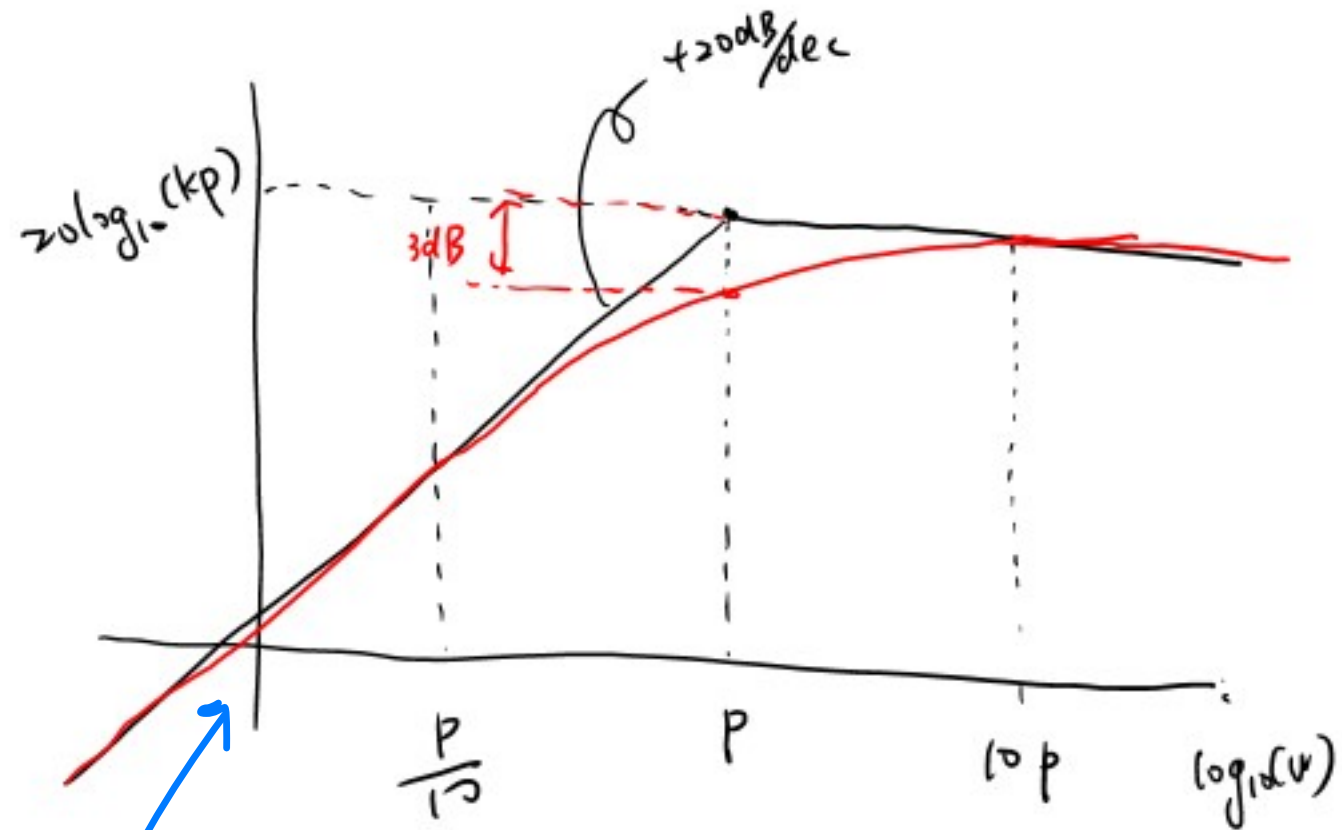
$$H(\omega) = K \frac{j\omega}{1 + j\frac{\omega}{p}}$$




- a capacitor gives a pole or a zero
- Two poles may lie together with  $-40 \text{ dB/dec}$
- zero: positive  $+20 \text{ dB/dec}$  and  $+90^\circ$
- pole: negative  $-20 \text{ dB/dec}$  and  $-90^\circ$

does not necessarily pass the origin

ex 2.

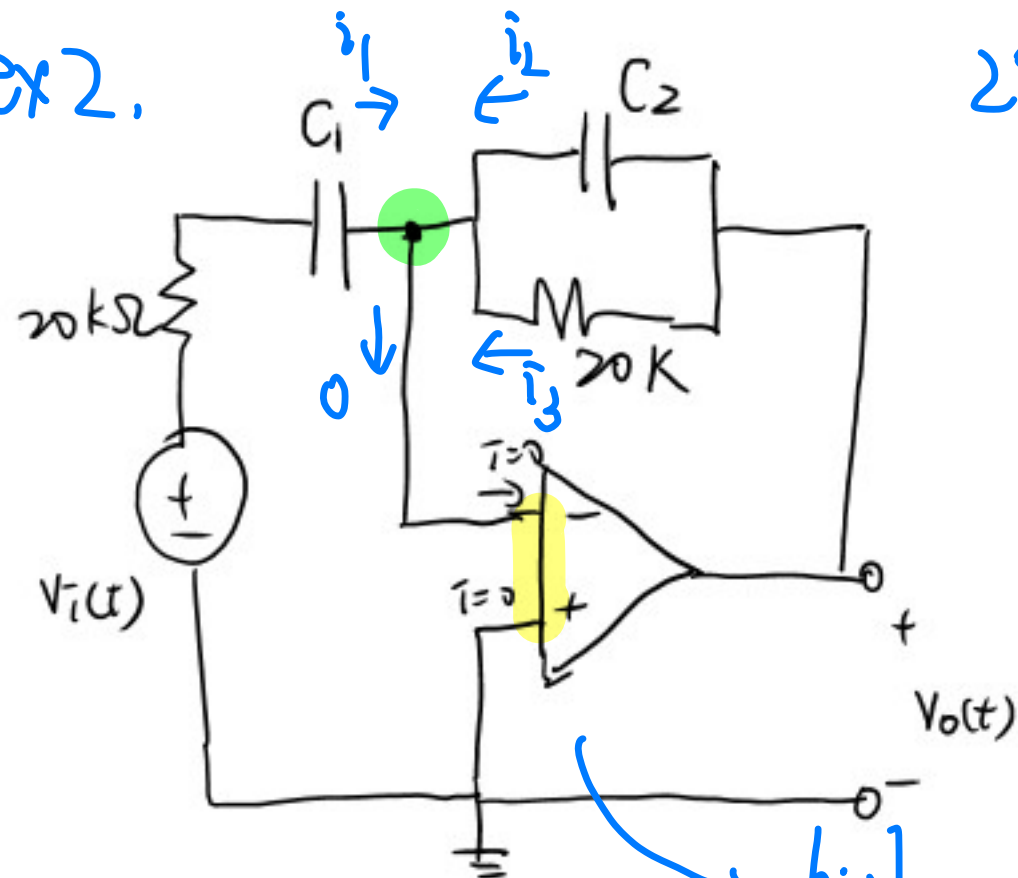

2°  $20 \log |H|$  transfer function

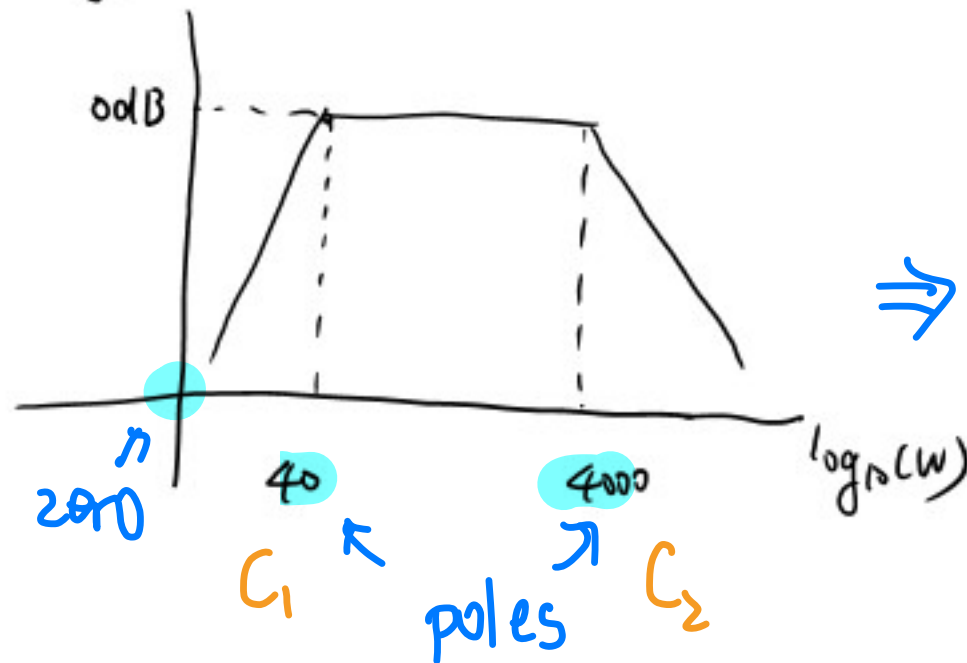

$$\Rightarrow H(\omega) = A \frac{j\omega}{(1 + j\frac{\omega}{40})(1 + j\frac{\omega}{4000})}$$

$$40 \leq \omega \leq 4000 \quad |H(\omega)| = A \cdot \frac{|j\omega|}{|(1 + j\frac{\omega}{40})|} \approx 40 A$$

midband

$$20 \log_{10}(40A) = 0 \rightarrow 40A = 1 \rightarrow A = 0.025$$

1°  $V^+ = V^- = 0$

$$\bar{I}^+ = \bar{I}^- = 0$$

$$\frac{V_1}{20k} + \frac{1}{j\omega C_1} + \frac{V_o}{j\omega C_2} + \frac{V_o}{20k} = 0$$


KCL

3°

$$H(\omega) = \frac{V_o}{V_i} = \frac{-j\omega C_1 (20k)}{[1 + j\omega C_1 (20k)][1 + j\omega C_2 (20k)]} = -C_1 (20k) \frac{j\omega}{[1 + j\omega C_1 (20k)][1 + j\omega C_2 (20k)]}$$


$$C_1(20k) = A = 0.025 \rightarrow C_1 = \frac{0.025}{20 \times 10^3} = 1.25 \times 10^{-6} F = 1.25 \mu F \quad \#$$
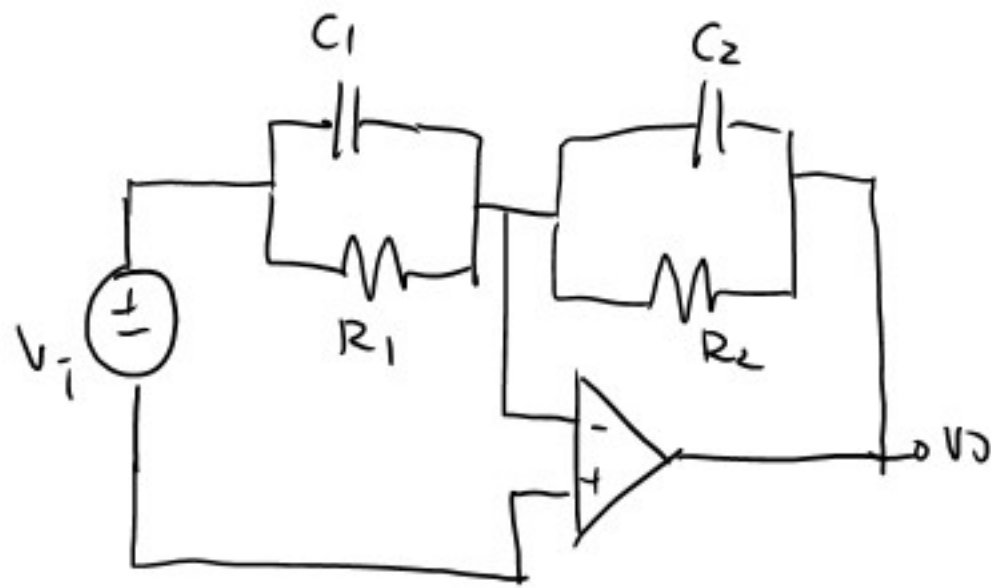
$$C_1(20k) = \frac{1}{40} \text{ valid} \quad C_2(20k) = \frac{1}{4000} \rightarrow C_2 = \frac{1}{20 \times 10^3 \times 4 \times 10^3} = 1.25 \times 10^{-8} F = 12.5 nF \quad \#$$



$$H(\omega) = \frac{R_2}{R_1} \frac{1 + j\frac{\omega}{z}}{1 + j\frac{\omega}{p}}$$

gain

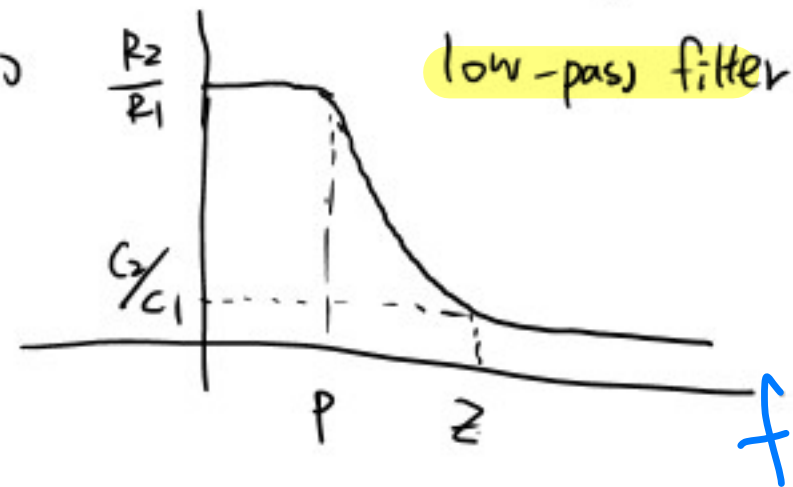


pole < zero

$$z = \frac{1}{C_1 R_1} \quad p = \frac{1}{C_2 R_2}$$

gain

high-pass filter

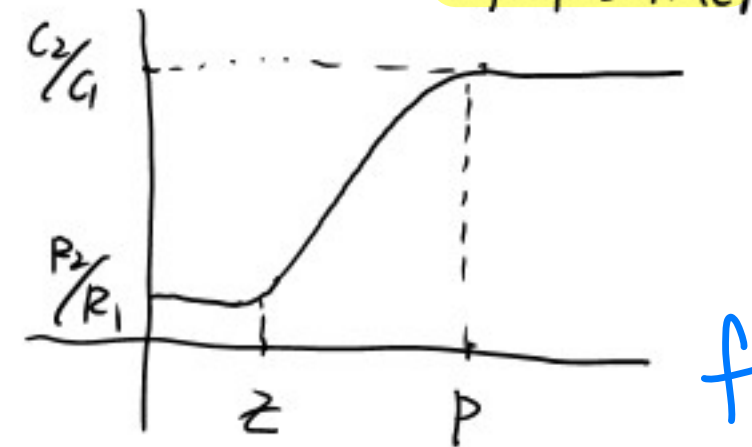

zero < pole



2nd order filter

$$H(\omega) = \frac{k\omega_0^2}{(\underbrace{j\omega}^{\text{double root}})^2 + j2\zeta\omega_0\omega + \omega_0^2} = \frac{k - \omega_0^2}{\omega_0^2 - \omega^2 + j2\zeta\omega_0\omega} \quad (\zeta : \text{zeta})$$

$k=1$   $\omega \ll \omega_0$   $|H(\omega)| \approx 1$   $20 \log_{10}|H| = 0 \text{ dB}$

$\omega \gg \omega_0$   $|H(\omega)| = \left(\frac{\omega_0}{\omega}\right)^2$   $20 \log_{10}|H| = 40 \log_{10}\omega_0 - 40 \log_{10}\omega$   $\left[-40 \text{ dB/dec}, -120 \text{ dB/oct}\right]$

$\omega \approx \omega_0$   $|H(\omega)| \approx \frac{1}{2\zeta}$   $20 \log_{10}|H| = -20 \log_{10}(2\zeta) = -6 - 20 \log_{10}(\zeta) \text{ dB}$

